

## Fall-2020 UM-SJTU JI Ve311 Homework #2

Instructor: Dr. Chang-Ching Tu


Due: 11:59 am, October 10, 2020 (Saturday)

Note:

- (1) Please use A4 size papers.
- (2) The homework should be submitted online.
- (2) Please use the SPICE model below for simulation.

`.model Dbreak D Is=3e-12 Rs=0 N=1 TT=0 Cjo=0pF`

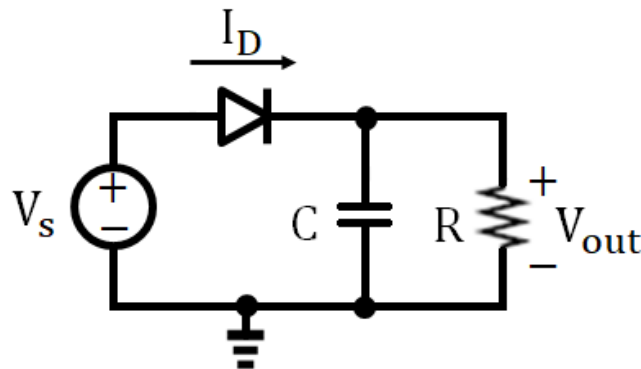1. [Half-Wave Rectifier] Design a half-wave rectifier circuit, such as below, which can convert a sinusoidal voltage input,  $V_s = 6\sin(2\pi 60 \cdot \text{time})$ , to an almost constant voltage output.
  - (a) [20%] Assuming  $V_{on} = 0.7 \text{ V}$  and  $R = 1 \text{ k}\Omega$ , calculate  $C$  which makes the ripple voltage ( $V_r$ ) is smaller than  $0.1 \text{ V}$ . Estimate  $V_{dc}$ ,  $I_{dc}$ ,  $\theta_c$ ,  $\Delta T$ ,  $I_{peak}$ ,  $I_{surge}$  and PIV of the designed half-wave rectifier.
  - (b) [15%] In Pspice, plot  $V_s$  and  $V_{out}$  versus time on the sample graph to find out the values of  $V_{dc}$ ,  $I_{dc}$ ,  $V_r$  and PIV. Comment on the simulation results compared to the hand-calculated ones.
  - (c) [15%] In Pspice, plot  $I_D$  versus time to find out the values of  $I_{peak}$  and  $I_{surge}$ . Comment on the simulation results compared to the hand-calculated ones.



2. [Full-Wave Bridge Rectifier] Design a full-wave bridge rectifier circuit, such as below, which can convert a sinusoidal voltage input,  $V_s = 6\sin(2\pi 60 \cdot \text{time})$ , to an almost constant voltage output.
- (a) [20%] Assuming  $V_{on} = 0.7 \text{ V}$  and  $R = 1 \text{ k}\Omega$ , calculate  $C$  which makes the ripple voltage ( $V_r$ ) smaller than  $0.1 \text{ V}$ . Estimate  $V_{dc}$ ,  $I_{dc}$ ,  $\theta_C$ ,  $\Delta T$ ,  $I_{peak}$ ,  $I_{surge}$  and PIV of the designed full-wave bridge rectifier.
- (b) [15%] In Pspice, plot  $V_s$  (using “voltage differential marker” function) and  $V_{out}$  versus time on the sample graph to find out the values of  $V_{dc}$ ,  $I_{dc}$ ,  $V_r$  and PIV. Comment on the simulation results compared to the hand-calculated ones.
- (c) [15%] In Pspice, plot  $I_{D2}$  and  $I_{D3}$  versus time on the same graph to find out the values of  $I_{peak}$  and  $I_{surge}$ . Comment on the simulation results compared to the hand-calculated ones.

