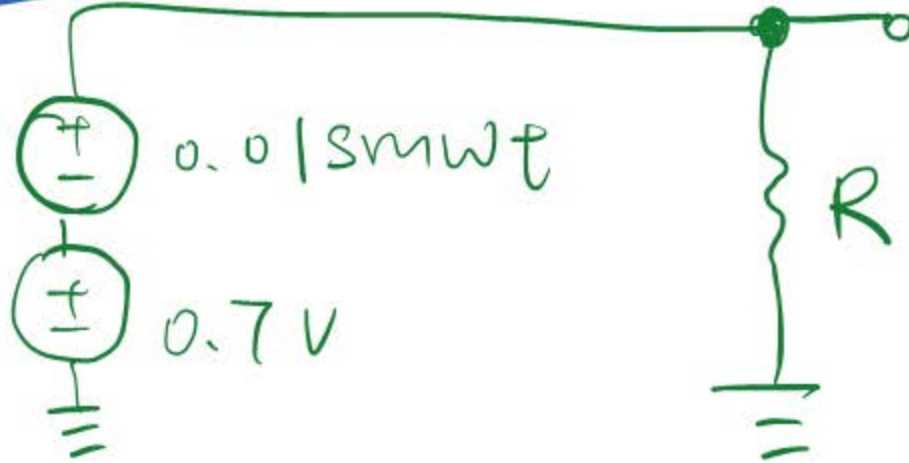



Steps for converting complete circuits to small-signal circuits

- 1° Draw the complete small-signal model of the transistors.
- 2° Finish the external wiring.
DC voltage \rightarrow short
DC current \rightarrow open

complete



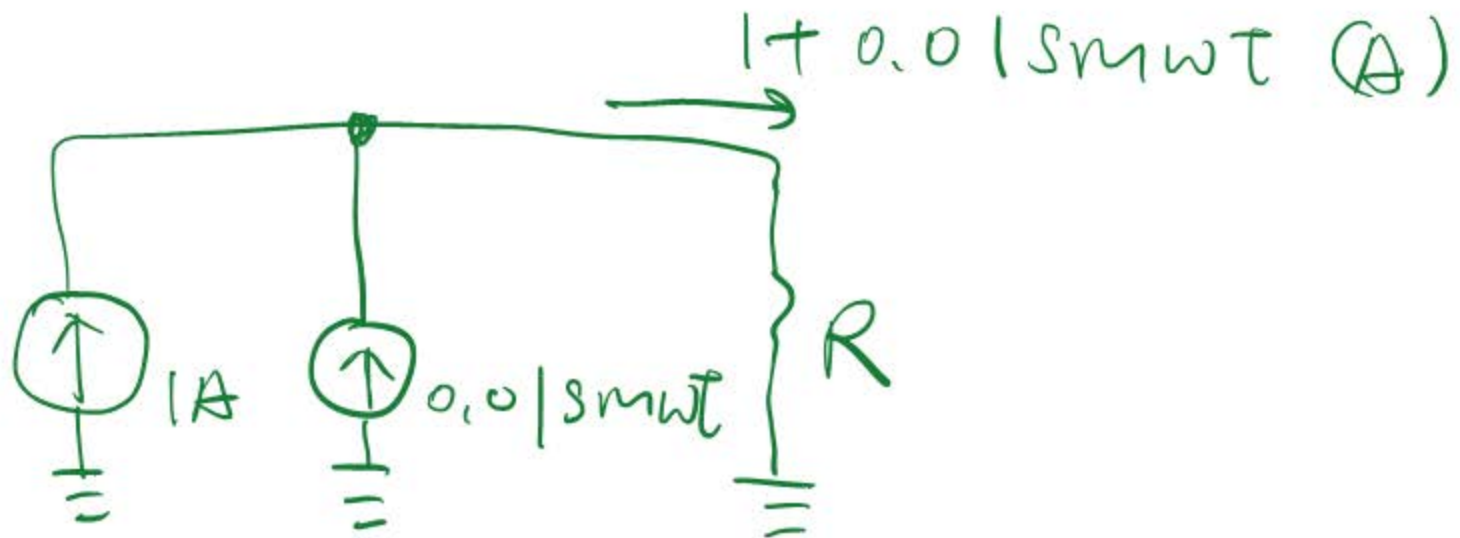
$$0.7 + 0.01 \text{ smwt} \quad (\text{V})$$




$$1 + 0.01 \text{ smwt} \quad (\text{A})$$

Small-signal

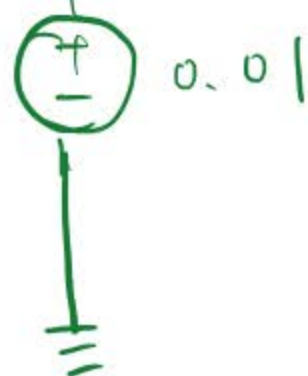


0.01 V

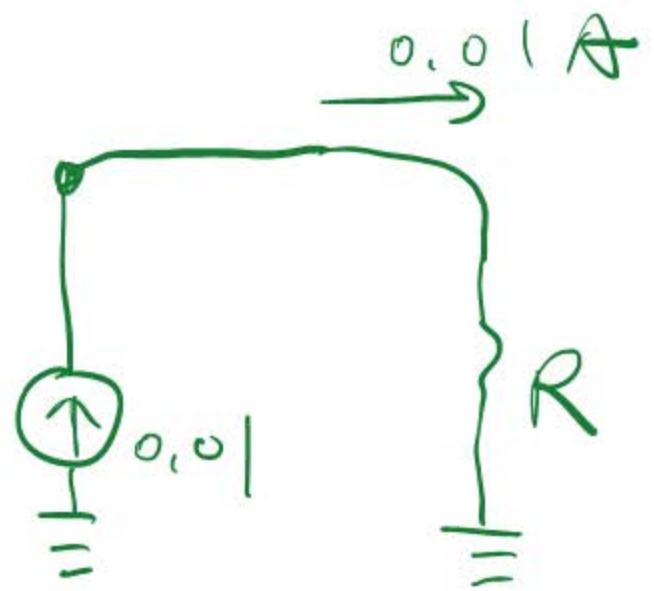

.model Qbreakn NPN IS=1e-18 BF=100 VAF=100

complete

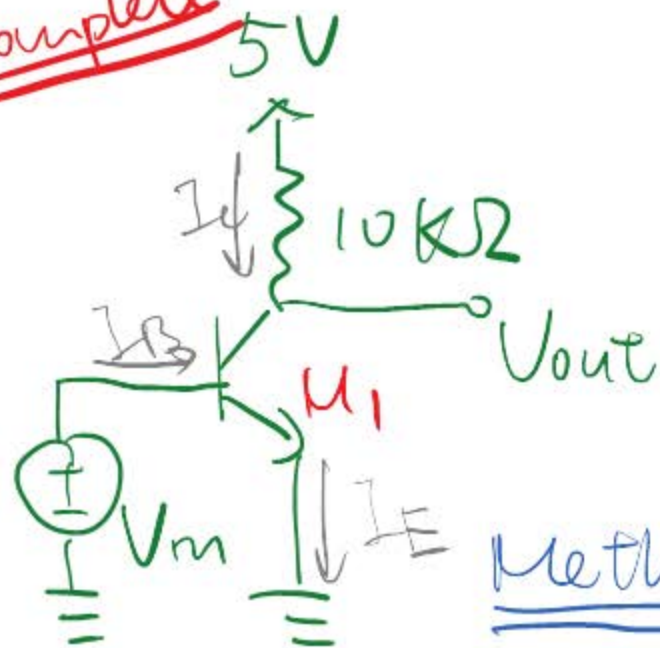

$$V_{in} = V_{IN} + V_m$$

$$= 0.7 + 0.018m(2\pi 60t)$$

$$V_{out} = V_{OUT} + V_{out} = ?$$

Method 1


Make sure
 $V_{OUT} \geq 0.7$

$$\begin{cases} 5 - (10k) I_c = V_{OUT} \\ I_c = (1 \times 10^{-18}) \left(e^{\frac{0.7}{0.026}} - 1 \right) \left(1 + \frac{V_{OUT}}{100} \right) \end{cases}$$

For getting the DC biasing condition

$$A_v = \frac{V_{out}}{V_m} = -g_{m1}(r_{o1} \parallel 10k)$$



$$0.01 g_{m1}$$

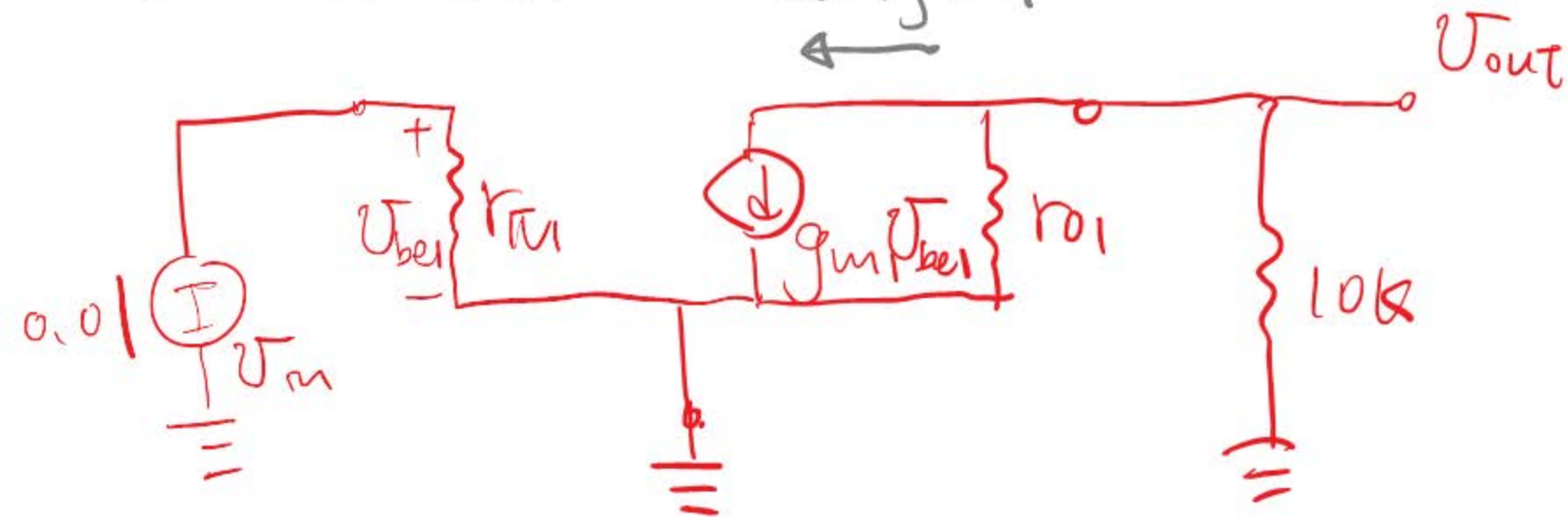


$$V_{out} = -(0.01 g_{m1})(r_{o1} \parallel 10k)$$

$$\begin{cases} g_{m1} = \frac{I_c}{0.026} \quad (A/V) \\ r_{o1} = \frac{100}{I_c} \quad (\Omega) \end{cases}$$

Amplitude
of V_{out} in
complete circuit.

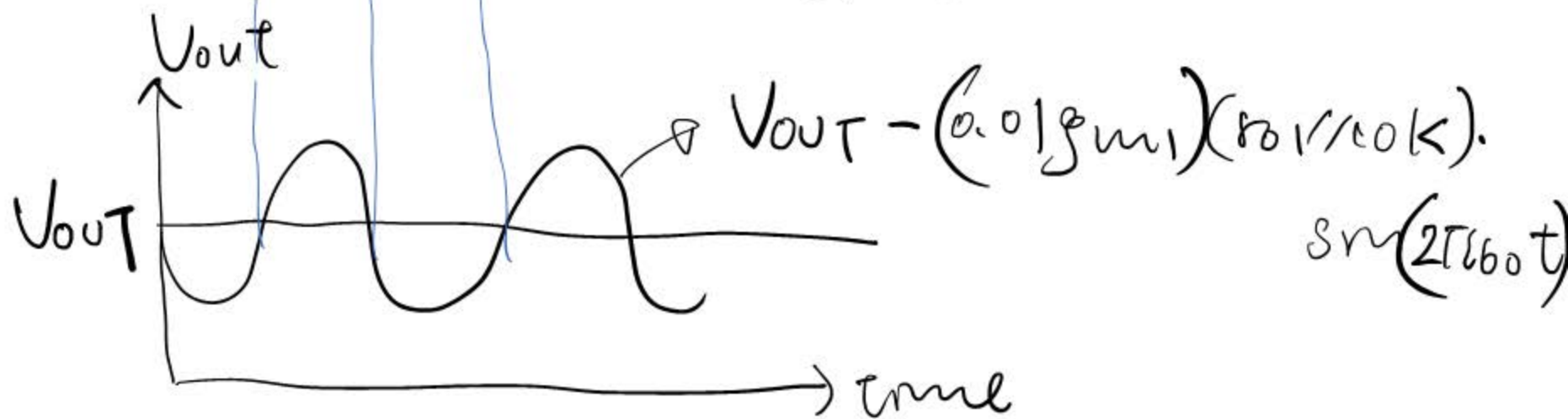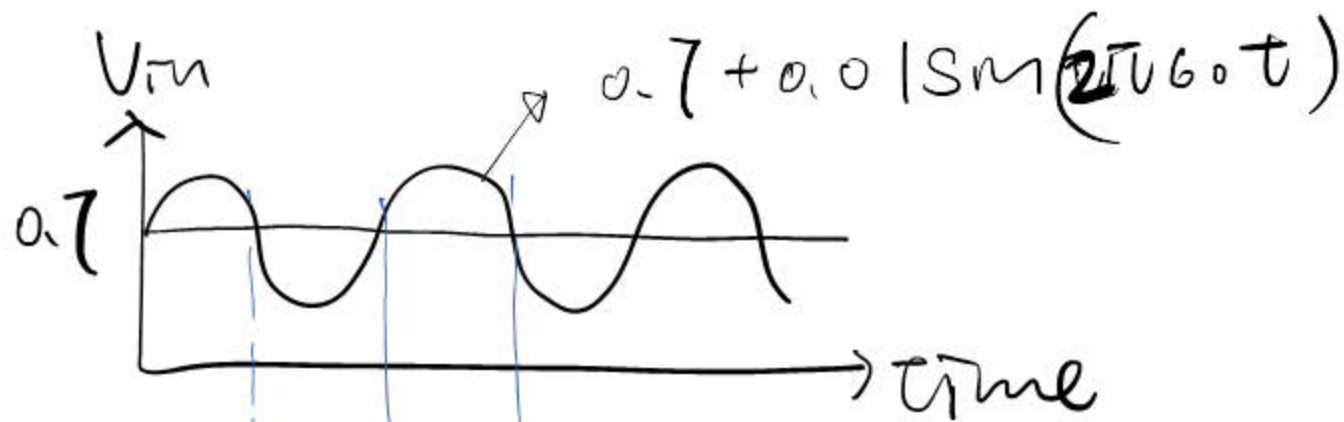

Method 2

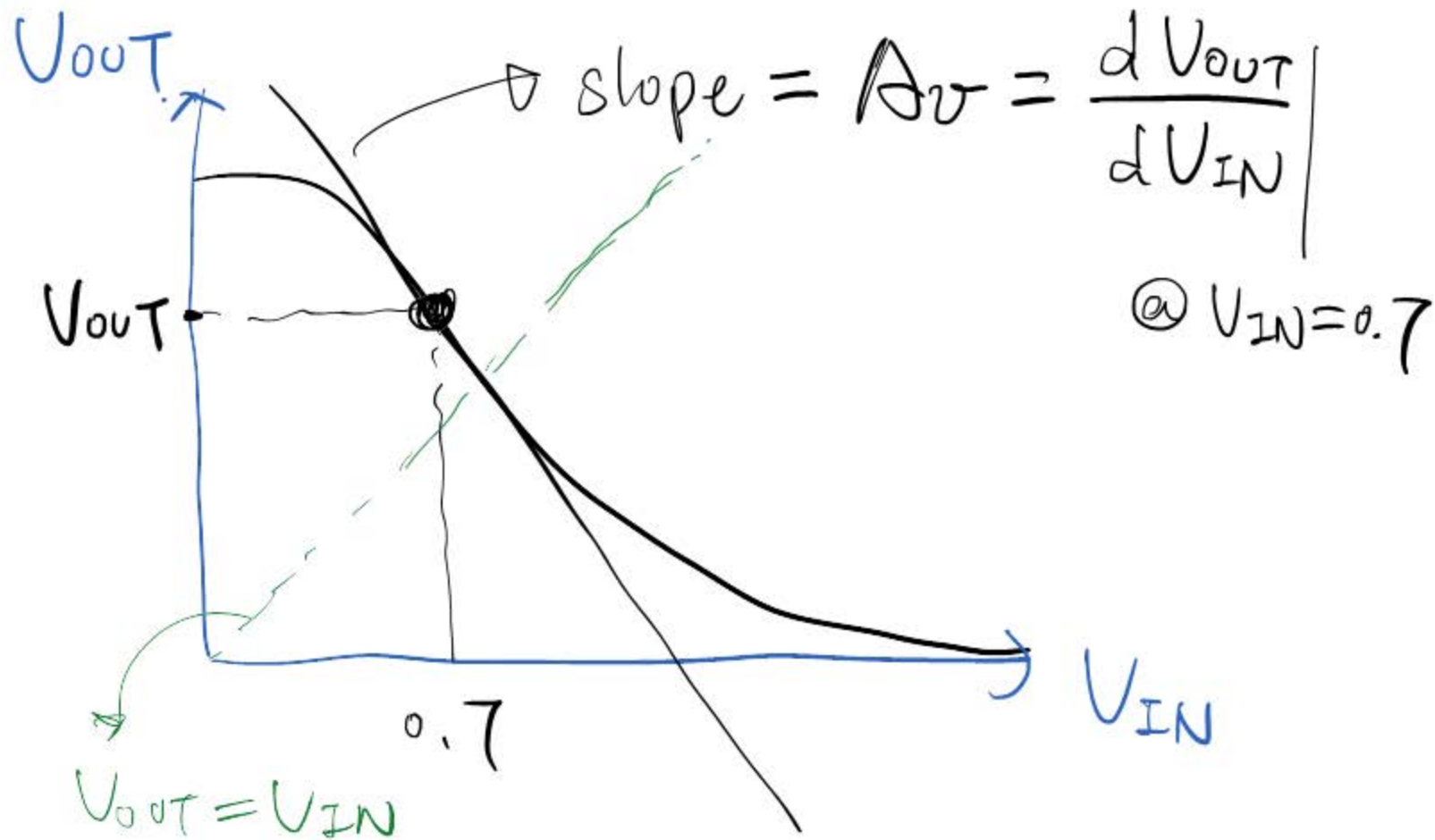

$$A_v = \frac{V_{out}}{V_{in}} = \frac{dV_{out}}{dV_{in}}$$

npn BJT Cross Section

