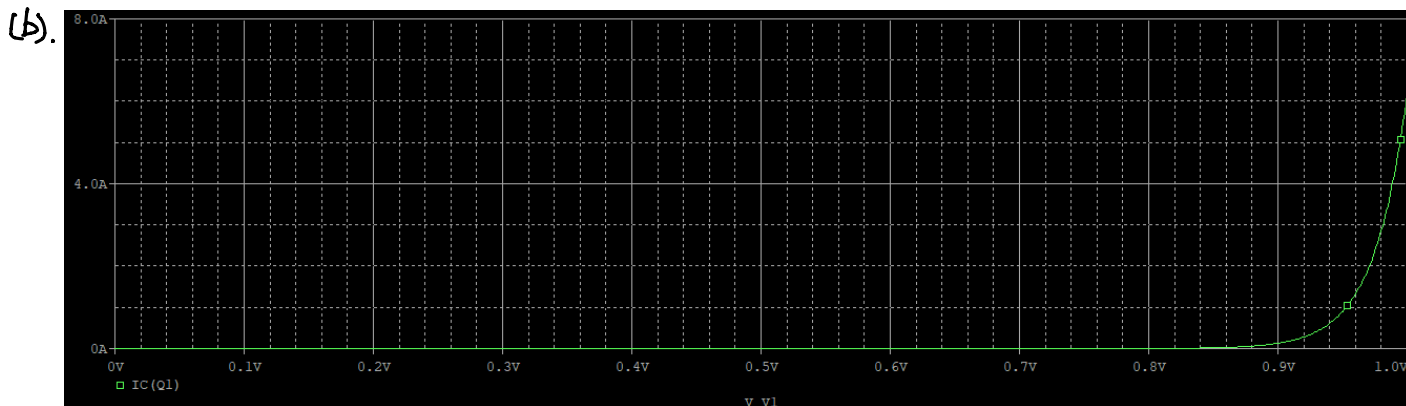



1.(a).

$$I_c = I_s \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AF}} \right) = 10^{-16} \cdot \left(e^{\frac{0.5}{0.026}} - 1 \right) \left(1 + \frac{1}{100} \right) = 2.27 \times 10^{-8} \text{ A}$$

$$g_m = \frac{I_c}{kT/q} = 8.73 \times 10^{-7} \text{ A/V} \quad r_o = \frac{V_{AF}}{I_c} = 4.40 \times 10^9 \Omega$$



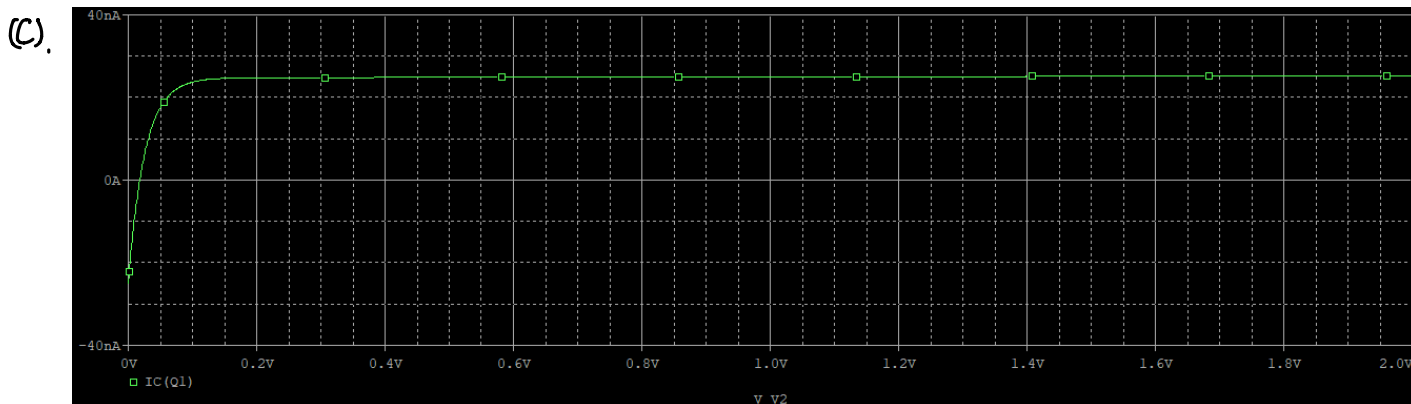From the plot, we have (0.498, 2.3154 × 10⁻⁸), (0.502, 2.7045 × 10⁻⁸).
The slope is 9.6775 × 10⁻⁷. It is close to the g_m in (a).



From the plot, we have (0.999, 2.4995 × 10⁻⁸), (1.001, 2.4996 × 10⁻⁸).

We have $\frac{1.001 - 0.999}{2.4996 \times 10^{-8} - 2.4995 \times 10^{-8}} = 2 \times 10^9$. Generally, the order of magnitudes are equal, the difference between 2 and 4.40 maybe because of the precision of the software. We may consider they are close.

$$2.(a). A_v = -g_m (R_c \parallel r_o)$$


$$\begin{cases} I_c = I_s \left(e^{\frac{q V_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{OUT}}{V_{AF}} \right) = 10^{-16} \left(e^{\frac{0.5}{0.026}} - 1 \right) \left(1 + \frac{V_{OUT}}{100} \right) \\ 3 - 5000 I_c = V_{OUT} \end{cases}$$

$$\Rightarrow I_c = 2.32 \times 10^{-8} \text{ A}$$

$$g_m = \frac{I_c}{0.026} = 8.91 \times 10^{-7} \text{ A/V}$$



$$r_o = \frac{100}{I_c} = 4.32 \times 10^9 \Omega$$
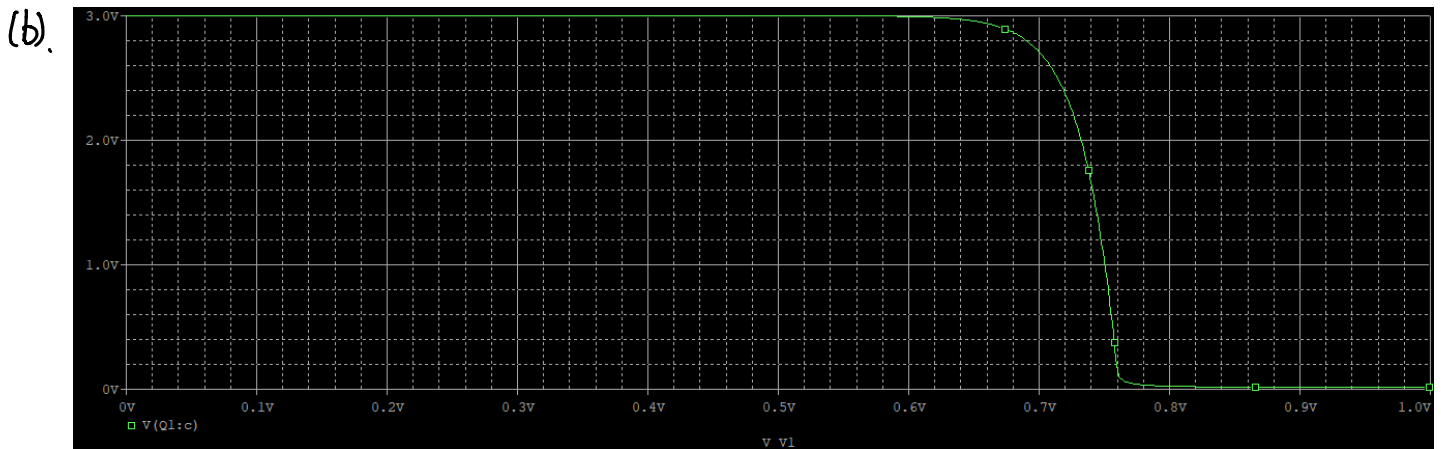
$$A_v = -8.91 \times 10^{-7} \times \left(\frac{5000 \times 4.32 \times 10^9}{5000 + 4.32 \times 10^9} \right) = -4.45 \times 10^{-3}$$



From the plot, we have (0.48, 2.9999) (0.52, 2.9997). The slope is -5×10^{-3} .
It is close to the voltage gain in (a).

(c).

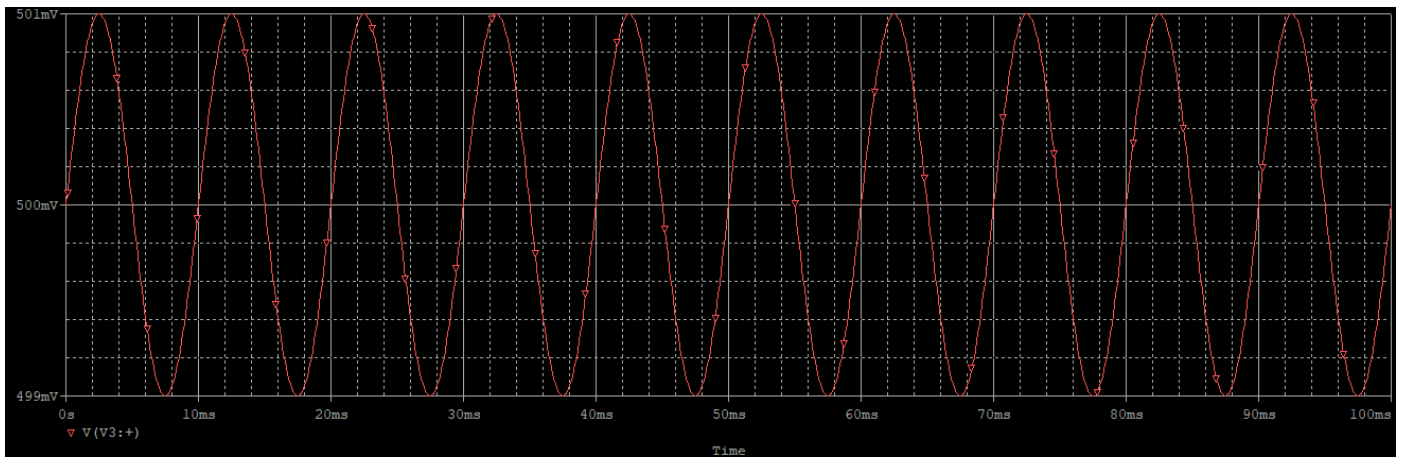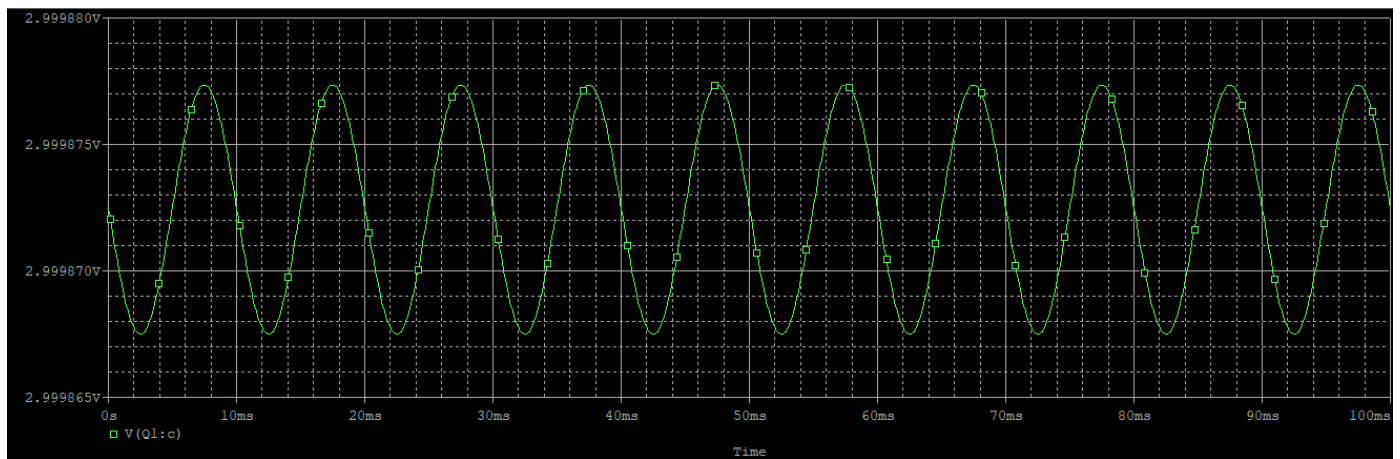

From the plot, we know that $|A_v| = \left| \frac{v_{out}}{v_{in}} \right| = \left| \frac{4.9285 \times 10^{-6}}{0.001} \right| = 4.9285 \times 10^{-3}$,
which is close to the voltage gain calculated in (a)