

Summer-2020 UM-SJTU JI Ve311 Final


Instructor: Dr. Chang-Ching Tu

Due: August 05, 2020 (Wednesday) in class

Note:

- (1) Please write your answer on A4- or Letter-size papers.
- (2) One A4- or Letter-size double-sided paper of notes is allowed.

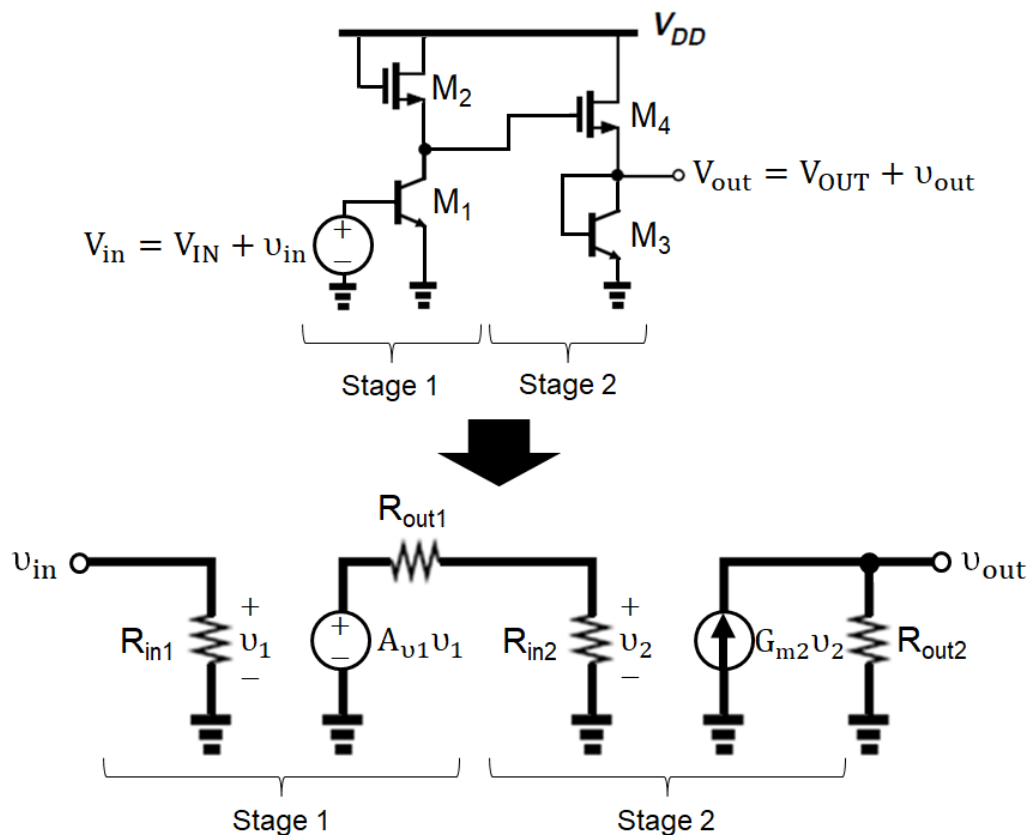
1. [Small-Signal Equivalent Circuit, 30%] Assume M_1 and M_3 operate in the forward-active region and M_2 and M_4 operate in the saturation region. **Take Early Effect, Channel-Length Modulation and Body Effect into consideration.** Derive the analytical expressions of R_{in1} [5%], R_{out1} [5%], A_{v1} [5%], R_{in2} [5%], R_{out2} [5%] and G_{m2} [5%].




2. [Common-Source with Diode-Connected Load, 30%] Assume $\lambda = \gamma = 0$.

A. [15%] $(W_{\text{drawn}}/L_{\text{drawn}})_1 = 100\mu\text{m}/2.18\mu\text{m}$ and $(W_{\text{drawn}}/L_{\text{drawn}})_2 = 1\mu\text{m}/5.16\mu\text{m}$. Draw the waveform of V_{out} .

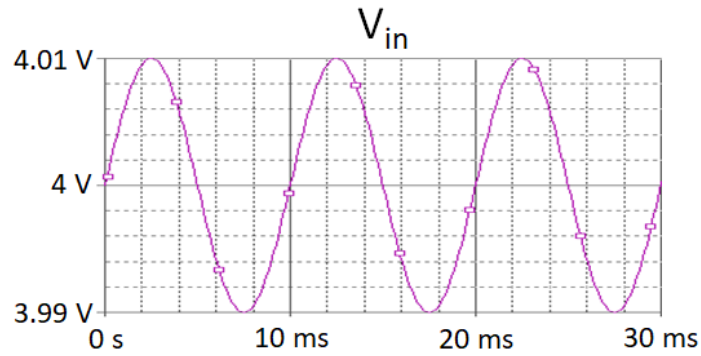
B. [15%] For circuit B, $(W_{\text{drawn}}/L_{\text{drawn}})_1 = (W_{\text{drawn}}/L_{\text{drawn}})_3 = 50\mu\text{m}/2.18\mu\text{m}$ and $(W_{\text{drawn}}/L_{\text{drawn}})_2 = 1\mu\text{m}/5.16\mu\text{m}$. Draw the waveform of V_{out} .



A

 

B

 

3. [Small-Signal Analysis, 21%] Assume all transistors operate in saturation. All answers in analytical expressions.

A. [7%] ($\lambda = 0$ and $\gamma = 0$) V_A , V_B and V_C are DC biasing voltages.


Derive the voltage gain, $A_v = \frac{v_{out}}{v_{in}}$.

B. [3% and 4%] ($\lambda \neq 0$ and $\gamma \neq 0$) I_{SS} is ideal current source. Derive the


voltage gains, $A_{v1} = \frac{v_{out1}}{v_{in}}$ and $A_{v2} = \frac{v_{out2}}{v_{in}}$.

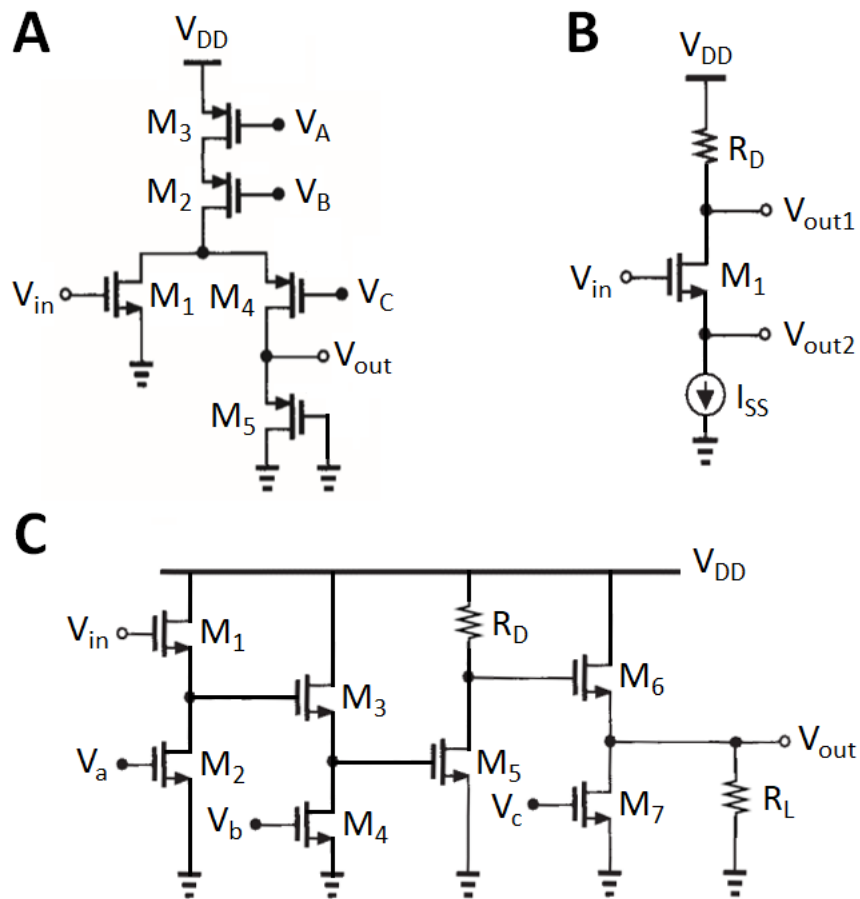C. [7%] ($\lambda = 0$ and $\gamma = 0$) V_a , V_b and V_c are DC biasing voltages.

Derive the voltage gain, $A_v = \frac{v_{out}}{v_{in}}$.



 4. [Diode-Connected Load, 9%, and Current Source Load, 10%] Assume $\lambda \neq 0$ and $\gamma \neq 0$. The size of M_1 is $W_{\text{drawn}}/L_{\text{drawn}} = 20 \mu\text{m}/2.16 \mu\text{m}$. Plot I_X versus V_X increasing from 0 V to 3 V.



NMOS Model

| | | | |
|---------------------|---------------------|----------------------|------------------------|
| LEVEL = 1 | VTO = 0.7 | GAMMA = 0.45 | PHI = 0.9 |
| NSUB = 9e+14 | LD = 0.08e-6 | UO = 350 | LAMBDA = 0.1 |
| TOX = 9e-9 | PB = 0.9 | CJ = 0.56e-3 | CJSW = 0.35e-11 |
| MJ = 0.45 | MJSW = 0.2 | CGDO = 0.4e-9 | JS = 1.0e-8 |

PMOS Model

| | | | |
|---------------------|---------------------|----------------------|------------------------|
| LEVEL = 1 | VTO = -0.8 | GAMMA = 0.4 | PHI = 0.8 |
| NSUB = 5e+14 | LD = 0.09e-6 | UO = 100 | LAMBDA = 0.2 |
| TOX = 9e-9 | PB = 0.9 | CJ = 0.94e-3 | CJSW = 0.32e-11 |
| MJ = 0.5 | MJSW = 0.3 | CGDO = 0.3e-9 | JS = 0.5e-8 |

VTO: threshold voltage with zero V_{SB} (unit: V)

GAMMA: body effect coefficient (unit: $V^{1/2}$)

PHI: $2\Phi_F$ (unit: V)

TOX: gate oxide thickness (unit: m)

NSUB: substrate doping (unit: cm^{-3})

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit: $cm^2/V/s$)

LAMBDA: channel-length modulation coefficient (unit: V^{-1})

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m²)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)

JS: source/drain leakage current per unit area (unit: A/m²)

Vacuum permittivity (ϵ_0) = 8.85×10^{-12} (F / m)

Silicon oxide dielectric constant (ϵ_r) = 3.9

In case you cannot upload your pdf file to Canvas, please email it or send WeChat photo to TA immediately. Thanks.

liuzuheng@sjtu.edu.cn

