
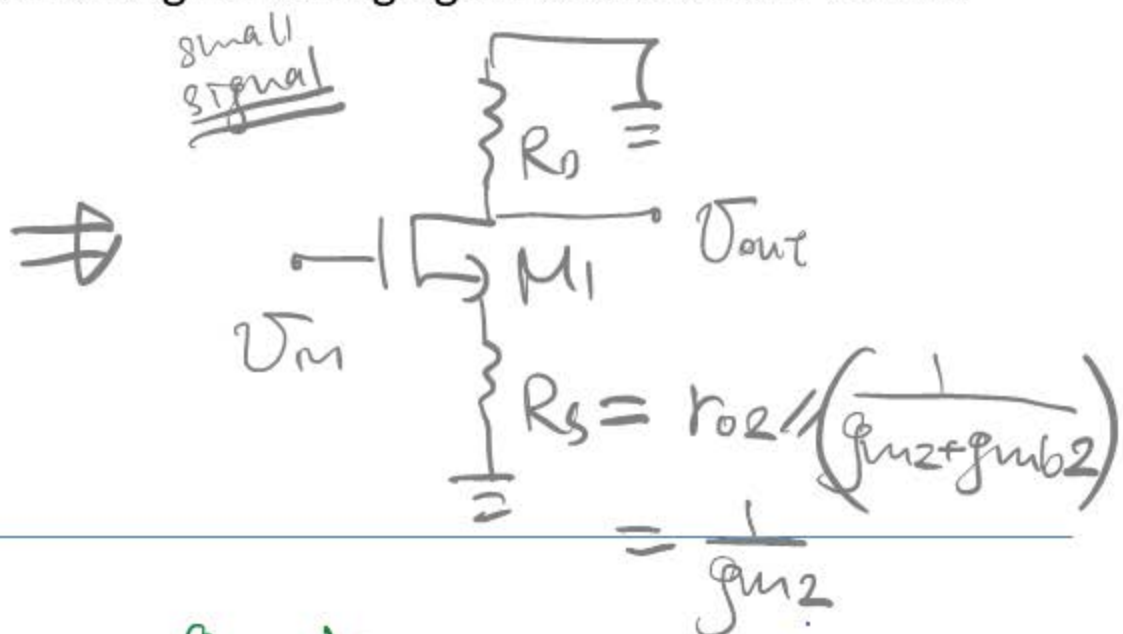

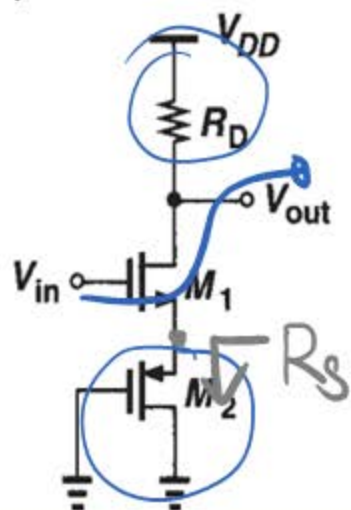
# Example

Assuming  $\lambda = \gamma = 0$ , calculate the small signal voltage gain of the circuit below.




Solution:

$$G_m = -\frac{1}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} = \frac{-g_{m1} r_{o1}}{R_S + r_{o1} + (g_{m1} + g_{mb1}) r_{o1} R_S}$$

$$R_{out} = R_D$$

$$A_v = G_m R_{out}$$
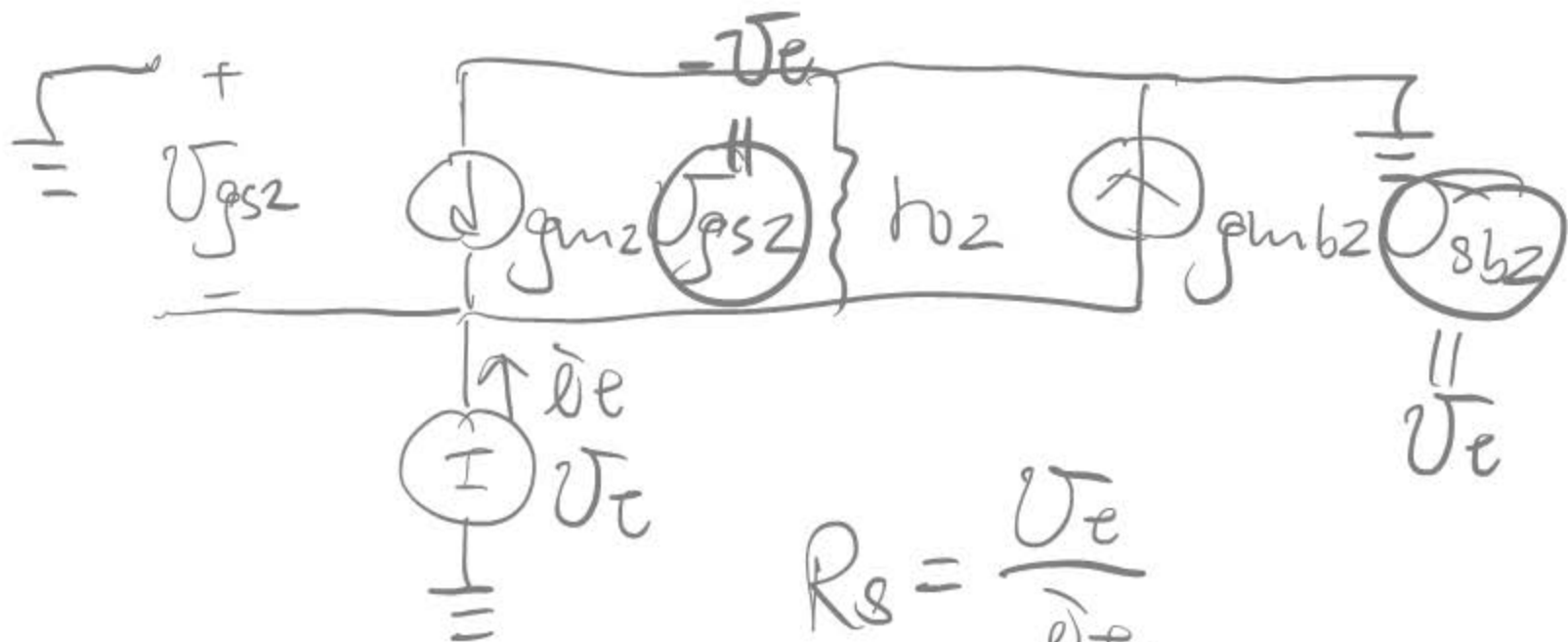
$$= \frac{-g_{m1} r_{o1}}{r_{o1} + g_{m1} r_{o1} R_S}$$




$$R_s = \frac{V_e}{v_e}$$

$$= r_{o2} \parallel \left( \frac{1}{g_{m2} + g_{mbs2}} \right)$$
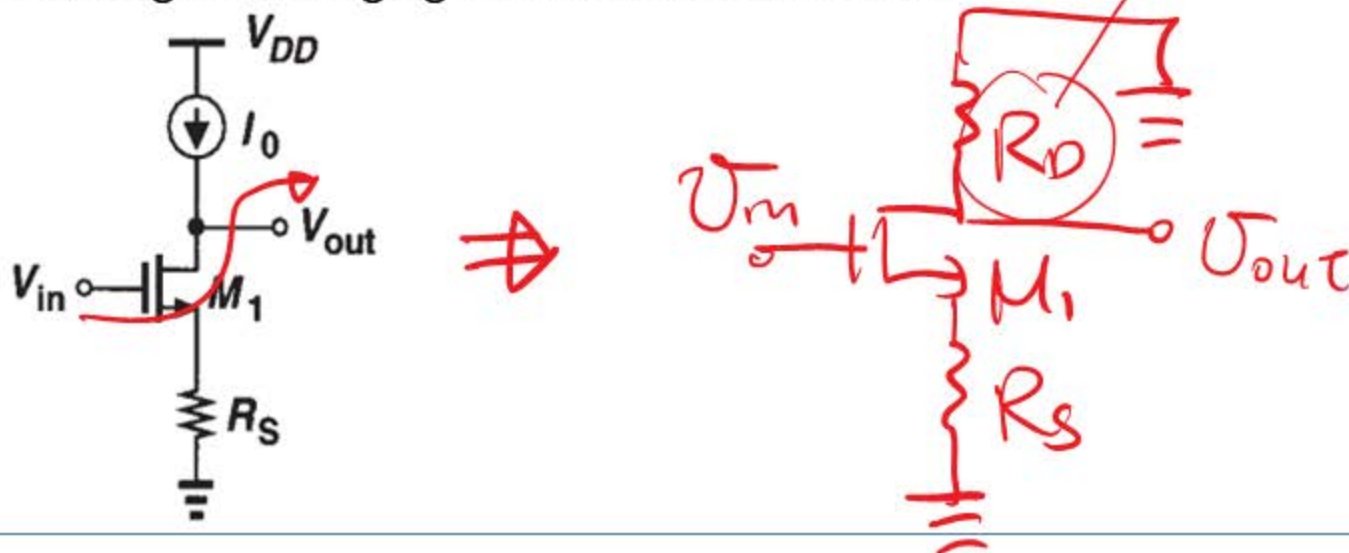
# Example

Calculate the small signal voltage gain of the circuit below.




Solution:

$$G_m = \frac{-g_{m1} r_{o1}}{r_{o1} + R_S + (g_{m1} + g_{mb1}) r_{o1} R_S}$$

$$R_{out} = r_{o1} + R_S + (g_{m1} + g_{mb1}) r_{o1} R_S$$

$$A_v = G_m R_{out} = -g_{m1} r_{o1}$$

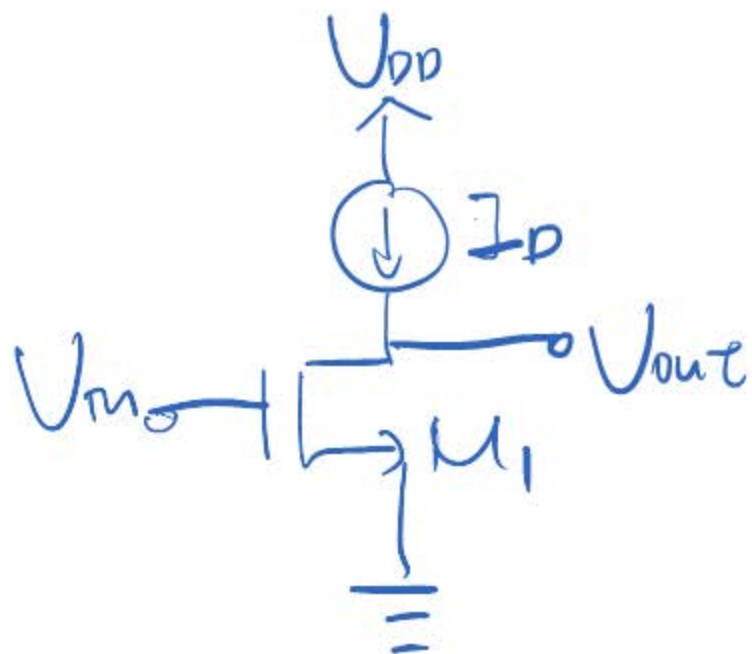
- $I_0$  is ideal current source  $\rightarrow$  Voltage across  $R_S$  is constant  $\rightarrow M_1$  source shorted to ground
- $R_D$  replaced by current source  $\rightarrow$  Nonlinearity issue arises again



$$V_{SB1} = 0$$

$$V_{sb1} = 0$$



$$A_v = -g_{m1} r_{o1}$$

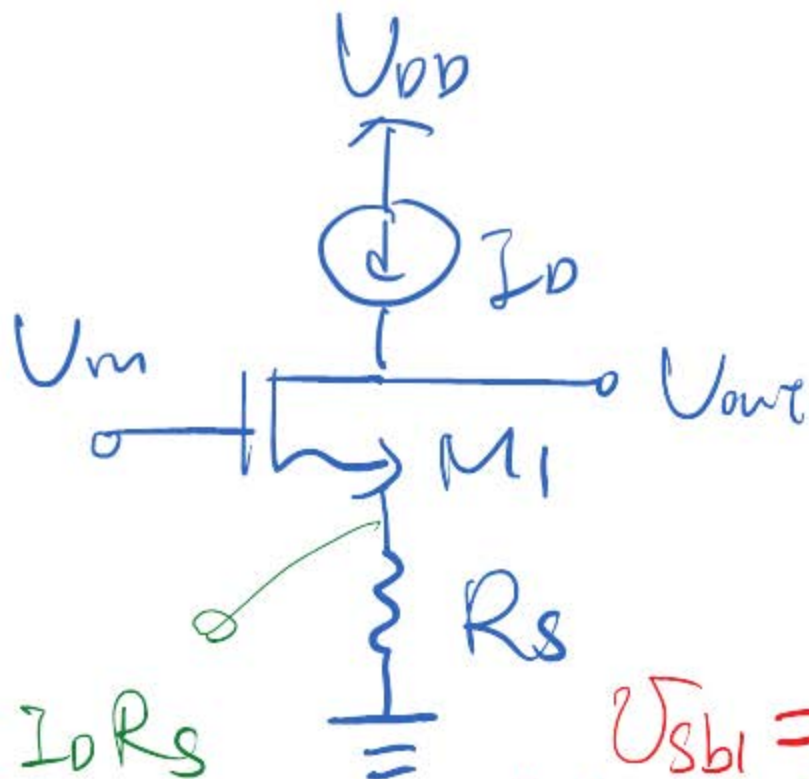

$$V_{sb1} = 0$$


$$V_{SB1} = I_D R_s$$

$$A_v = -g_{m1} r_{o1}$$

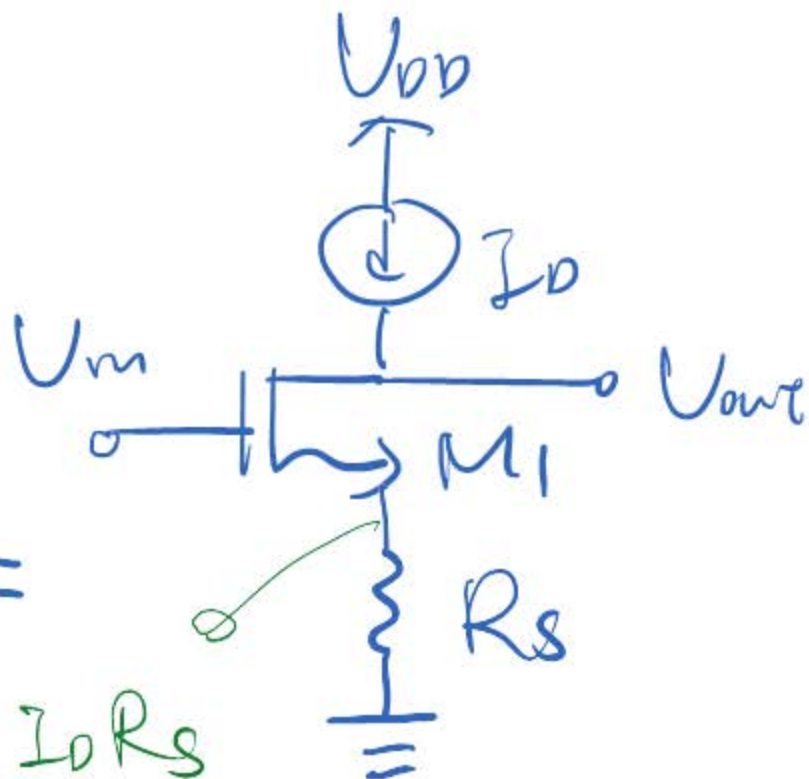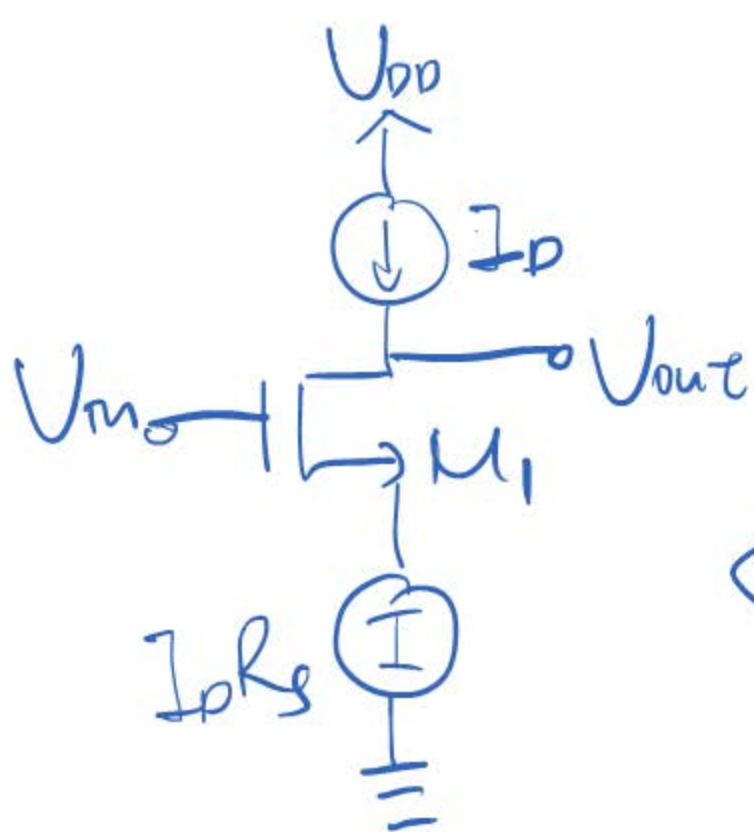

$$A_v = -g_{m1} I_{D1}$$

Example

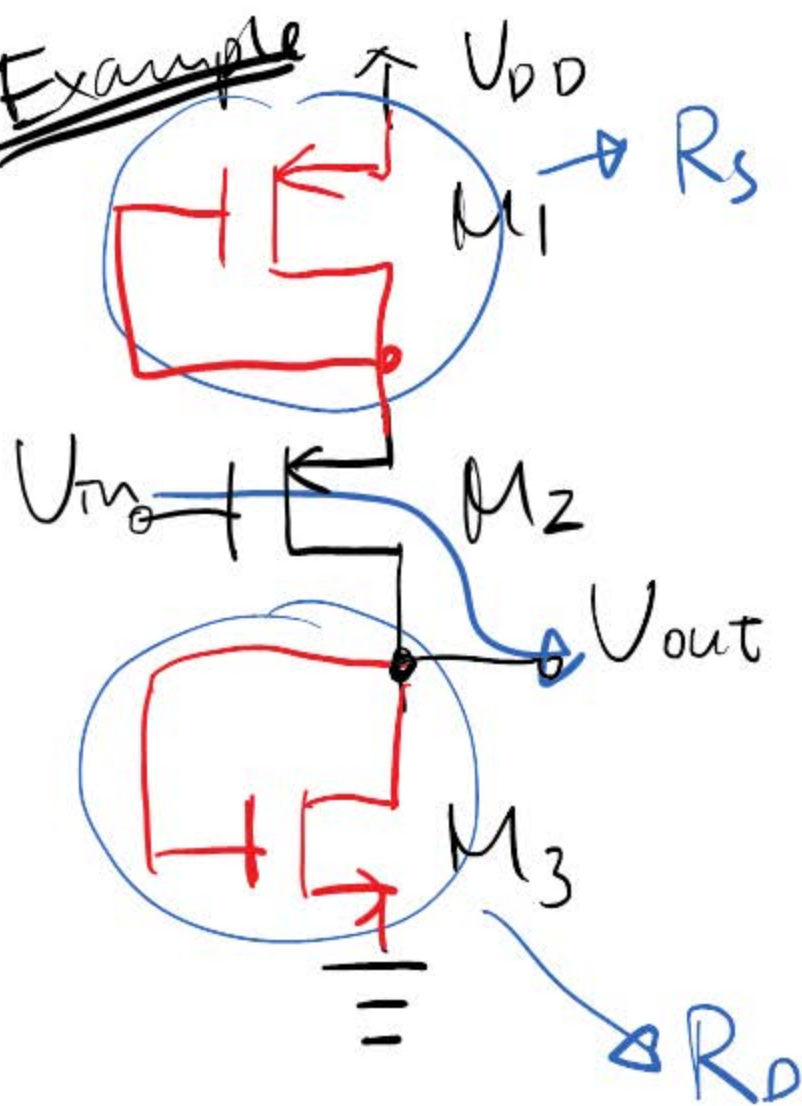

$$G_m = ? \quad R_{out} = ?$$


$$\lambda = 0, r \neq 0$$

$$R_s = r_{o1} \parallel \frac{1}{g_{m1}} = \frac{1}{g_{m1}}$$

$$R_D = \frac{1}{g_{m3}}$$
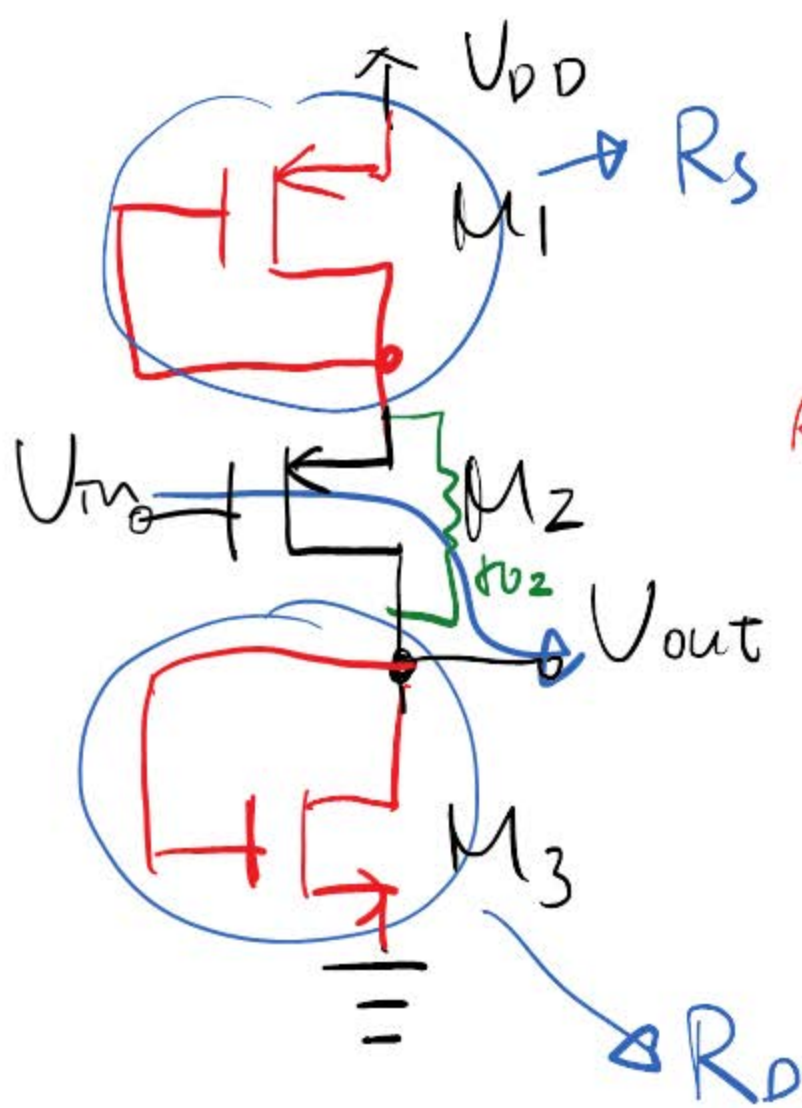
$$G_m = \frac{-g_{m2} r_{o2}}{r_{o2} + R_s + (g_{m2} + g_{mb2}) r_{o2} R_s} = \frac{-g_{m2}}{1 + (g_{m2} + g_{mb2}) R_s}$$





$$G_m = ? \quad R_{out} = ?$$

$$\lambda = 0, \quad r \neq 0$$

Assume all transistors in sat.

$$R_S = r_{o1} \parallel \frac{1}{g_{m1}} = \frac{1}{g_{m1}}$$



$$R_D = \frac{1}{g_{m3}}$$

$$R_{out} = R_D \parallel \left( r_{o2} + R_S + \overbrace{\left( g_{m2} + g_{mb2} \right) r_{o2} R_S}^{\text{mirror gain of } M_2} \right) = \frac{1}{g_{m3}}$$



Common-Draft

Source Follower (Buffer)



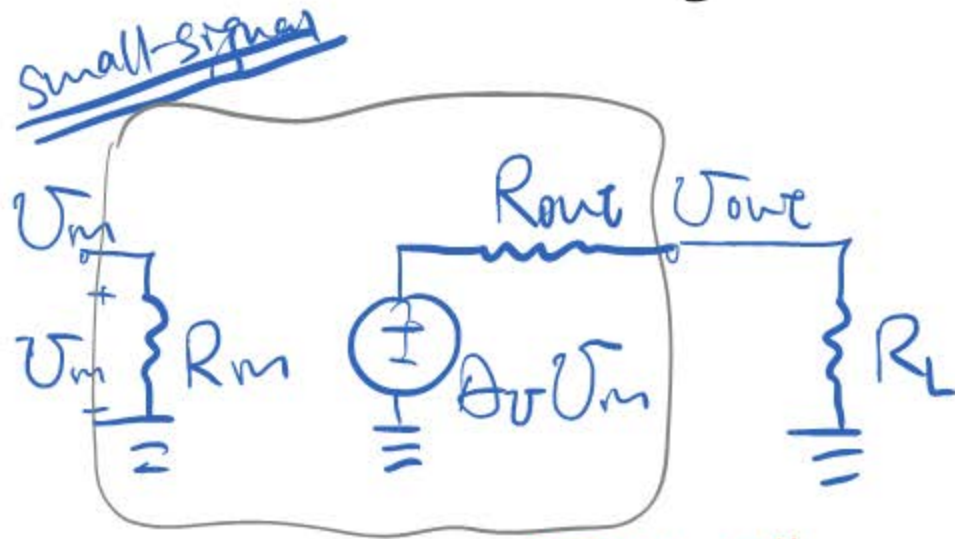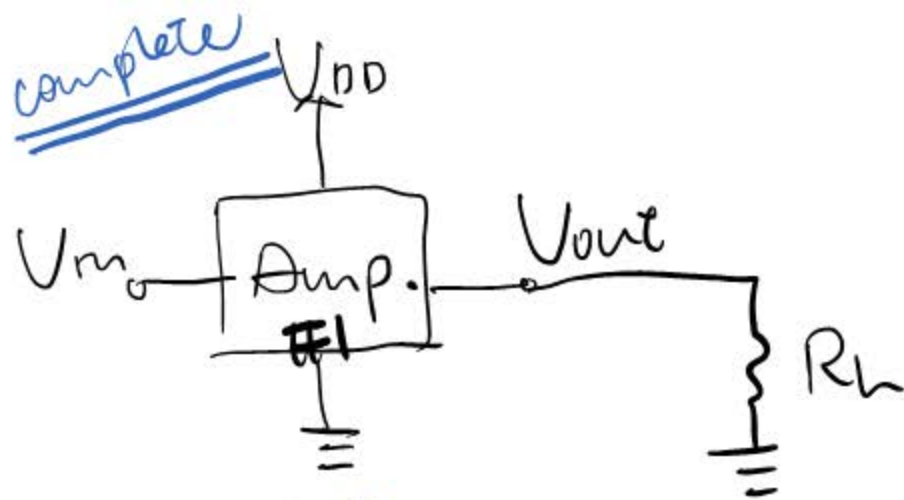

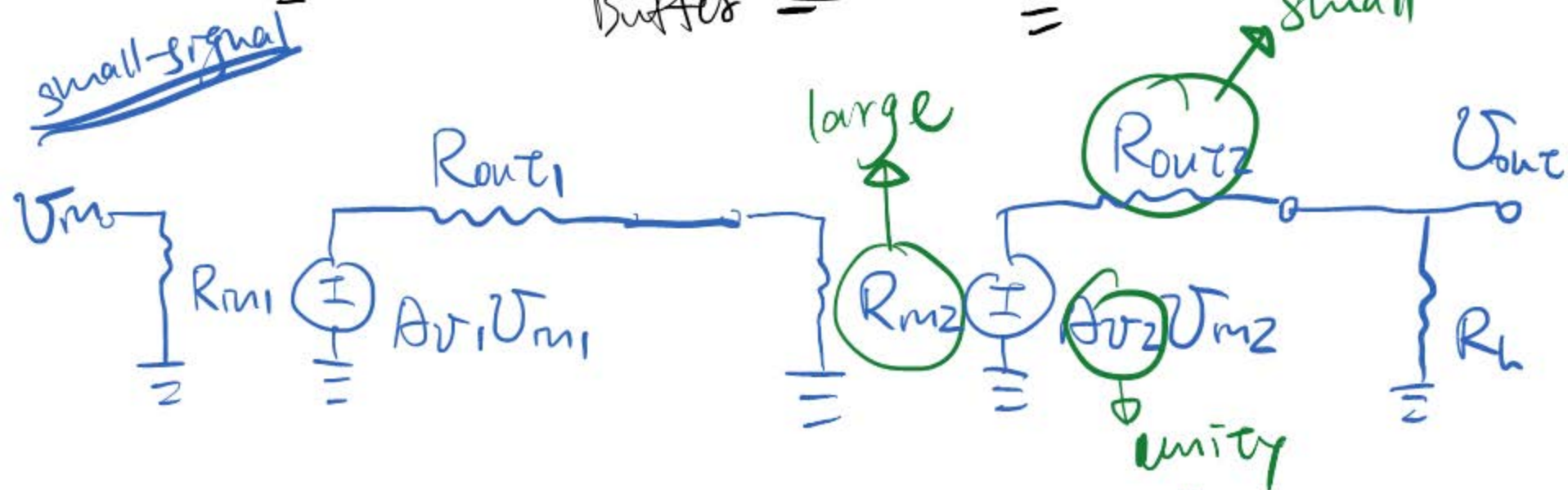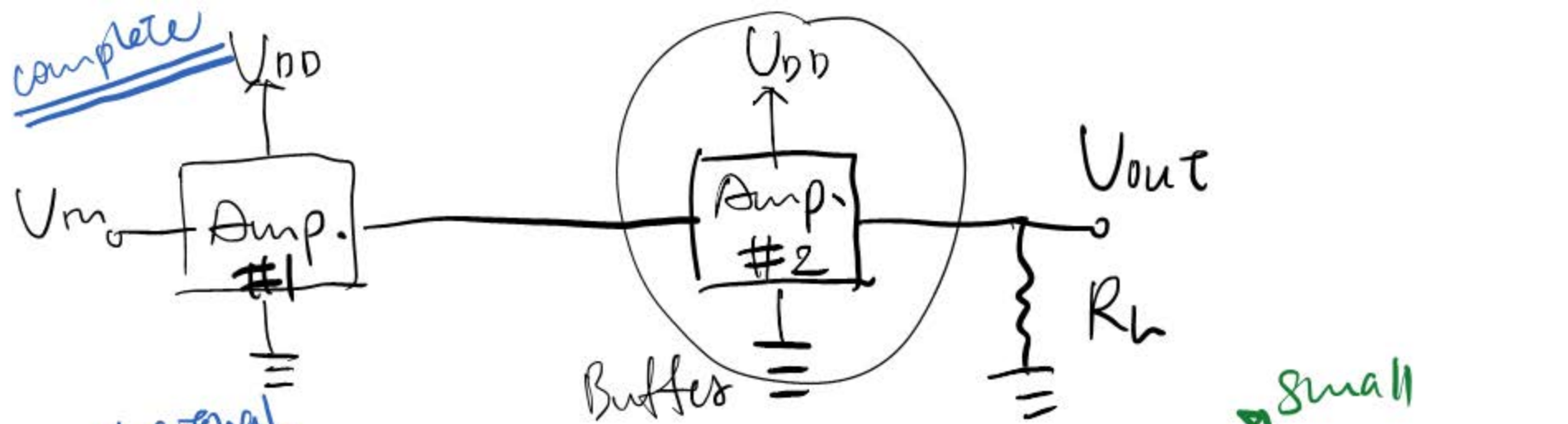
$$\frac{V_{out}}{V_m} = A_v \cdot \frac{\overset{\text{small}}{R_L}}{\underset{\text{large}}{R_{out} + R_L}} \Rightarrow A_v \text{ consumed by the factor } \frac{R_L}{R_{out} + R_L}$$



$$\frac{V_{out}}{V_{in}} = A_{v1} \frac{R_{m2}}{\underbrace{R_{out1} + R_{m2}}_{\text{large}}} A_{v2} \frac{\underbrace{R_L}_{\text{small}}}{R_{out2} + R_L}$$


# Ideal Amplifier

Voltage Amp.

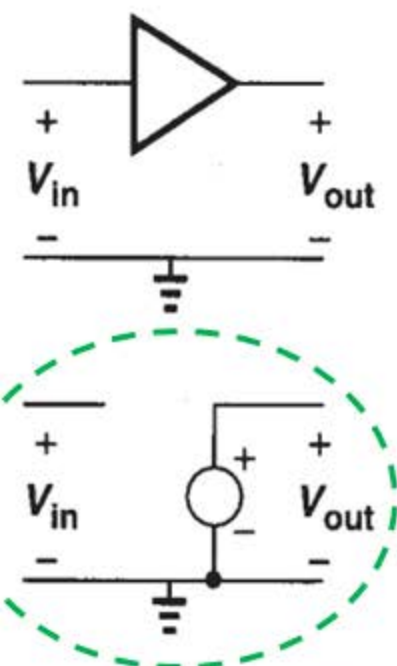


CS + Source Follower


Transimpedance Amp.

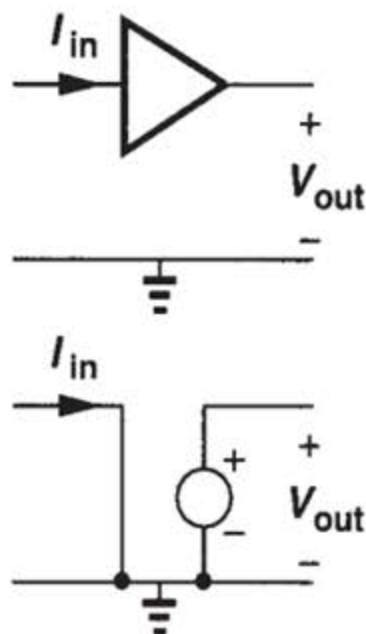


Transconductance Amp.

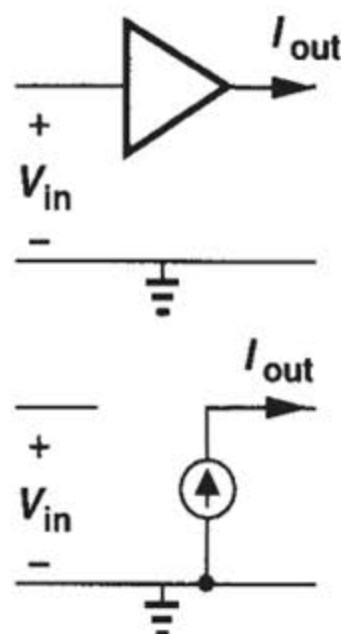

Current Amp.

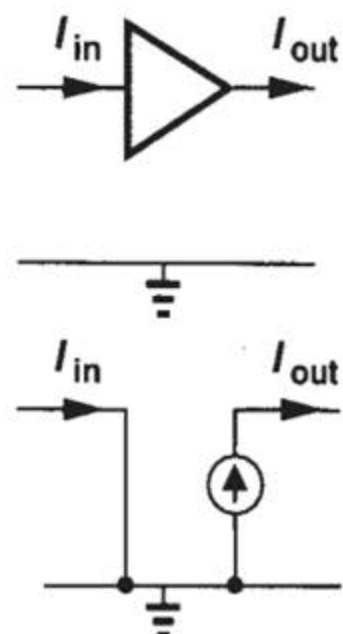

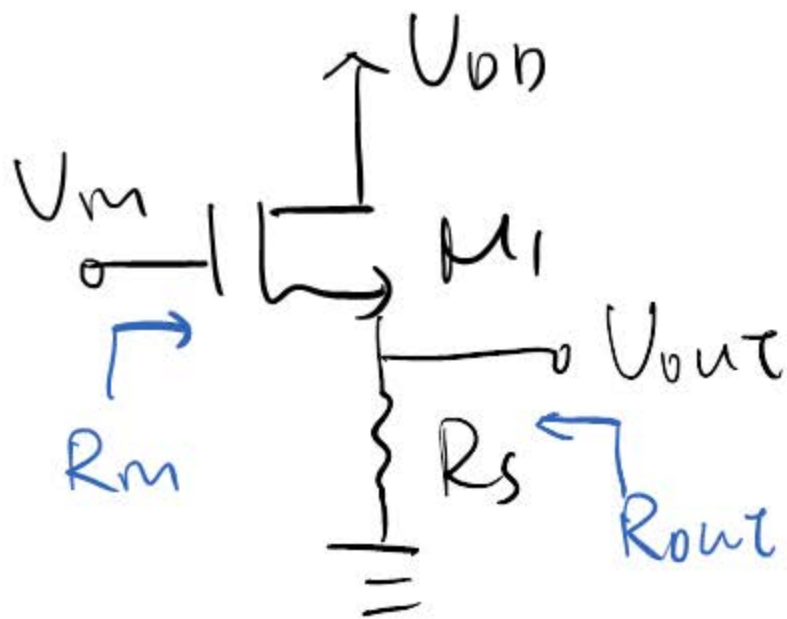
- For driving a low impedance load, source follower, as a buffer, provides **no gain** but **large input impedance** and **low output impedance**.




Small-Signal

$$R_m = \infty$$
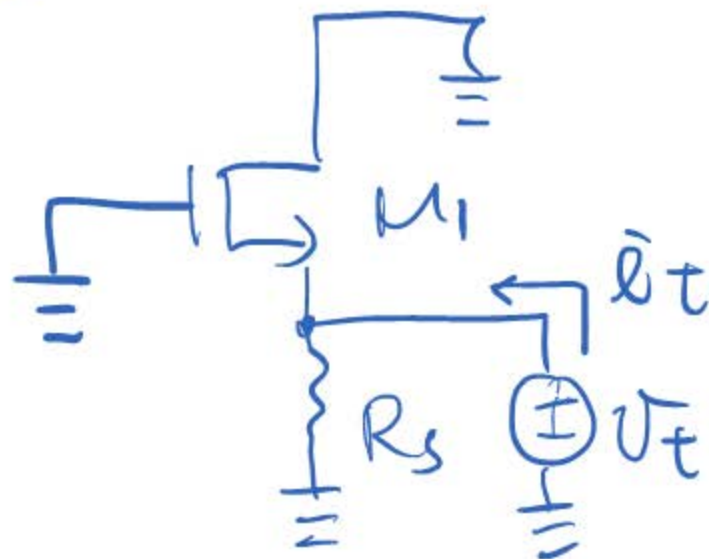
$$R_{out} = R_s \parallel r_{o1} \parallel \left( \frac{1}{g_{m1} + g_{mb1}} \right)$$



$$R_{out} = \frac{V_t}{\hat{i}_t}$$

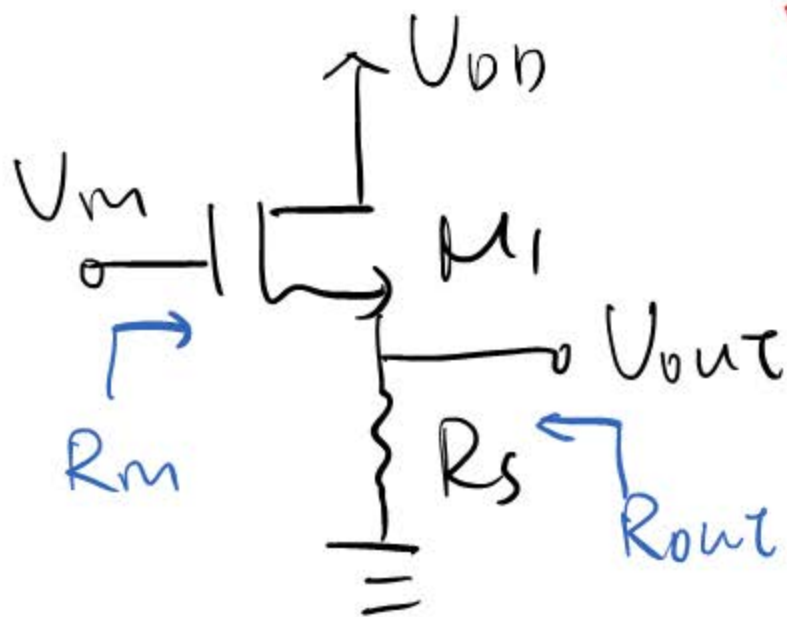

$$\lambda \neq 0, r \neq 0$$


$$R_m = \infty$$

$$R_{out} = R_S \parallel r_{o1} \parallel \left( \frac{1}{g_{m1} + g_{mb1}} \right)$$


$$A_v = \frac{V_{out}}{V_m}$$

Small-Signal
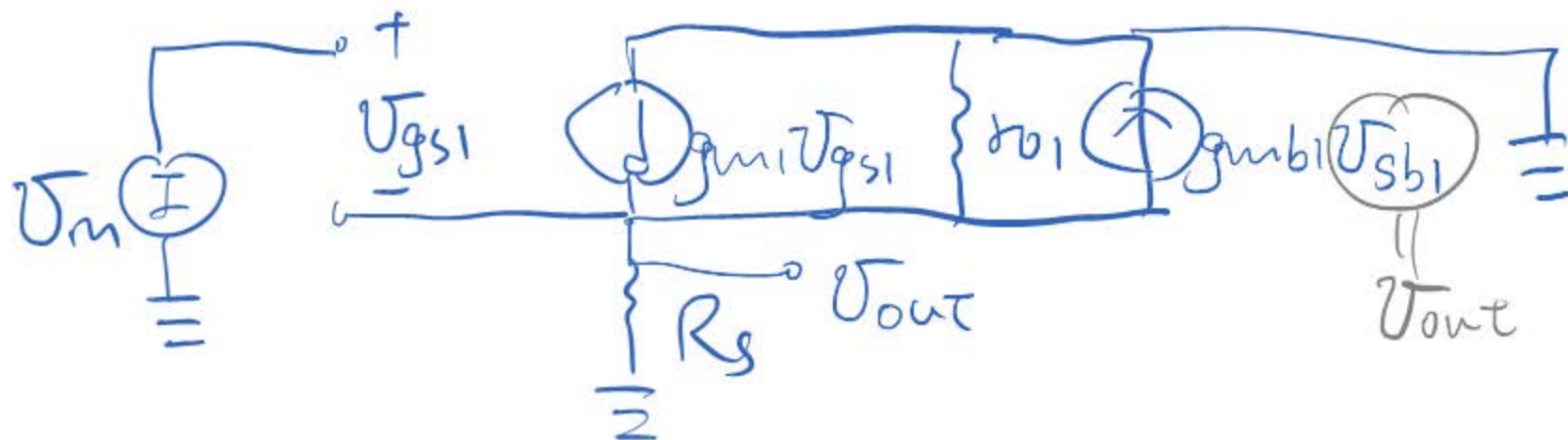
$$\frac{V_{out}}{R_S} + (V_{out} - V_m)g_{m1} + \frac{V_{out}}{r_{o1}} + g_{mb1}V_{out} = 0$$





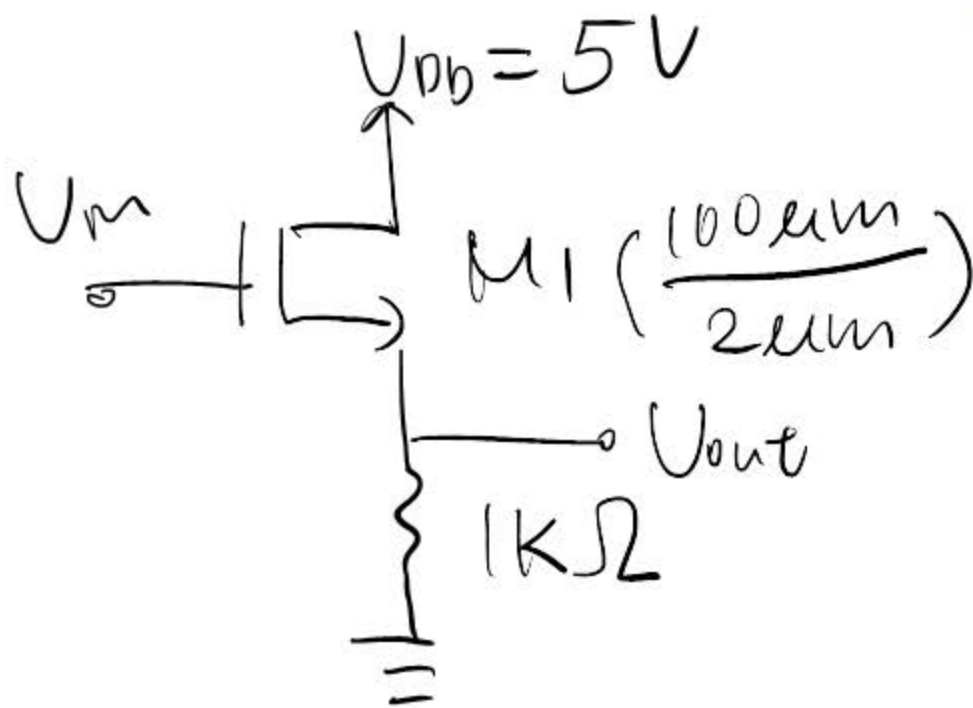

$$\lambda \neq 0, r \neq 0$$

$$V_{OUT} = ?$$

DC biasing analysis.

$M1$  must be in sat.

$$\frac{V_{OUT}}{1k} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L_{eff}} \right) (3 - V_{OUT} - V_{TH})^2$$

$$V_m = 3 + 0.0018m(2\pi 100t)$$

$$V_{out} = ?$$

$$(3 - V_{OUT} - V_{TH})^2$$

$$[1 + \lambda(5 - V_{out})]$$





# Source Follower

## DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

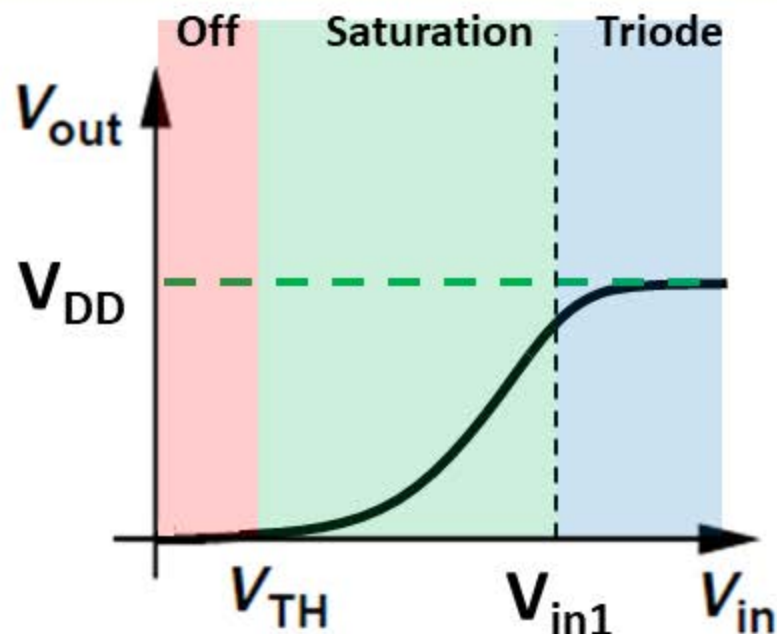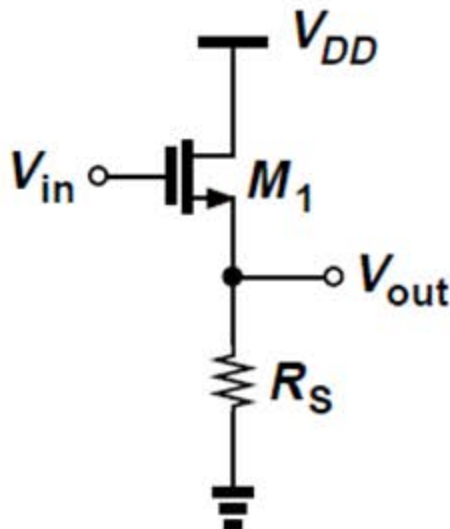

- $V_{in} < V_{TH} \rightarrow M_1$  Off

$$V_{out} = 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$  in Saturation

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

- $V_{in} > V_{in1} \rightarrow M_1$  in Triode

$$R_S \mu_n C_{ox} \frac{W}{L_{eff}} \left[ (V_{in} - V_{out} - V_{TH})(V_{DD} - V_{out}) - \frac{1}{2} (V_{DD} - V_{out})^2 \right] = V_{out}$$

$$\begin{aligned} V_{DD} - V_{out} &= V_{in1} - V_{out} - V_{TH} \\ \rightarrow V_{in1} &= V_{DD} + V_{TH} \end{aligned}$$

# Source Follower

## DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$  in Saturation

$$V_{out} = V_{SB}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{out} - V_{TH}) \left( 1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$$R_S \underbrace{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})}_{= gm} \left( 1 - \frac{\partial V_{out}}{\partial V_{in}} - \underbrace{\frac{\partial V_{TH}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}}}_{\substack{+V_{TH} \\ +V_{SB}}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$$\eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$A_v = \frac{gm R_S}{1 + gm R_S (1 + \eta)} = \frac{gm R_S}{1 + (gm + gmb) R_S} \approx \frac{1}{1 + \eta}$$


$$\text{If } (gm + gmb) R_S \gg 1$$

# Source Follower

## Small-signal Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

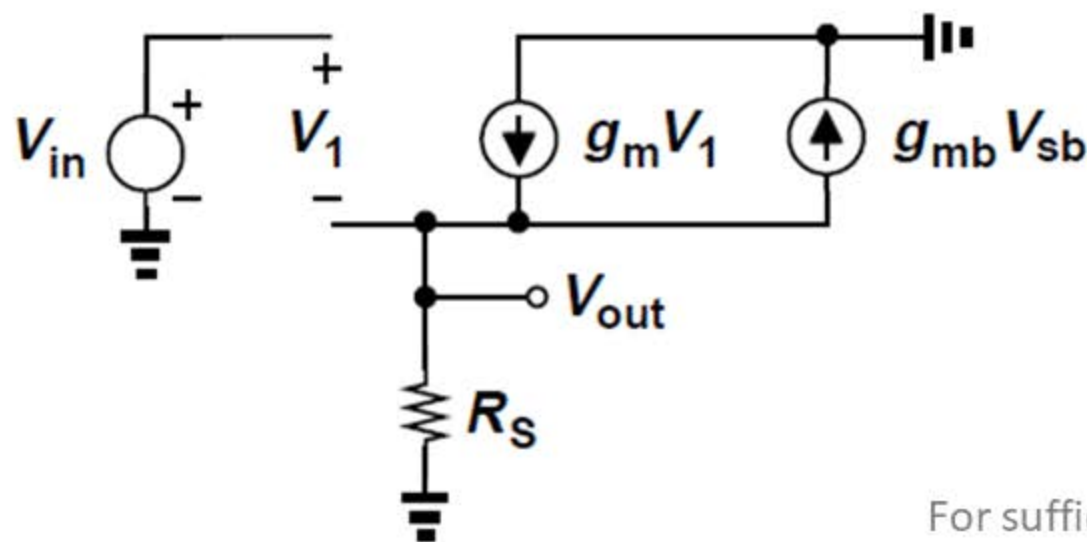


$$G_m = g_m$$

$$R_{out} = R_S \parallel \left( \frac{1}{g_m + g_{mb}} \right)$$

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{1}{1 + \eta}$$

$$\text{If } (g_m + g_{mb}) R_S \gg 1$$

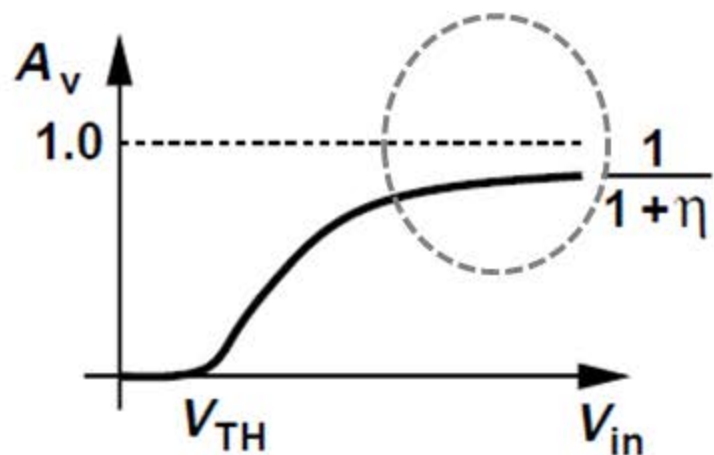For sufficiently large  $V_{in}$ ,  $I_D$  and thus  $g_m$ .




# Source Follower

## Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

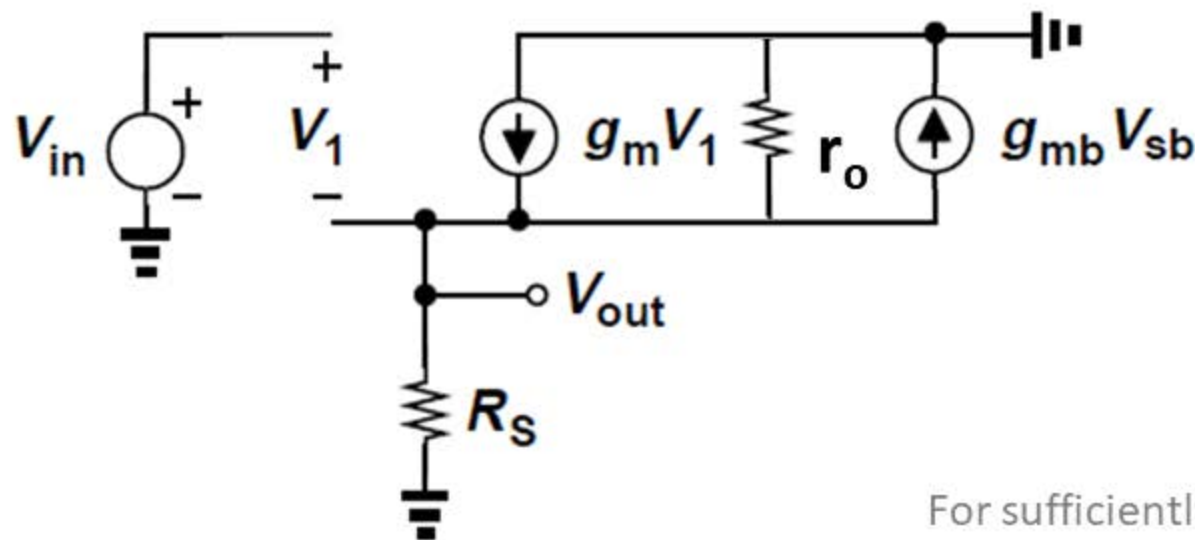


$$G_m = g_m$$

$$R_{out} = r_o \parallel R_S \parallel \left( \frac{1}{g_m + g_{mb}} \right)$$

$$A_v = \frac{g_m r_o R_S}{r_o + R_S + (g_m + g_{mb}) r_o R_S} \approx \frac{1}{1 + \eta}$$

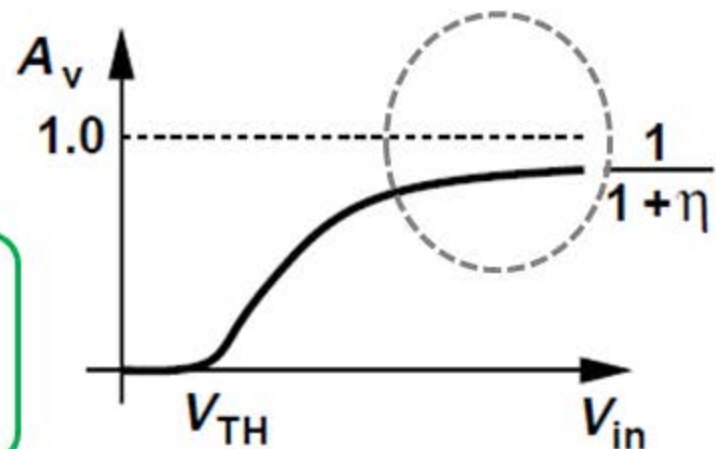For sufficiently large  $V_{in}$ ,  $I_D$  and thus  $g_m$ .



If  $(g_m + g_{mb}) r_o R_S \gg r_o$  and  $R_S$