



# JOINT INSTITUTE

## 交大密西根学院

Bipolar  
Junction  
Transistors.

### BJT and BJT Circuit


Ve311 Electronic Circuits (Fall 2020)

Dr. Chang-Ching Tu

# BJT (Before Contact)

## Emitter

n-type

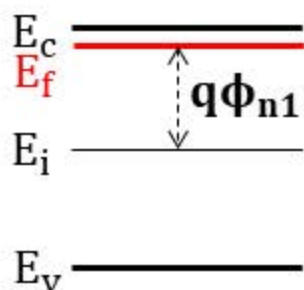


*p concentration*

$$n \cong N_{d1} = n_i e^{\frac{q\phi_{n1}}{kT}}$$

$$p \cong \frac{n_i^2}{N_{d1}} = n_i e^{\frac{-q\phi_{n1}}{kT}}$$

## Base

p-type

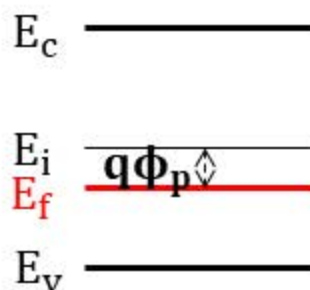


*n concentration*

$$p \cong N_a = n_i e^{\frac{q\phi_p}{kT}}$$

$$n \cong \frac{n_i^2}{N_a} = n_i e^{\frac{-q\phi_p}{kT}}$$

## Collector

n-type

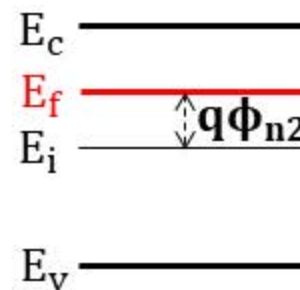


$$n \cong N_{d2} = n_i e^{\frac{q\phi_{n2}}{kT}}$$

$$p \cong \frac{n_i^2}{N_{d2}} = n_i e^{\frac{-q\phi_{n2}}{kT}}$$

$$N_{d1} \gg N_a$$

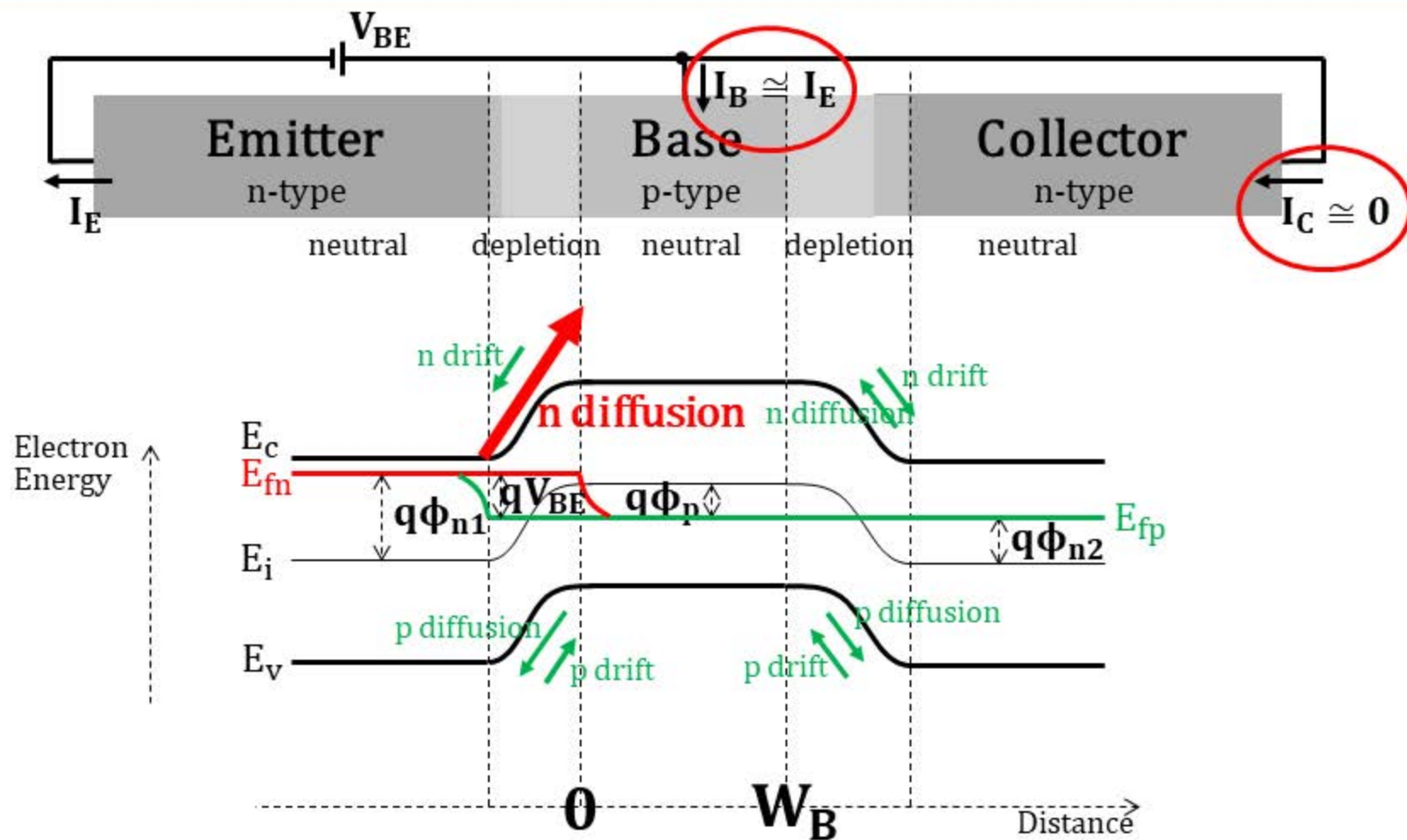
$$V_{BE} > 0 \text{ and } V_{CB} = 0 \text{ (} W_B \text{ long)}$$



$$N_{d1} \gg N_a$$

The n (electron) diffusion is much larger than the p (hole) diffusion at the Base-Emitter junction.

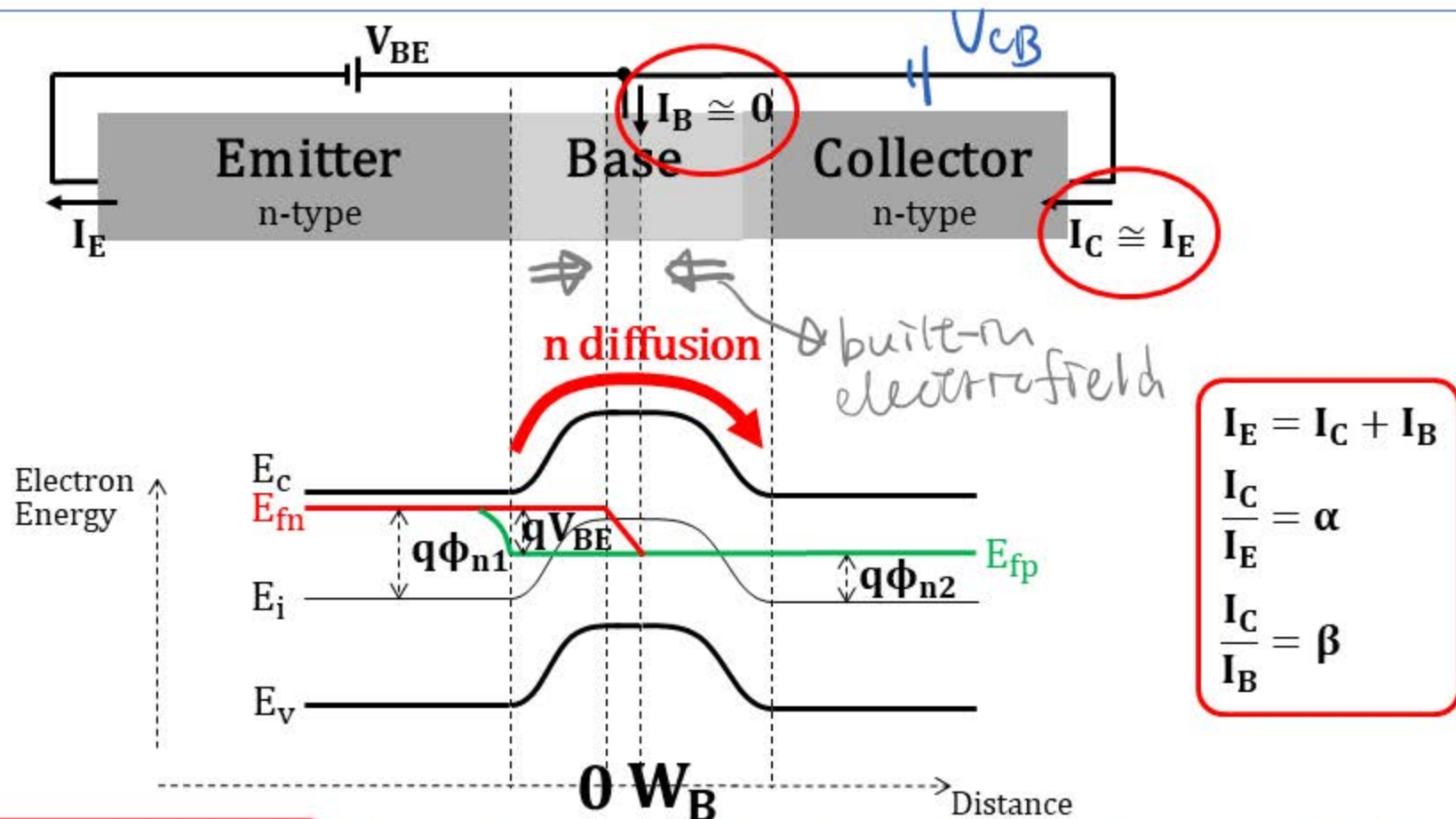$V_{BE} > 0$  and  $V_{CB} = 0$  ( $W_B$  very short)



$$N_{d1} \gg N_a$$


The  $n$  (electron) diffusion is much larger than the  $p$  (hole) diffusion at the Base-Emitter junction.

**$W_B$  very short**

Nearly all the  $n$  (electron) diffusion from the Base-Emitter junction pass through the Base, enter into the depletion region of the Base-Collector junction, and are swept to the Collector side by the built-in electric field.



# Summary

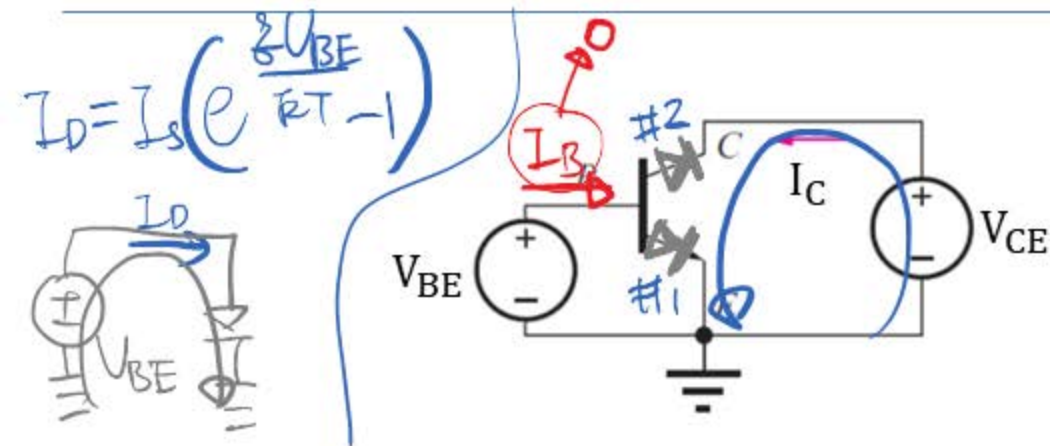

$$V_{CE} \geq V_{BE} \\ \Rightarrow \text{Forward - Active}$$

\* Junction #1  
in forward bias  
\* Junction #2  
in zero or reverse bias

**Ideal case**

$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} \cong 1$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$$I_C + I_B = I_E$$


$I_S$  is a constant in the spice model.



$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} = 1$$

$$\beta = \frac{I_C}{I_B} = \infty$$

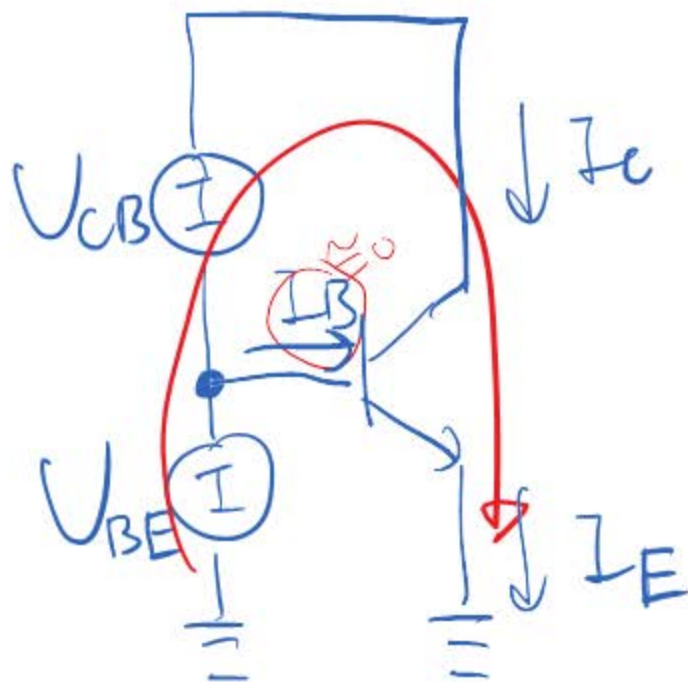

$$V_{CB} \geq 0$$



forward-active region

$I_C$  vs  $V_{CE}$  and  $I_C$  vs  $V_{BE}$   
in Forward-Active Region

---

# $I_C$ vs $V_{CE}$ (not considering Early Effect)



At given  $V_{BE}$ , DC sweep  $V_{CE}$

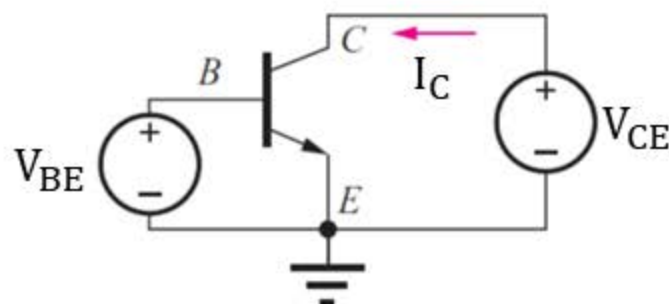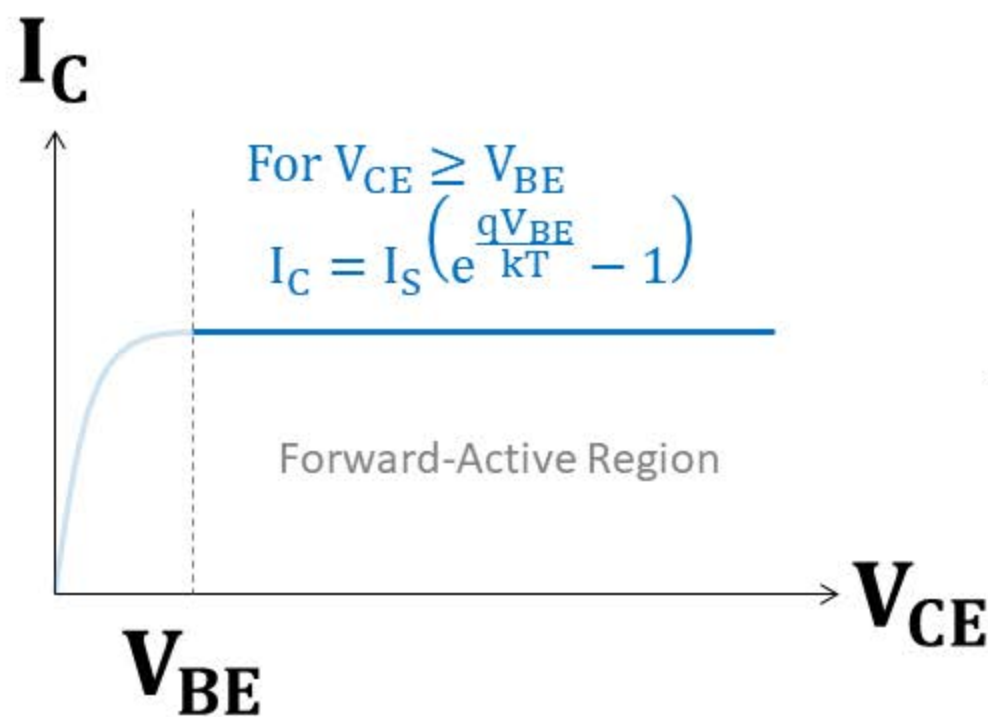



# $I_C$ vs $V_{CE}$ (considering Early Effect)

At given  $V_{BE}$ , DC sweep  $V_{CE}$

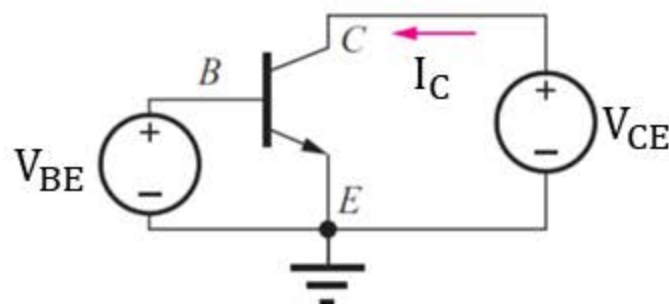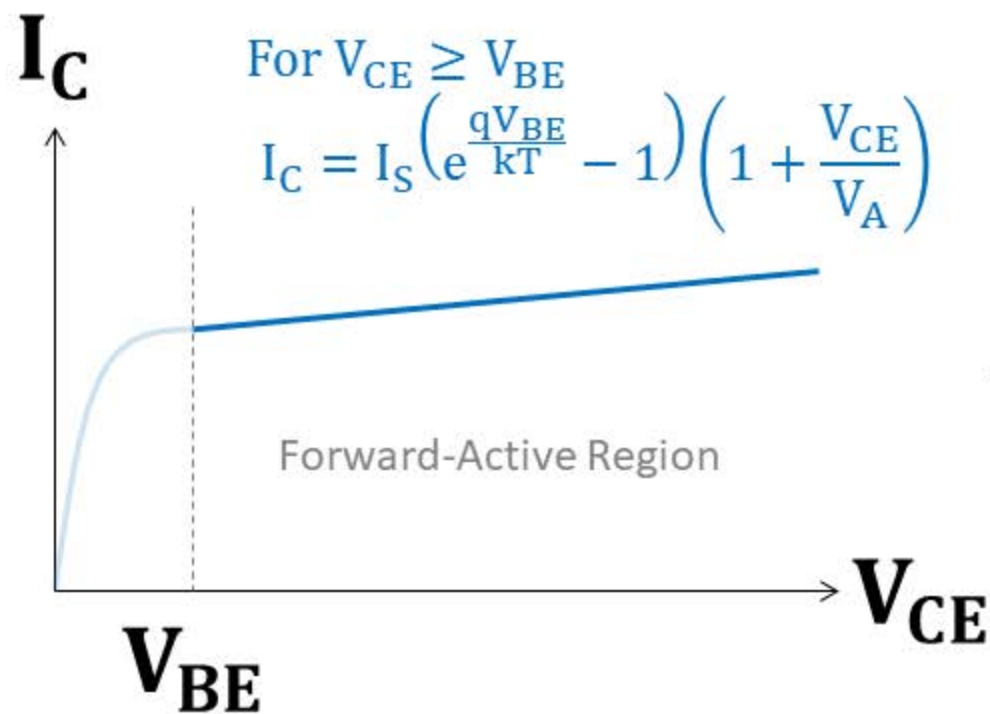



$V_A$  is a constant in the spice model.

# $I_C$ vs $V_{BE}$

At given  $V_{CE}$ , DC sweep  $V_{BE}$

For  $V_{CE} \geq V_{BE}$
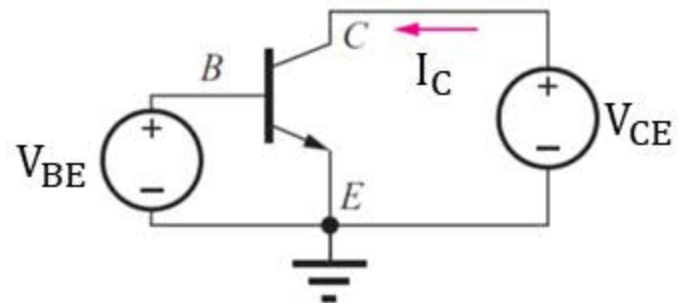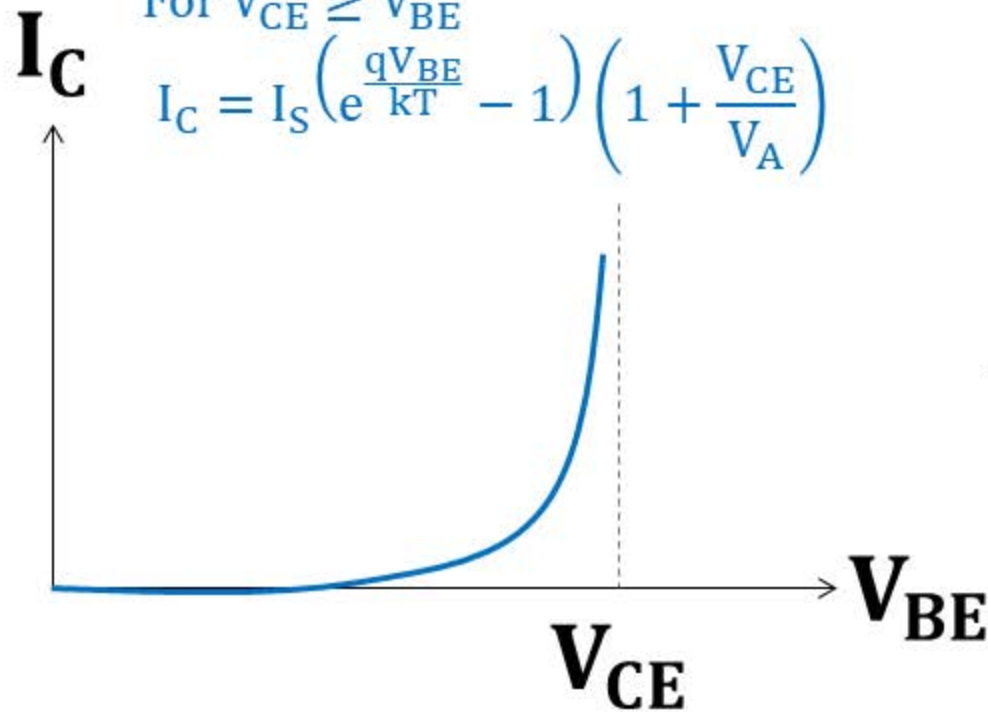
$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$




# Small-Signal Model

---

# Hybrid- $\pi$ Model (how to get $g_m$ and $r_\pi$ )

Complete circuit:

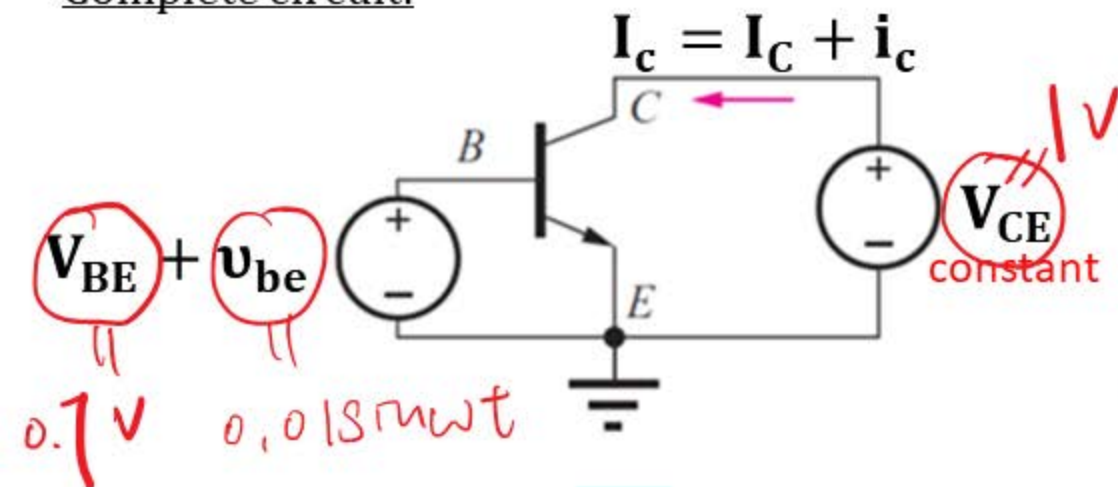

$$V_{CE} \geq V_{BE}$$


$\Rightarrow$  Forward – Active

$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

Handwritten note:  $V_A = 100$




Small-signal circuit:

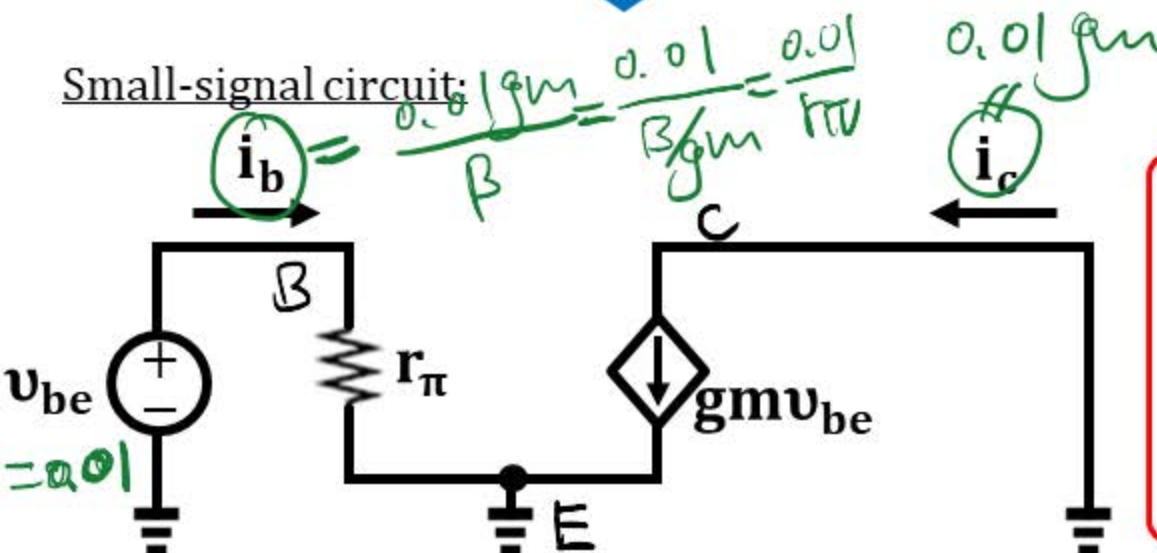

$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{g_m}{\beta}} = \frac{\beta}{g_m}$$

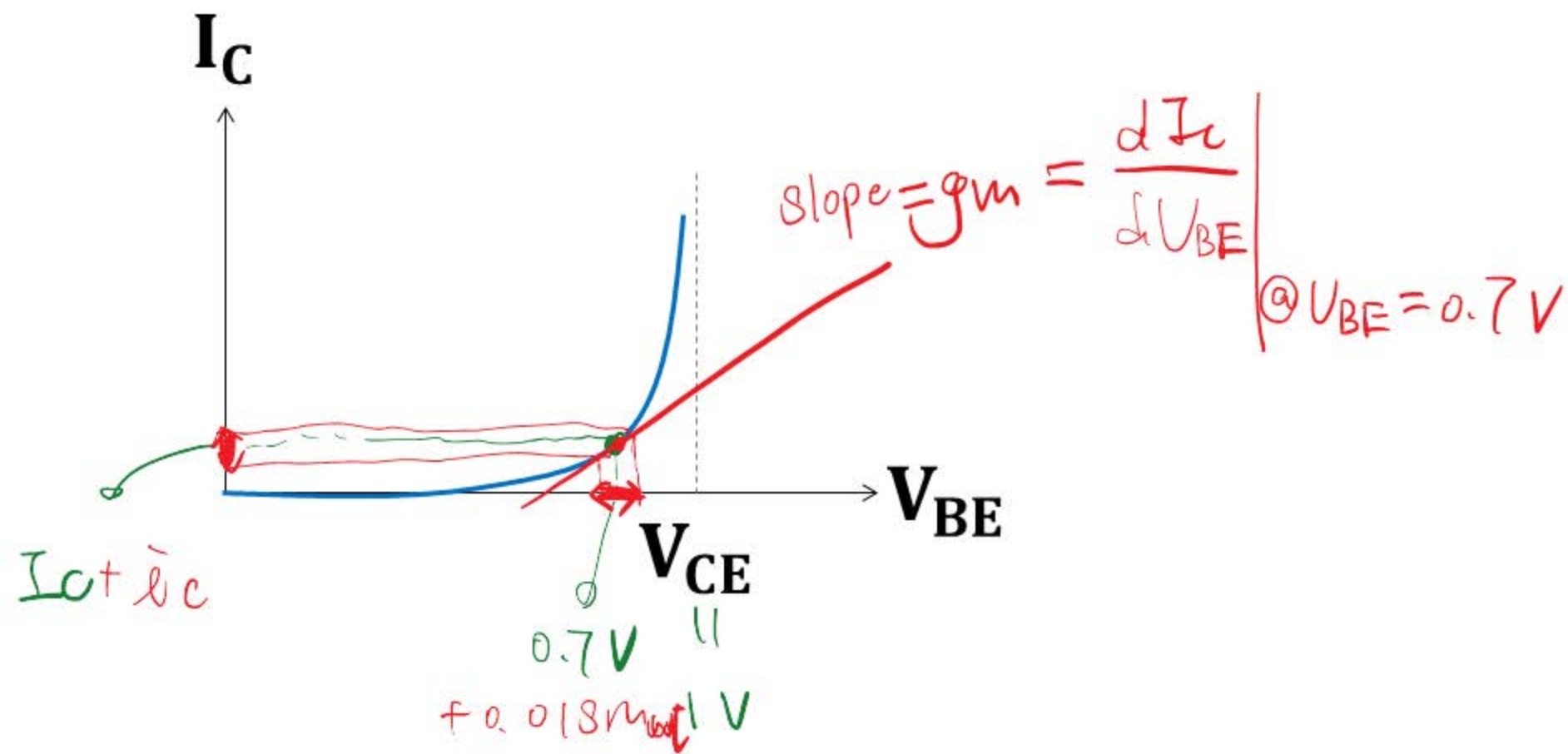
$$g_m = \frac{dI_C}{dV_{BE}} \approx \frac{I_C}{kT/q}$$



$$I_C = I_S \left( e^{\frac{0.7}{0.026}} - 1 \right) \left( 1 + \frac{1}{V_A} \right), \quad i_c = (0.018 mV) g_m$$

# Hybrid- $\pi$ Model (how to get $r_o$ )

Complete circuit:

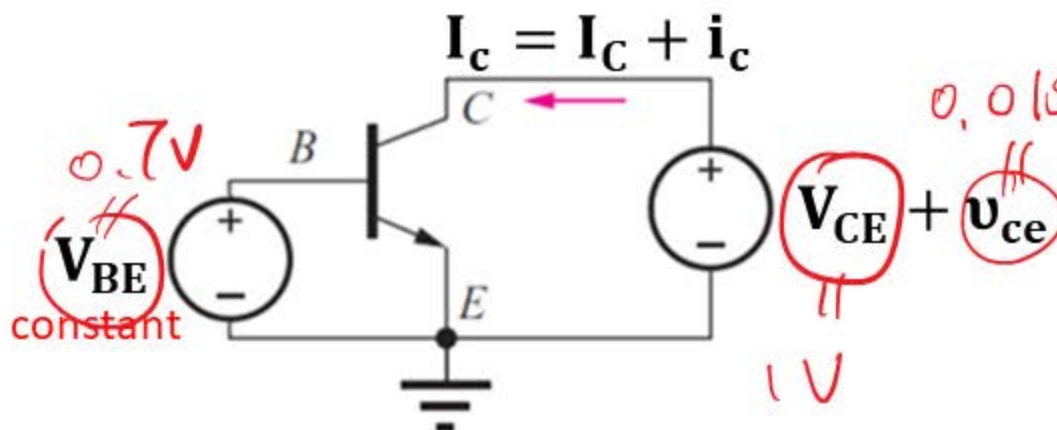


$$V_{CE} \geq V_{BE} \Rightarrow \text{Forward-Active}$$

$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$



Small-signal circuit:

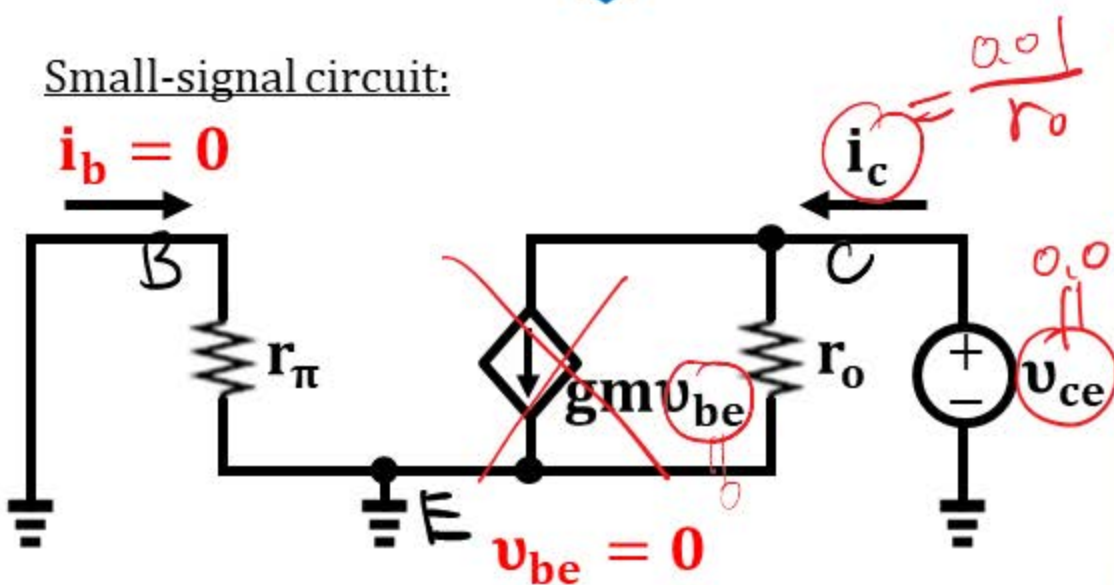


$$r_\pi = \frac{1}{\frac{dI_B}{dV_{BE}}} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{gm}{\beta}} = \frac{\beta}{gm}$$

$$gm = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q}$$
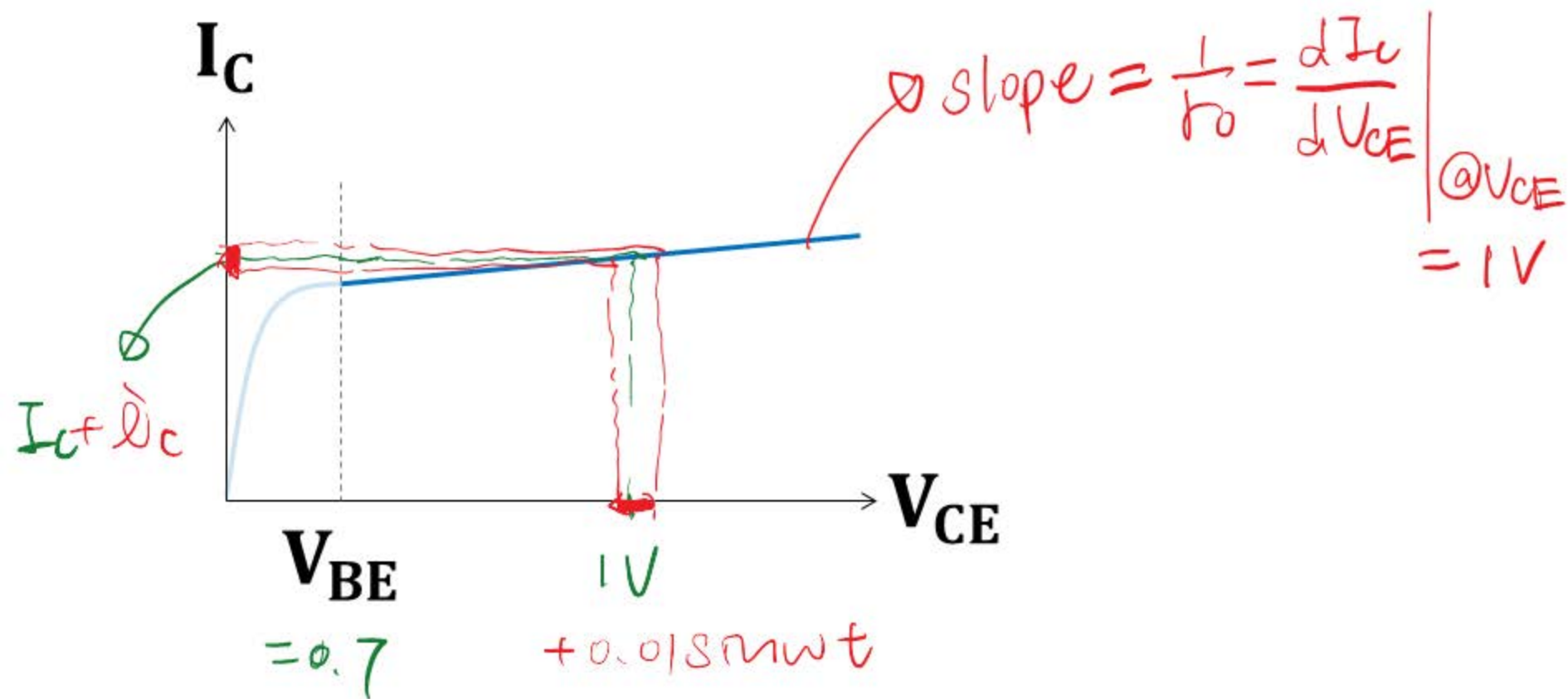
$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \cong \frac{V_A}{I_C}$$





$$I_C = I_S \left( e^{\frac{0.7}{0.026}} - 1 \right) \left( 1 + \frac{1}{V_A} \right), \quad \bar{I}_C = \frac{0.018mwt}{r_o}$$