
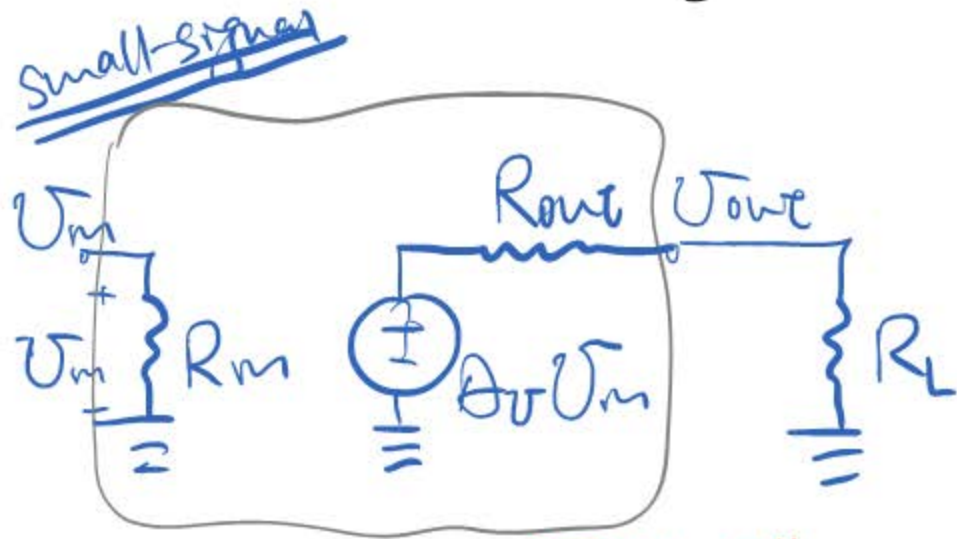



Common-Draft

Source Follower (Buffer)

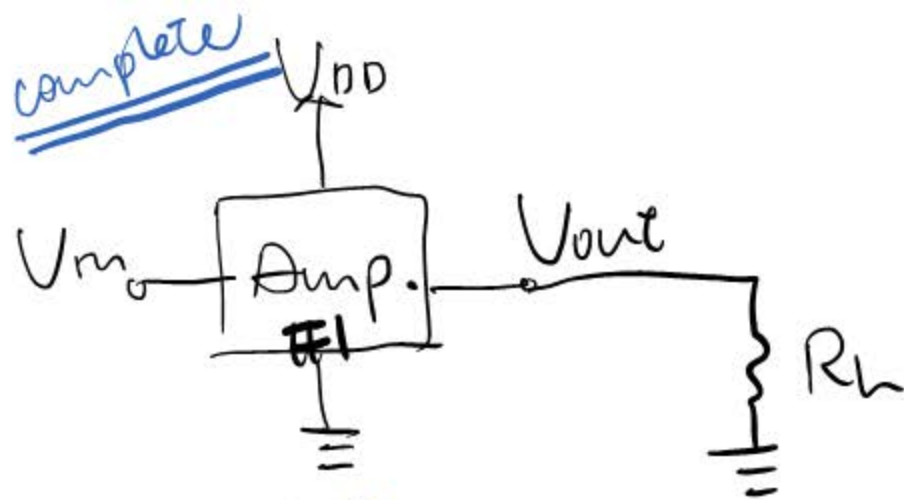

$$\frac{V_{out}}{V_m} = A_v \cdot \frac{\overset{\text{small}}{R_L}}{\underset{\text{large}}{R_{out} + R_L}}$$

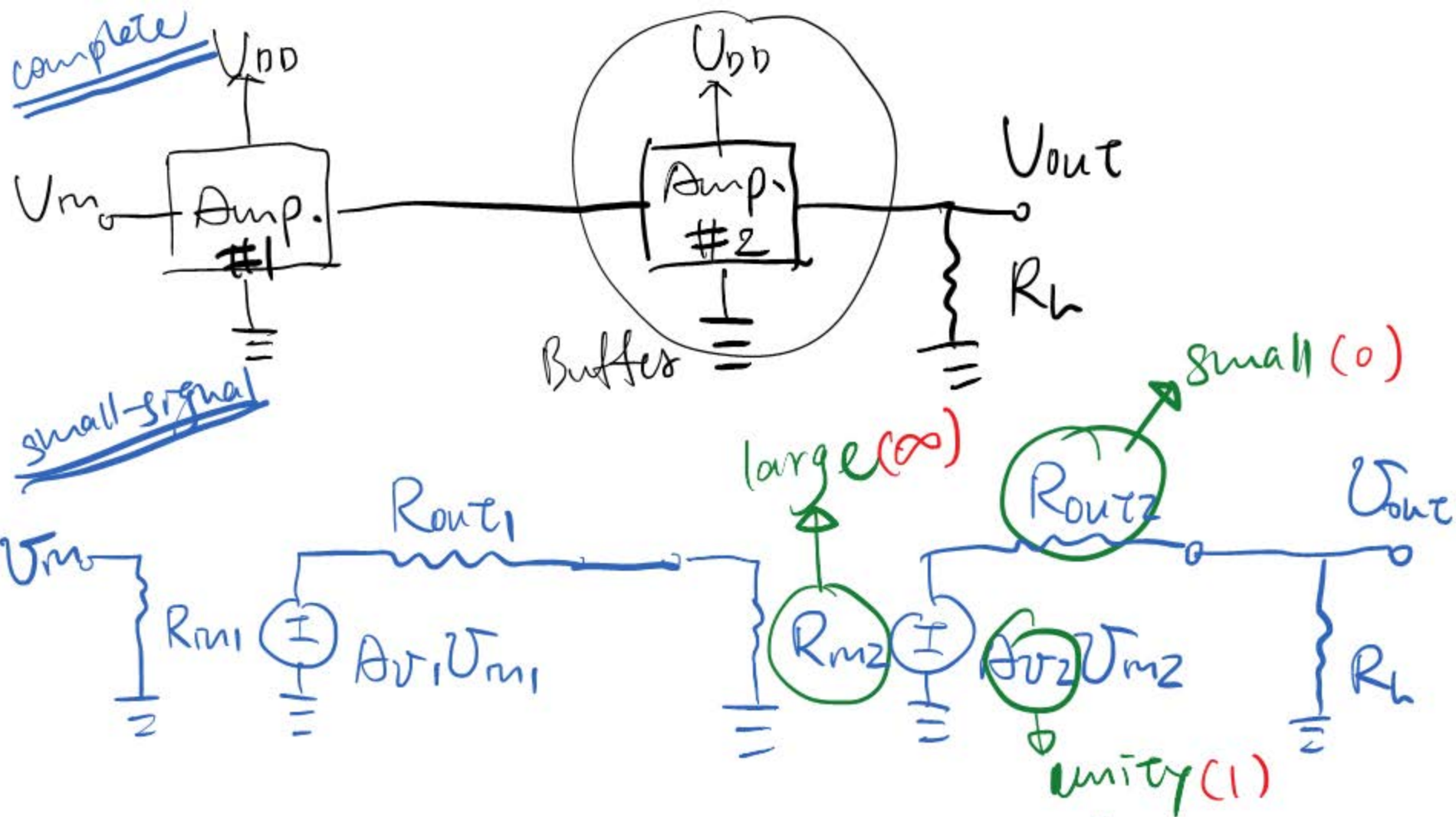
\Rightarrow A_v consumed
by the factor $\frac{R_L}{R_{out} + R_L}$



$$\frac{V_{out}}{V_m} = A_{v1} \frac{R_{m2}}{\underbrace{R_{out1} + R_{m2}}_{\text{large}}} A_{v2} \frac{\underbrace{R_L}_{\text{small}}}{R_{out2} + R_L}$$


Ideal Amplifier

Voltage Amp.

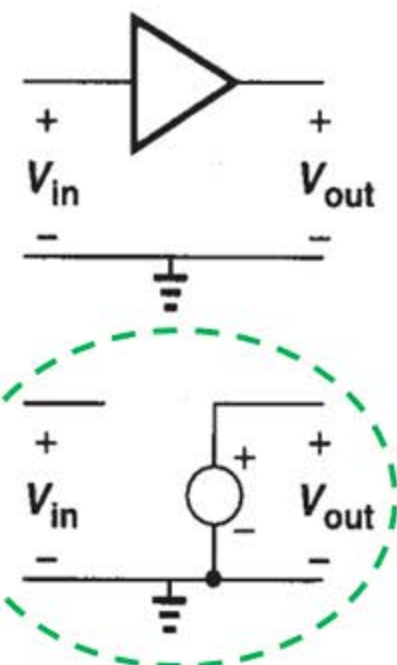


CS + Source Follower


Transimpedance Amp.

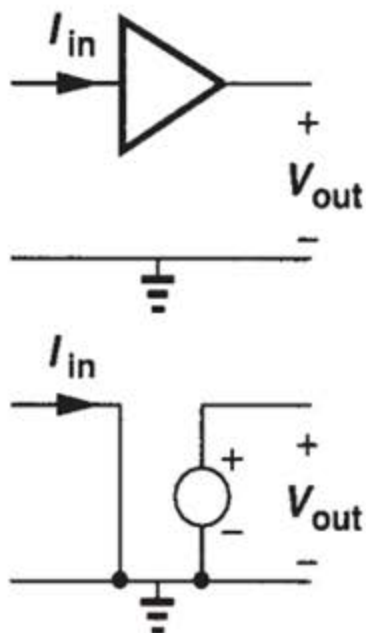


Transconductance Amp.

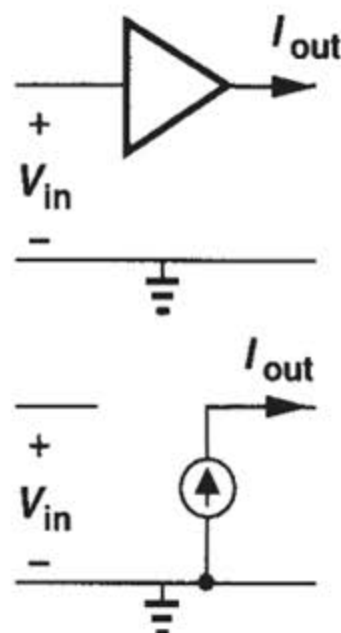

Current Amp.

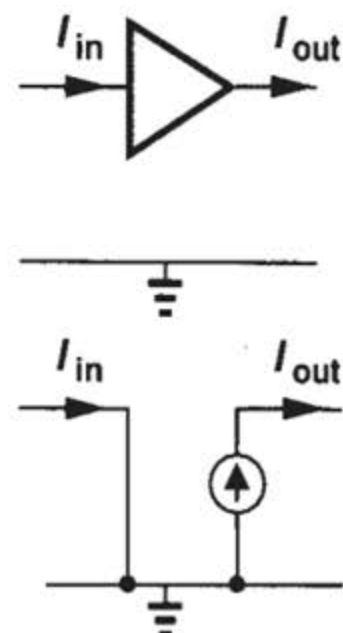

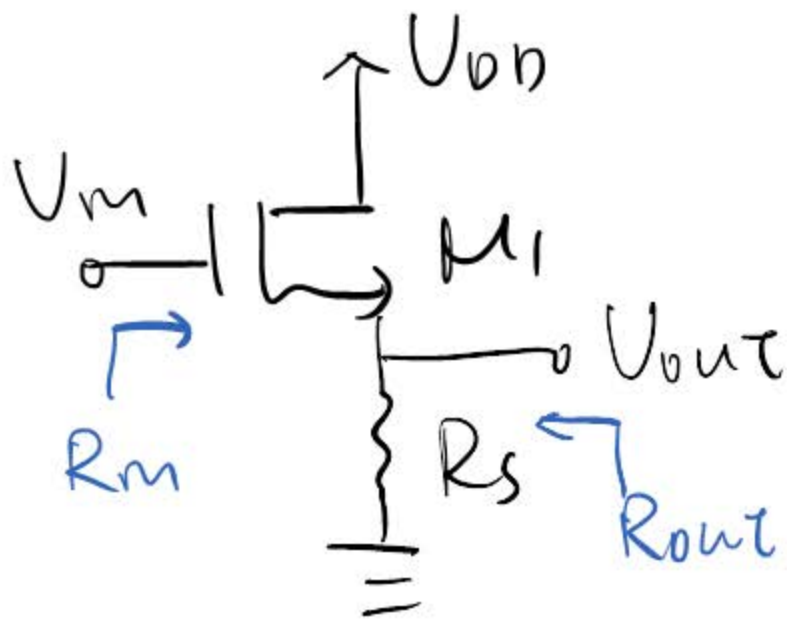
- For driving a low impedance load, source follower, as a buffer, provides **no gain** but **large input impedance** and **low output impedance**.




$$R_m = \infty$$

$$R_{out} = R_s \parallel r_{o1} \parallel \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$

Small-Signal

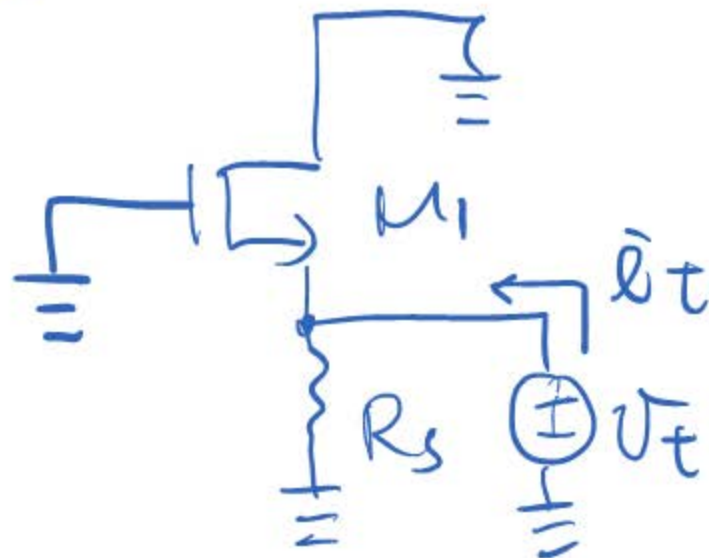

$$R_{out} = \frac{V_t}{\hat{I}_t}$$

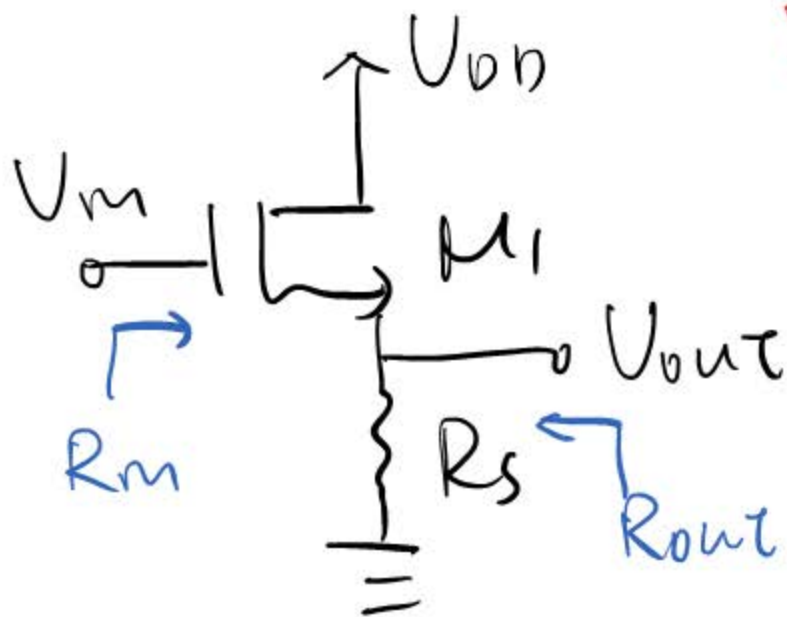

$$\lambda \neq 0, r \neq 0$$


$$R_m = \infty$$


$$R_{out} = R_S \parallel r_{o1} \parallel \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$

$$A_v = \frac{V_{out}}{V_m}$$

Small-Signal
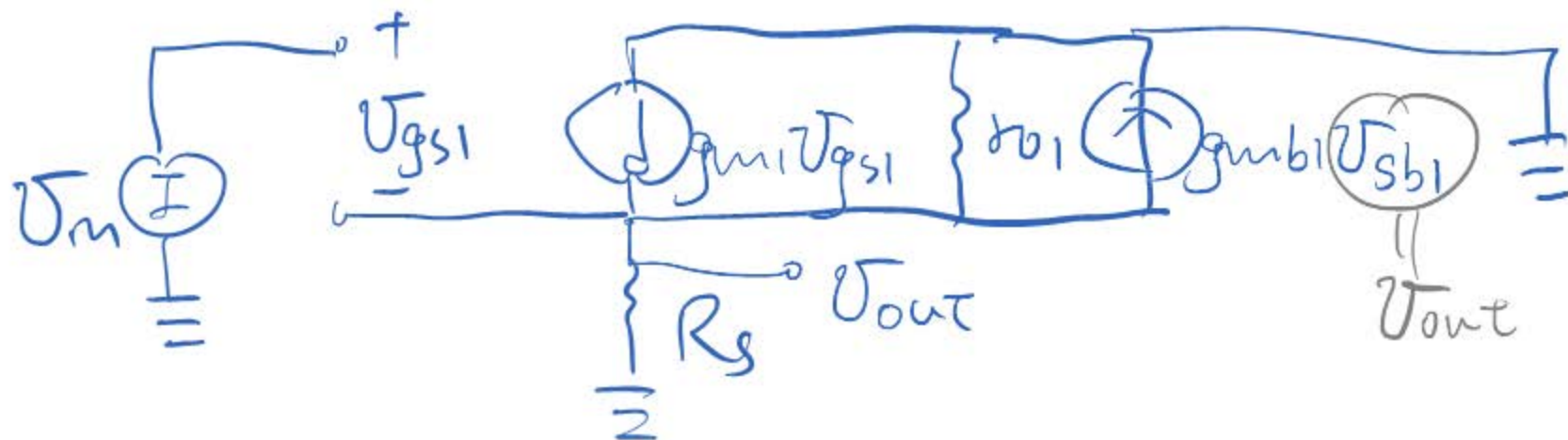
$$\frac{V_{out}}{R_S} + (V_{out} - V_m)g_{m1} + \frac{V_{out}}{r_{o1}} + g_{mb1}V_{out} = 0$$



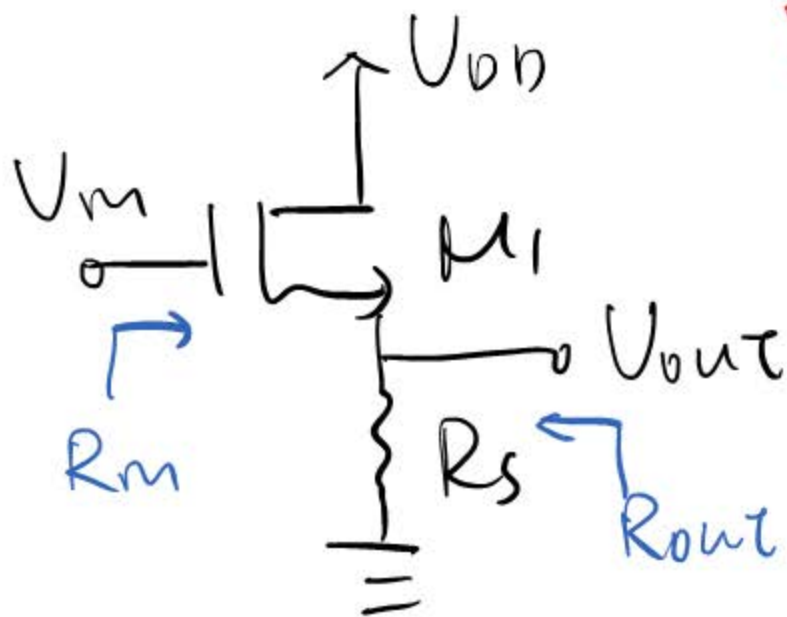



$$\lambda \neq 0, r \neq 0$$

$$G_m = ? = \frac{i_{out}}{V_m} = g_{m1}$$

$$i_{out} = g_{m1} V_m$$

Small-signal

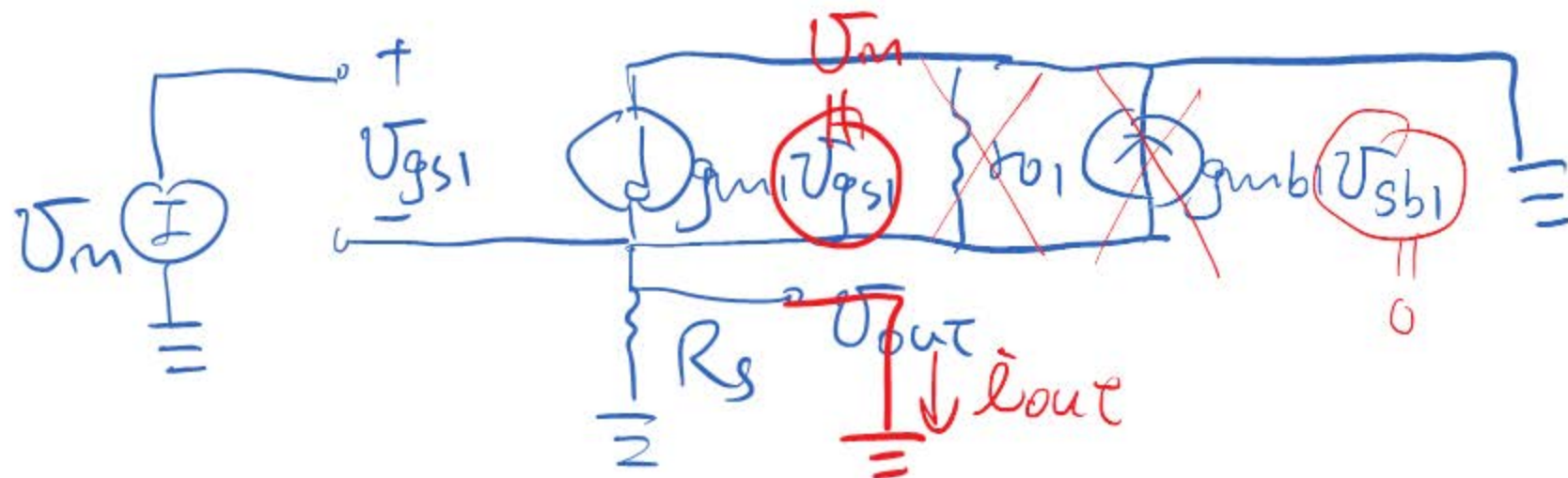

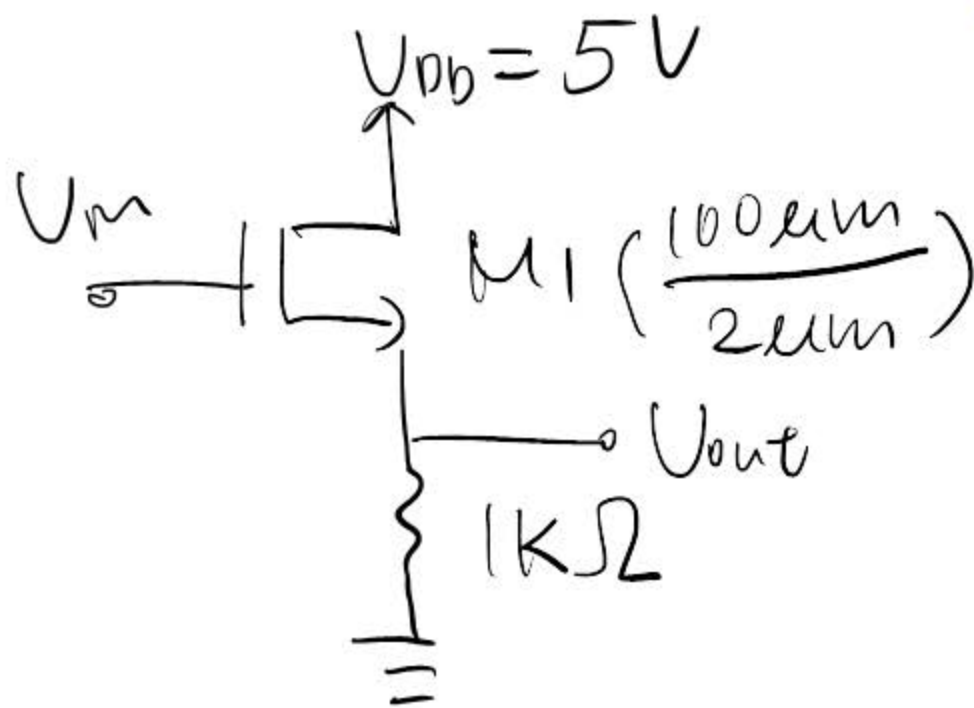

$$\lambda \neq 0, r \neq 0$$

$$V_{OUT} = ?$$

DC biasing analysis.

M_1 must be in sat.

$$\frac{V_{OUT}}{1k} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (3 - V_{OUT} - V_{TH})^2$$

$$V_m = 3 + 0.0018m(2\pi 100t)$$

$$V_{out} = ?$$

$$(3 - V_{OUT} - V_{TH})^2$$



$$[1 + \lambda(5 - V_{out})]$$

Source Follower

DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

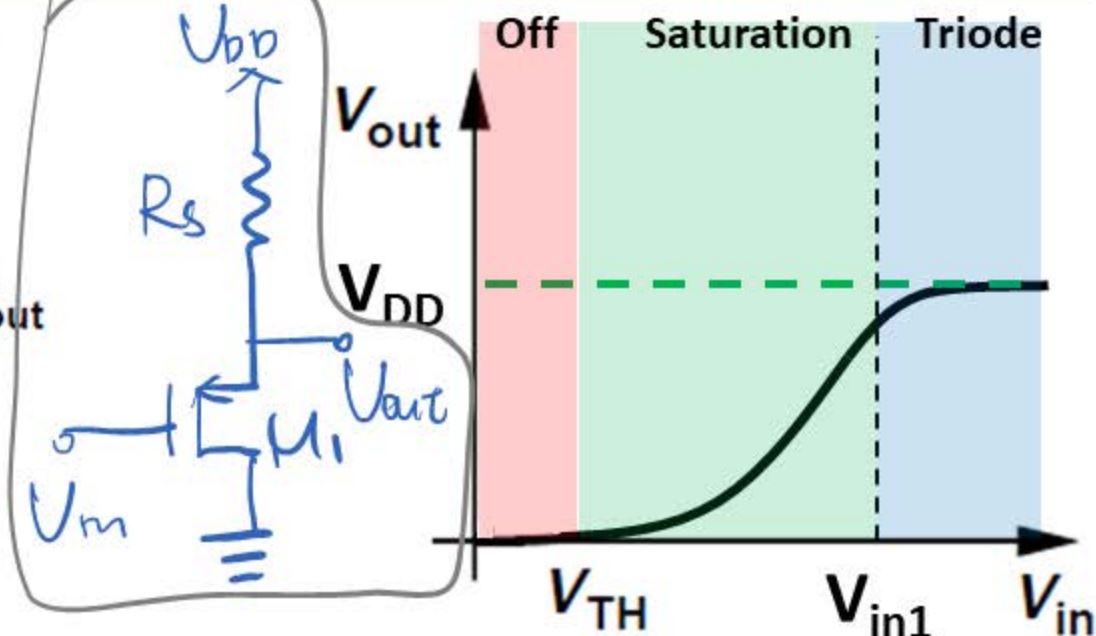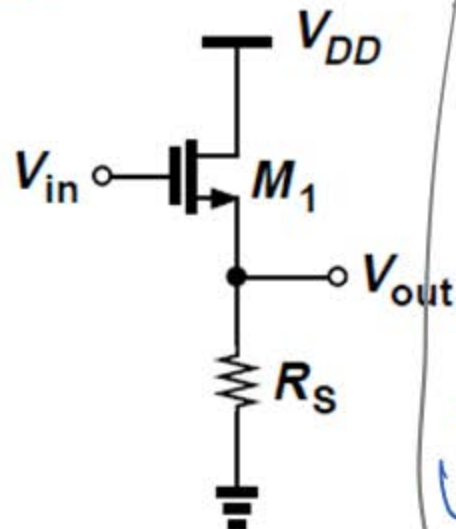

- $V_{in} < V_{TH} \rightarrow M_1$ Off

$$V_{out} = 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$ in Saturation

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

- $V_{in} > V_{in1} \rightarrow M_1$ in Triode

$$R_S \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{in} - V_{out} - V_{TH})(V_{DD} - V_{out}) - \frac{1}{2} (V_{DD} - V_{out})^2 \right] = V_{out}$$

$$\begin{aligned} V_{DD} - V_{out} &= V_{in1} - V_{out} - V_{TH} \\ \rightarrow V_{in1} &= V_{DD} + V_{TH} \end{aligned}$$

Source Follower

DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$ in Saturation

$$V_{out} = V_{SB}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$$R_S \underbrace{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})}_{= gm} \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \underbrace{\frac{\partial V_{TH}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}}}_{\substack{+V_{TH} \\ +V_{SB}}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$$\eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$A_v = \frac{gm R_S}{1 + gm R_S (1 + \eta)} = \frac{gm R_S}{1 + (gm + gmb) R_S} \approx \frac{1}{1 + \eta}$$


$$\text{If } (gm + gmb) R_S \gg 1$$

Source Follower

Small-signal Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

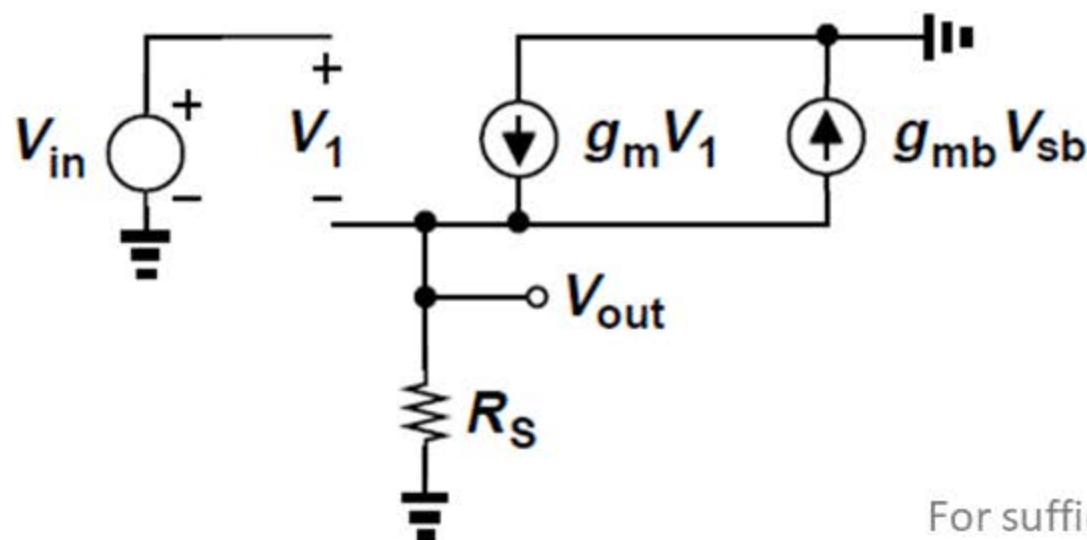


$$G_m = g_m$$

$$R_{out} = R_S \parallel \left(\frac{1}{g_m + g_{mb}} \right)$$

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{1}{1 + \eta}$$

$$\text{If } (g_m + g_{mb}) R_S \gg 1$$

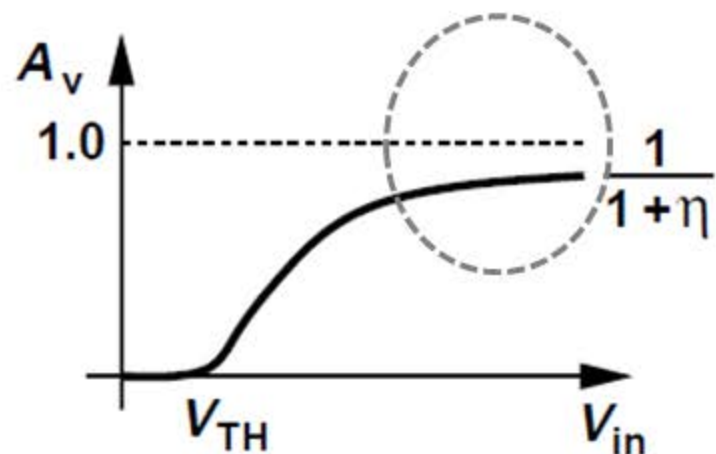For sufficiently large V_{in} , I_D and thus g_m .




Source Follower

Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

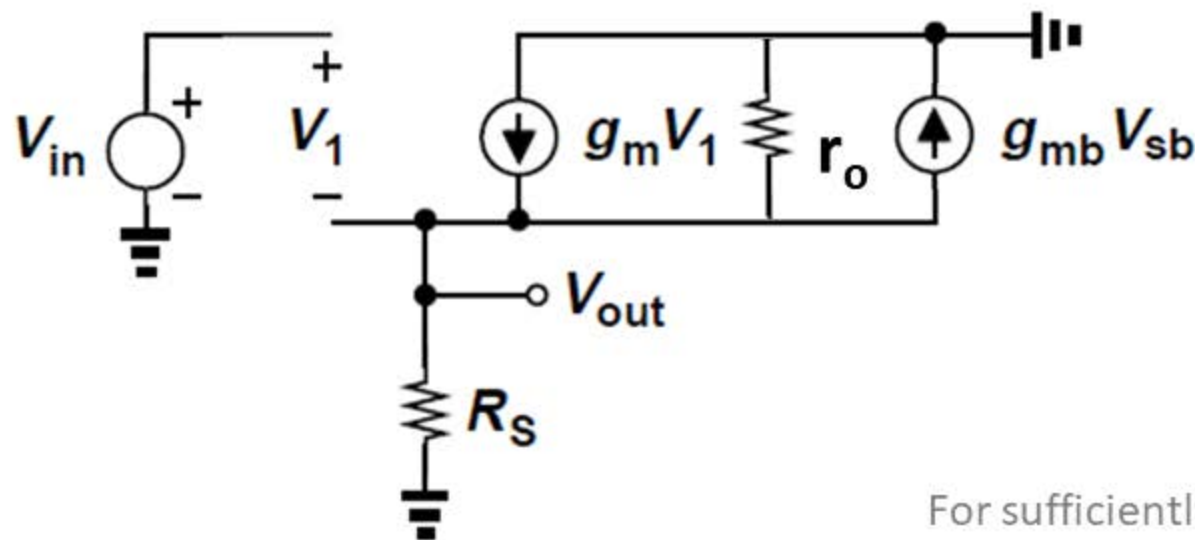


$$G_m = g_m$$


$$R_{out} = r_o \parallel R_S \parallel \left(\frac{1}{g_m + g_{mb}} \right)$$

$$A_v = \frac{g_m r_o R_S}{r_o + R_S + (g_m + g_{mb}) r_o R_S} \approx \frac{1}{1 + \eta}$$

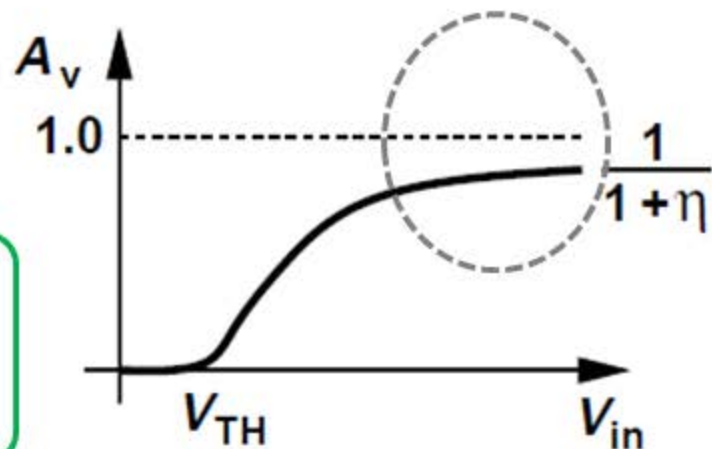For sufficiently large V_{in} , I_D and thus g_m .



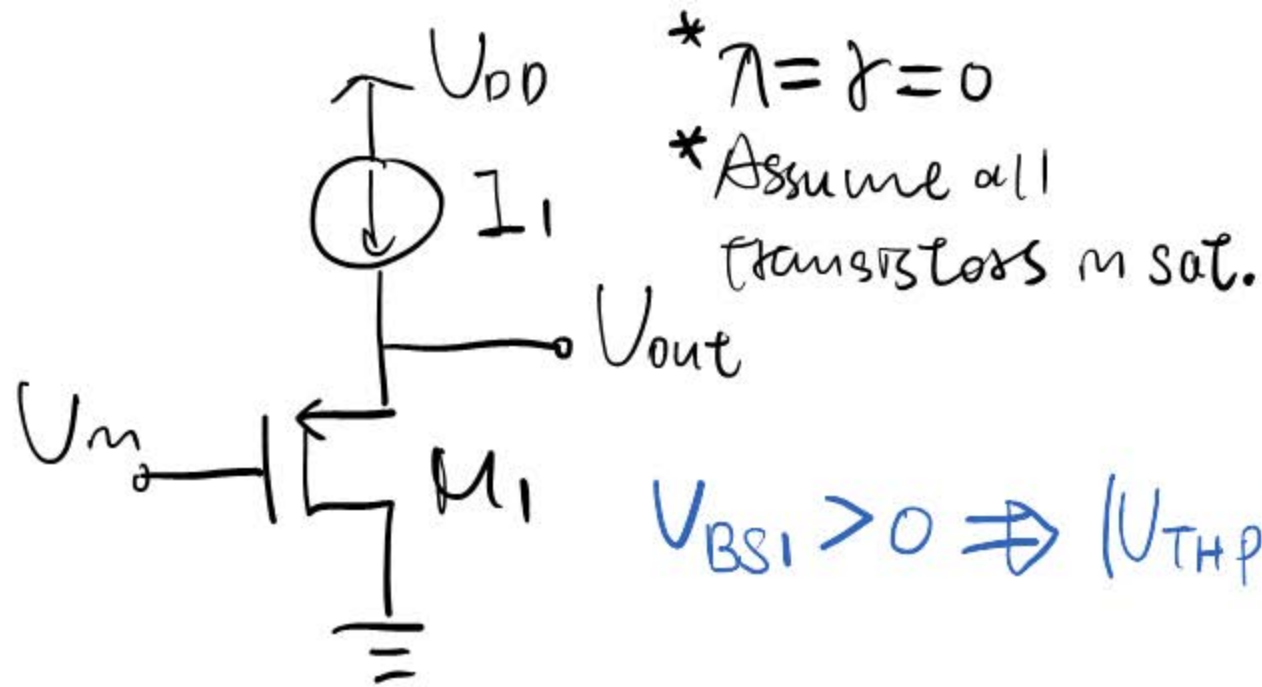
If $(g_m + g_{mb}) r_o R_S \gg r_o$ and R_S



$$V_{BS1} > 0 \Rightarrow |V_{THP}| > 0.8 \text{ if } r \neq 0$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{out} - V_{in} - |V_{THP}|)^2 = I_1$$

constants

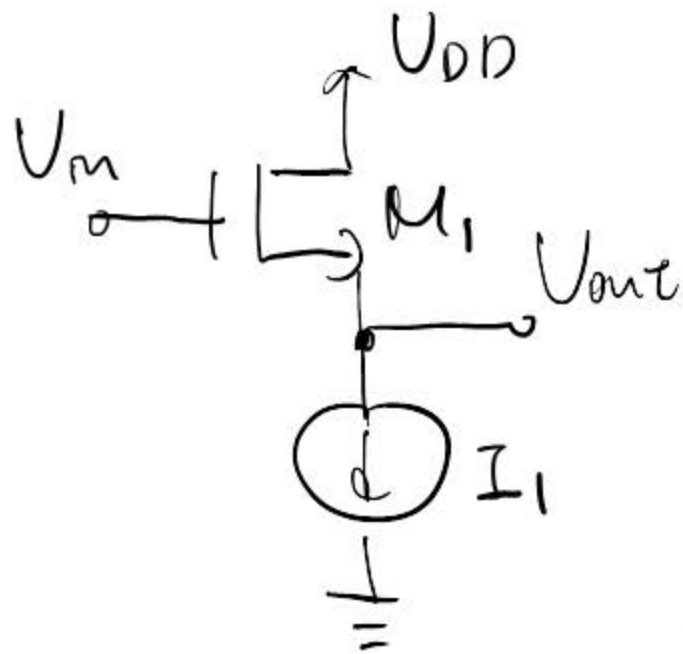

$$\lambda \neq 0, \theta \neq 0$$



All transistors operate in Sat.

$$R_m = ? \quad R_{out} = ? \quad A_v = ?$$


$$R_m = \infty$$

$$R_{out} = r_{o2} \parallel r_{o1} \parallel \left(\frac{1}{g_{m1} + g_{m1b1}} \right)$$

Small Signal

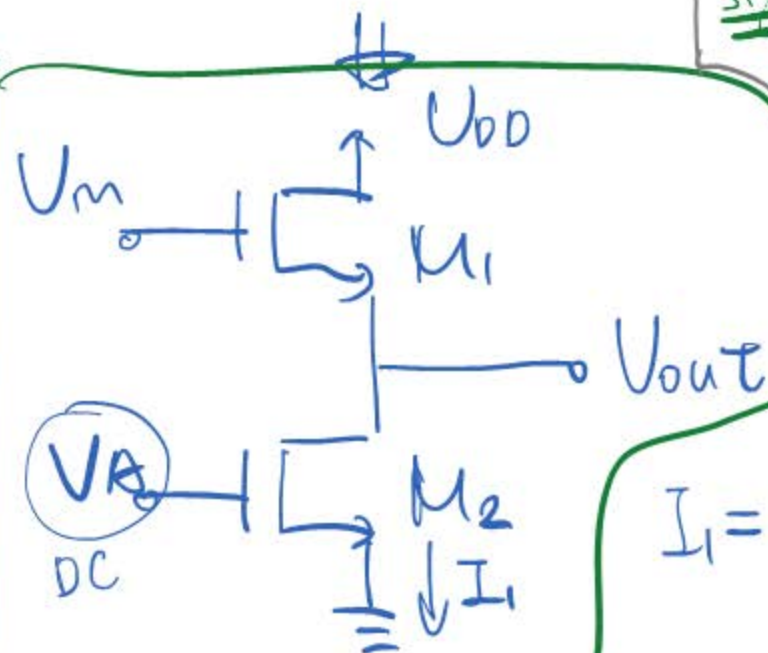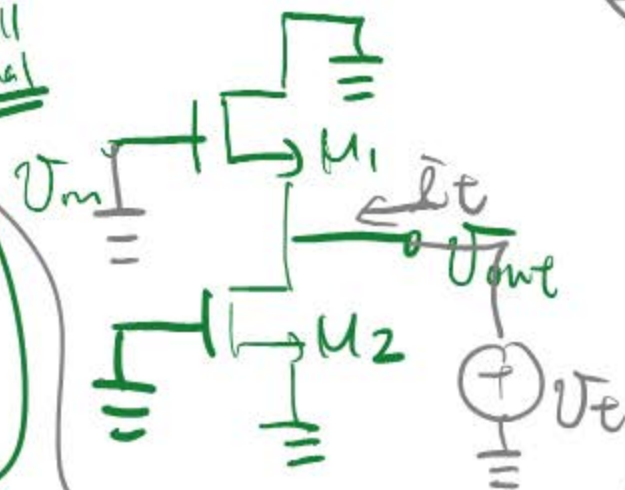
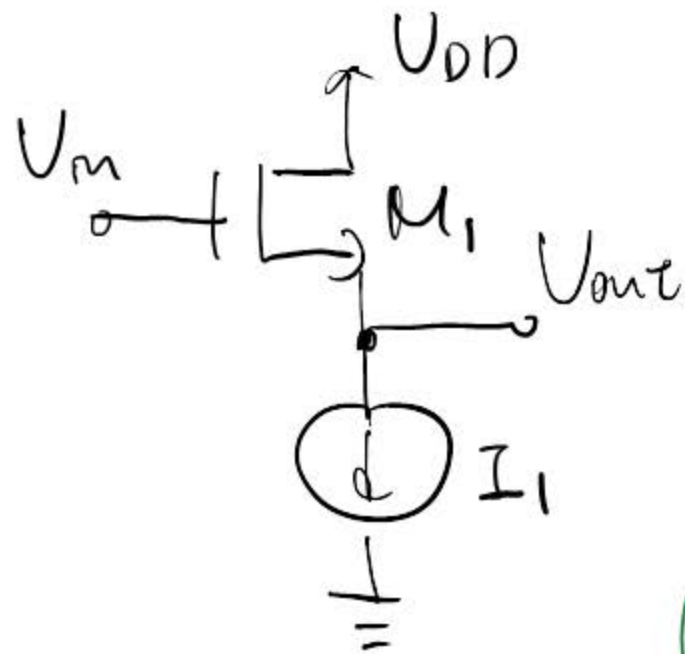
$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_A - 0.7)^2 (1 + \lambda V_{out})$$



$$\lambda \neq 0, \theta \neq 0$$

All transistors operate in Sat.


$$R_m = ? \quad R_{out} = ? \quad A_v = ?$$

$$= g_m R_{out}$$


$$R_m = \infty$$

$$R_{out} = r_{o2} \parallel r_{o1} \parallel \left(\frac{1}{g_{m1} + g_{m1}} \right)$$

Small Signal

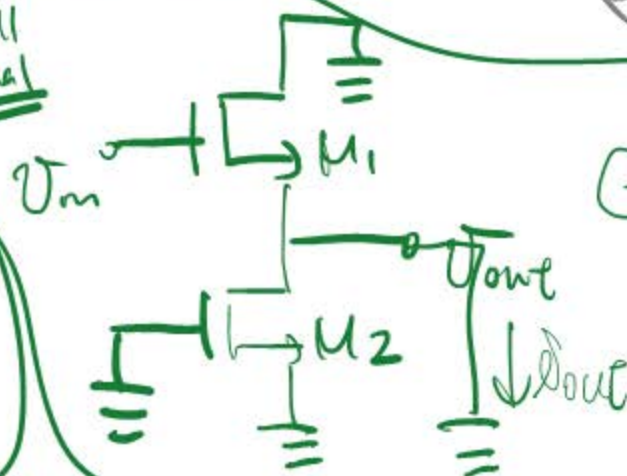

$$G_m = g_{m1}$$

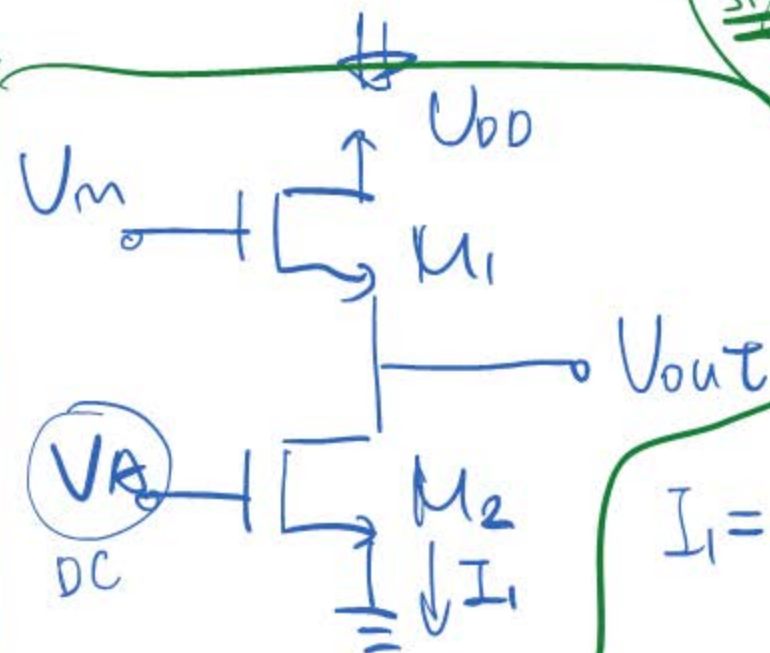



$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_A - 0.7)^2 (1 + \lambda V_{out})$$

Source Follower with Current Source

DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

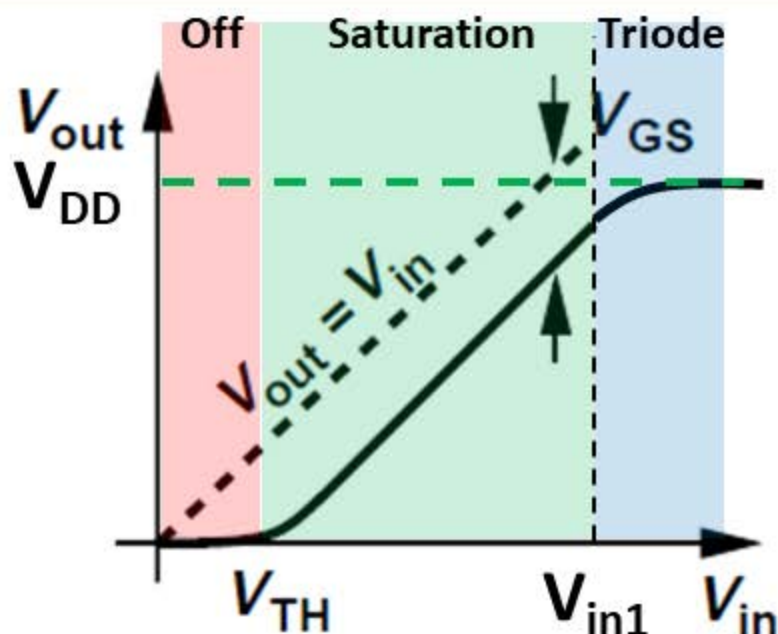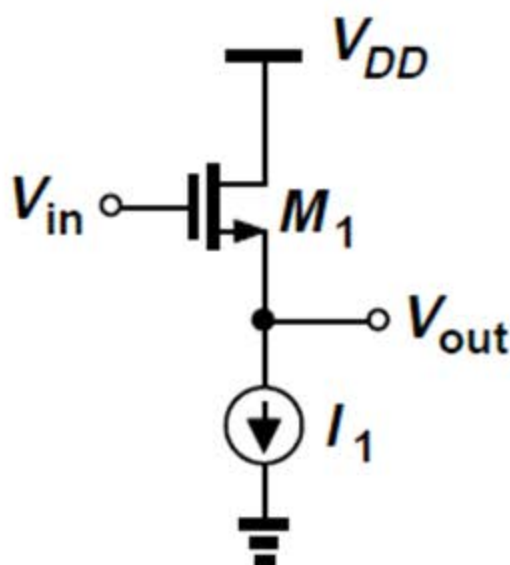

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 = I_1$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) = 0$$

$$\boxed{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})} \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \boxed{\frac{\partial V_{TH}}{\partial V_{out}}} \frac{\partial V_{out}}{\partial V_{in}} \right) = 0$$

$= g_m$ $= \eta$

$$A_v = \frac{1}{1 + \eta}$$


$$\text{If } \gamma = 0, A_v = 1.$$

Source Follower with Current Source

Small-signal Analysis

$$\lambda = 0$$


$$\gamma \neq 0$$

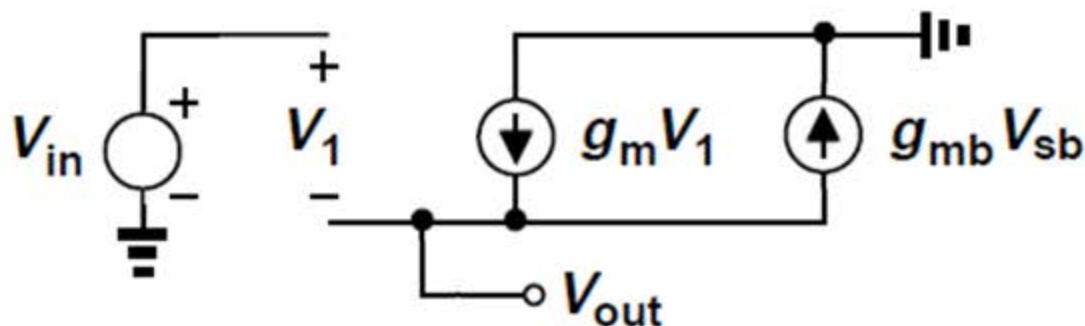

$$G_m = g_m$$

$$R_{out} = \frac{1}{g_m + g_{mb}}$$
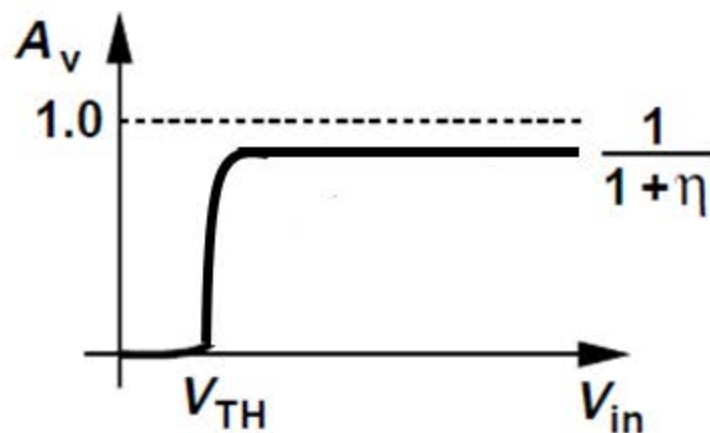
$$A_v = \frac{1}{1 + \eta} \quad \text{If } \gamma = 0, A_v = 1.$$




Source Follower with Current Source

Small-signal
Analysis

$\lambda \neq 0$

$\gamma \neq 0$

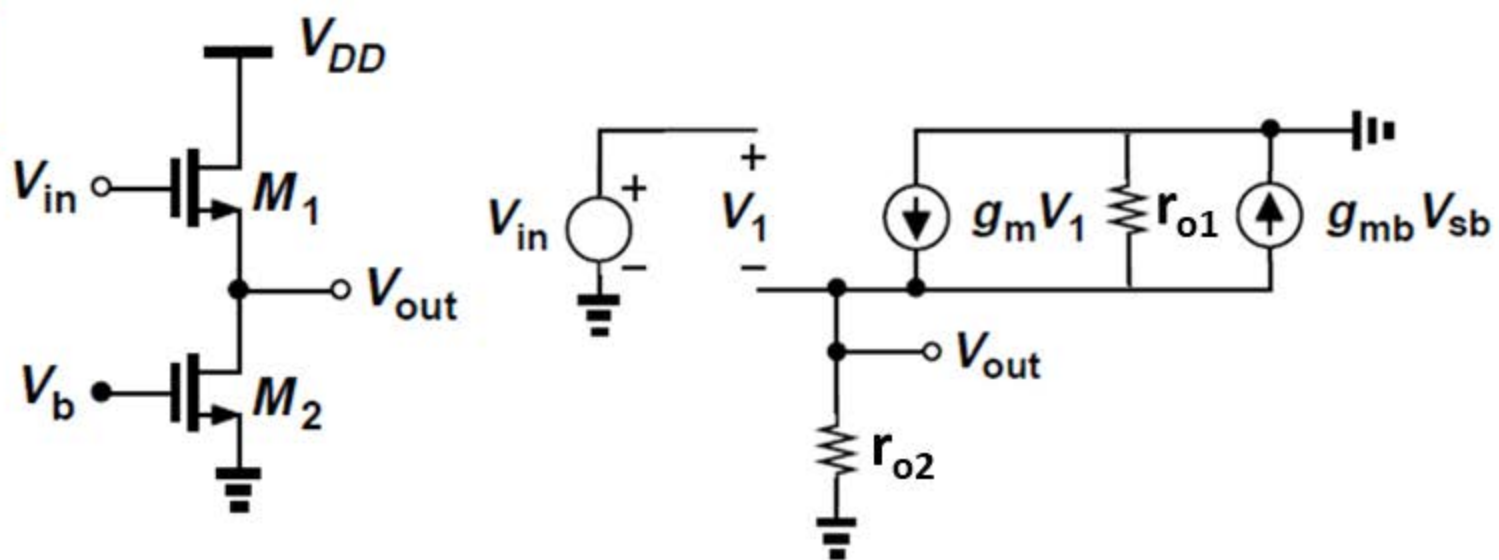

$$G_m = g_{m1}$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$

$$A_v = \frac{g_m r_{o1} r_{o2}}{r_{o1} + r_{o2} + (g_m + g_{mb}) r_{o1} r_{o2}}$$

If r_{o1} and r_{o2} large,
 A_v is linear.



Source Follower with Current Source ($V_{BS} = 0$)

19

Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

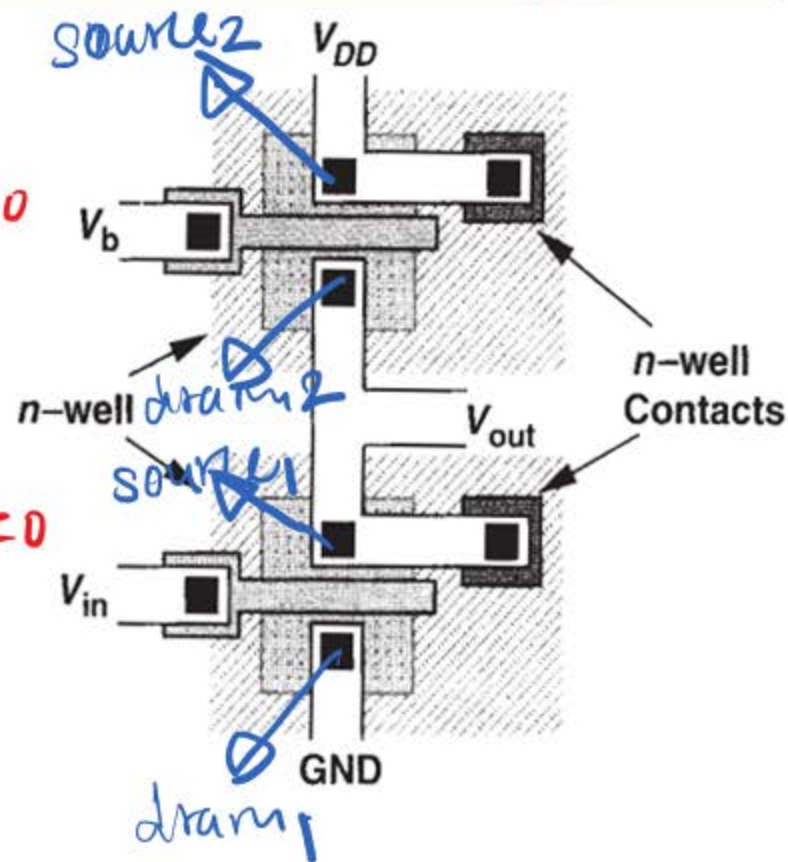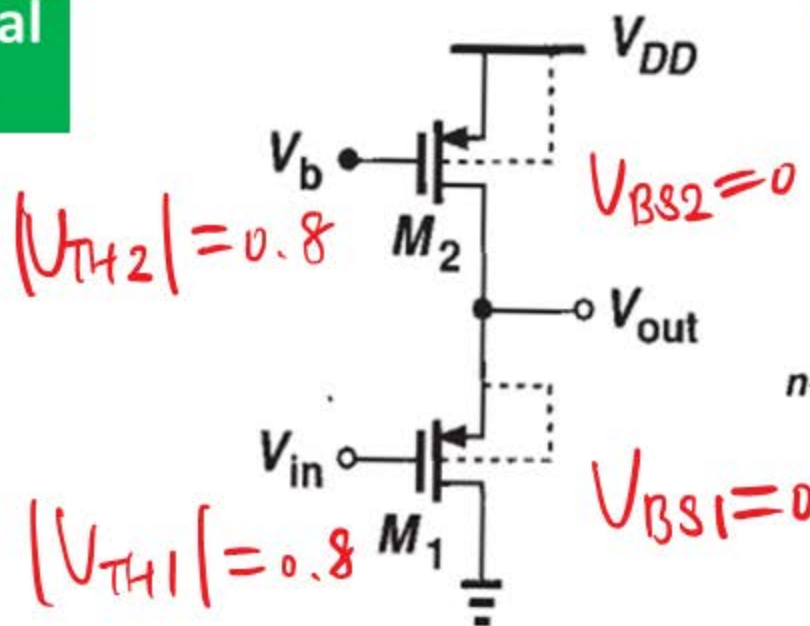


$$G_m = g_{m1}$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m1}}$$

$$A_v = \frac{g_{m1} r_{o1} r_{o2}}{r_{o1} + r_{o2} + g_{m1} r_{o1} r_{o2}}$$


- The sacrifice here is the higher output impedance due to smaller mobility of holes relative to electrons.

Source Follower as Level Shifter

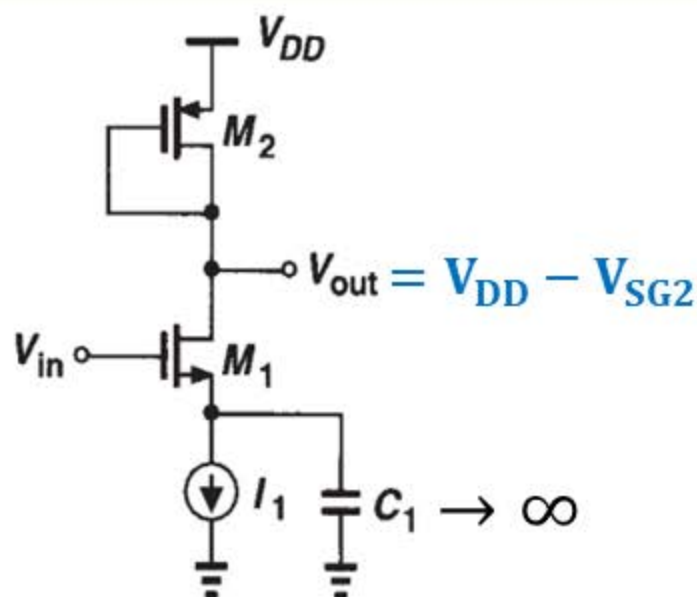

$$V_{in} \leq V_{DD} - V_{SG2} + V_{TH1}$$
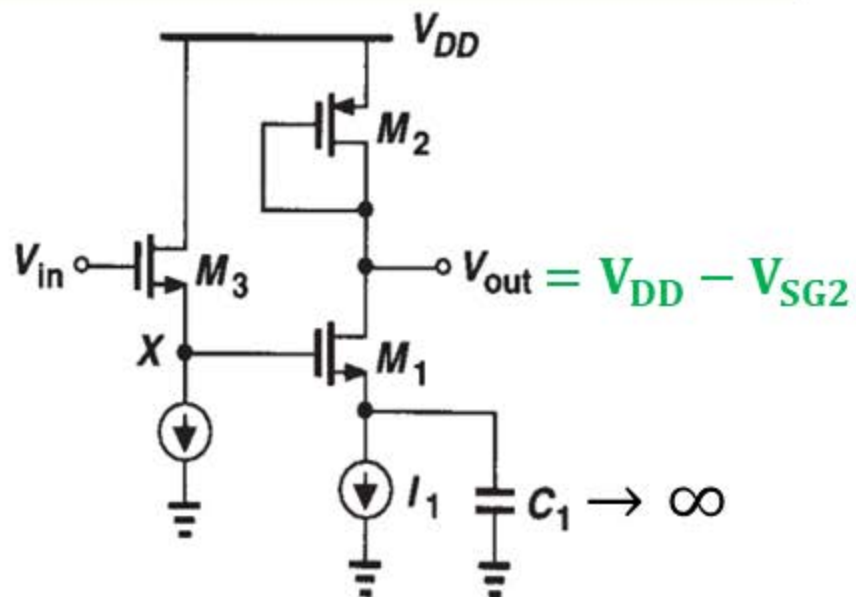
$$\begin{cases} G_m = -gm_1 \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$




$$V_{in} - V_{GS3} \leq V_{DD} - V_{SG2} + V_{TH1}$$

$$\begin{cases} G_{m(left)} = gm_3 \\ R_{out(left)} = r_{o3} \parallel \frac{1}{gm_3 + gmb_3} \end{cases}$$

$$\begin{cases} R_{in(right)} = \infty \\ G_{m(right)} = -gm_1 \\ R_{out(right)} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$

Source Follower as Level Shifter

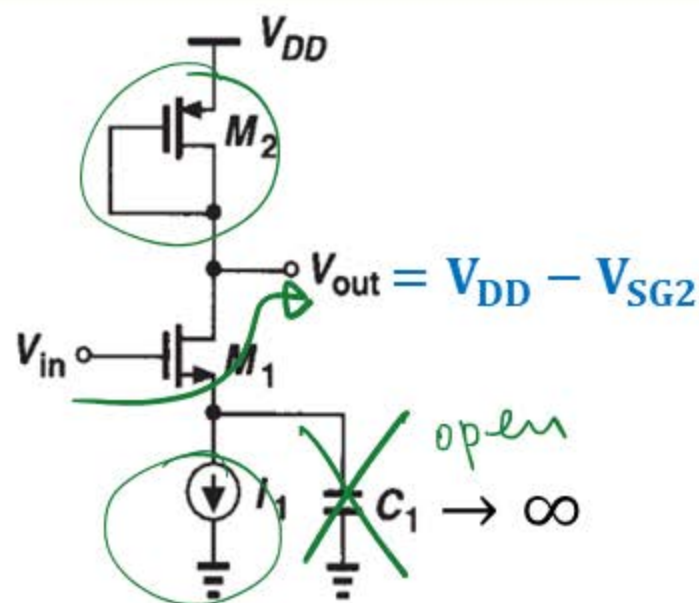

$$V_{in} \leq \underbrace{V_{DD} - V_{SG2}}_{V_{OUT}} + V_{TH1}$$

When V_{in} higher than $V_{OUT} + V_{TH1}$, M_1 will be driven into triode.

1^o DC biasing analysis


$$I_1 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \cdot$$

$$\left(V_{DD} - V_{OUT} - \underbrace{(V_{TH2})}_{0.8} \right)^2 \cdot$$

$$[1 + \lambda (V_{DD} - V_{OUT})]$$

$$V_{OUT} = ?$$

Source Follower as Level Shifter

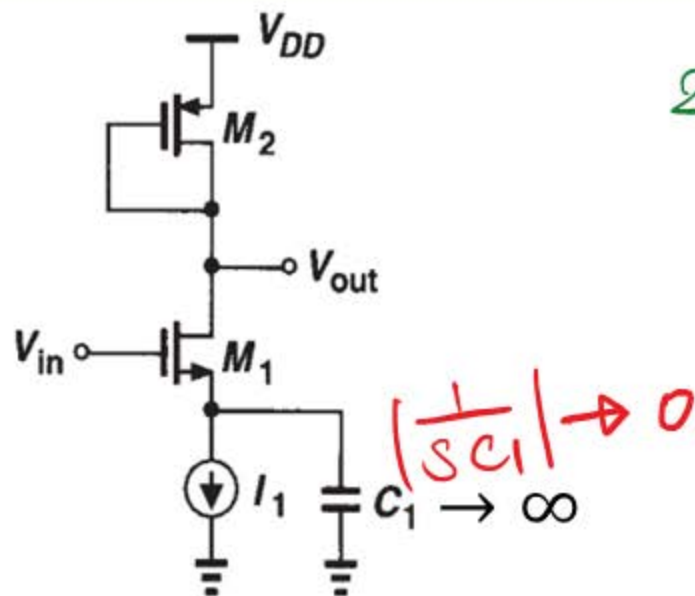

2^o small signal analysis

$$\begin{cases} G_m = -g_{m1} \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}} \\ R_m = \infty \end{cases}$$

