
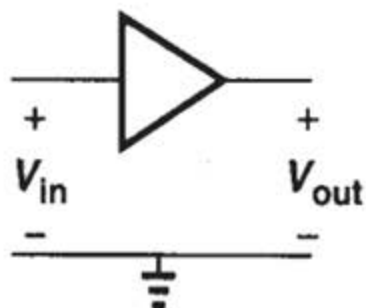


# Ideal Amplifier


Voltage Amp.

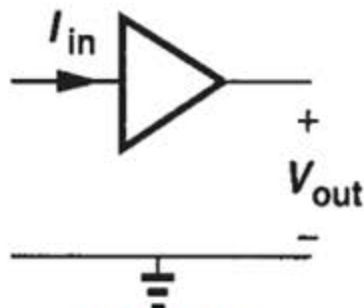




Transimpedance Amp.





Transconductance Amp.

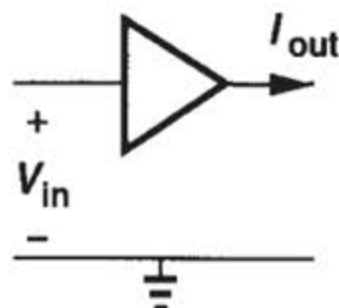

Current Amp.

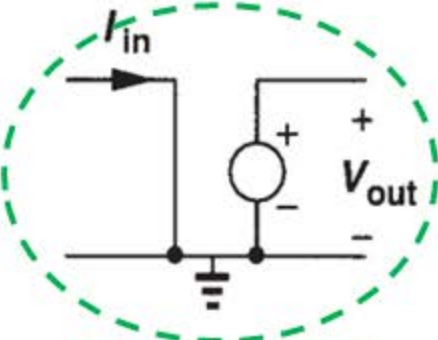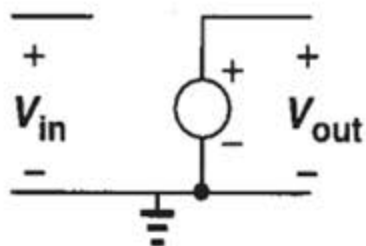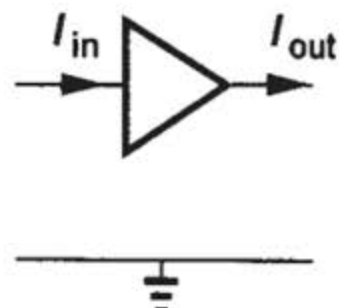

Common-Gate  
+ Source Follower

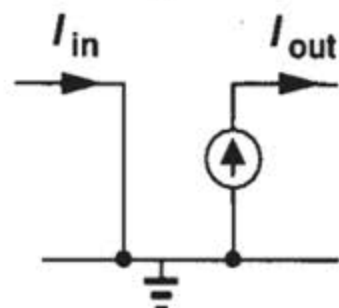
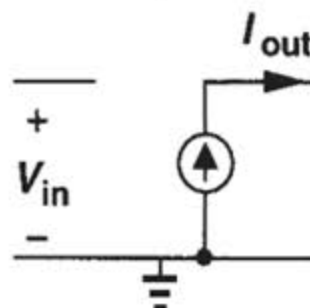


- For converting and amplifying small-signal current to voltages, common-gate provides **low input impedance** and **moderate gain**, but relatively **large output impedance**.

# NOT Ideal Amplifier

2



Voltage Amp.

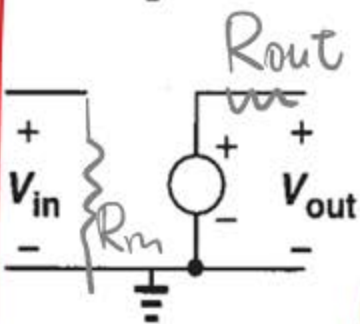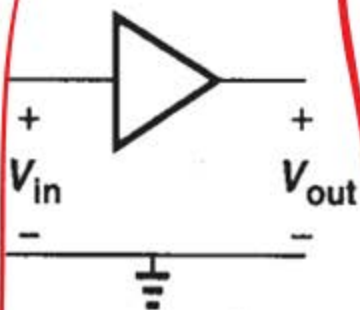

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$



Transimpedance Amp.

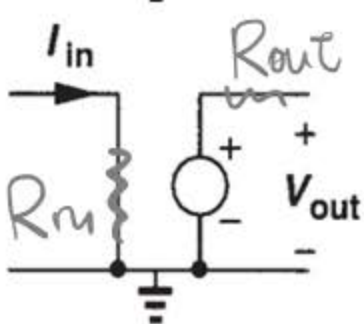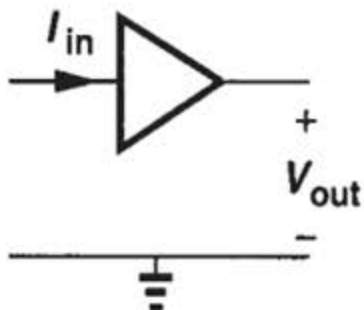

$$R_{in} \rightarrow 0$$

$$R_{out} \rightarrow 0$$



Transconductance Amp.

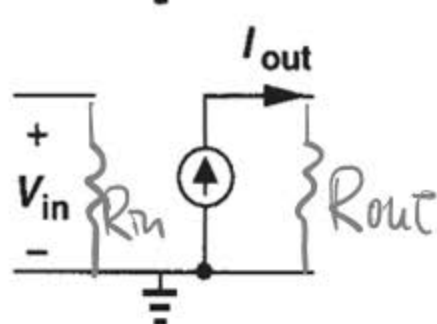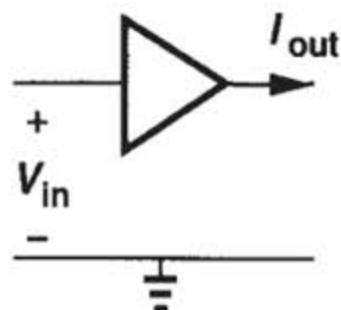

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow \infty$$


Current Amp.

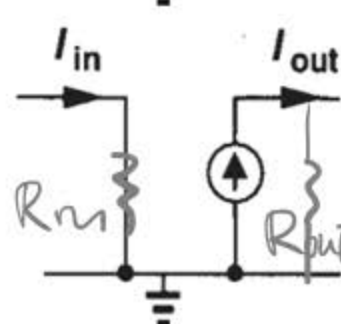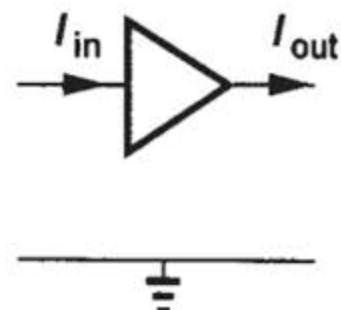


$$R_{in} \rightarrow 0$$

$$R_{out} \rightarrow \infty$$


complete

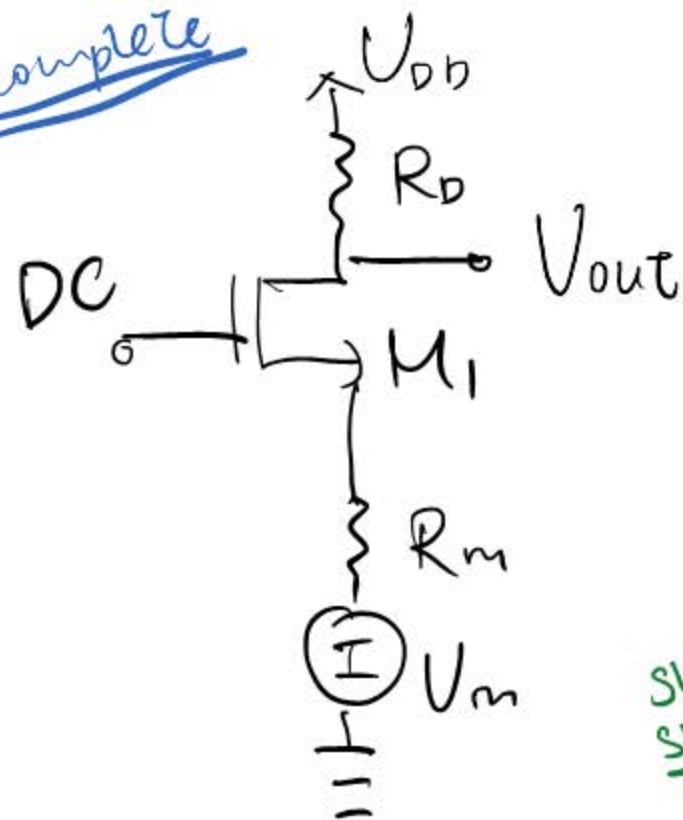

small signal

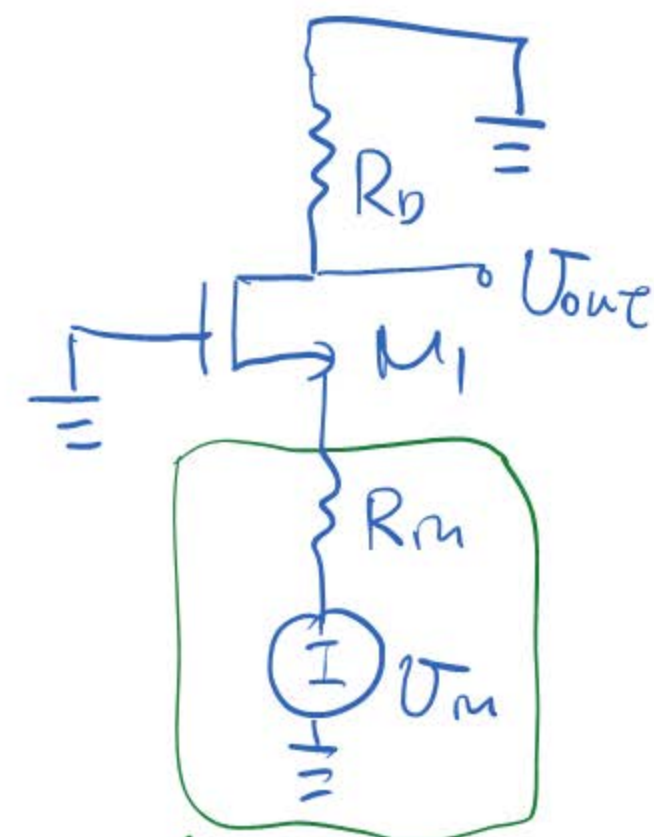


small signal

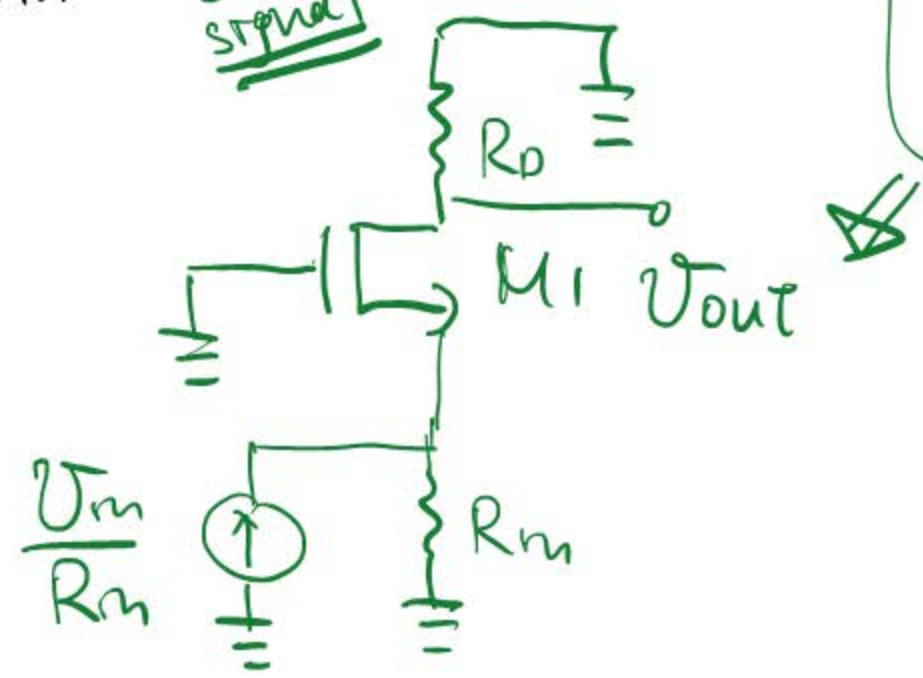

When calculating  $G_m = ?$

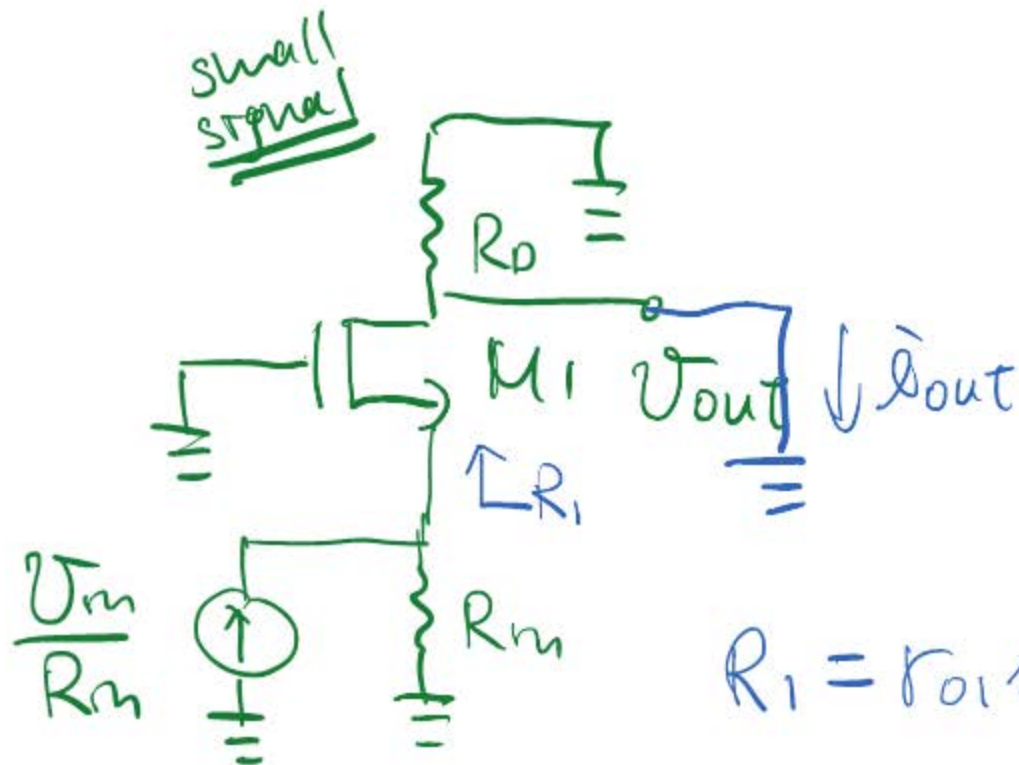
$$\hat{i}_{out} = \frac{V_m}{R_m} \cdot \frac{\cancel{R_m}}{R_1 + R_m} = V_m \left( \cancel{r_{o1}} \parallel \frac{1}{g_{m1} + g_{mb1}} \right) + R_m$$



$$R_1 = r_{o1} \parallel \frac{1}{g_{m1} + g_{mb1}}$$

When calculating  $R_{out} = ?$
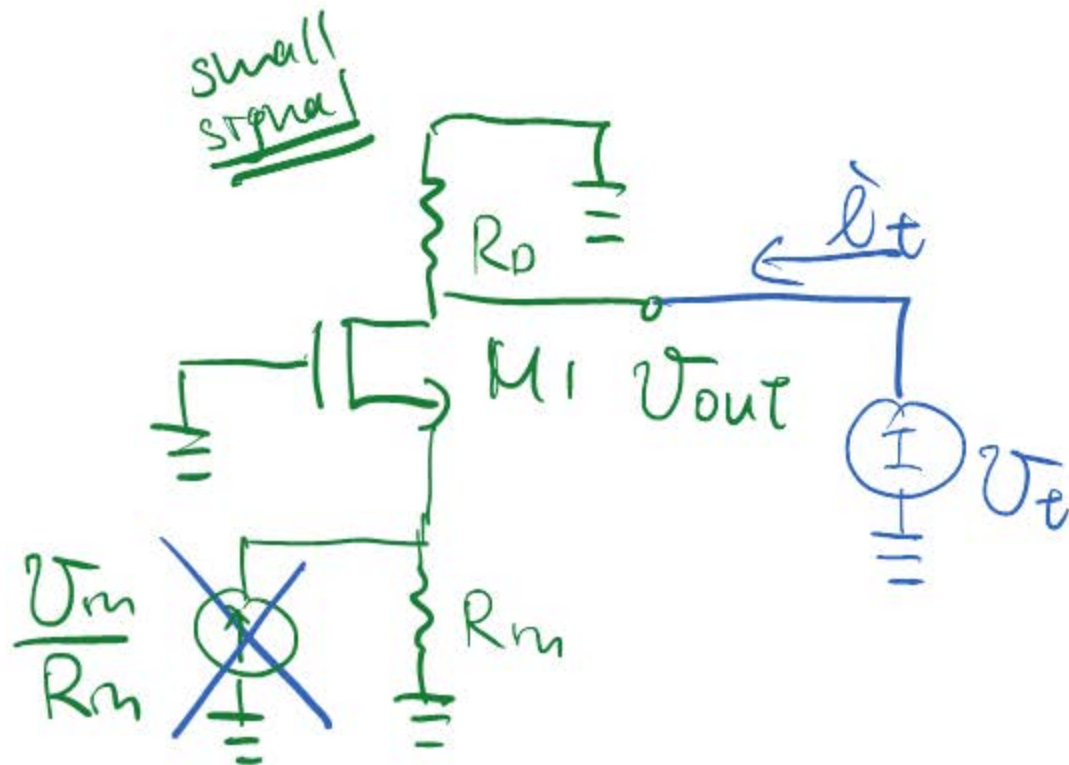
$$R_{out} = \frac{V_e}{\hat{v}_e} = R_D \parallel \left[ r_{o1} + R_m + (g_{m1} + g_{m1} b_1) r_{o1} R_m \right]$$





# Common-Gate



## DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

$$V_{SB1} = V_{IN}$$

$$V_{sb1} = V_m$$

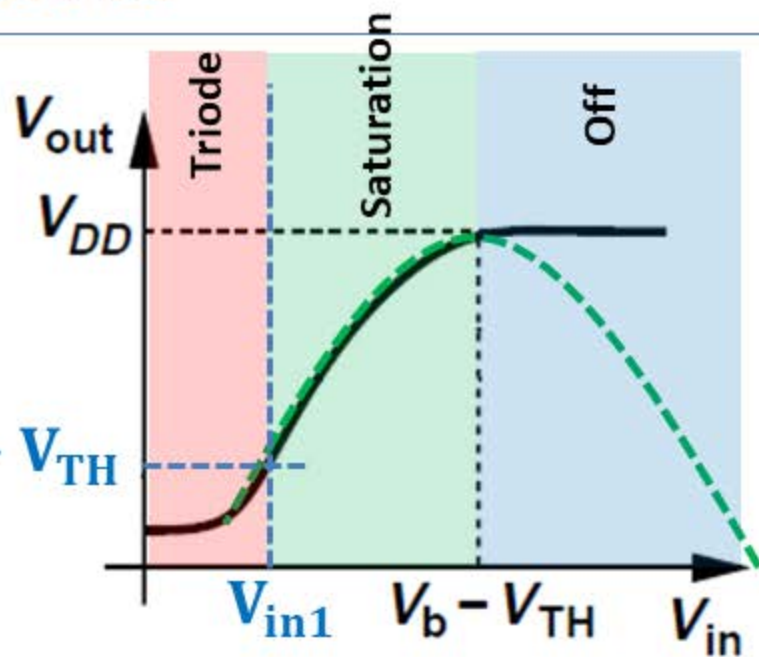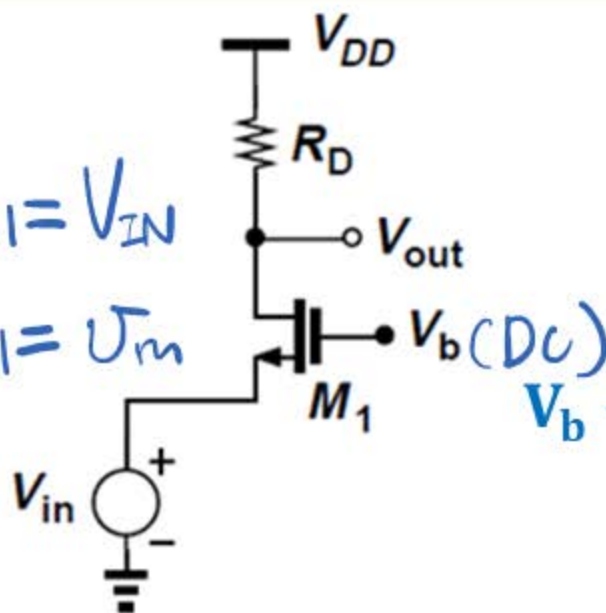

- $V_{in} > V_b - V_{TH} \rightarrow M_1$  Off

$$V_{out} = V_{DD}$$

- $V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1$  in Saturation

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$

- $V_{in} < V_{in1} \rightarrow M_1$  in Triode

$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} [(V_b - V_{in} - V_{TH})(V_{out} - V_{in}) - \frac{1}{2} (V_{out} - V_{in})^2]$$

$$V_{out} = V_b - V_{TH}$$

$$= V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_b - V_{in1} - V_{TH})^2$$

# Common-Gate

## DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

- $V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1$  in Saturation

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$


$$\frac{\partial V_{out}}{\partial V_{in}} = -R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_b - V_{in} - V_{TH}) \left( -1 - \frac{\partial V_{TH}}{\partial V_{in}} \right)$$

$$= R_D \underbrace{\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})}_{= gm} \left( 1 + \underbrace{\frac{\partial V_{TH}}{\partial V_{in}}}_{= \eta} \right) \quad V_m = V_{SB} \quad \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = R_D gm(1 + \eta) \neq R_D (gm + g_{mb})$$

- $gm$  is a function of  $I_D$  and  $\eta$  is a function of  $V_{SB}$ .
- $A_v$  is not quite linear.

complete

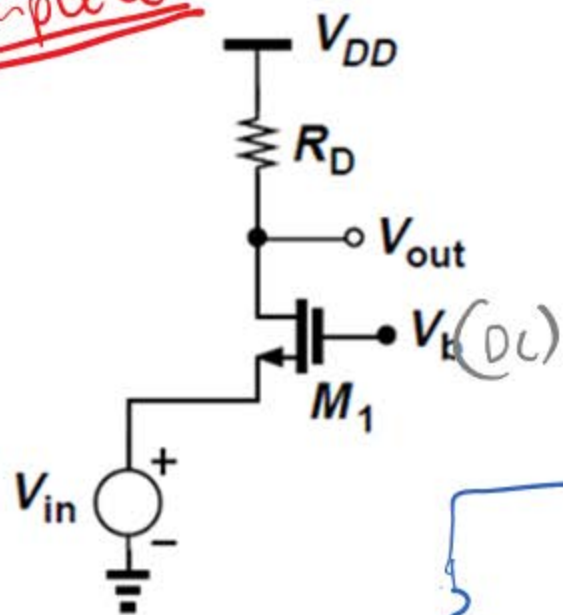

Assume  $\lambda = 0$ ,  $r \neq 0$



Assume  $M_1$  in sat.

$\therefore G_m = ?$

$$G_m = \frac{\hat{v}_{out}}{\hat{v}_m}$$


$$= g_{m1} + g_{mb1}$$

small signal

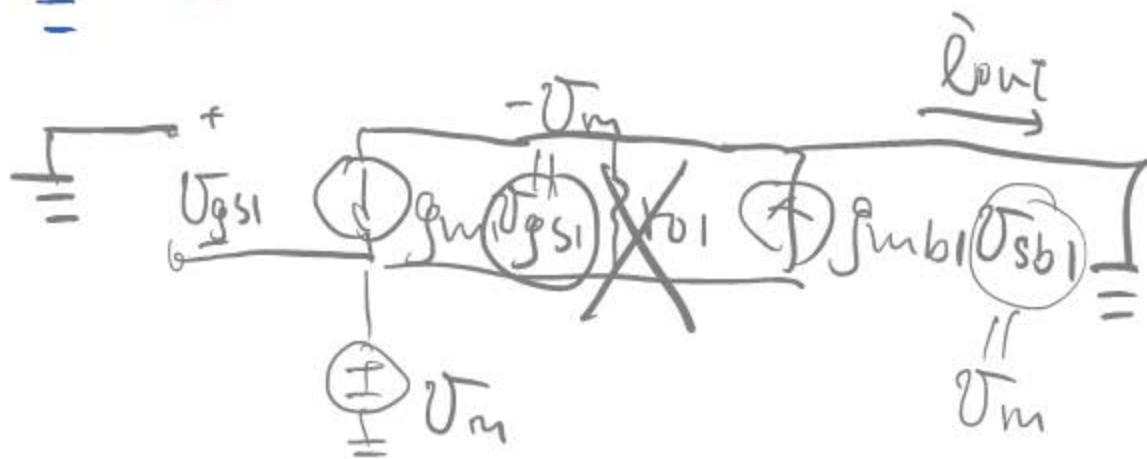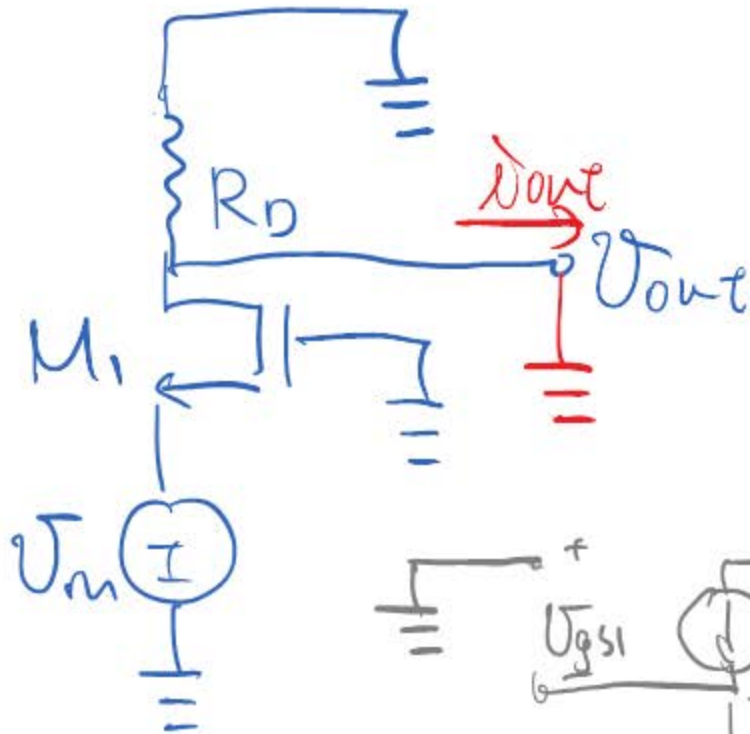



complete

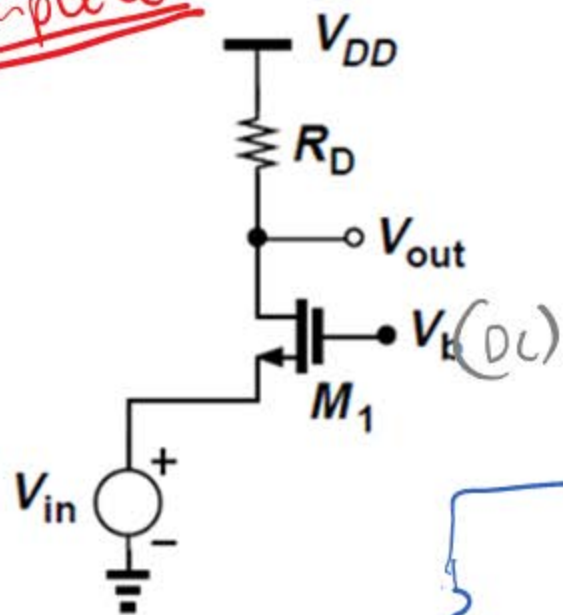



Assume  $\lambda = 0$ ,  $r \neq 0$

Assume  $M_1$  in sat.

2°  $R_{out} = ?$

$$R_{out} = \frac{V_t}{\bar{i}_t} = R_D$$

small signal

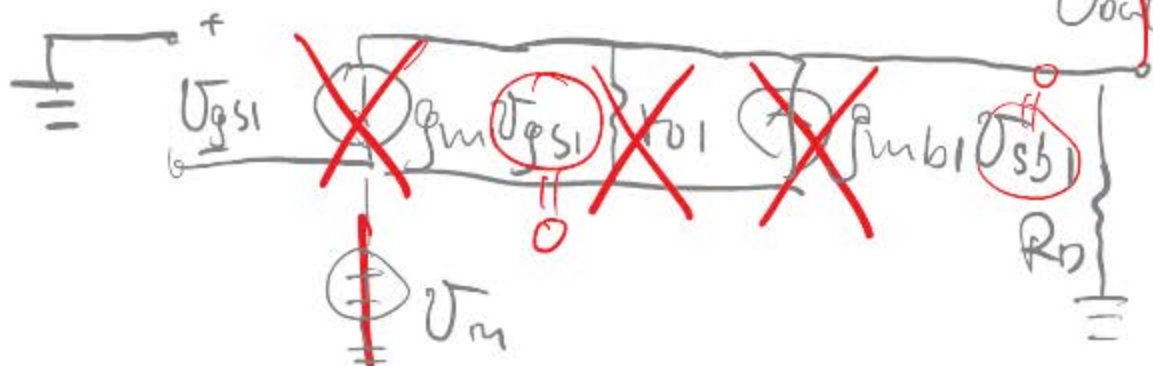
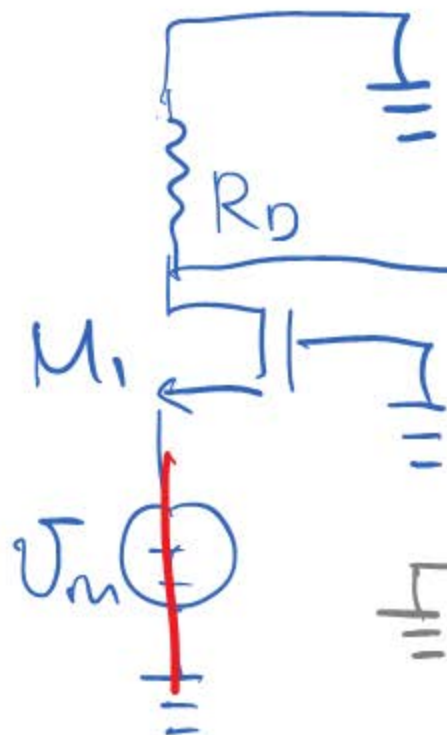


# Common-Gate

Small-signal  
Analysis

$\lambda \neq 0$

$\gamma \neq 0$

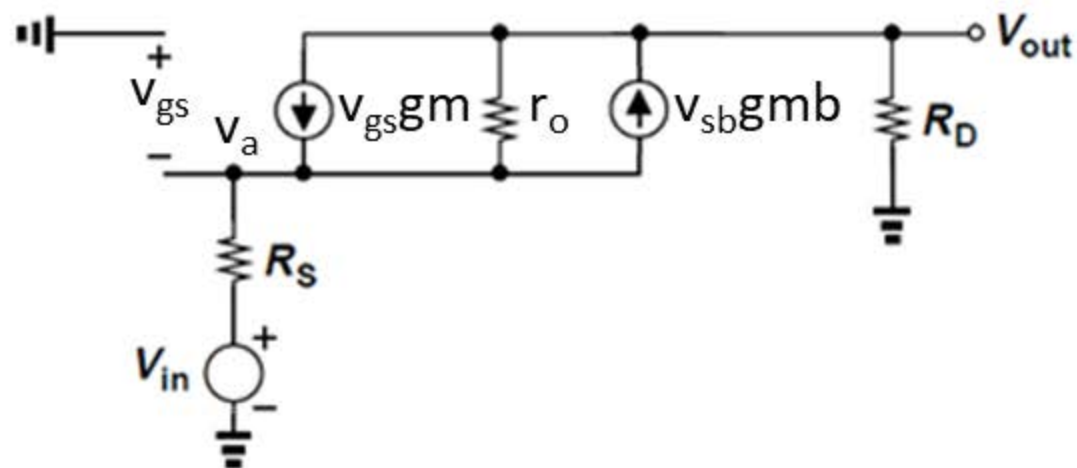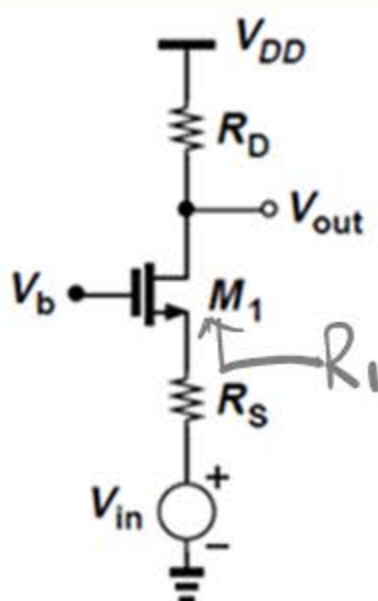

$$G_m = \frac{(g_m + g_{mb})r_o + 1}{r_o + R_S + (g_m + g_{mb})r_o R_S}$$

$$R_{out} = R_D \parallel [r_o + R_S + (g_m + g_{mb})r_o R_S]$$

$$A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + R_S + (g_m + g_{mb})r_o R_S + R_D} R_D \approx R_D g_m (1 + \eta)$$


If  $R_S = 0$  and  $r_o = \infty$

# Common-Gate (Input Impedance)

Small-signal  
Analysis

$\lambda \neq 0$

$\gamma \neq 0$

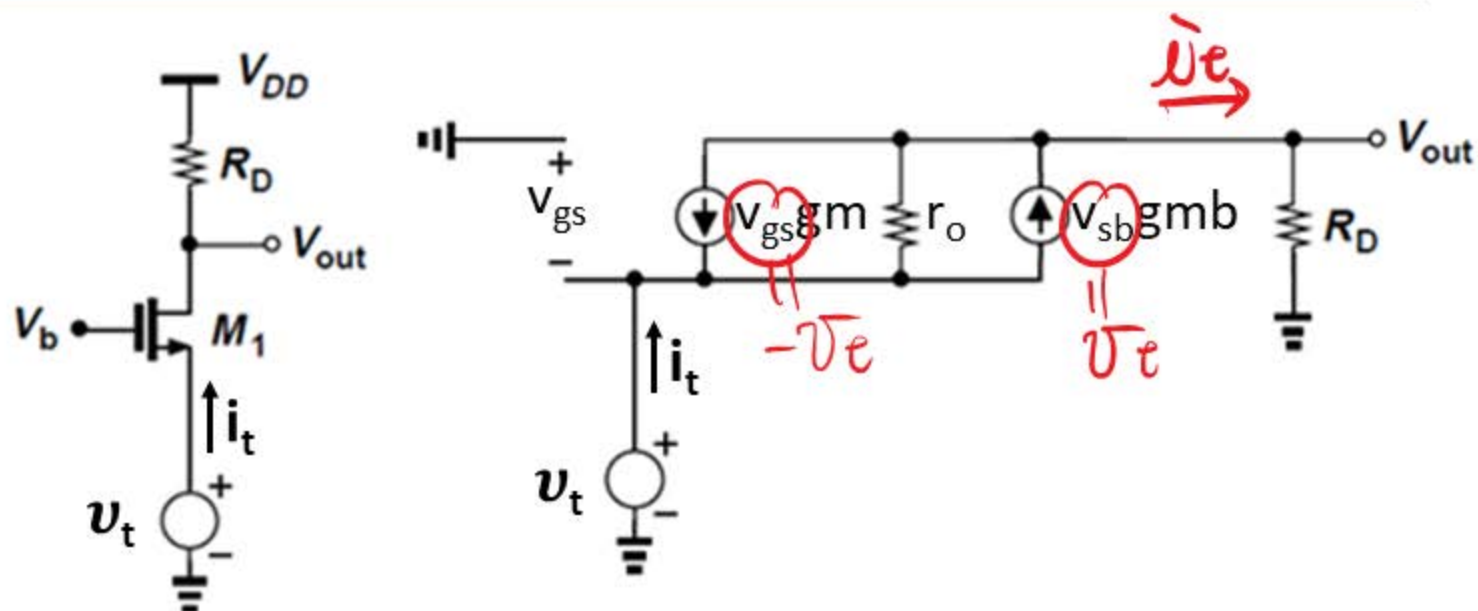


$$\begin{cases} i_t = v_t(gm + gmb) + \frac{v_t - v_{out}}{r_o} \\ v_{out} = R_D i_t \end{cases}$$


$$R_{in} = \frac{R_D + r_o}{1 + (gm + gmb)r_o}$$

If  $R_D = 0$   $R_{in} = r_o \parallel \frac{1}{gm} \parallel \frac{1}{gmb}$

If  $R_D = \infty$   $R_{in} = \infty$

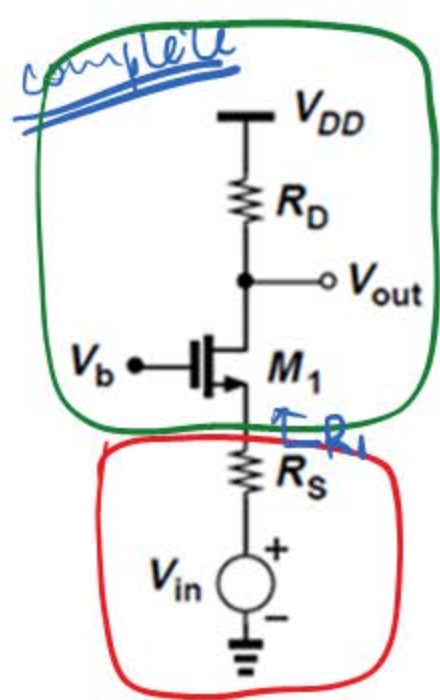

Equivalent  
small-signal

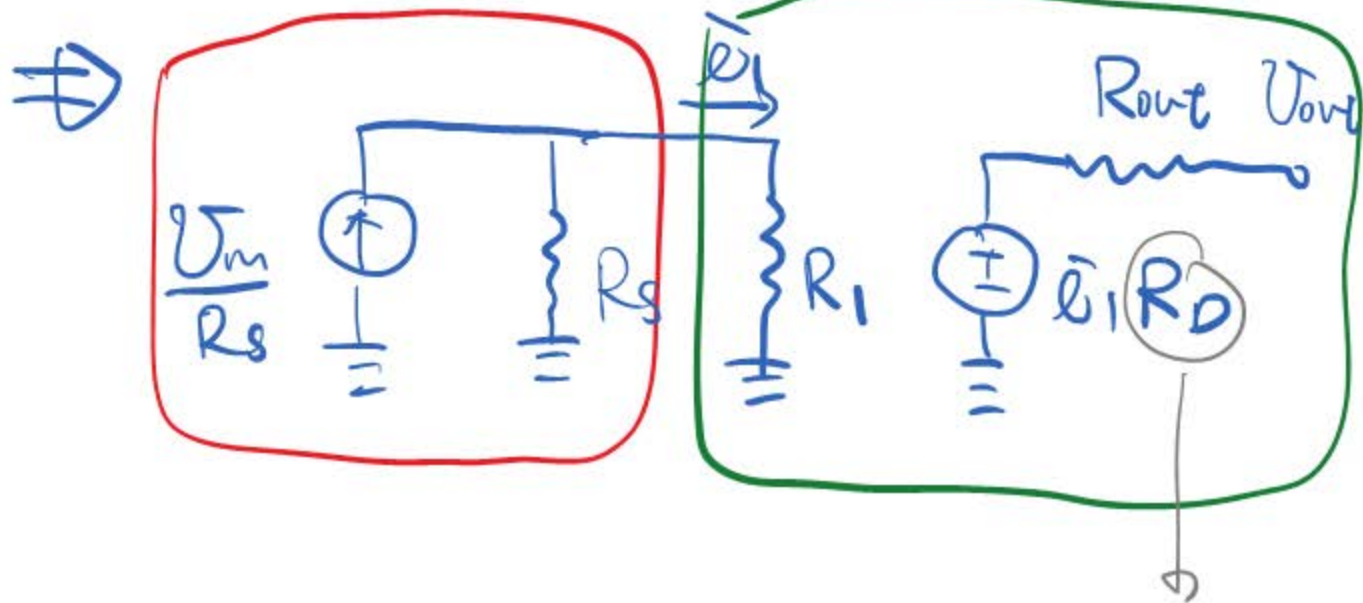

$$R_1 = \frac{R_D + r_{o1}}{1 + (g_{m1} + g_{mb1})r_{o1}}$$

$$V_{gs1} = \frac{R_S}{R_S + R_1} V_{in}$$


Trans-  
Impedance  
gain.

# Common-Gate (Output Impedance)

## Small-signal Analysis

$\lambda \neq 0$

$\gamma \neq 0$

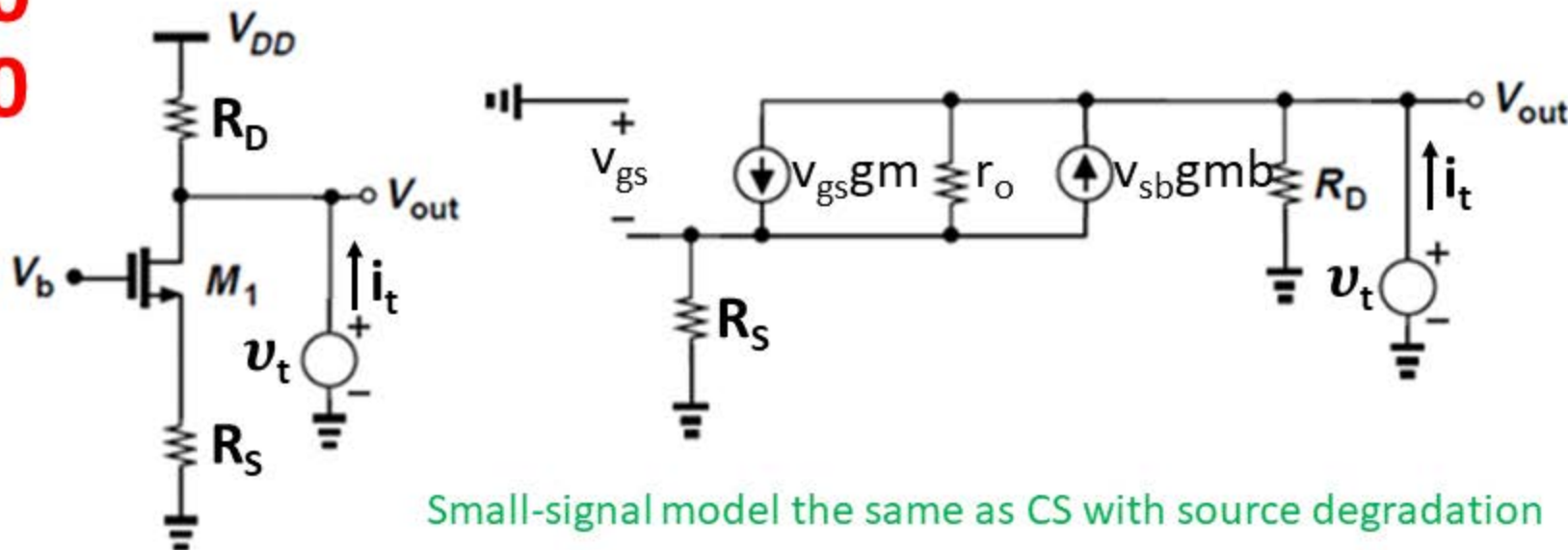

Small-signal model the same as CS with source degradation


$$R_{out} = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D$$




# Example

Calculate the small-signal voltage gain at low frequencies of the circuits below. To minimize wave reflection at point X, the input impedance must be equal to  $50\ \Omega$ .

Assume  $\lambda = 0$

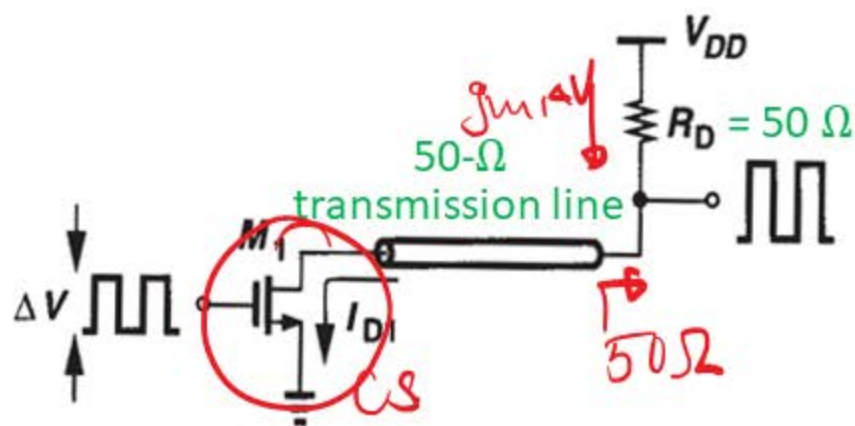


$$A_v = -g_{m1} R_D = 50\ \Omega$$

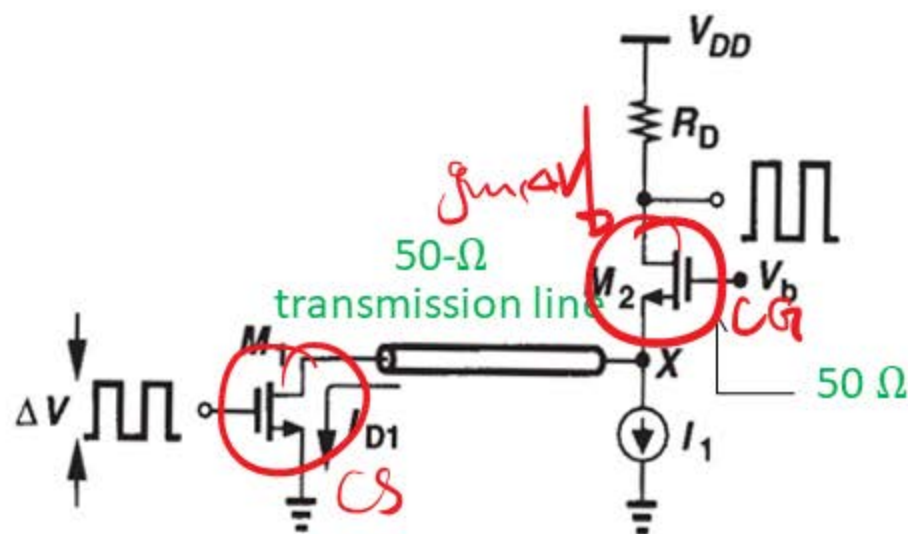

$$A_v = -g_{m1} R_D$$

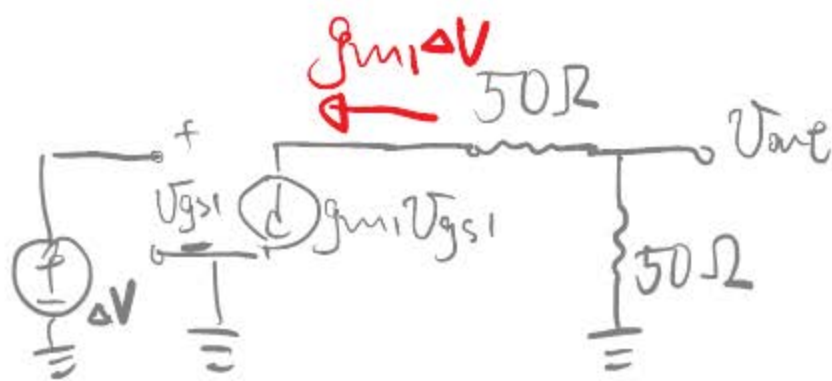can be much larger than  $50\ \Omega$ , so as to achieve a much higher gain.



$$R_{in} = \frac{R_D + r_{o2}}{1 + (g_{m2} + g_{mb2})r_{o2}} = 50\ \Omega$$

# Example

Calculate the small-signal voltage gain of the circuit below. ( $\lambda \neq 0$ ,  $\gamma \neq 0$ )

