
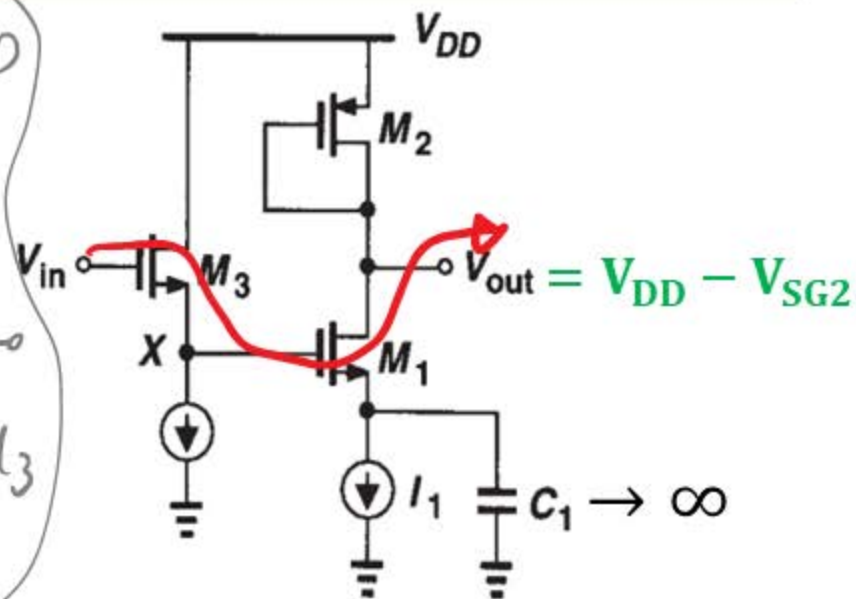
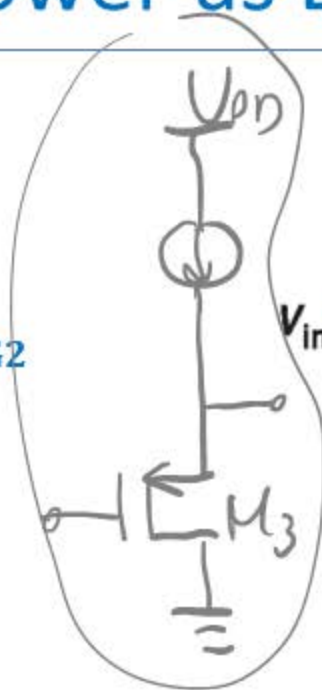


Source Follower as Level Shifter

1

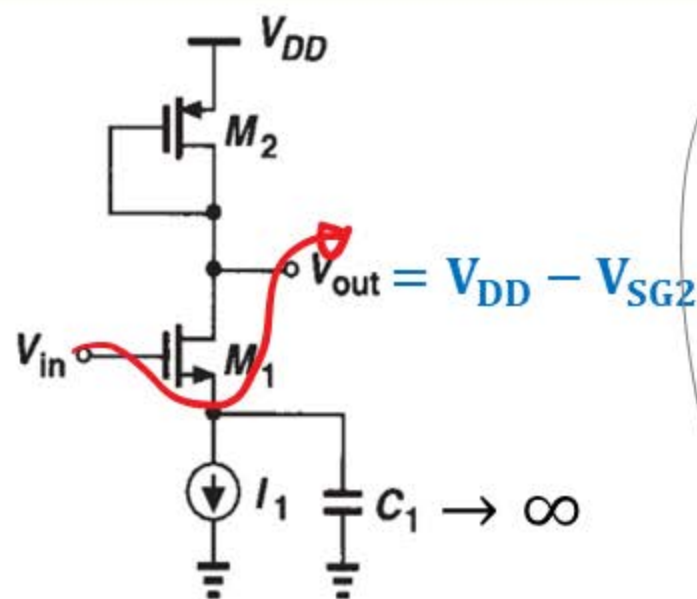

$$V_{in} \leq V_{DD} - V_{SG2} + V_{TH1}$$


$$V_{in} - V_{GS3} \leq V_{DD} - V_{SG2} + V_{TH1}$$

$$\begin{cases} G_m = -gm_1 \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$

$$\begin{cases} G_{m(left)} = gm_3 \\ R_{out(left)} = r_{o3} \parallel \frac{1}{gm_3 + gmb_3} \end{cases}$$

$$\begin{cases} R_{in(right)} = \infty \\ G_{m(right)} = -gm_1 \\ R_{out(right)} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$

Source Follower as Level Shifter

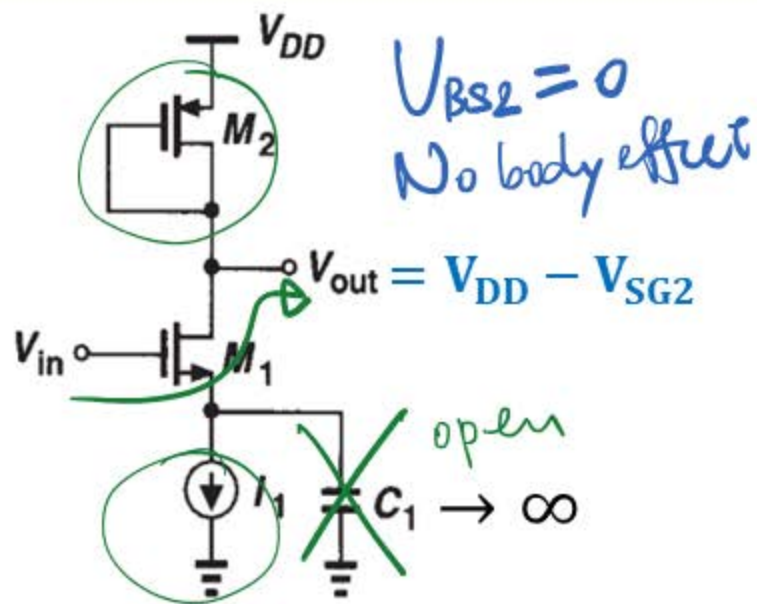

$$V_{in} \leq \underbrace{V_{DD} - V_{SG2}}_{V_{out}} + V_{TH1}$$

When V_{in} higher than $V_{out} + V_{TH1}$, M_1 will be driven into triode.



1^o DC biasing analysis

$$I_1 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right)_2 \cdot$$

$$\frac{(V_{DD} - V_{out} - (V_{TH2}))^2}{2} \cdot [1 + \lambda(V_{DD} - V_{out})]$$

$$V_{out} = ?$$


Source Follower as Level Shifter

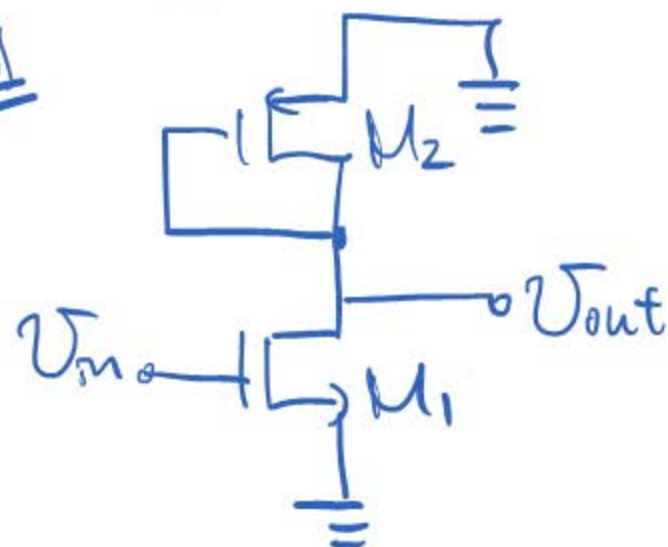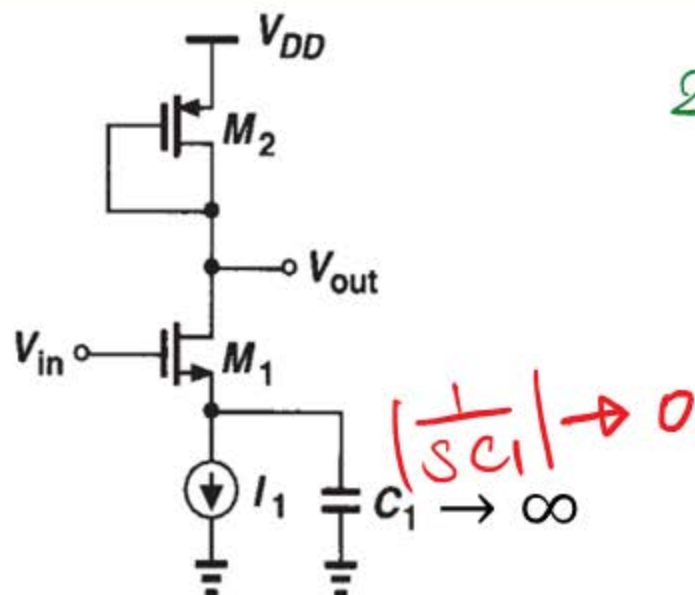


2^o small signal analysis

$$\begin{cases} G_m = -g_{m1} \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}} \\ R_{in} = \infty \end{cases}$$

$$G_m = \frac{I_{out}}{V_{in}}$$

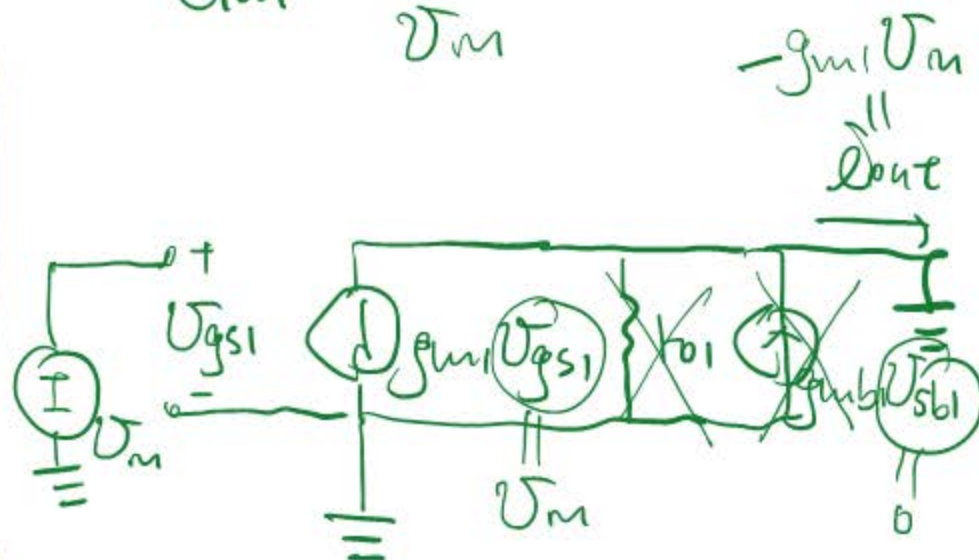


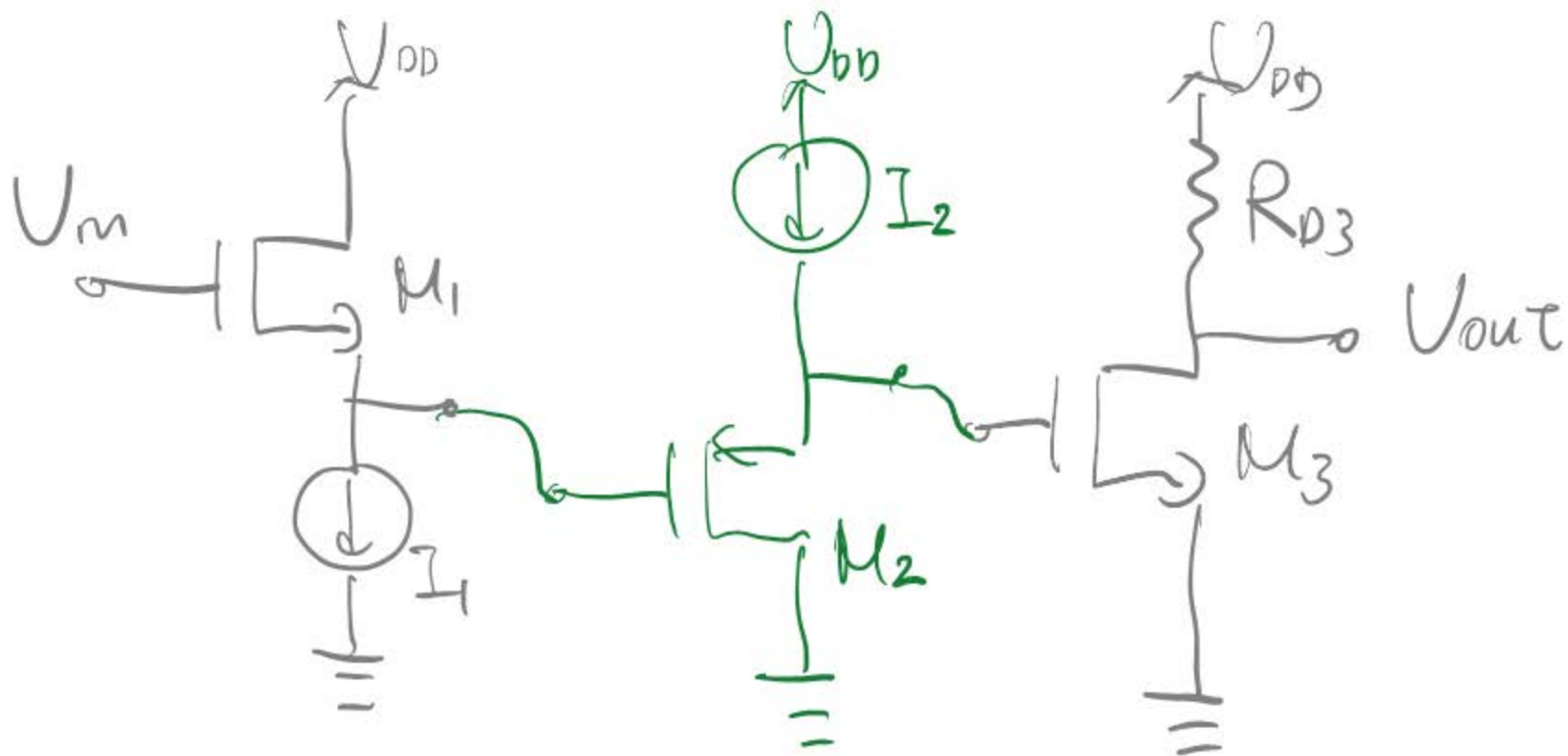

Assume $\lambda = r = 0$, $A_v = ?$


$$A_v = | \times | \times (-g_{m3} R_{D3})$$

CS + Source Follower

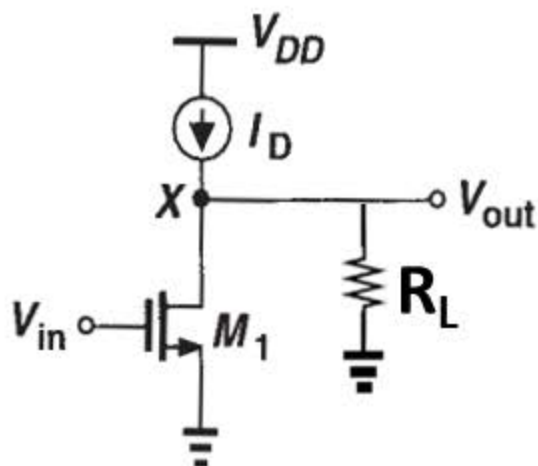

$$A_v = -g_{m1}(r_{o1} \parallel R_L)$$

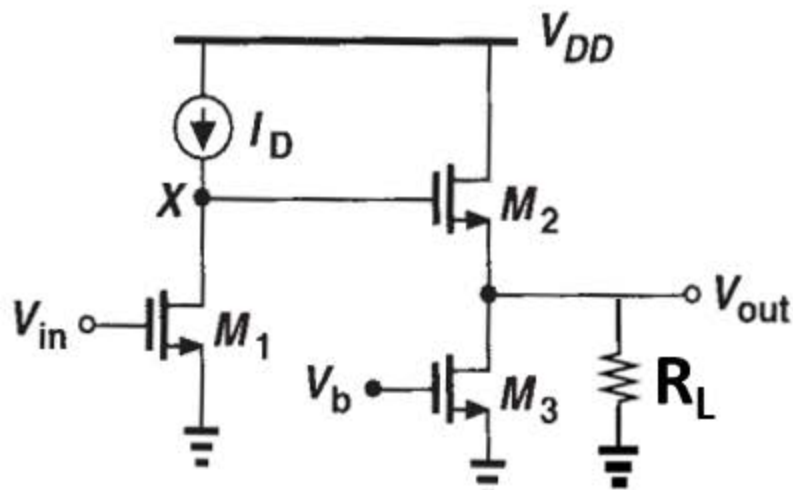- Voltage gain severely reduced when R_L very small




$$A_v = -g_{m1}r_{o1} \times$$

$$g_{m2} \left(r_{o2} \parallel \overset{\text{small}}{\frac{1}{g_{m2} + g_{mb2}}} \parallel r_{o3} \parallel R_L \right)$$


- Voltage gain maintained when R_L very small

Voltage Gain Buffer

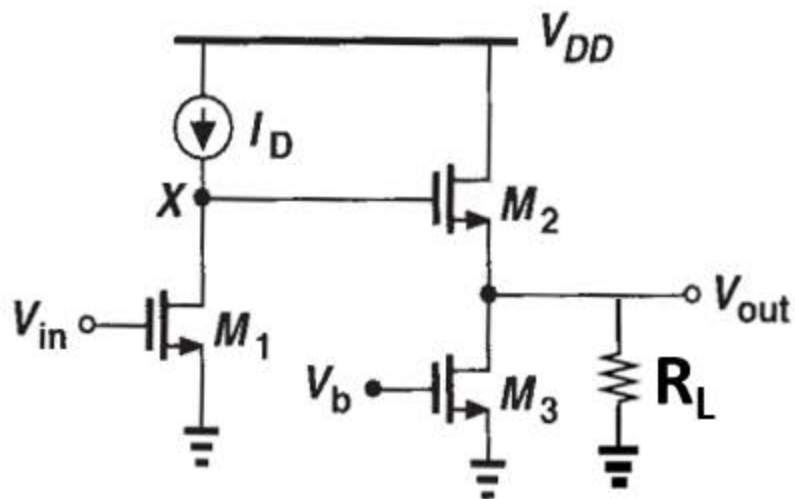

$$A_v = -g_{m1} r_{o1} \times$$
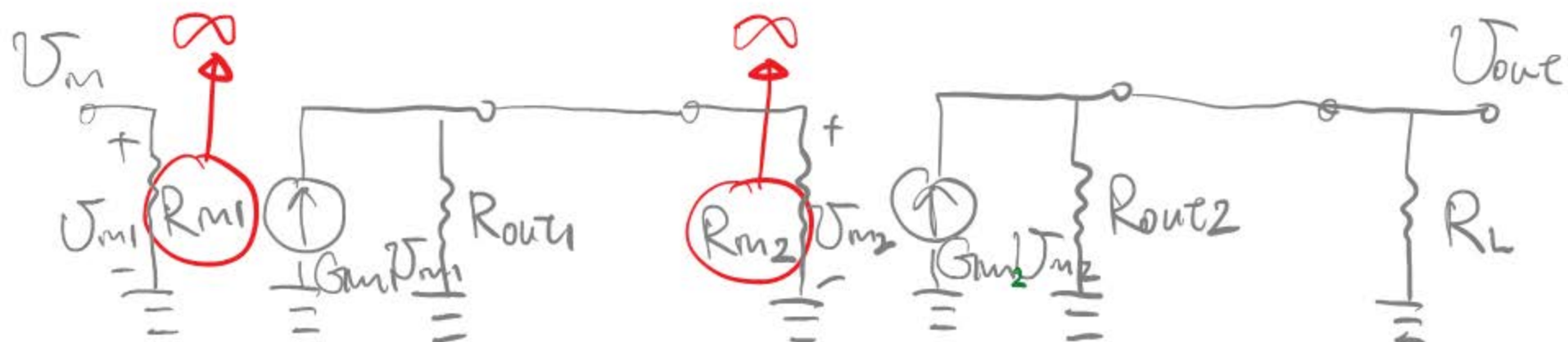
$$g_{m2} \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o3} \parallel R_L \right)$$



$$G_{m1} = -g_{m1}$$


$$R_{out1} = r_{o1}$$

$$G_{m2} = g_{m2}$$

$$R_{out2} = r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o3}$$

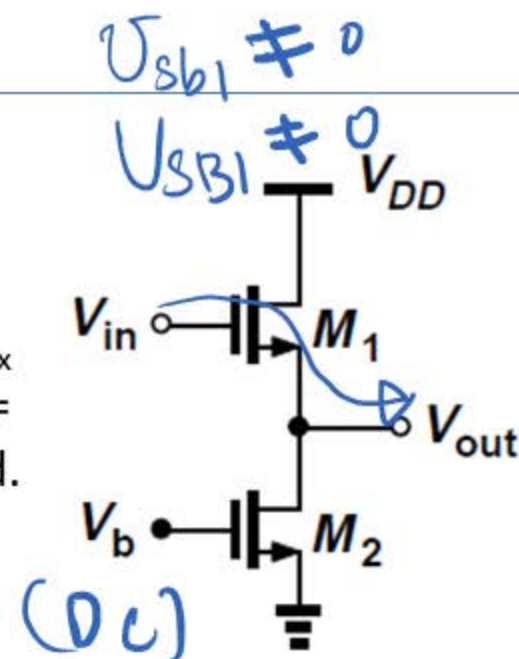Example

$(W/L)_1 = 20/0.5$, $I_D = 0.2$ mA, $V_{TH0} = 0.6$ V, $2\Phi_F = 0.7$ V, $\mu_n C_{ox} = 50$ $\mu\text{A/V}^2$, $\gamma = 0.4$ $\text{V}^{1/2}$ and $\lambda = 0$. (a) Calculate V_{out} for $V_{in} = 1.2$ V. (b) Minimum $(W/L)_2$ for which M_2 remains saturated.



Solution:

$$(a) \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH1})^2 \rightarrow V_{out} = 0.153 \text{ V} = V_{sb1}$$

$$V_{TH1} = V_{TH0} + \gamma (\sqrt{2\Phi_F + V_{out}} - \sqrt{2\Phi_F}) = 0.635 \text{ V} \rightarrow V_{out} \approx 0.118 \text{ V}$$

$$(b) \quad V_{out} = 0.118 \text{ V} \geq V_{GS2} - V_{TH2} \text{ for } M_2 \text{ to stay in sat.}$$



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_{TH2})^2 \rightarrow \left(\frac{W}{L}\right)_2 \geq \frac{283}{0.5}$$

Example

Calculate the small signal voltage gain of the circuit below.

Assume all in sat.

Assume $\lambda \neq 0$, $\gamma \neq 0$

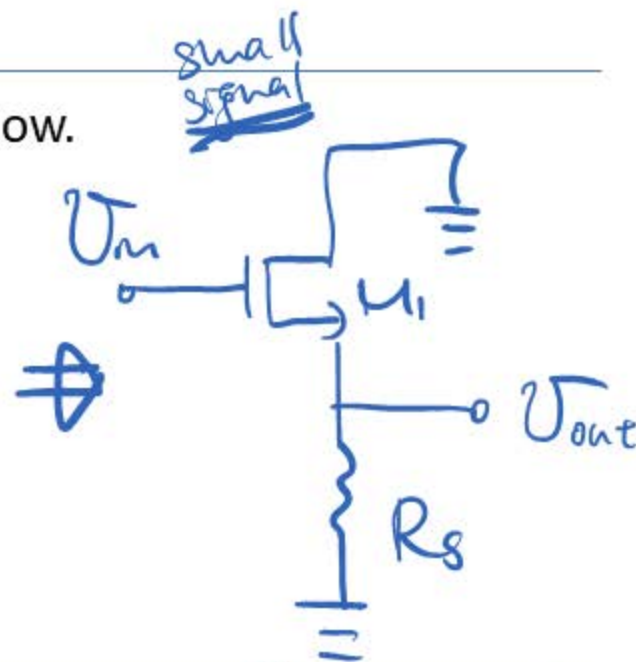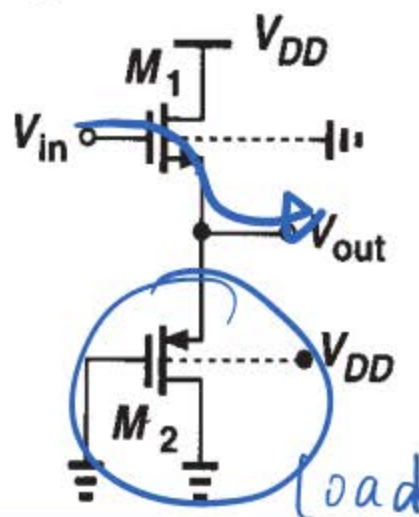

Solution:

$$G_m = g_{m1}$$

$$R_{out} = \frac{1}{g_{m1} + g_{mb1}} \parallel r_{o1} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2}$$


$$A_v = G_m R_{out}$$

$$R_s = r_{o2} \parallel \left(\frac{1}{g_{m2} + g_{mb2}} \right)$$

CS } both are Voltage-in-Voltage-out
SF } amplifiers.

Common-Gate (CG)

Current-in-Voltage-out

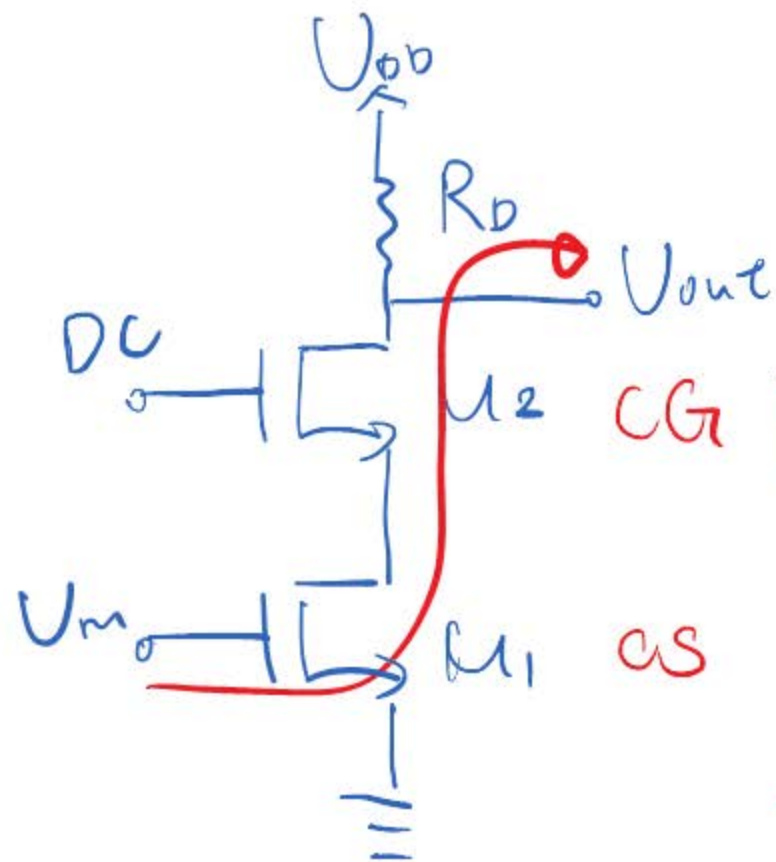


Assume M_1 and M_2 in Sat.

Assume $\lambda \neq 0$, $\theta \neq 0$

$A_V = ?$

Cascode

Small signal

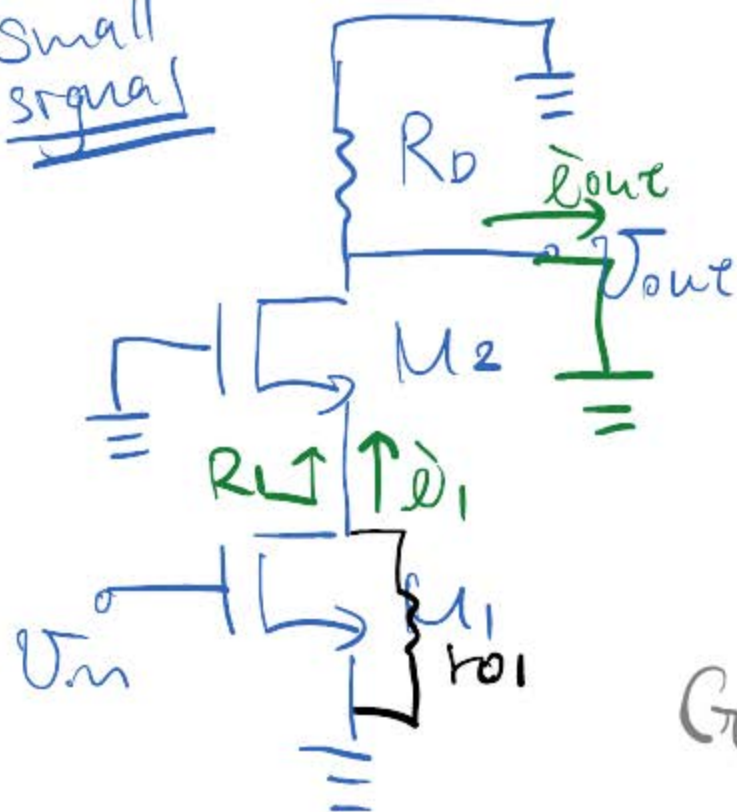

$$G_m = \tilde{i}_{out} / V_m$$

$$\tilde{i}_1 = \tilde{i}_{out}$$

$$R_1 = r_{o2} // \frac{1}{g_{m2} + g_{mb2}}$$

$$\tilde{i}_1 = (-g_{m1} V_m) \frac{r_{o1}}{r_{o1} + R_1}$$

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + (r_{o2} // \frac{1}{g_{m2} + g_{mb2}})}$$

$-g_{m1} V_m$ (red arrow pointing right)
 \tilde{i}_1 (green arrow pointing right)

