
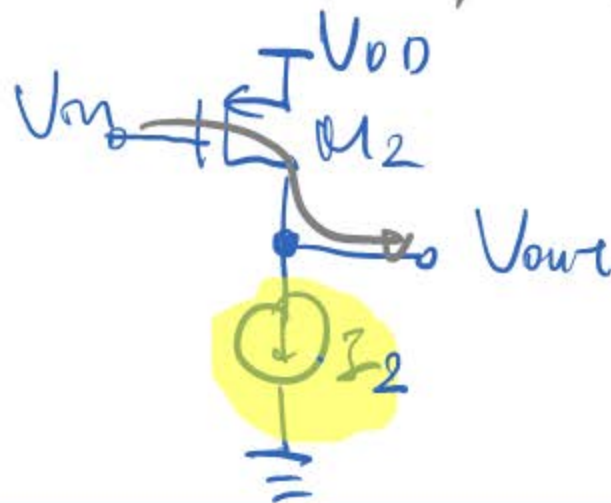


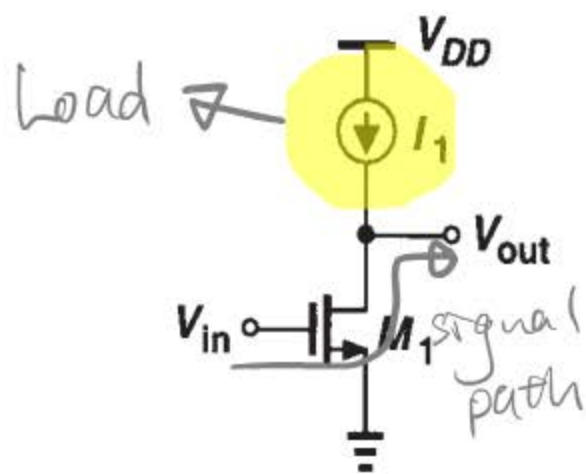Example

Assuming M_1 in saturation, calculate its small-signal gain. (analytical form)



Solution:

- Small-signal Analysis:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} r_{o1} \approx \frac{1}{\pi f_{o1}}$$



- DC Analysis:

$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{DS})$$

$r \neq 0$
 $\lambda \neq 0$

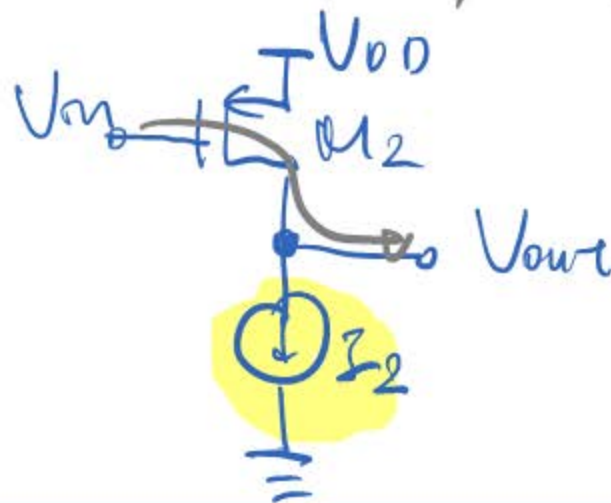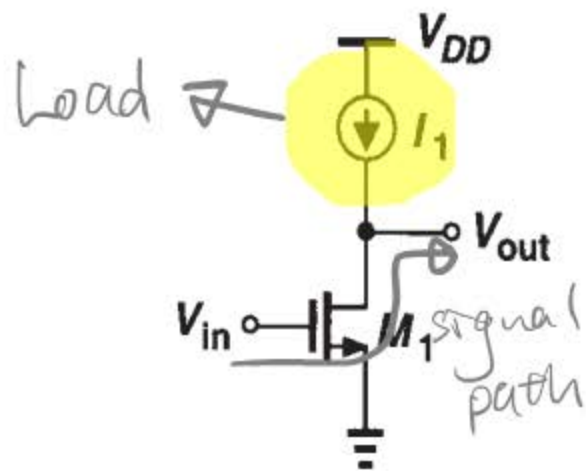Example

Assuming M_1 in saturation, calculate its small-signal gain. (analytical form)



Solution:

- Small-signal Analysis:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} r_{o1} \rightarrow \infty$$

- DC Analysis:


$$I_1 \neq \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \rightarrow V_{OOT} \text{ undefined. (floating)}$$

$$\tau = 0$$


$$r = 0$$

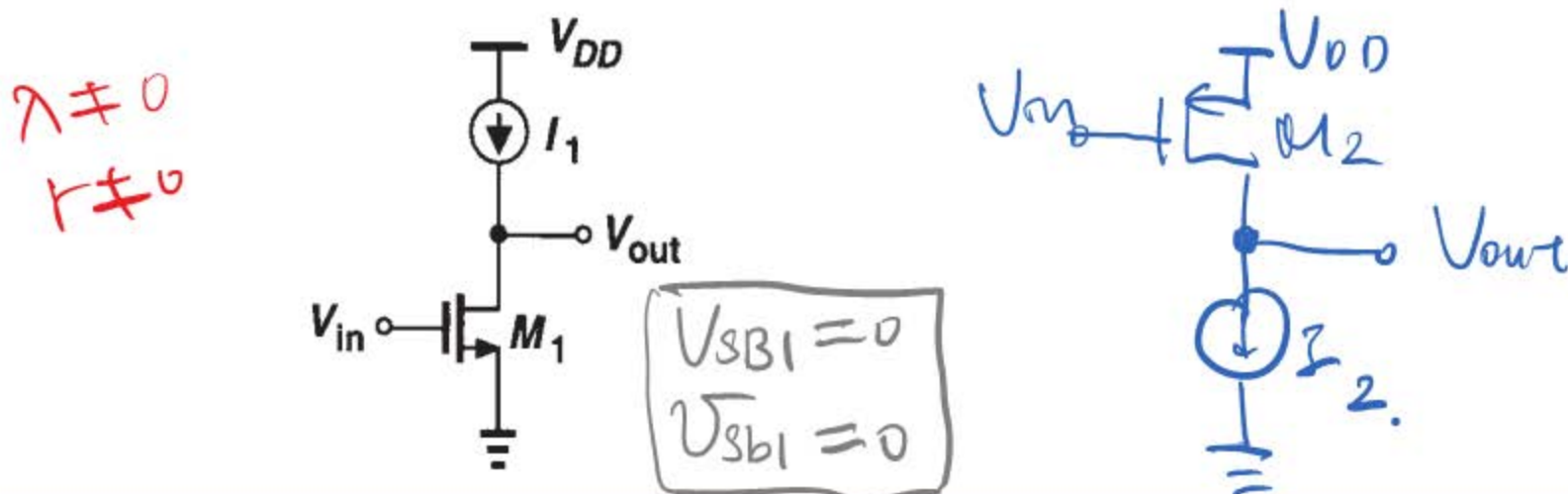Example


Assuming M_1 in saturation, calculate its small-signal gain.



Solution:

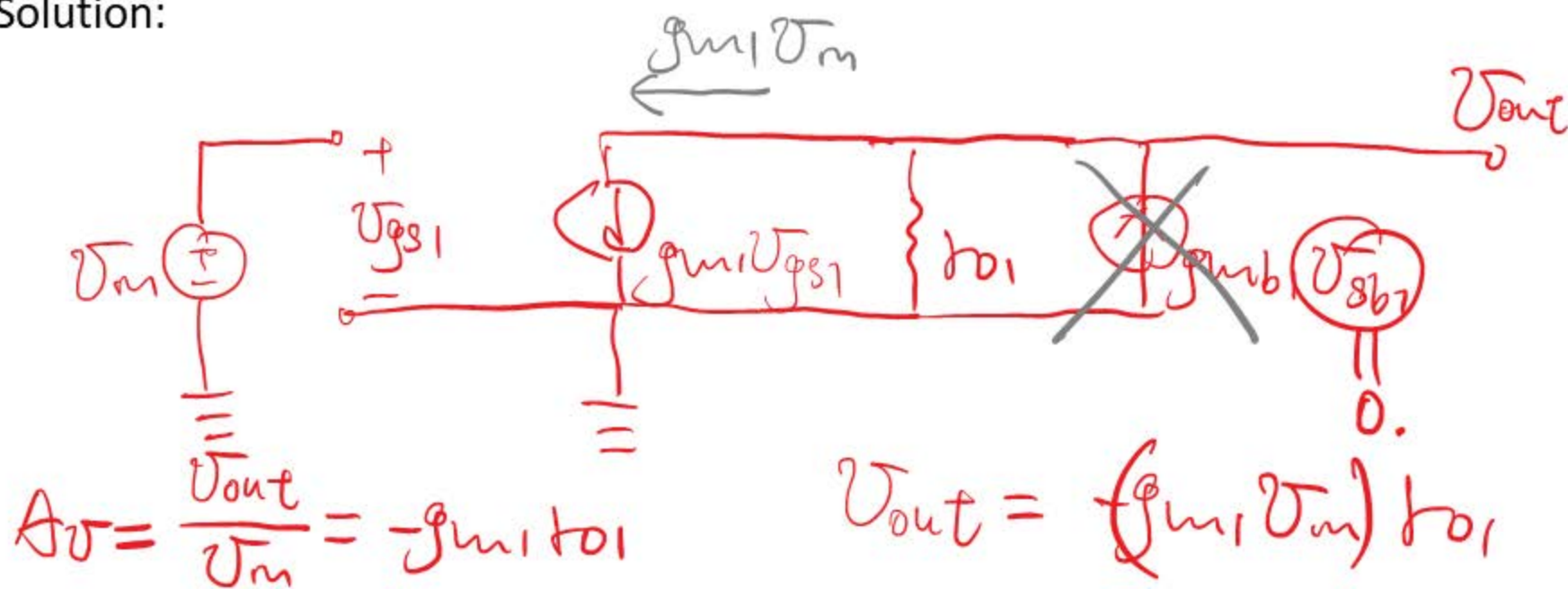

$r_{\pi} \neq 0$
 $r_{\pi} \neq 0$

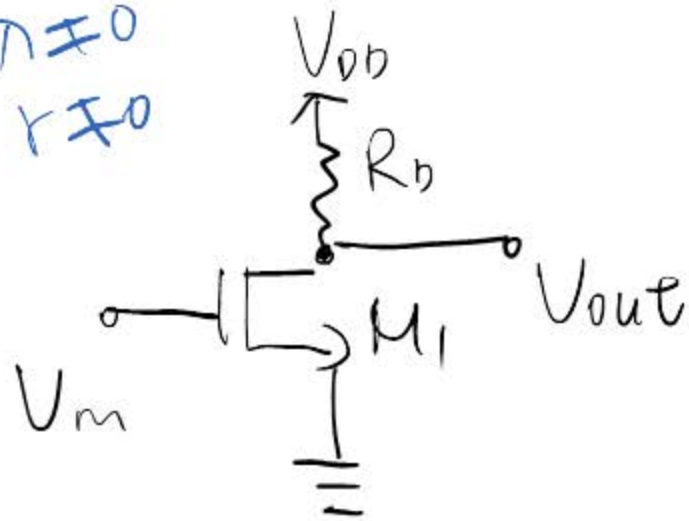


Find out the analytical expressions for A_v , R_{in} and R_{out} ?

$$1^{\circ} A_v = -g_{m1}(r_{o1} \parallel R_D)$$

2^o $R_{out} = ?$


- In small-signal circuit, turn V_m off.
- Put a test small-signal (V_t) at the output.
- Calculate small-signal current (\hat{i}_t) flowing into output.
- $R_{out} = V_t / \hat{i}_t$

$r_{\pi} \neq 0$
 $r_{\pi} \neq 0$

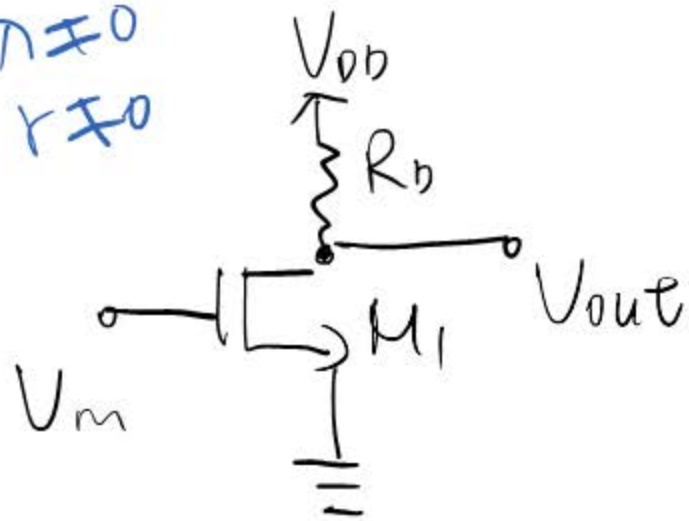


Find out the analytical expressions for A_v , R_m and R_{out} ?

2° $R_{out} = r_{o1} \parallel R_D$

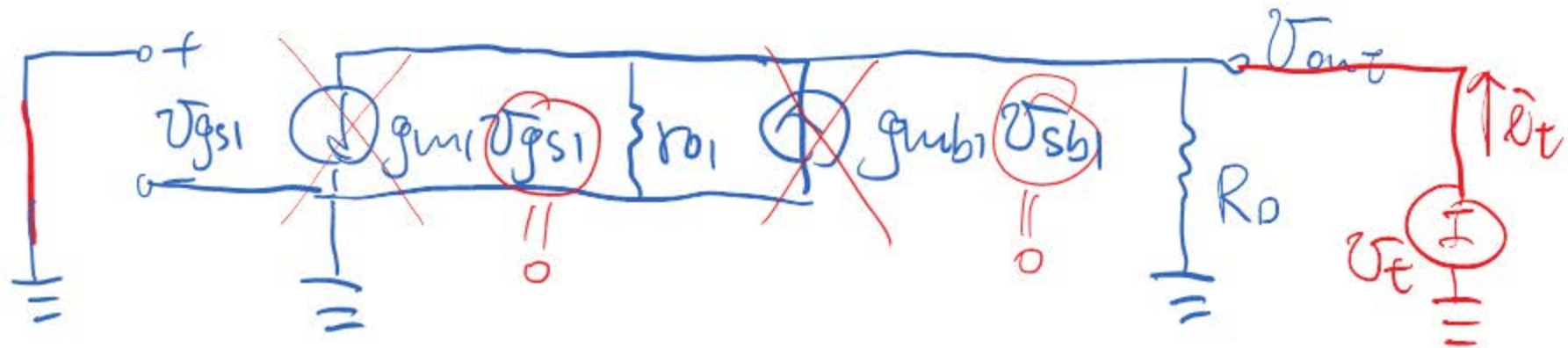



$r_{\pi} \neq 0$
 $r_{\pi} \neq 0$

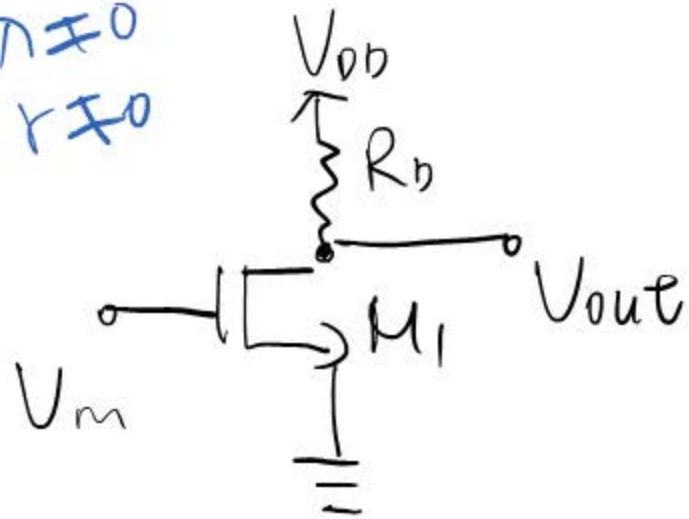

Find out the analytical expressions for A_v , R_m and R_{out} ?

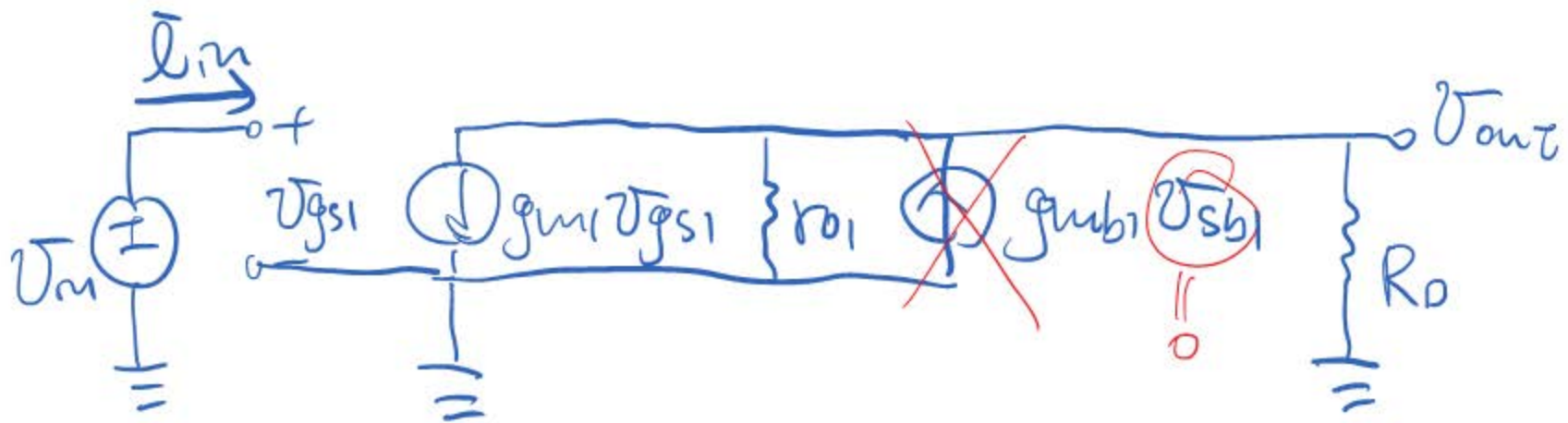
$$3^{\circ} R_m = \frac{V_m}{\bar{I}_m} = \infty$$






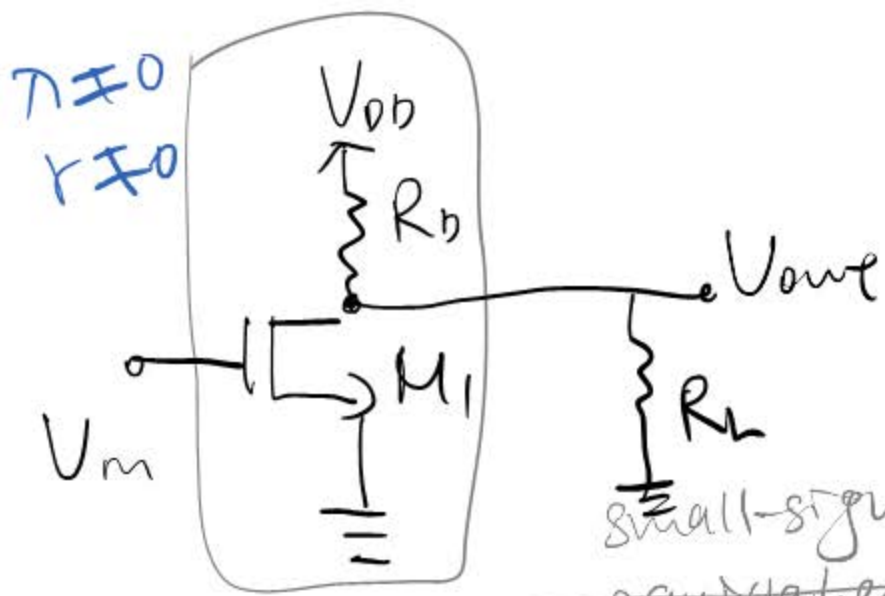


$$V_{out} = V_m A_v \frac{R_L}{R_{out} + R_L}$$

small-signal
equivalent circuit.

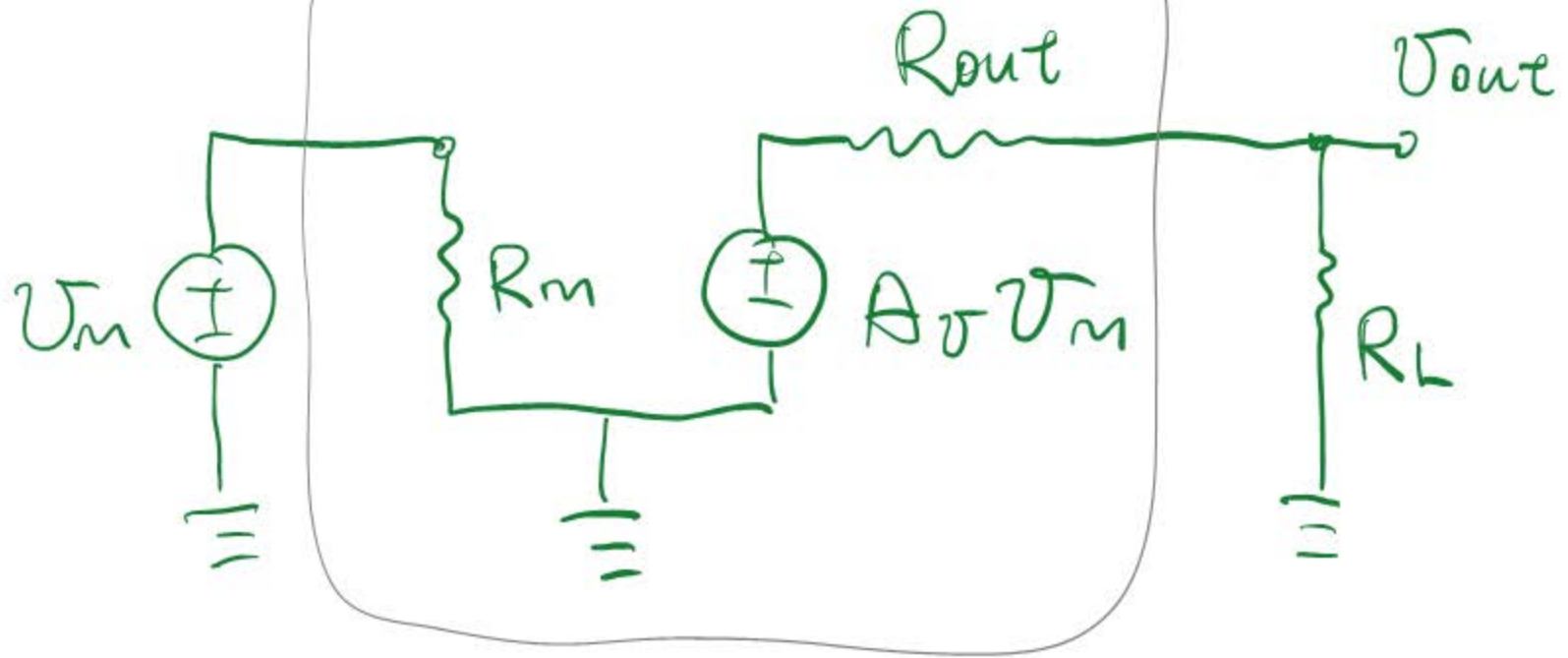


Common-Source with Diode-Connected Load

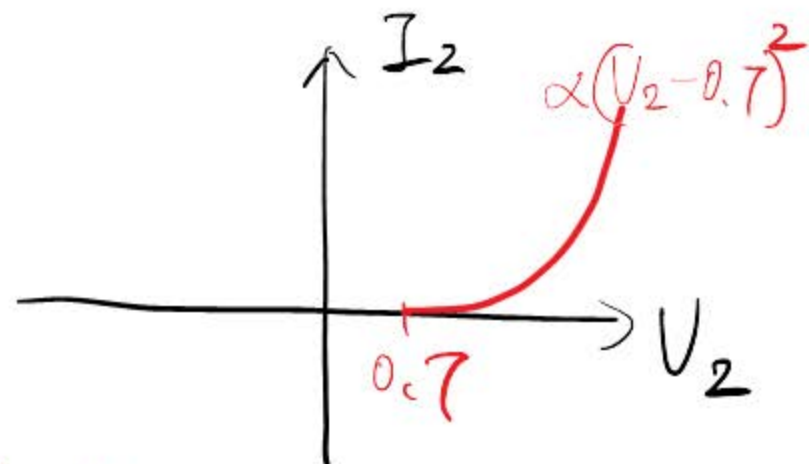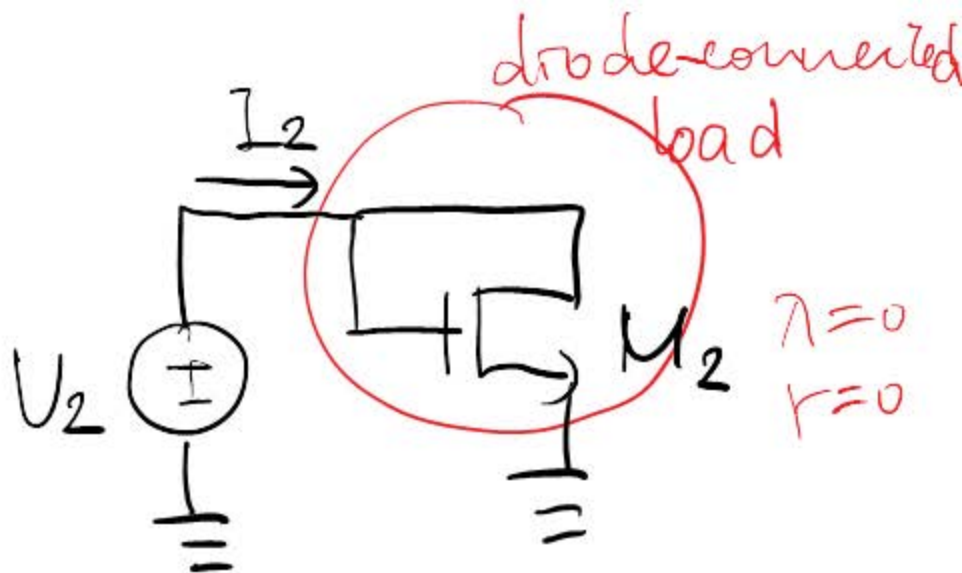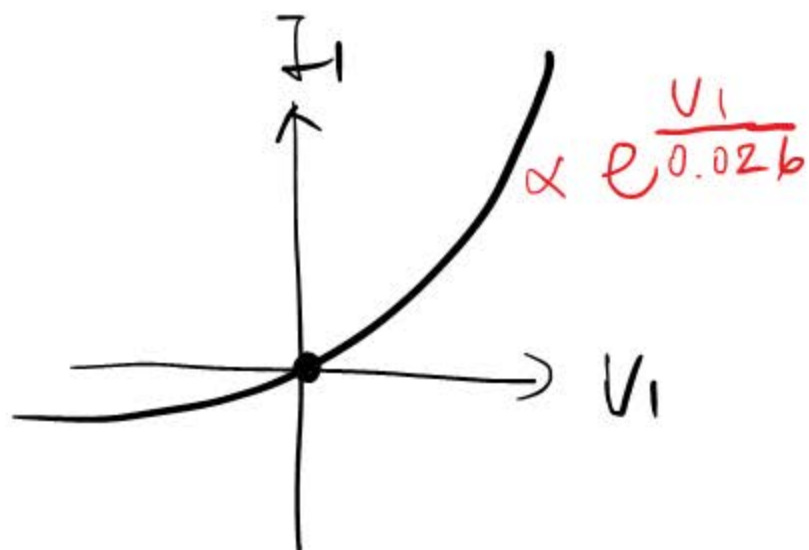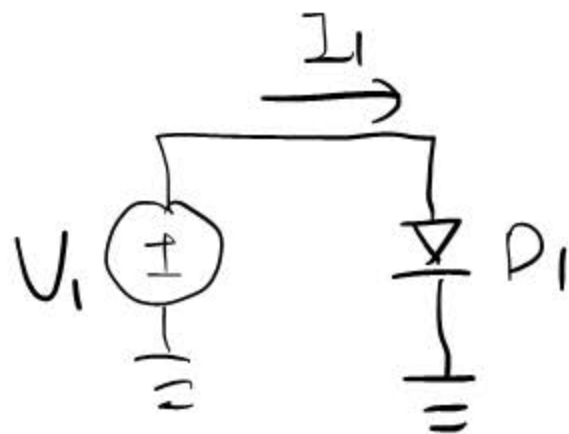

M_2 always in sat.
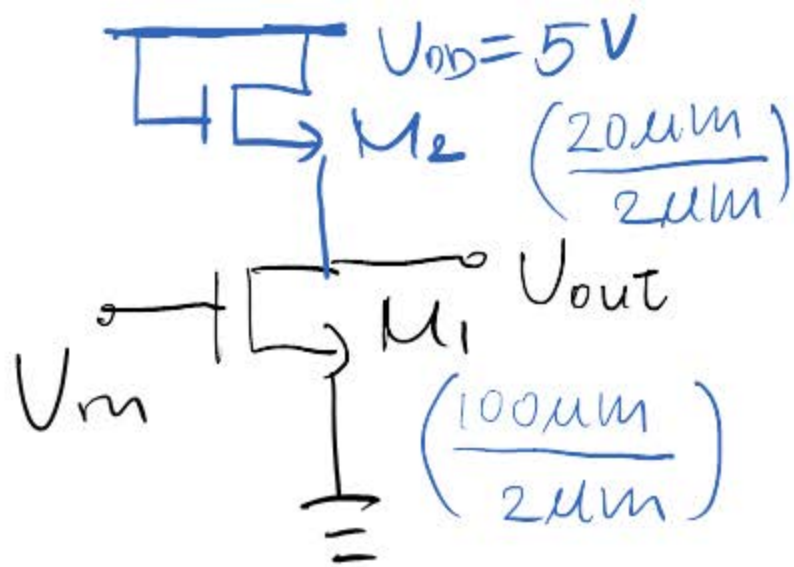
$$I_2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_2 - V_{TH})^2$$



1° Find out $V_{out} = ?$
 Then we make sure
 M_1 and M_2 in sat.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{100\mu m}{2\mu m - 2LD} \right) (0.8 - 0.7)^2 \cdot (1 + \lambda V_{out})$$

$$\lambda \neq 0, r \neq 0$$


$$V_m = 0.8 + 0.0018 \sin(2\pi 100t)$$

$$V_{out} = V_{outT} + V_{outc} = ?$$


$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{20\mu m}{2\mu m - 2LD} \right) \cdot$$

$$(5 - V_{out} - V_{th})^2 \cdot$$



$$[1 + \lambda(5 - V_{out})]$$

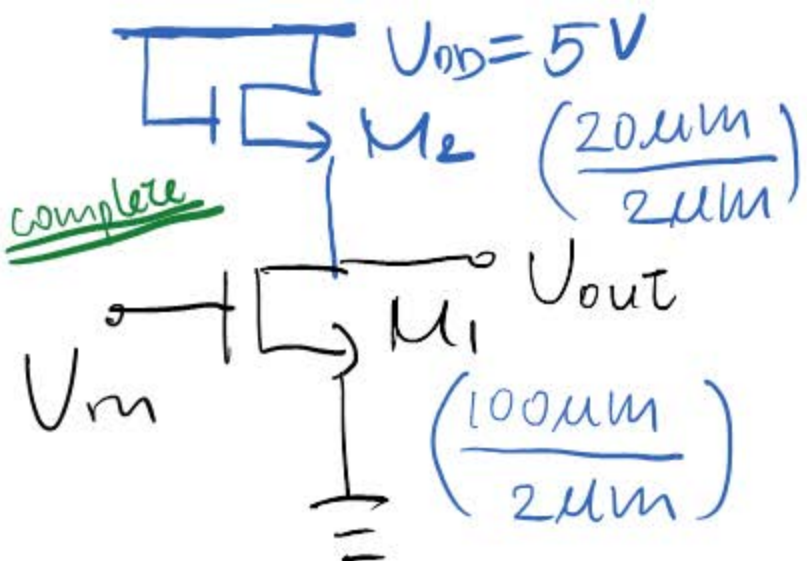


small-signal

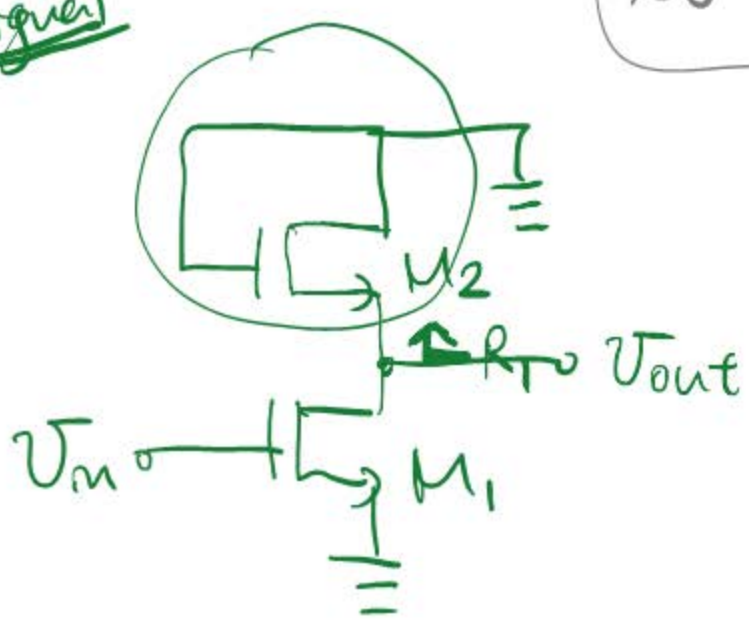

2° Find out $V_{out} = ?$

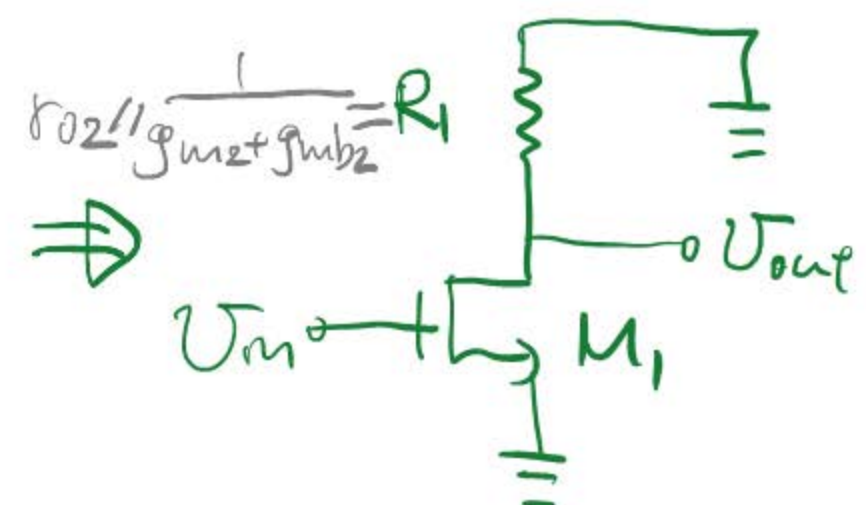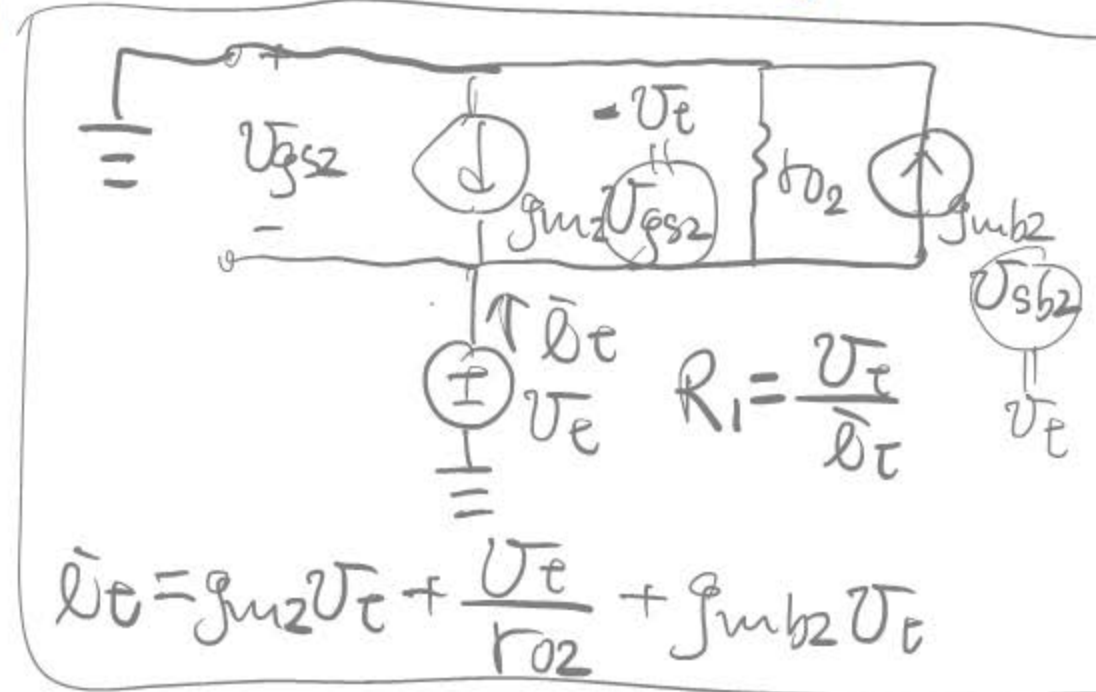

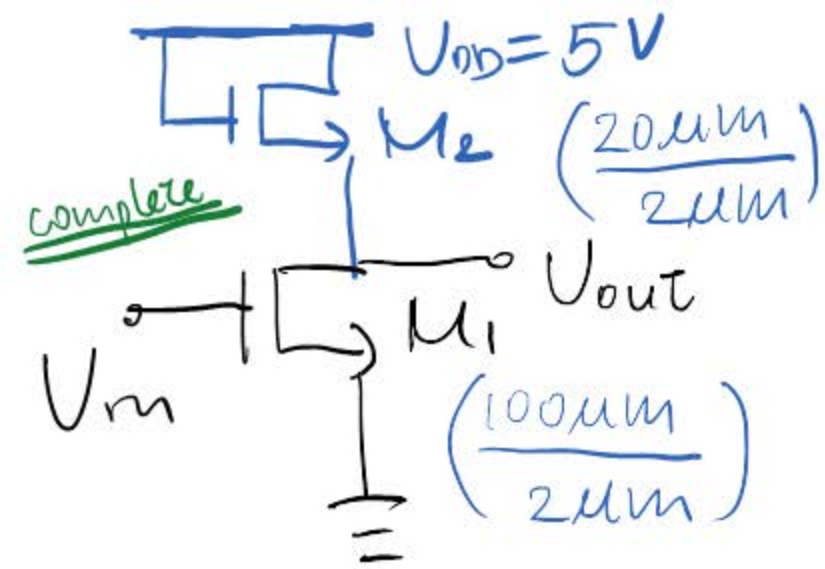

2 Find out $V_{out} = ?$

$$\begin{aligned}
 V_{out} &= -g_{m1} V_{in} (r_{o1} \parallel R_1) \\
 &= -g_{m1} V_{in} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right) \\
 &\approx -g_{m1} V_{in} \frac{1}{g_{m2} + g_{mb2}} \approx -V_{in} \frac{g_{m1}}{g_{m2}}
 \end{aligned}$$

small-signal

