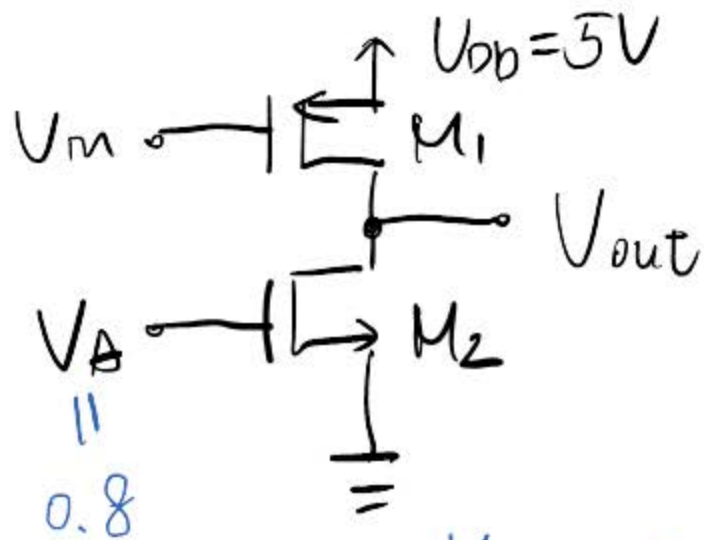


Common-Source with Current-Source Load



1° Find out $V_{out} = ?$
 Then we make sure
 M_1 and M_2 in sat.

$$V_{BS1} = 0 \Rightarrow V_{TH1} = 0.8$$

$$V_{BS2} = 0 \Rightarrow V_{TH2} = 0.7$$



$$\lambda \neq 0, r \neq 0$$

$$V_m = 4.1 + 0.0018 \sin(2\pi 100t)$$


$$V_{out} = V_{outT} + V_{outc} = ?$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (5 - 4.1 - 0.8)^2 [1 + \lambda (5 - V_{outT})]$$

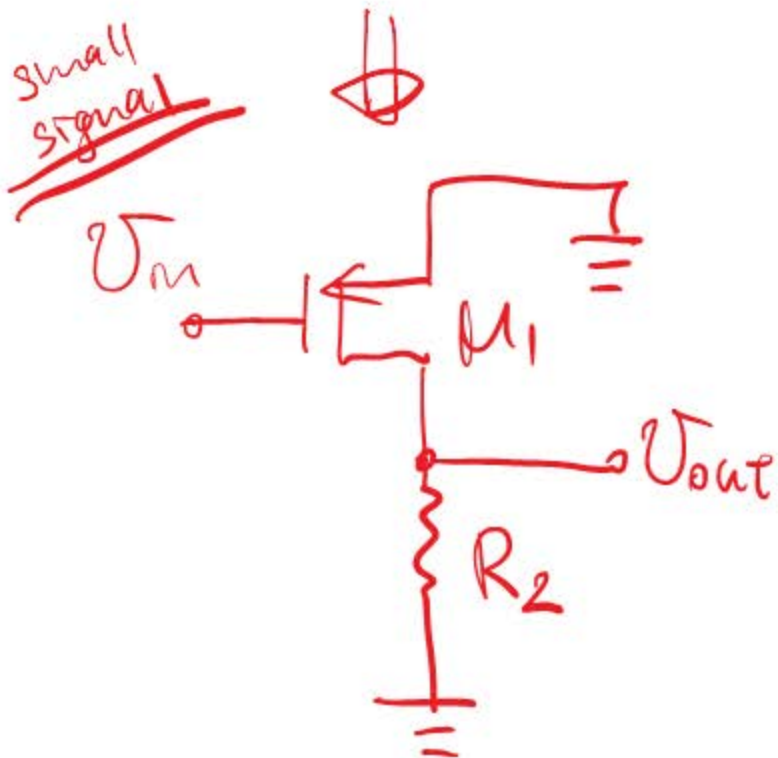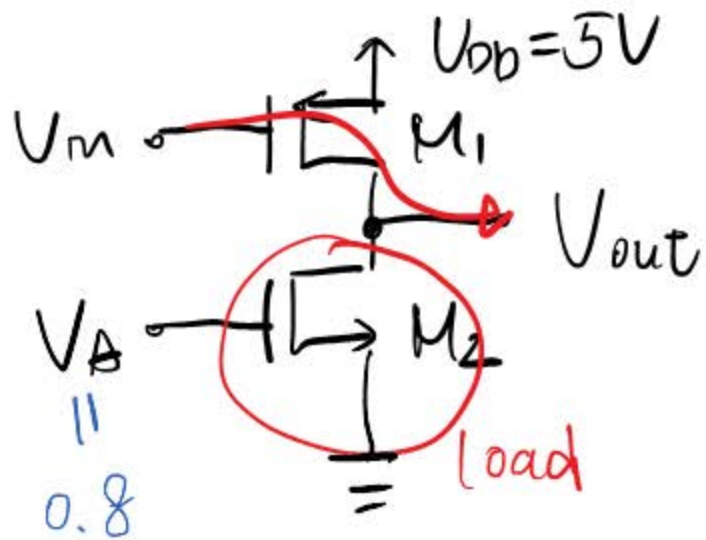
$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (0.8 - 0.7)^2 [1 + \lambda V_{outT}]$$



Find out $V_{out} = ?$

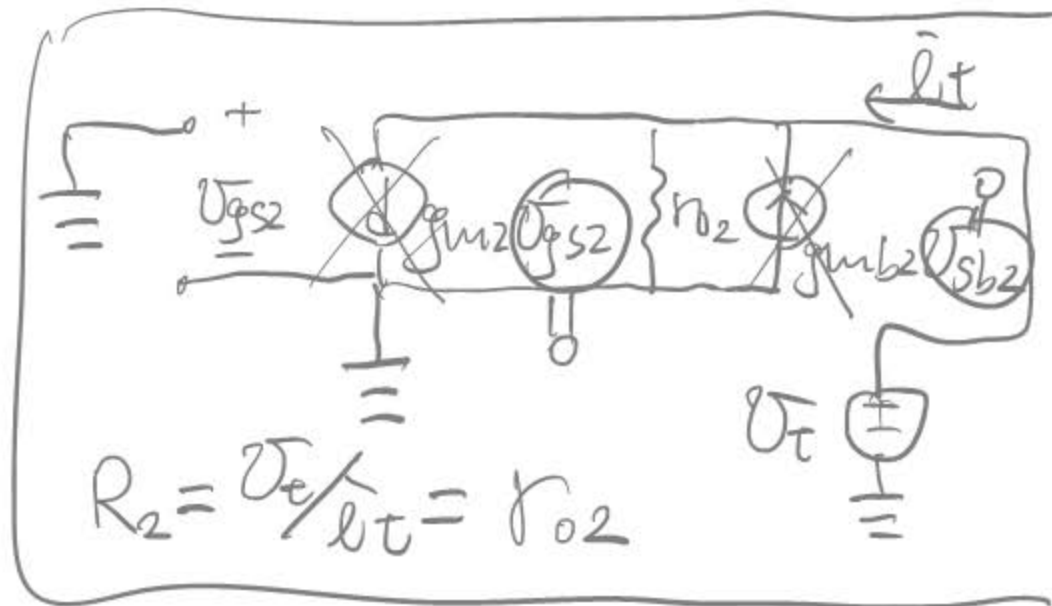
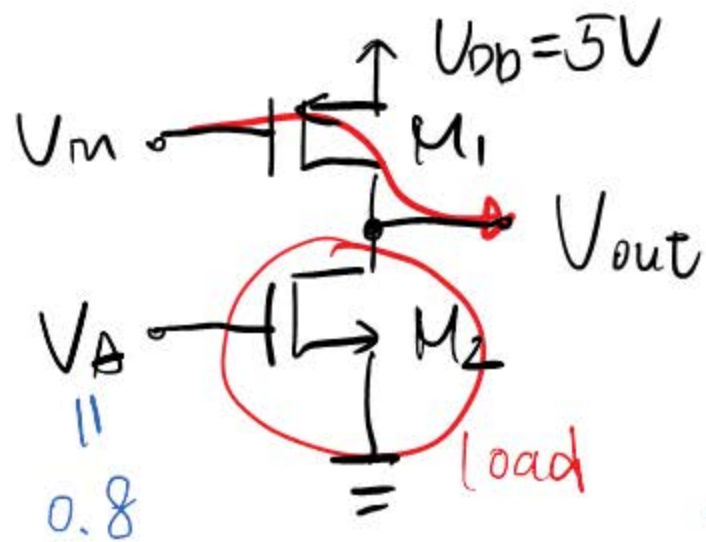
$$\begin{aligned}
 A_v &= \frac{V_{out}}{V_m} = -g_{m1}(r_{o1} \parallel R_2) \\
 &= g_{m1}(r_{o1} \parallel r_{o2})
 \end{aligned}$$




3° Find out $R_m = ?$

$$R_m = \infty$$


4° Find out $R_{out} = ?$


$$R_{out} = r_{o1} \parallel r_{o2}$$

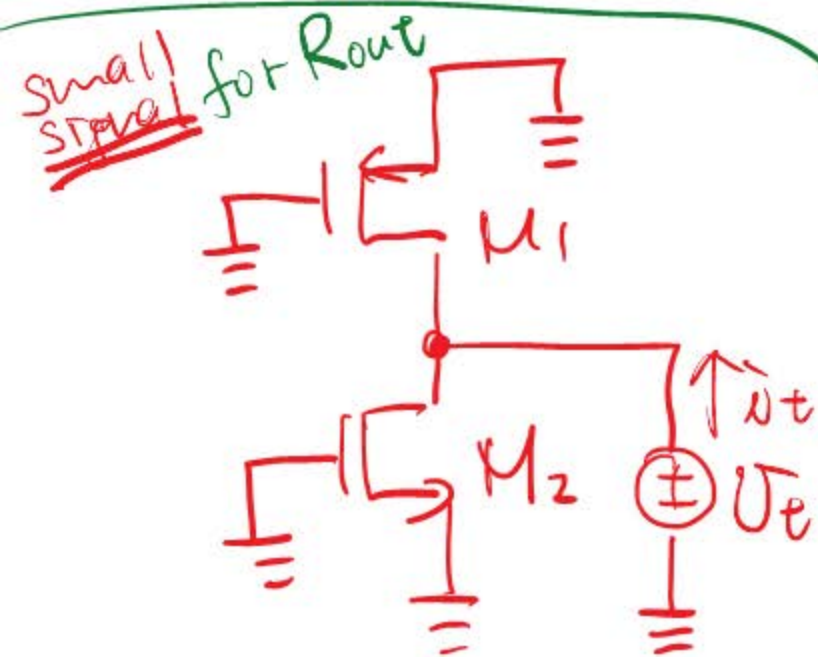

$$R_{out} = V_t / i_t$$


Equivalent Small Signal Circuit

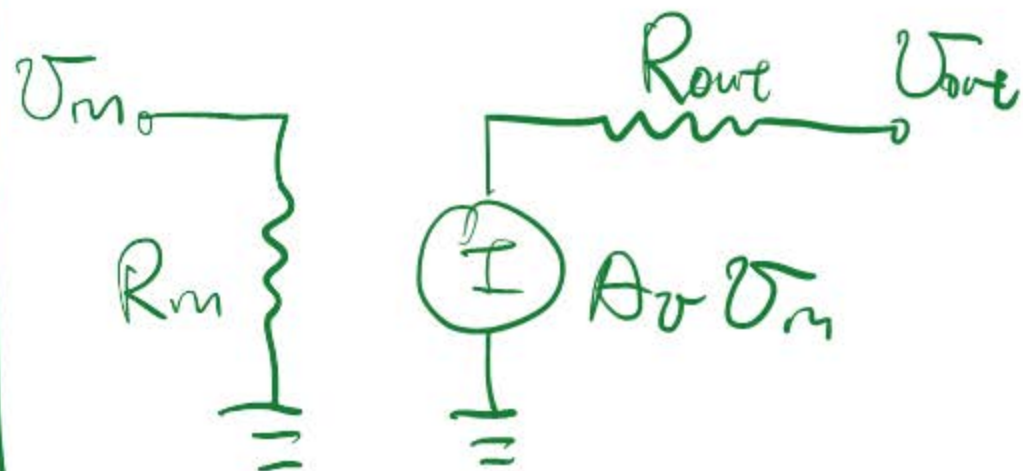


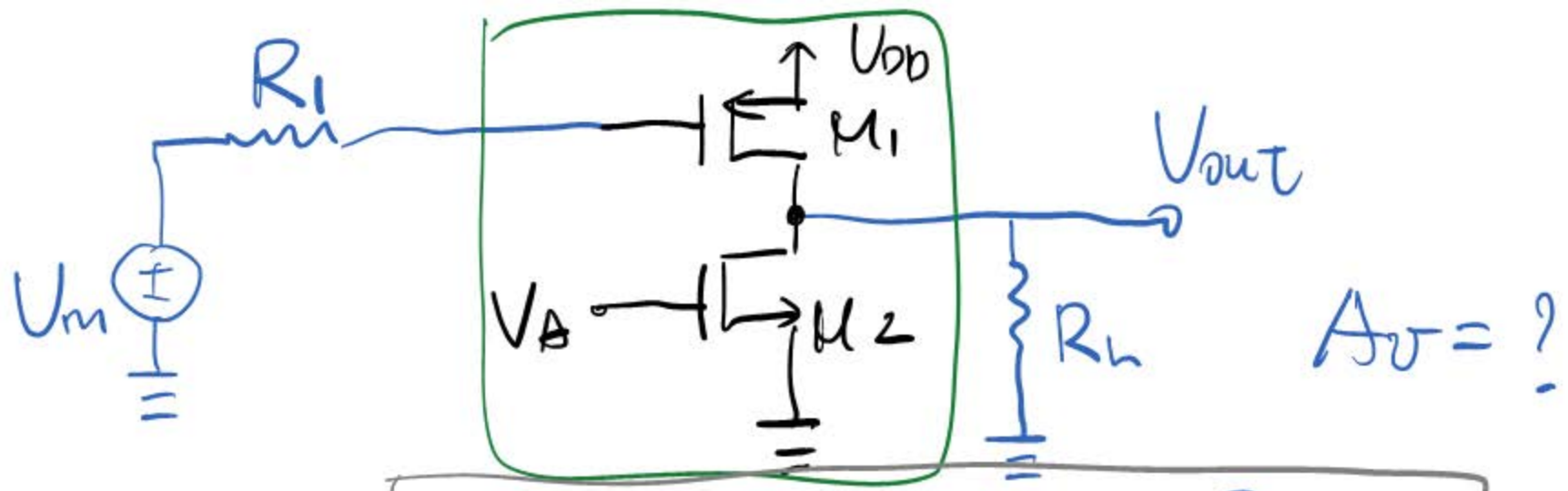

$$A_v = -g_{m1}(r_{o1} \parallel r_{o2}) \frac{R_L}{R_{out} + R_L}$$

Small
signal

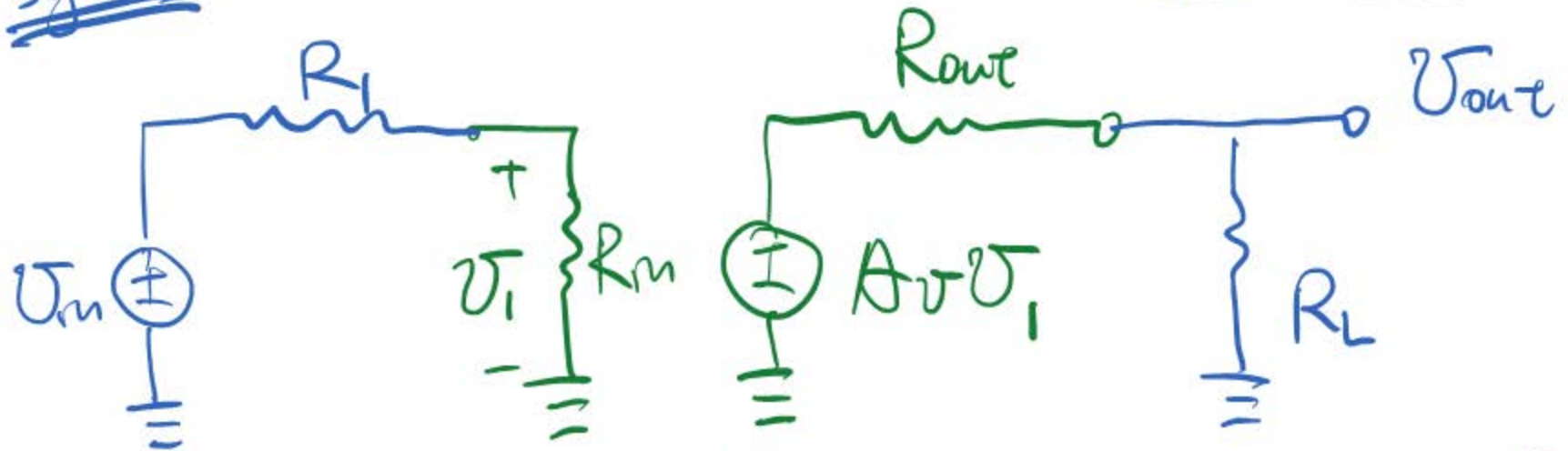

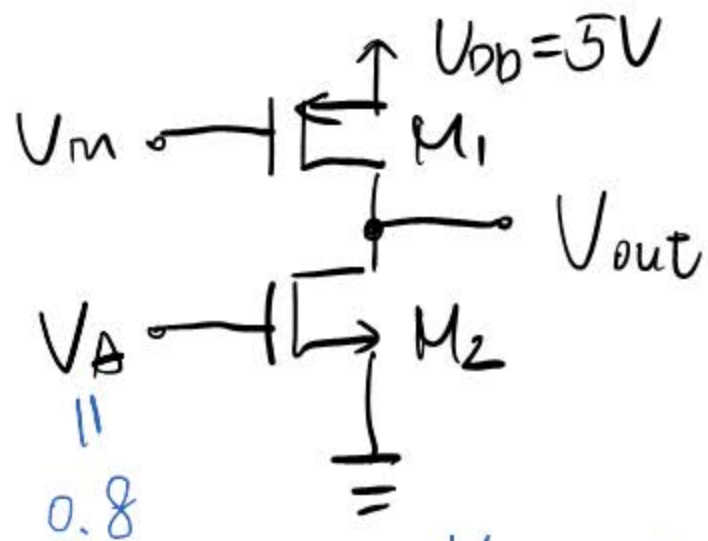

$$V_{BS1} = 0 \Rightarrow |V_{TH1}| = 0.8$$

$$V_{BS2} = 0 \Rightarrow V_{TH2} = 0.7$$

$$\lambda \neq 0, r \neq 0$$

$$V_m = 4.1 + 0.001 \sin(2\pi 1000 t)$$

$$V_{out} = V_{outT} + V_{outc} = ?$$

3° Find out available output swing range.
0.1 ~ 4.9

$$V_{out, max} = 5 - (5 - 4.1 - 0.8)$$

$$= 4.9$$

$$= V_{DD} - (V_{GS1} - |V_{TH1}|)$$

overdrive of M_1

$$V_{out, min} = 0.8 - 0.7$$

$$= V_{GS2} - V_{TH2}$$



$$= 0.1 \quad \text{overdrive of } M_2.$$

Common-Source with Current-Source Load

7


Small-signal
Analysis

$\lambda \neq 0$ $\gamma \neq 0$

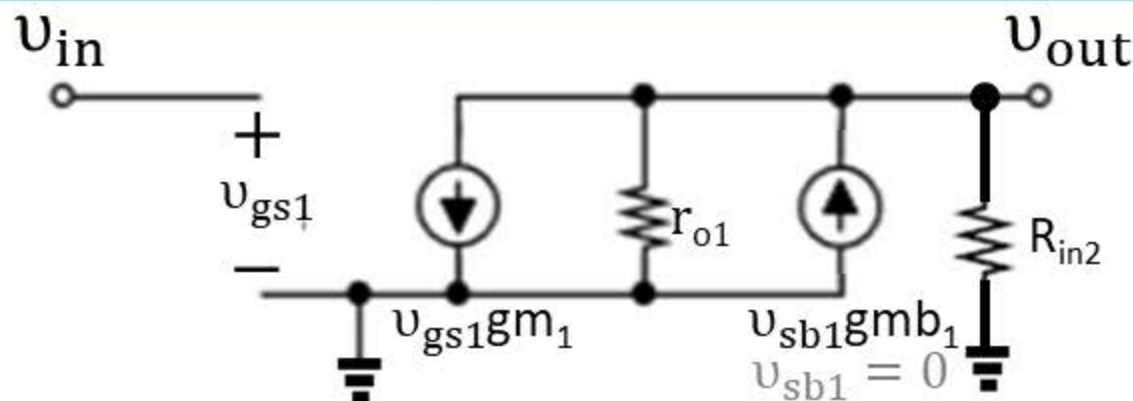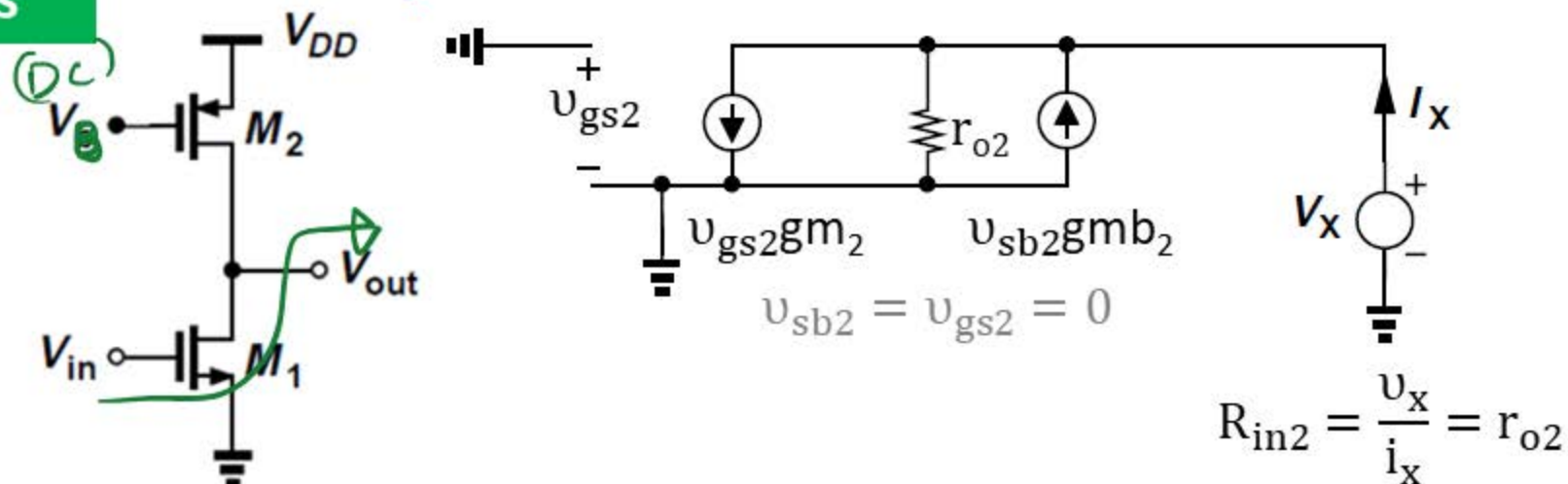


$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{o2} \parallel r_{o1})$$

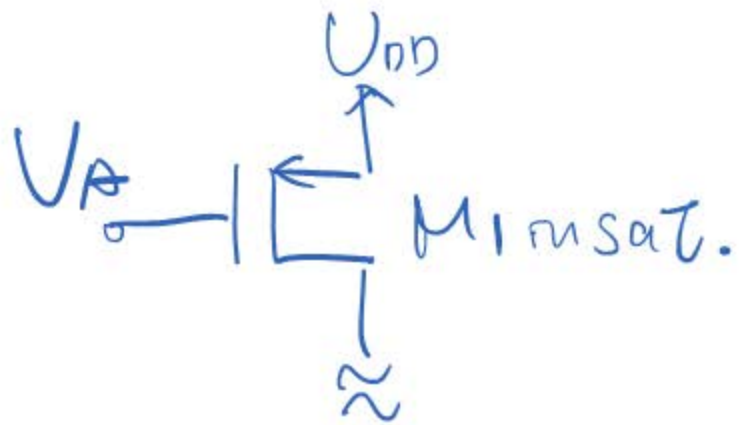
- To achieve high A_v , the output swing is severely limited in the CS stages with resistive load and diode-connected load.
- Here $V_{out, max} = V_{DD} - (V_{SG2} - V_{TH2})$, which can be quite close to V_{DD} .



$\lambda = 0$

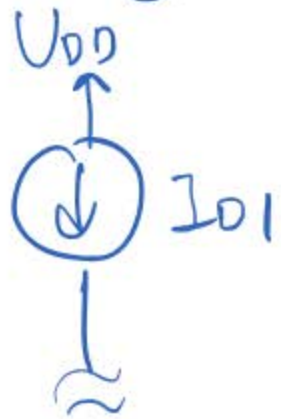


$\lambda \neq 0$

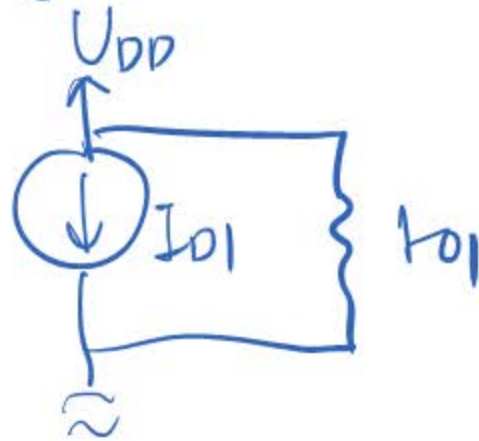

Common-Source with Current-Source Load

Small-signal Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

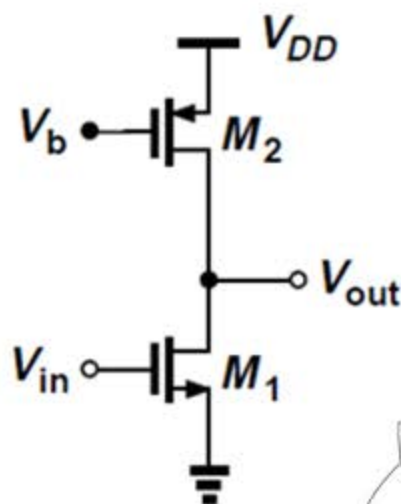

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{o2} \parallel r_{o1})$$

$$r_o \approx \frac{1}{\lambda I_D} \quad \lambda \propto \frac{1}{L}$$


$$g_{m1} = \underbrace{\mu_n C_{ox}}_{\text{large}} \underbrace{\left(\frac{W}{L_{eff}}\right)}_{\text{large}} \underbrace{(V_{GS1} - V_{TH1})}_{\text{small } (1 + \lambda V_{DS})}$$

- $V_{out, max} = V_{DD} - (V_{SG2} - V_{TH2})$
- $V_{out, min} = (V_{GS1} - V_{TH1})$
- For high g_{m1} and small $(V_{GS1} - V_{TH1})$, W of M_1 needs to be large.
- For high r_{o1} and r_{o2} , L of M_1 and M_2 need to be large and L of M_1 and M_2 needs to be increased proportionally. The cost is the **large parasitic drain junction capacitance** at the output.

Degeneration

Common-Source with Source Degradation



Amplifier Equivalent Circuit

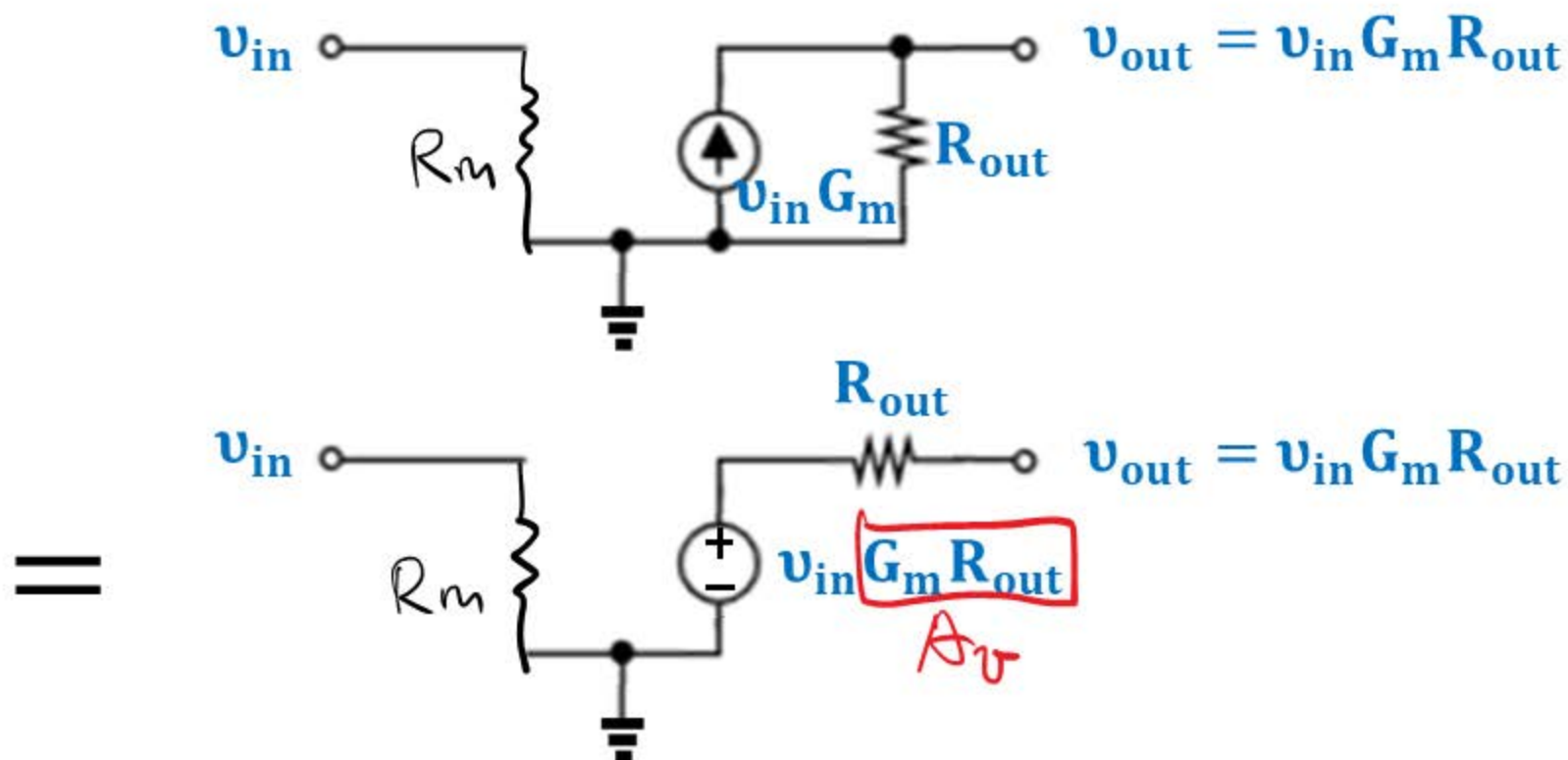



- How to calculate G_m ? v_{out} shorted to ground. $G_m = i_{out}/v_{in}$
- How to calculate R_{out} ? v_{in} shorted to ground and v_{out} connected to v_{test} .

$$R_{out} = v_{test}/i_{test}$$


Amplifier Equivalent Circuit

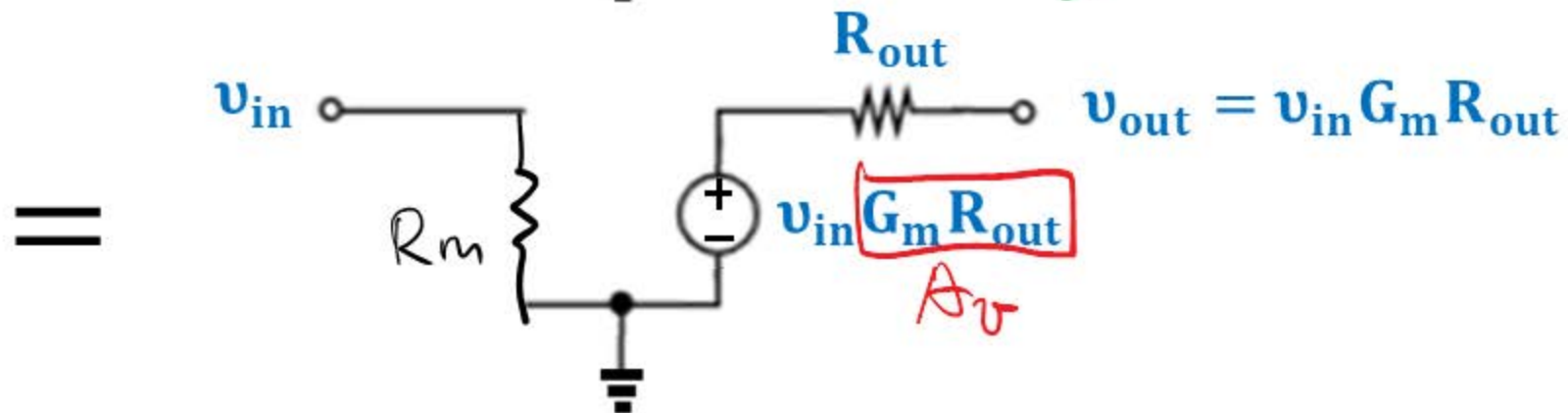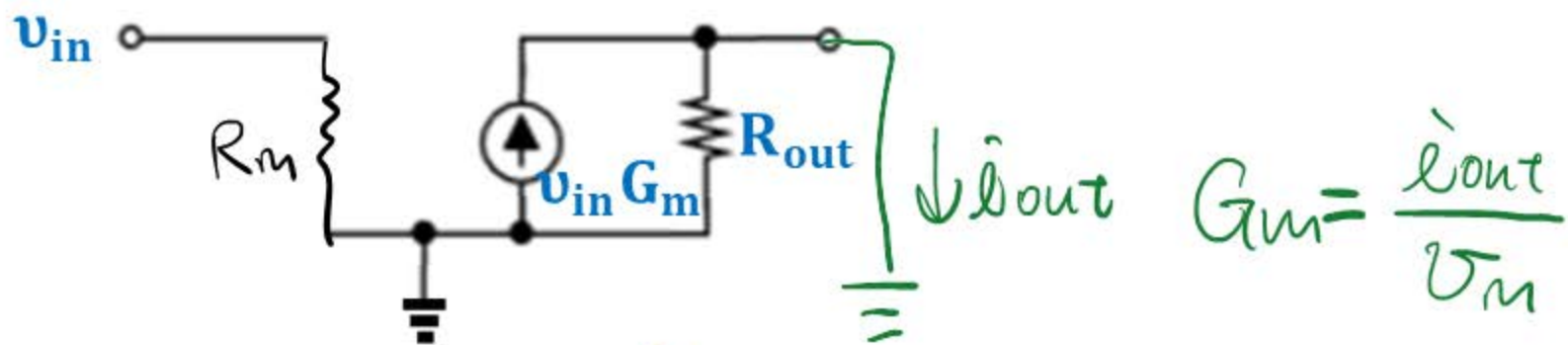

Amplifier Equivalent Circuit

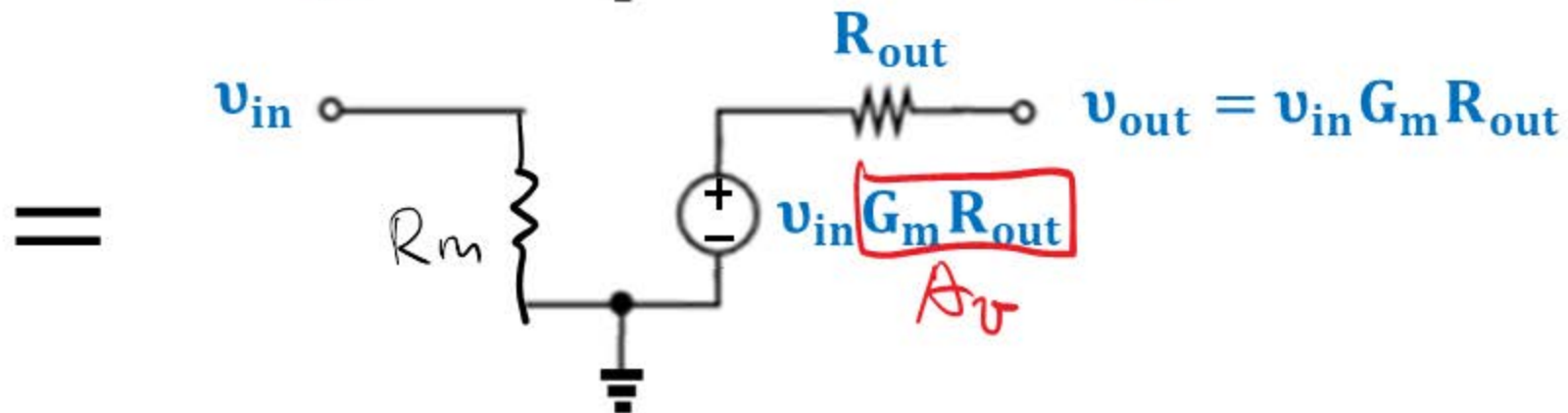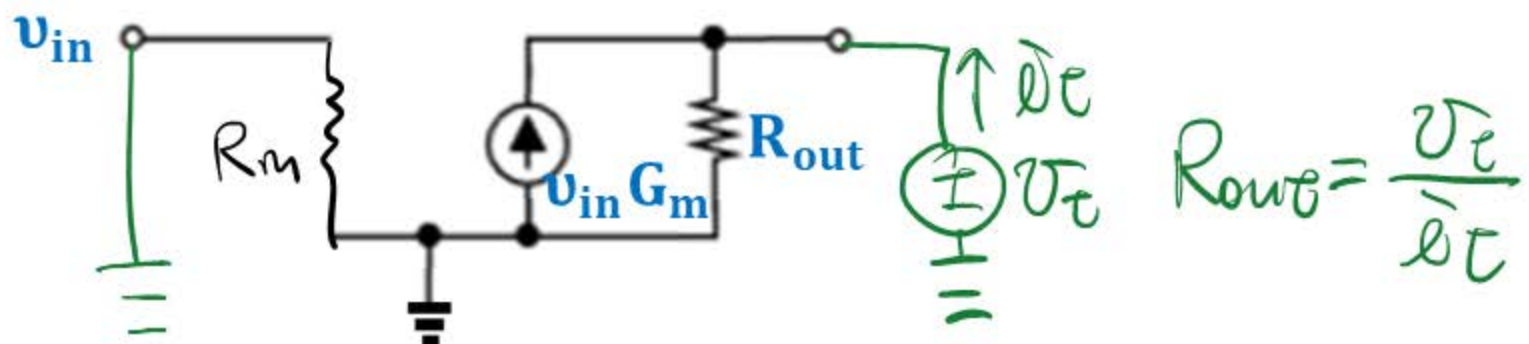

complete

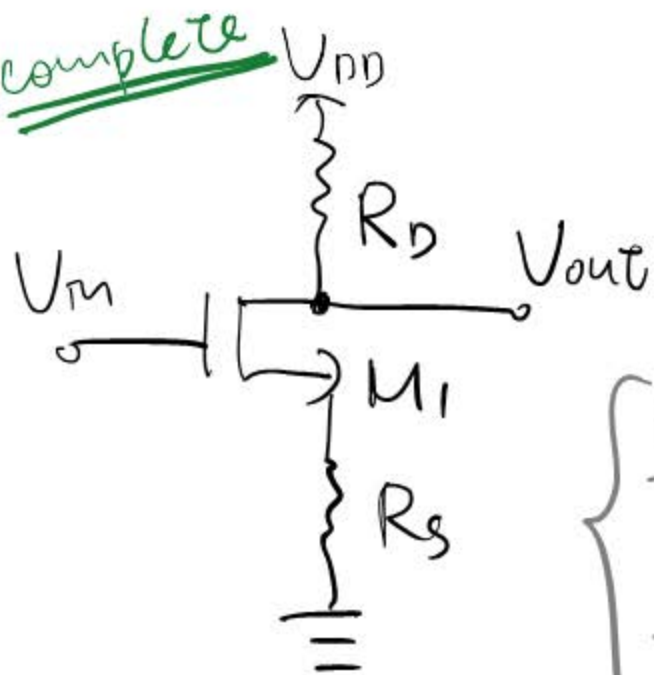

$$\eta \neq 0, r \neq 0$$


$$A_v = ?$$

$$G_m = \bar{Q}_{out} / V_m$$

$$\begin{cases} \frac{V_a}{R_s} + (V_a - V_m)g_{m1} + \frac{V_a}{r_{o1}} + g_{m1}V_a = 0 \\ -\frac{V_a}{R_s} = \bar{Q}_{out} \end{cases}$$

Equivalent small signal

Small signal

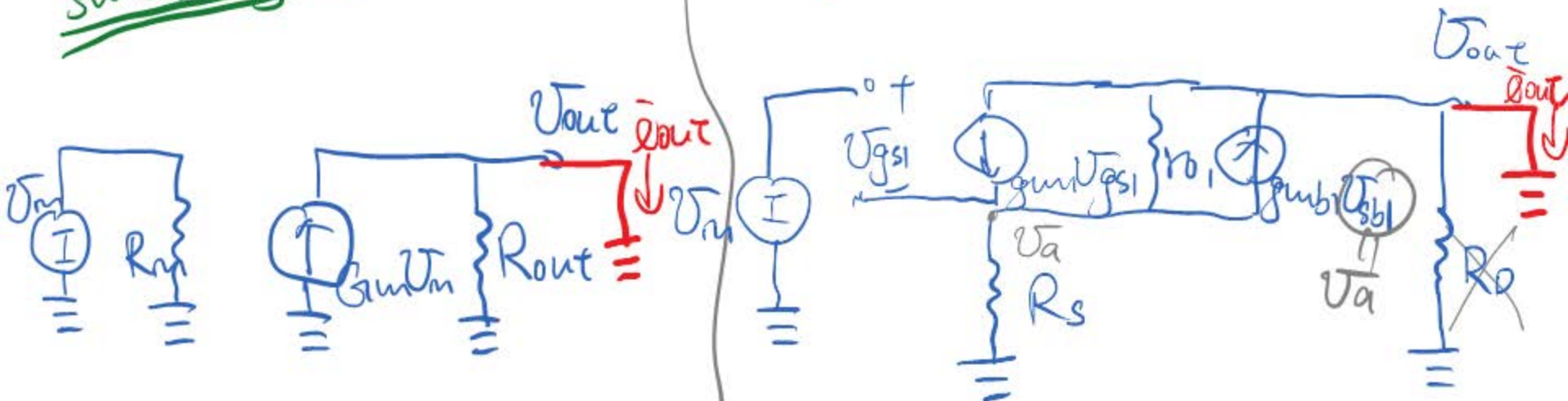


Common-Source with Source Degradation

Small-signal
Analysis

$\lambda \neq 0$ $\gamma \neq 0$

small signal circuit
for calculating G_m

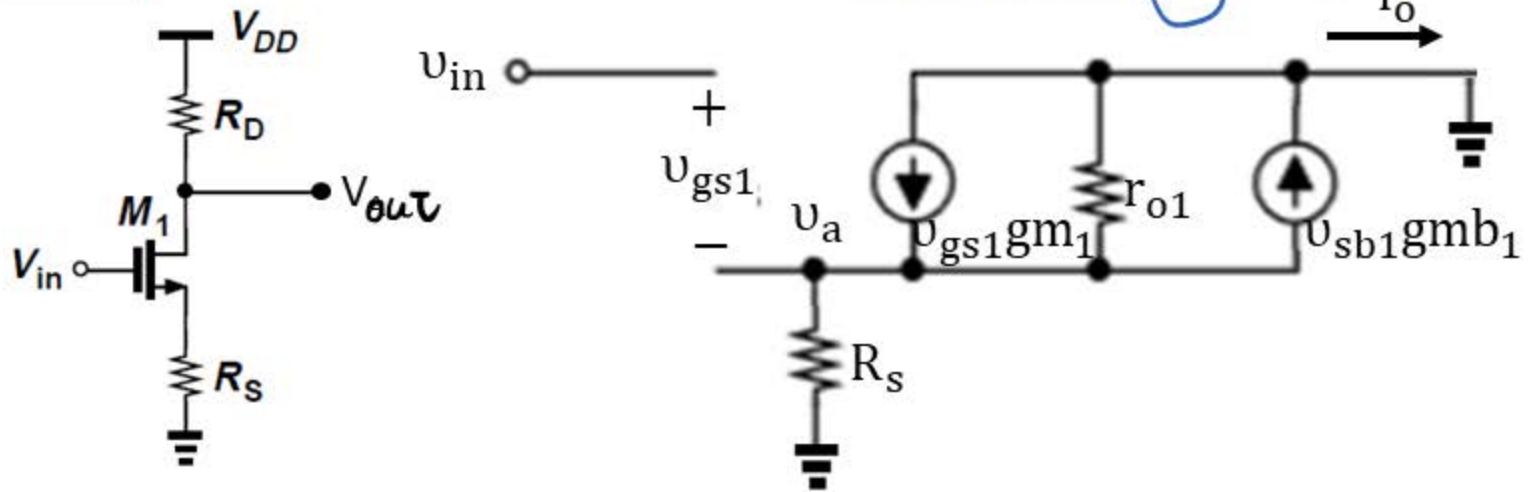

$$\begin{cases} i_o = \frac{-v_a}{R_S} \\ (v_{in} - v_a)g_{m1} + i_o = \frac{v_a}{r_{o1}} + v_a g_{mb1} \end{cases}$$

$$G_m = \frac{i_o}{v_{in}} = \frac{-g_{m1} r_{o1}}{R_S + r_{o1} + (g_{m1} + g_{mb1}) r_{o1} R_S} \approx -\frac{1}{R_S}$$

intrinsic g_m of M_1

if $g_{mb1} \ll g_{m1}$
if $(g_{m1} + g_{mb1}) r_{o1} R_S \gg r_{o1}$ and R_S