



JOINT INSTITUTE


交大密西根学院

FET

Ve311 Electronic Circuits (Fall 2020)


Dr. Chang-Ching Tu

PCB

 



silicon chip

transistors.

 

silicon chip

NMOS FET

  

$$L_{eff} = L_{drawn} - 2L_D$$

For forming an ohmic contact between p-sub. and copper metal wire

- MOS = Metal-Oxide-Semiconductor
- FET = Field effect Transistor
- **CMOS** Technology keeps on reducing t_{ox} and L_{eff} (Moore's Law).
- Substrate (Body) of NMOS is generally connected to ground.
- See Chapter 17 for the introduction of CMOS fabrication technology.

Latest: TSMC 5 nm FinFET Technology

CMOS

Schematic Design

NMOS

Drain

Gate

G

S


B

Body


$\frac{W}{L} = \frac{10\mu m}{2\mu m}$

Source

PMOS

 

V_{DD}

 



NMOS and PMOS can share one p-Sub.

- CMOS = Complementary MOS (a fabrication technology)
- Substrate (Body) of NMOS is generally connected to ground.
- N-well (Body) of PMOS is generally connected to V_{DD} .

Layout


NMOS

PMOS

  


$$L_{eff} = L_{drawn} - 2LD = (2 \times 10^{-6}) - 2(0.08 \times 10^{-6})$$

Threshold Voltage (V_{TH}) for NMOS

 


 - depletion region.*
- $V_G = 0\text{ V}$
 - No current flow




Threshold Voltage (V_{TH}) for NMOS


7

 

 
- As V_G increases from zero, holes in p -substrate are repelled, leaving negative ions (ionized boron dopants) behind to form a **depletion region**.
- Positive charges are mirrored at the gate.
- No charge carriers (electrons or holes) in the channel, so no current flow.




Threshold Voltage (V_{TH}) for NMOS

 

 
- Higher V_G further increases the width of the depletion region.




Threshold Voltage (V_{TH}) for NMOS

 

- When V_G reaches a sufficiently positive value, a channel of electrons (**inversion layer**) is formed beneath the gate oxide.
- Electrons flow from "source" to "drain". Equivalently, current flows from "drain" to "source".
- The value of V_G at which the inversion layer forms is the **threshold voltage (V_{TH})**.
- If V_G rises further, the charges in the depletion region remain relatively constant, whereas the charges in the inversion layer increase rapidly.

 

 

$$Q_1 = C V_1$$


$$= \frac{A(\epsilon_0 \epsilon_r)}{t_{ox}} V_1$$

C_{ox}

$$\epsilon_0: 8.85 \times 10^{-12} \text{ F/m}$$

$$\epsilon_r: 3.9$$

I-V Characteristics for NMOS (Triode)

 

For $V_{GS} \geq V_{TH} = 0.7\text{ V}$

$$Q = -WL_{\text{eff}}C_{\text{ox}}(V_{GS} - V_{TH}) \quad (\text{unit: coulomb})$$

$$Q_d = -WC_{\text{ox}}(V_{GS} - V_{TH}) \quad (\text{unit: coulomb} \cdot \text{m}^{-1})$$


C_{ox} (gate oxide capacitance per unit area)

$$= \epsilon_{\text{silicon oxide}} / t_{\text{ox}}$$

$$= [8.85 \times 10^{-12} \text{ (F/m)} \times 3.9] / t_{\text{ox}}$$

(F/m^2)

I-V Characteristics for NMOS (Triode)

 


$$I_D = Q_d \times v = Q_d \times (\mu_n \mathcal{E}) = -WC_{ox}[V_{GS} - V_{TH} - V(x)] \times (\mu_n \mathcal{E}) \quad \mathcal{E} = -dV(x)/dx$$

$$= WC_{ox}[V_{GS} - V_{TH} - V(x)] \times \mu_n \times \frac{dV(x)}{dx}$$

$$\int_{x=0}^{x=L_{eff}} I_D \cdot dx = \int_{V(0)=0}^{V(L)=V_{DS}} \mu_n C_{ox} W [V_{GS} - V_{TH} - V(x)] \cdot dV(x)$$

I_D : constant along channel
 
$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2]$$



$$\mu_1 = \frac{20\mu m}{5\mu m} = \frac{W_{drawn}}{L_{drawn}}$$

$$I_{D1} = \underbrace{350}_{\mu m} \left(\frac{cm^2}{V \cdot sec} \right) C_{ox} \left[\frac{20 \times 10^{-6}}{(5 \times 10^{-6}) - 2(0.08 \times 10^{-6})} \right]$$

$$\left[(1.2 - 0.7) 0.1 - \frac{1}{2} 0.1^2 \right]$$


$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


$$L_{drawn} - 2LD$$

$$I_D = \boxed{\text{constant}} V_{DS} \quad \text{can be neglected if } V_{DS} \text{ small}$$


$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TH})V_{DS} - \frac{1}{2} V_{DS}^2]$$

 DC sweep I_D v.s. V_{DS} @ given $V_{GS} = 1.2V > V_{TH}$



 


At given $V_{gs} > V_{TH}$

 

I-V Characteristics for NMOS (Triode)

$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

 
$$I_{D,max} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \quad V_{DS} = V_{GS} - V_{TH}$$



- For digital circuit, MOSFET, as a switch, usually operates in deep triode region.
- This is why reducing t_{ox} and L_{eff} can improve speed.

I-V Characteristics for NMOS (Saturation)



17

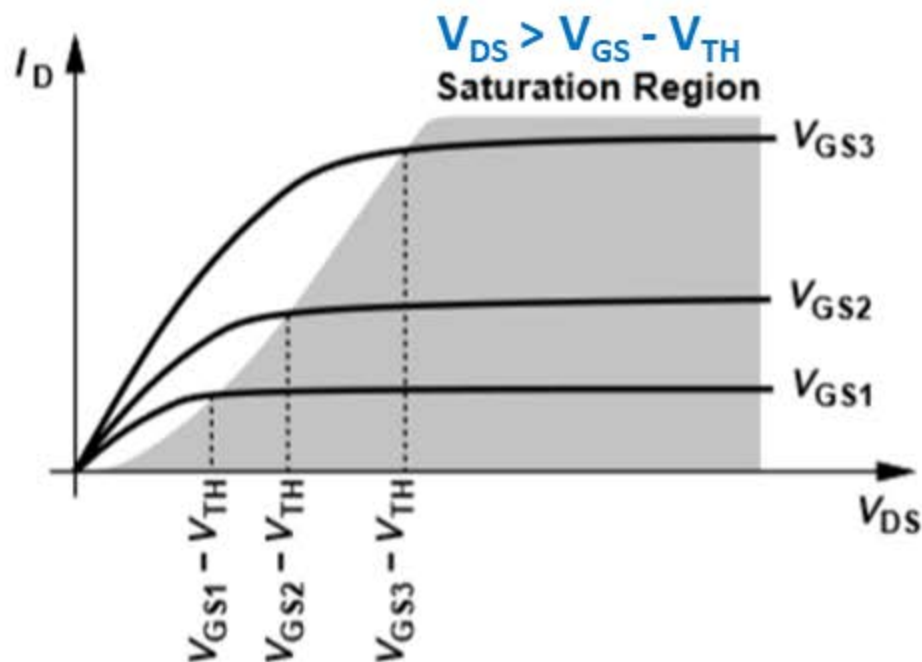

- In reality, for $V_{DS} > V_{GS} - V_{TH}$, I_D becomes relatively constant.
- $V_{DS} = V_{GS} - V_{TH}$ is the minimum value for the NMOS to operate in saturation region.

I-V Characteristics for NMOS (Saturation)

18

  

$$\int_{x=0}^{x=L'} I_D \cdot dx = \int_{V(0)=0}^{V(L')=V_{GS}-V_{TH}} \mu_n C_{ox} W [V_{GS} - V_{TH} - V(x)] \cdot dV(x)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$

I_D : constant along channel

L' : the point at which Q_d drops to zero

$V_{GS} - V_{TH}$: the overdrive voltage

- Electron velocity ($v = I_D / Q_d$) becomes tremendously high at the pinch off point ($Q_d \rightarrow 0$), such that electrons shoot through the depletion region and arrive at the drain terminal.

Channel-Length Modulation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$



$$L' = L_{eff} - \Delta L$$

$$\frac{1}{L'} = \frac{1}{L_{eff} - \Delta L} = \frac{1}{L_{eff}} \cdot \frac{1}{1 - \frac{\Delta L}{L_{eff}}} \approx \frac{1}{L_{eff}} \cdot \left(1 + \frac{\Delta L}{L_{eff}}\right)$$

small

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \left(1 + \frac{\Delta L}{L_{eff}}\right) \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \end{aligned}$$


$\lambda = 0$ means don't consider "channel-length modulation"

Channel-Length Modulation





$$\begin{aligned} r_o &= \frac{\partial V_{DS}}{\partial I_D} = 1 / \frac{\partial I_D}{\partial V_{DS}} \\ &= \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \cdot \lambda} \\ &\approx \frac{1}{I_D \cdot \lambda} \end{aligned}$$

⊕: ionized phosphorus dopants

$$V_{SG} = 0.8 \text{ V}$$

 


NMOS vs PMOS

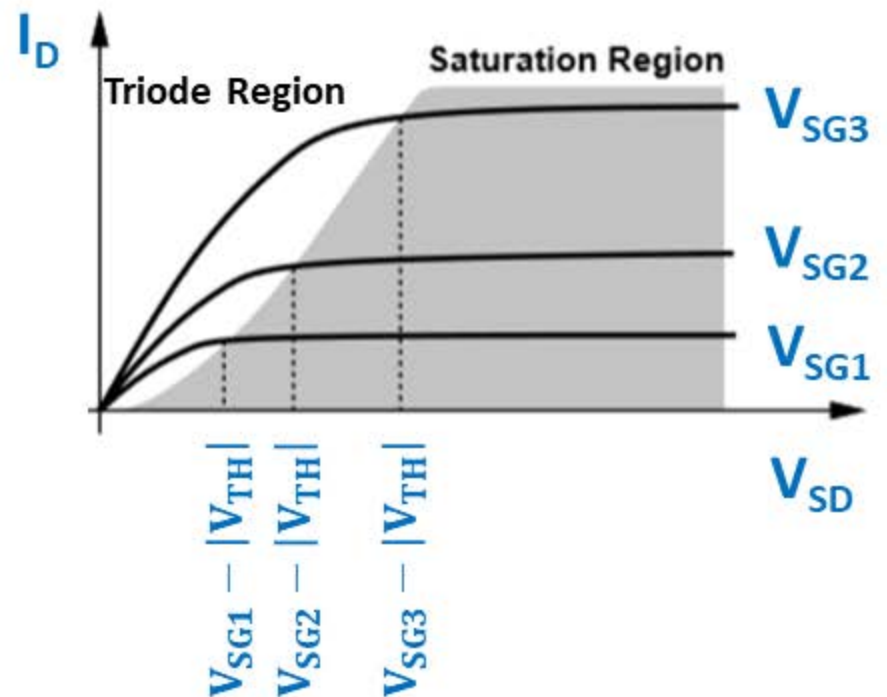   

NMOS vs PMOS

NMOS

 


triode: $I_D = \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) \left((V_{GS} - V_{THN}) V_{DS} - \frac{1}{2} V_{DS}^2 \right)$

sat: $I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{THN})^2 (1 + \eta V_{DS})$

$V_{GS} \rightarrow V_{SG}$ $\mu_n \rightarrow \mu_p$
 $V_{THN} \rightarrow |V_{THP}|$
 $V_{DS} \rightarrow V_{SD}$


PMOS

 

triode: $I_D = \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) \left((V_{SG} - |V_{THP}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right)$

sat: $I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SG} - |V_{THP}|)^2 (1 + \eta V_{SD})$

When $V_x = 0$

 


$$V_{DS} = 1V$$


$$V_{GS} = 1.9V$$

$$V_{DS} < V_{GS} - 0.7$$

(triode)

 


when $V_x = 0.1$

 

$$V_{DS} = 0.9V$$



$$V_{GS} = 1.8V$$

npn BJT

 


For $V_{CE} \geq V_{BE}$
in forward-active
  
$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$





NMOS

 

$V_{GS} > V_{TH}$
For $V_{DS} \geq V_{GS} - V_{TH}$
in sat.



$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$
  
$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$




PMOS

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SG} - |V_{TH}|)^2 (1 + \lambda V_{SD})$$

  



NMOS

 


$V_{GS} > V_{TH}$
For $V_{DS} \geq V_{GS} - V_{TH}$
in sat.

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$
  
$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$




$$I_D = ? \quad \bar{V}_D = ?$$

 


$$\begin{aligned}
 V_{DS} &= 1V \\
 &> V_{GS} - V_{TH} = 0.3V \\
 &\Rightarrow M_1 \text{ in Sat.}
 \end{aligned}$$
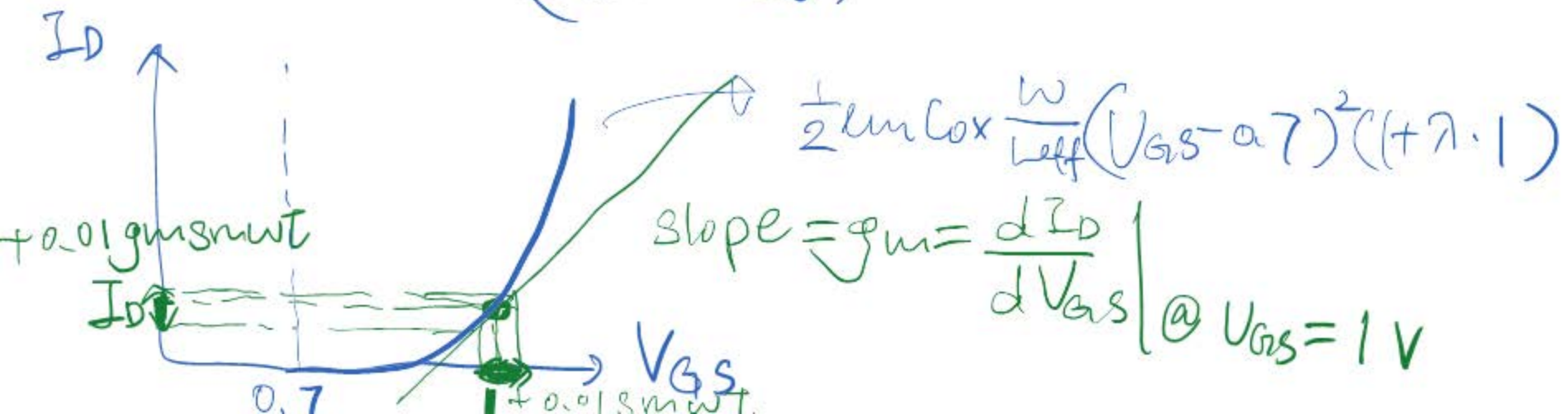
$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{20 \times 10^6}{2 \times 10^{-6} - 2LD} \right) (1 - 0.7)^2 (1 + \lambda \cdot 1)$$




small-signal

 

$$g_m = \frac{dI_D}{dV_{gs}} = \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{gs} - V_{th}) (1 + \lambda V_{ds})$$


$$= \mu_n C_{ox} \left(\frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2L_D} \right) (1 - 0.7) (1 + \lambda \cdot 1)$$

$$I_D = ? \quad \tilde{I}_D = ?$$

 

$$\begin{aligned}
 V_{DS} &= 1V \\
 &> V_{GS} - V_{TH} = 0.3V \\
 &\Rightarrow M_1 \text{ in sat.}
 \end{aligned}$$

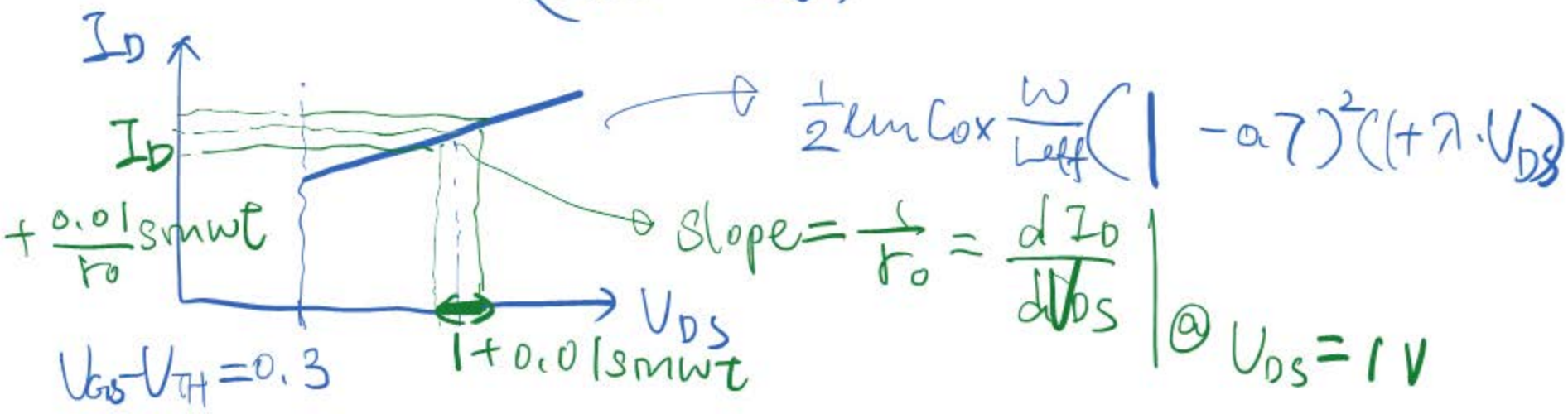
$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{20 \times 10^6}{2 \times 10^{-6} - 2LD} \right) (1 - 0.7)^2 (1 + \lambda \cdot 1)$$



Small-signal

(G)


(D)

 

$$r_o = \frac{1}{\text{slope}} = \frac{1}{dI_D/dV_{gs}} \approx \frac{1}{I_D \lambda}$$

Transconductance

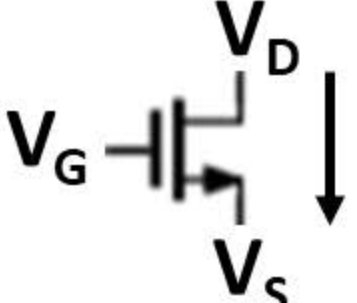- For the NMOS operating in the saturation region ($V_{DS} \geq V_{GS} - V_{TH}$):








$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

- ΔV_{GS} results in $\Delta I_D = g_m \times \Delta V_{GS}$.

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH}) (1 + \lambda V_{DS})$$

$$= \sqrt{2 \mu_n C_{ox} \frac{W}{L_{eff}} I_D} = \frac{2 I_D}{V_{GS} - V_{TH}} \cdot (1 + \lambda V_{DS})$$

Transconductance

     

- For a given NMOS, g_m changes according to the DC biasing condition.
- If a small signal is applied to a NMOS with defined biasing values, we assume the signal amplitude is small enough that the variation in g_m is negligible.

Body Effect

$$|V_{TH}| = |V_{TH0}| + \left(\gamma \sqrt{|2\Phi_F + V_{BS}|} - \sqrt{|2\Phi_F|} \right) \text{ for PMOS}$$

$$V_{TH} = V_{TH0} + \gamma (\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|}) \text{ for NMOS}$$

$$\Phi_F = \frac{kT}{q} \ln \frac{N_{sub}}{n_i}$$

$$\gamma = \frac{\sqrt{2q\epsilon_{Si}N_{sub}}}{C_{ox}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$

Ignored in Vt311
will learn in Vt320.

Body Effect


$$\begin{aligned}
 \mathbf{gmb} &= \frac{\partial I_D}{\partial V_{SB}} = \frac{\partial I_D}{\partial V_{TH}} \cdot \frac{\partial V_{TH}}{\partial V_{SB}} \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \cdot \frac{\partial V_{TH}}{\partial V_{SB}} \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \cdot \frac{\gamma}{2} \frac{1}{\sqrt{|2\Phi_F + V_{SB}|}} \\
 &= -\mathbf{gm} \cdot \boldsymbol{\eta}
 \end{aligned}$$




- V_{GS} increases, I_D increases.
- V_{SB} increases, V_{TH} increases and thus I_D decreases.

Small-Signal Model for NMOS

$$\begin{aligned}
 V_d &= V_D + v_d \\
 V_g &= V_G + v_g \\
 V_s &= V_S + v_s
 \end{aligned}$$

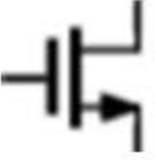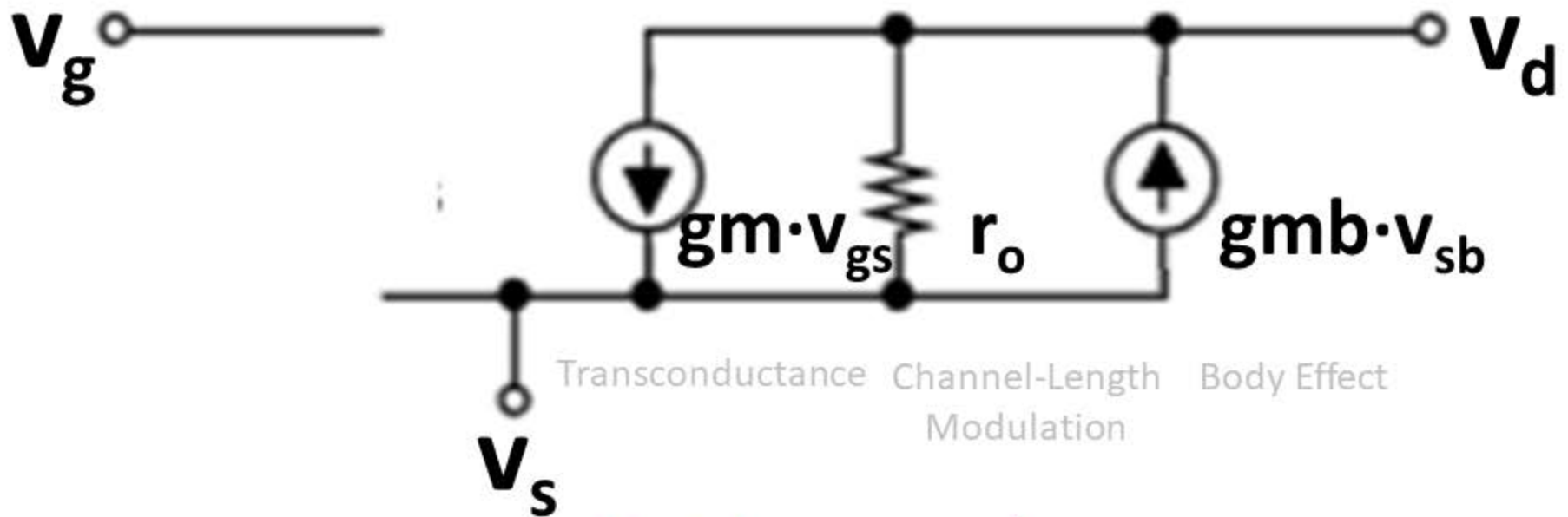
 $i_d = g_m \cdot v_{gs}$
 $i_d = g_{mb} \cdot v_{sb}$




$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \eta V_{DS})$$


Small-Signal Model for PMOS

$$V_s = V_S + v_s$$


$$V_g = V_G + v_g$$
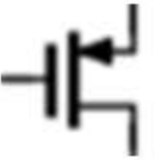
$$V_d = V_D + v_d$$

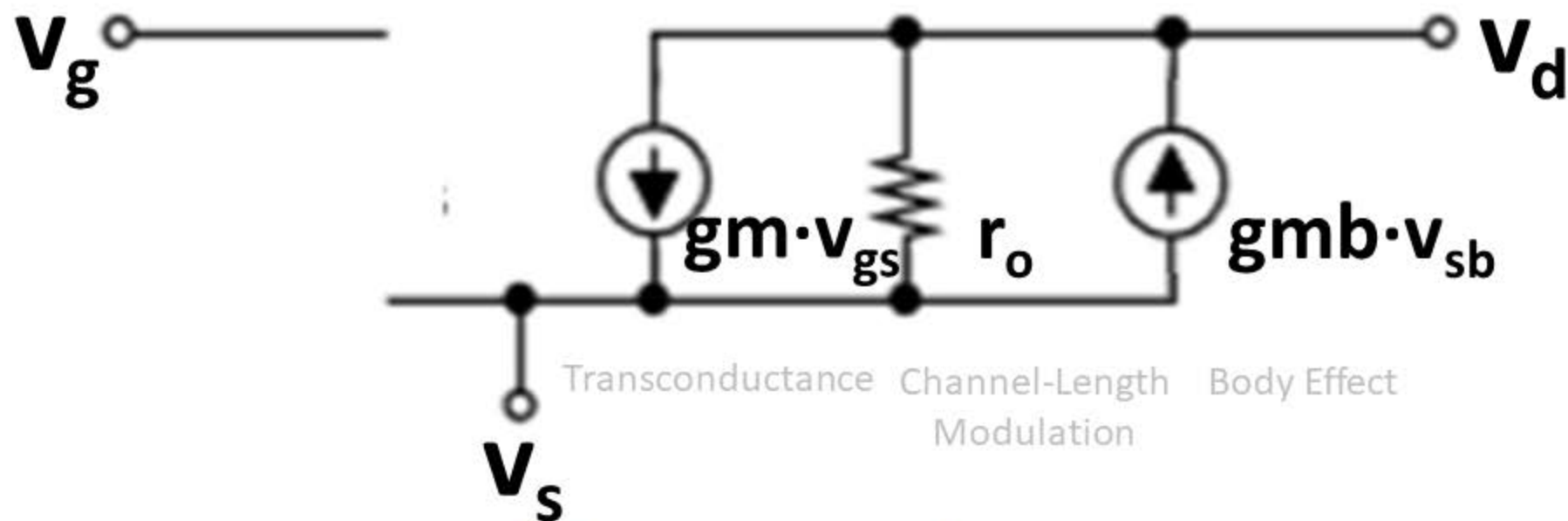 
 
$$i_d = g_m \cdot v_{gs} \quad i_d = g_{mb} \cdot v_{sb}$$



$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SG} - V_{TH})^2 (1 + \lambda V_{SD})$$



$$\boxed{\begin{matrix} \lambda \neq 0 \\ r \neq 0 \end{matrix}}$$



$$V_{DS1} = 4V \quad V_{SB} = 1V$$

$$V_{GS1} = 2V$$

$$V_{TH1} = 0.7 + 0.45(\sqrt{0.9+1} - \sqrt{0.9})$$

$$V_{DS1} > V_{GS1} - V_{TH1}$$

$$V_{SD2} = 4V$$


$$V_{SG2} = 1V \quad V_{BS2} = 1V$$

$$|V_{TH2}| = 0.8 + 0.4(\sqrt{0.8+1} - \sqrt{0.8})$$


$$V_{SD2} > V_{SG2} - |V_{TH2}|$$

 Example

Sketch I_D as a function of V_X increasing from $-\infty$ to 0. Assume $V_{TH} = 0.6$ V, $\gamma = 0.4$ $V^{1/2}$ and $2\Phi_F = 0.7$ V.



Solution:

 


$$1.2 = 0.6 + 0.4(\sqrt{0.7 - V_{X1}} - \sqrt{0.7}), V_{X1} = -4.76 \text{ V.}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (\underbrace{V_{GS}}_{1.2} - V_{TH})^2 (1 + \gamma \underbrace{V_{DS}}_2)$$

Layout

NMOS

 

PMOS

 

- W/L is chosen to determine gm. Minimum L is dictated by the process.
- Design rules: (1) Poly-Si extends beyond the channel area by some amount. (2) Enough n⁺, p⁺ or poly-Si area surrounding each via. (3) Enough distance between two vias. (4) Many others.

SPICE Model

NMOS Model

LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = $9e+14$	LD = $0.08e-6$	UO = 350	LAMBDA = 0.1
TOX = $9e-9$	PB = 0.9	CJ = $0.56e-3$	CJSW = $0.35e-11$
MJ = 0.45	MJSW = 0.2	CGDO = $0.4e-9$	JS = $1.0e-8$

*related to parasitic capacitances
will learn how to use these in*

PMOS Model

LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = $5e+14$	LD = $0.09e-6$	UO = 100	LAMBDA = 0.2
TOX = $9e-9$	PB = 0.9	CJ = $0.94e-3$	CJSW = $0.32e-11$
MJ = 0.5	MJSW = 0.3	CGDO = $0.3e-9$	JS = $0.5e-8$

Ve4/3

- Simulators such as SPICE and Cadence need accurate models for each device.
- Above is the simplest MOS SPICE model, known as "Level 1," and provide typical values for each parameter corresponding to 0.5- μm technology.

VTO: threshold voltage with zero V_{SB} (unit: V)
GAMMA: body effect coefficient (unit: $V^{1/2}$)
PHI: $2\Phi_F$ (unit: V)
TOX: gate oxide thickness (unit: m)
NSUB: substrate doping (unit: cm^{-3})
LD: source/drain side diffusion (unit: m)
UO: channel mobility (unit: $\text{cm}^2/\text{V}/\text{s}$)
LAMBDA: channel-length modulation coefficient (unit: V^{-1})
CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m^2)
CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)
PB: source/drain junction built-in potential (unit: V)
MJ: exponent in CJ equation (unitless)
MJSW: exponent in CJSW equation (unitless)
CGDO: gate-drain overlap capacitance per unit width (unit: F/m)
CGSO: gate-source overlap capacitance per unit width (unit: F/m)
JS: source/drain leakage current per unit area (unit: A/m^2)

NMOS vs PMOS in Performance

- PMOS devices are quite inferior to NMOS in most CMOS technology.
- Lower mobility of holes ($\mu_p C_{ox} \approx 0.5 \mu_n C_{ox}$) yield lower current drive and conductance.
- NMOS exhibit higher output resistance, providing more ideal current sources and higher voltage gain.
- It is preferable to use NMOS rather than PMOS wherever possible.