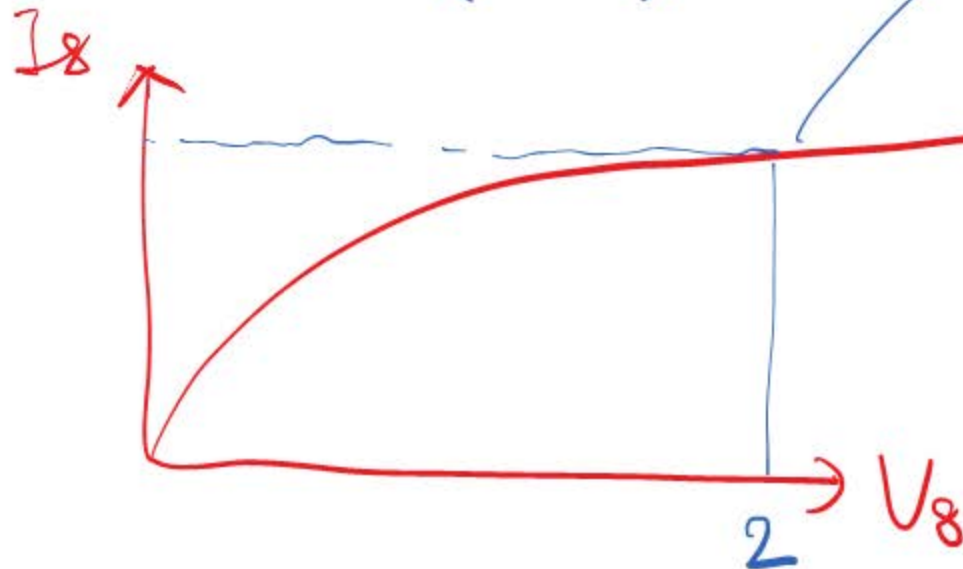


$V_A$  and  $V_B$  are DC voltages properly chosen so that  $M_{8,9}$  are in the sat.




slope =  $\frac{1}{r_{o8} + r_{o9} + (g_{m9} + g_{mb9})r_{o9}r_{o8}}$

CS } both are Voltage-in-Voltage-out  
SF } amplifiers.

Common-Gate (CG)

Current-in-Voltage-out

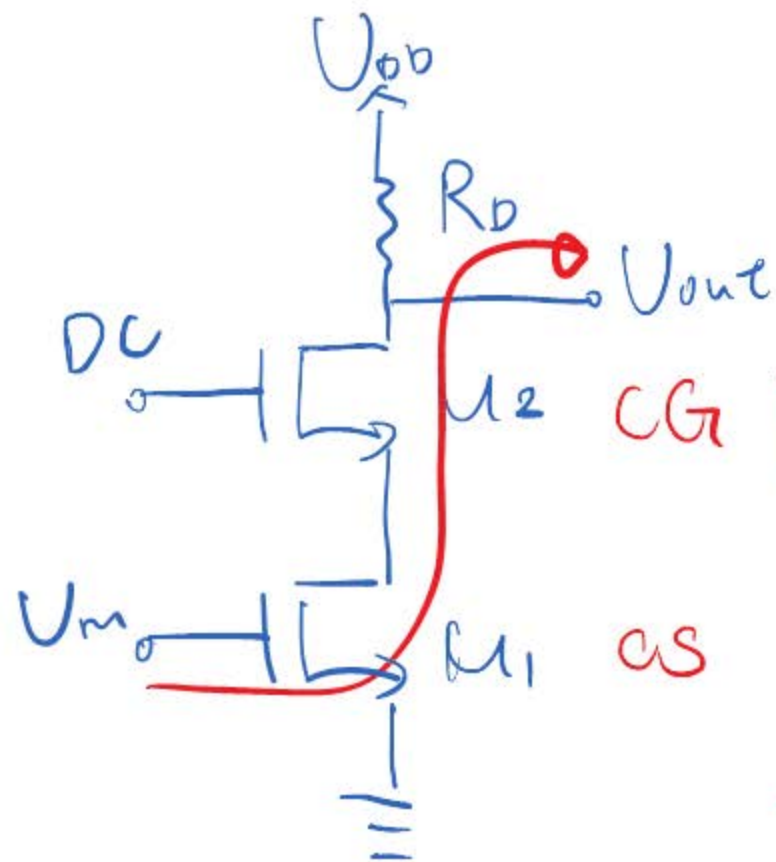


Assume  $M_1$  and  $M_2$  in Sat.

Assume  $\lambda \neq 0$ ,  $\theta \neq 0$

$A_V = ?$

Cascode

Small signal

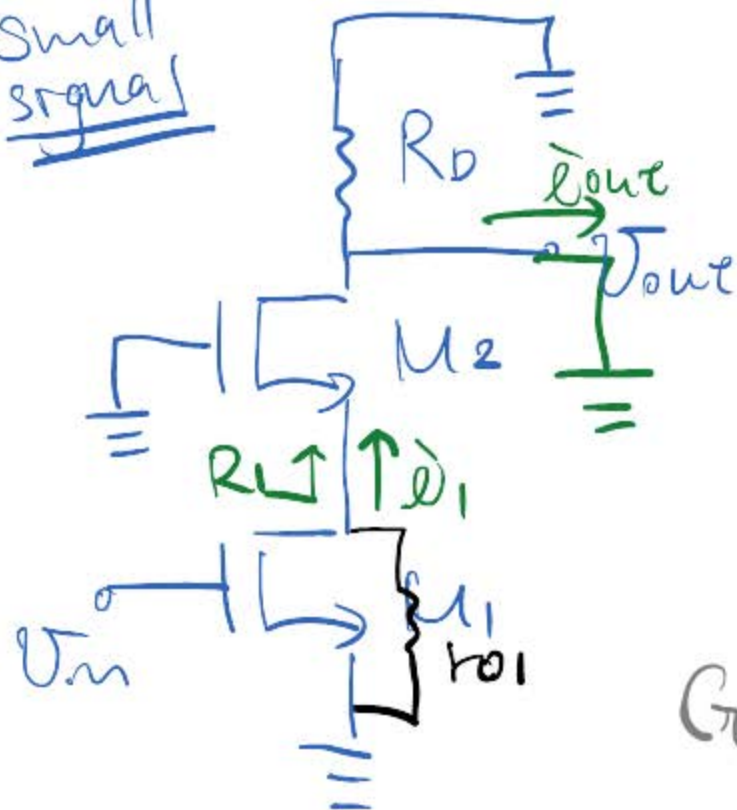

$$G_m = \bar{i}_{out} / V_m$$


$$\bar{i}_1 = \bar{i}_{out}$$

$$R_1 = r_{o2} // \frac{1}{g_{m2} + g_{mb2}} \quad (\text{small})$$


$$\bar{i}_1 = (-g_{m1} V_m) \frac{r_{o1}}{r_{o1} + R_1}$$

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left( r_{o2} // \frac{1}{g_{m2} + g_{mb2}} \right)}$$

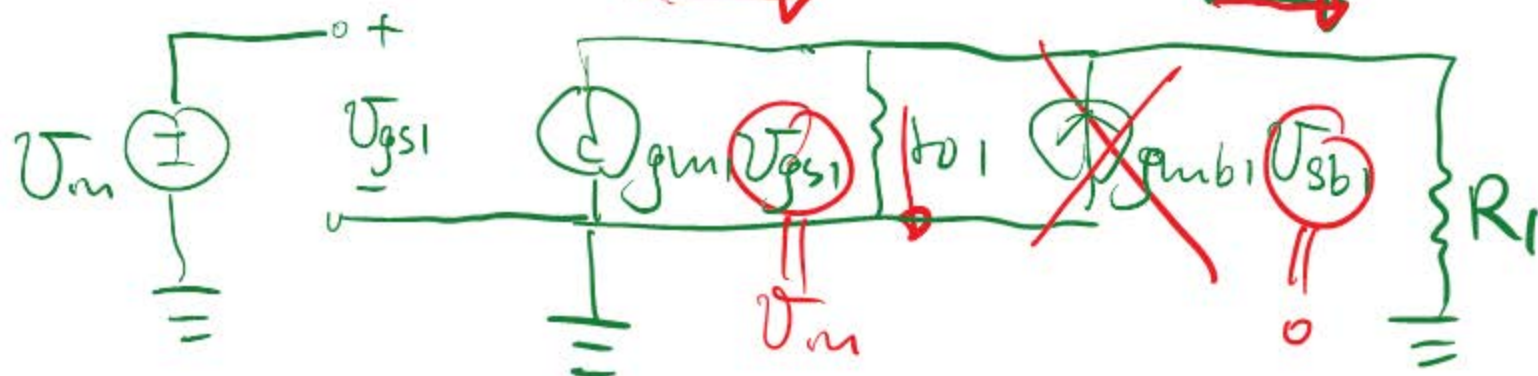
$\xrightarrow{-g_{m1} V_m}$ 
 $\xrightarrow{\bar{i}_1}$



Small signal

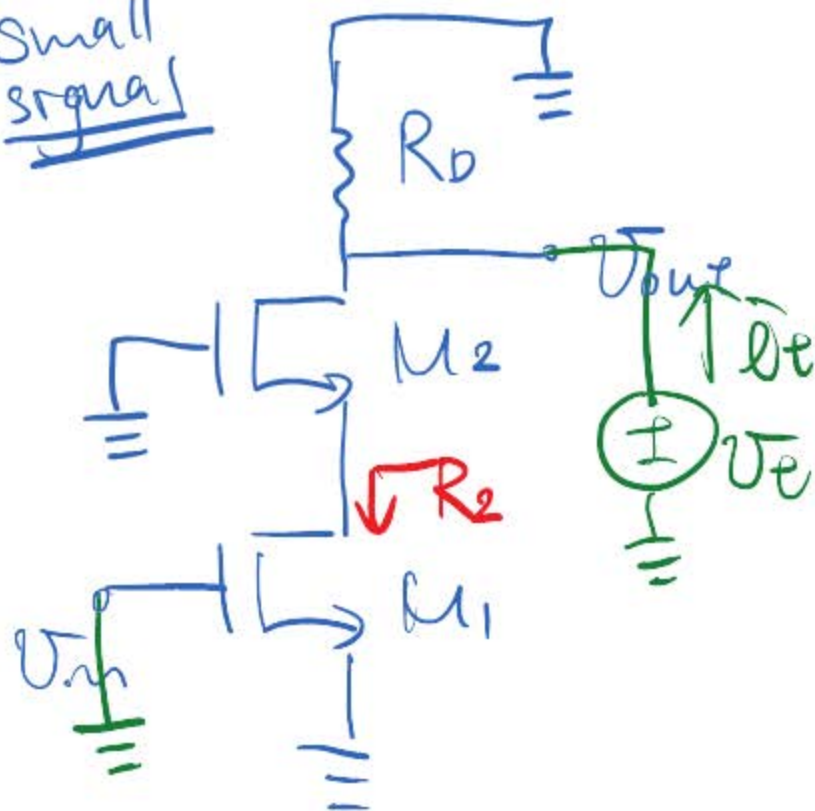

$\Rightarrow$

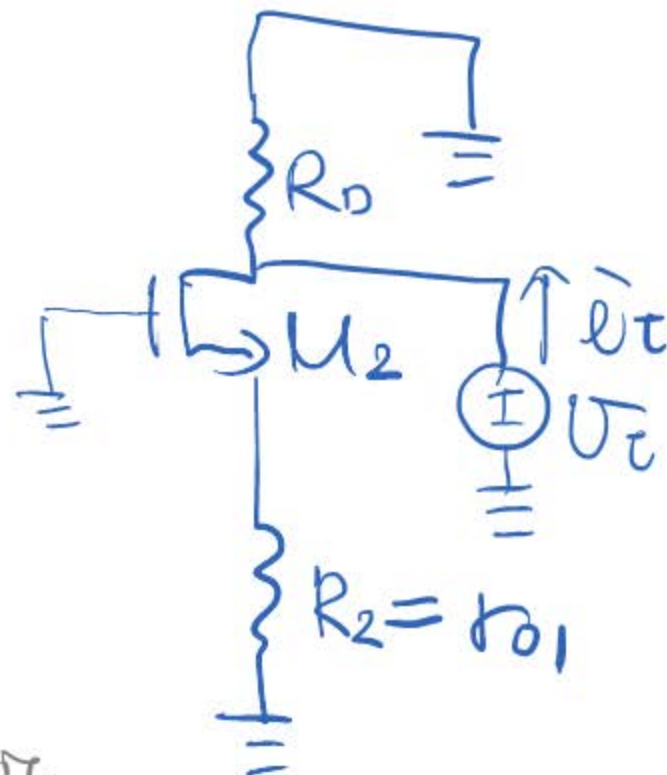


intrinsic  
gain of  $M_2$

$$R_{out} = R_D // \left[ r_{o2} + r_{o1} + \underbrace{(g_{m2} + g_{mb2}) r_{o2} r_{o1}}_{\text{intrinsic gain of } M_2} \right]$$




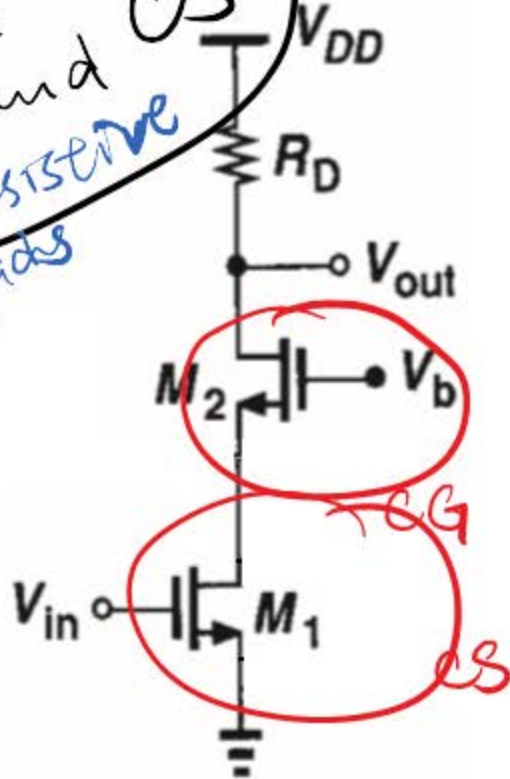Comparison  
between  
 $C_G + C_S$  and  $C_S$   
with resistive loads




$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left( r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)}$$

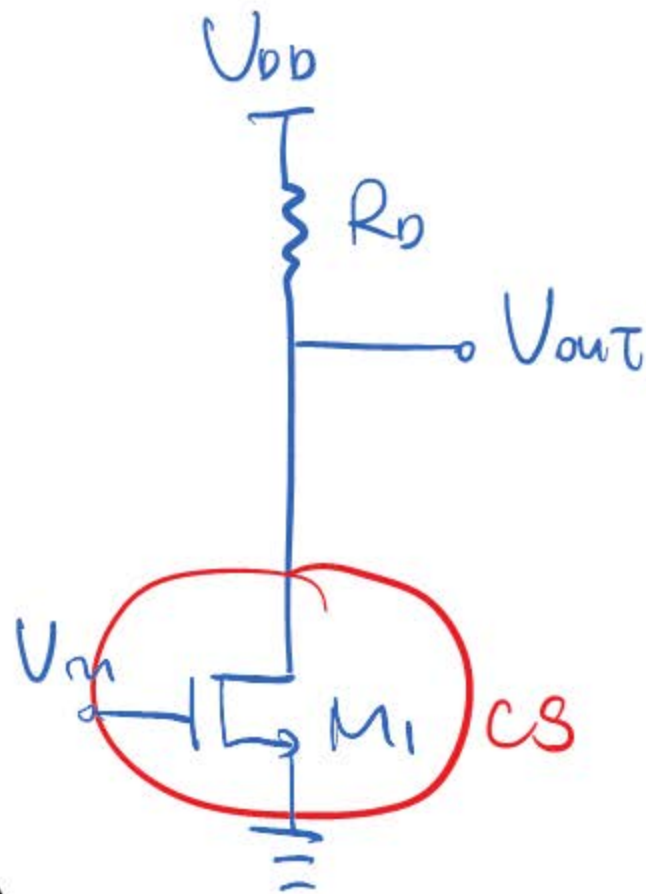
$$R_{out} = R_D \parallel \left[ r_{o2} + r_{o1} + (g_{m2} + g_{mb2}) r_{o2} r_{o1} \right] \quad R_{out} = r_{o1} \parallel R_D$$




$$G_m = -g_{m1}$$

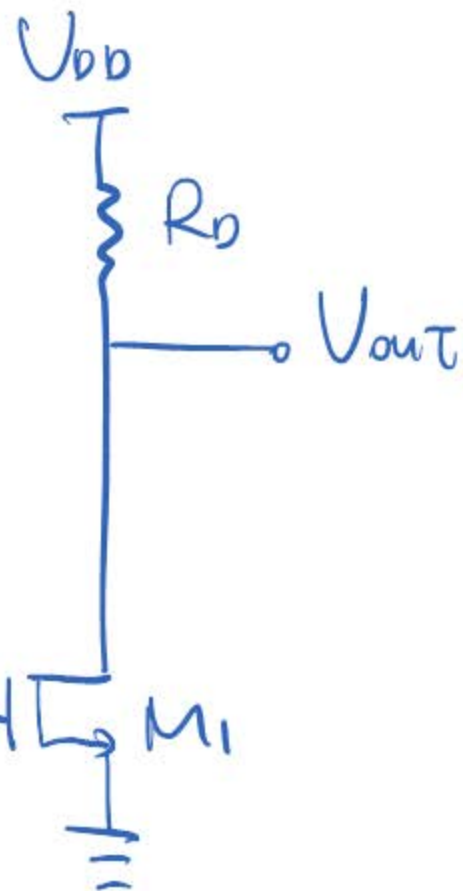

$$G_m = -g_{m1}$$

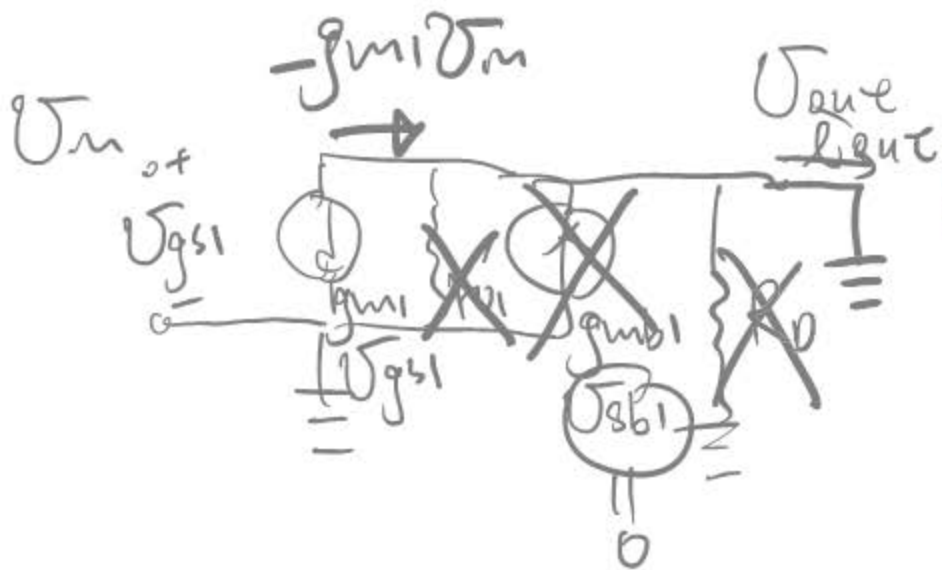

$$V_{out} = -g_{m1} V_m$$

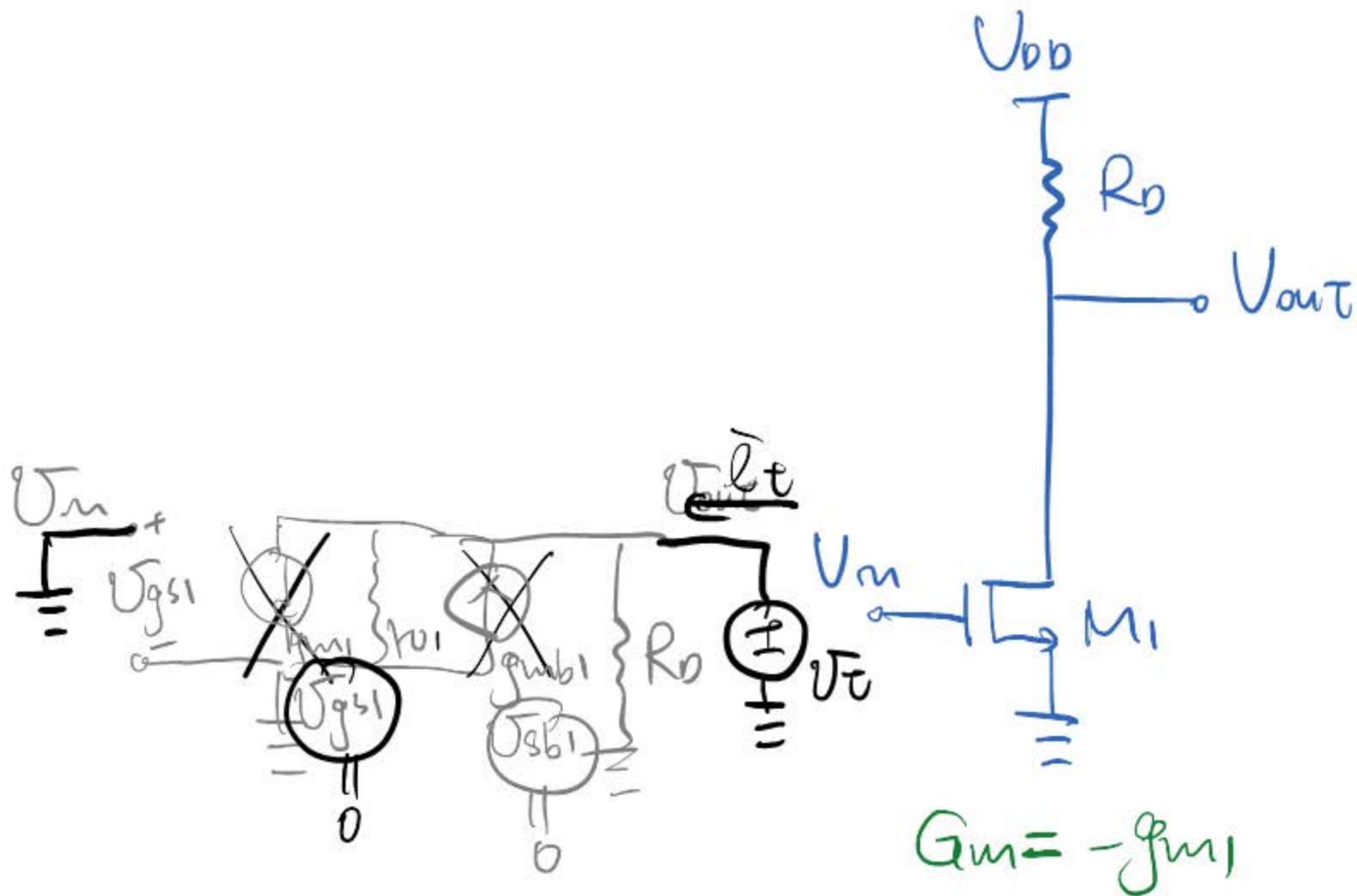

$$R_{out} = \frac{V_t}{I_t} = R_o \parallel r_{o1}$$




Comparison  
between  
CG + CS and CS  
with current  
source loads

\* Assume all  
msat.


\* Assume  
 $\lambda \neq 0, r \neq 0$

\*  $V_a, b, c, d$  are DC

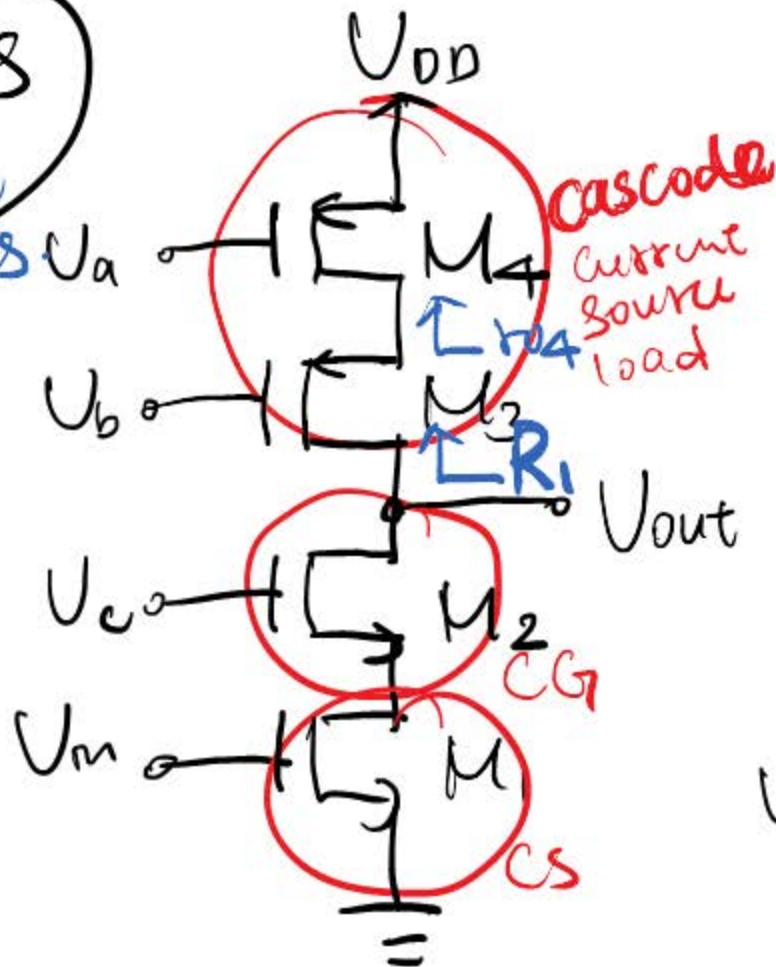

$$R_1 = r_{o3} + r_{o4} + (g_{m3} + g_{mb3}) r_{o3} r_{o4}$$



intrinsic gain  
of  $M_3$

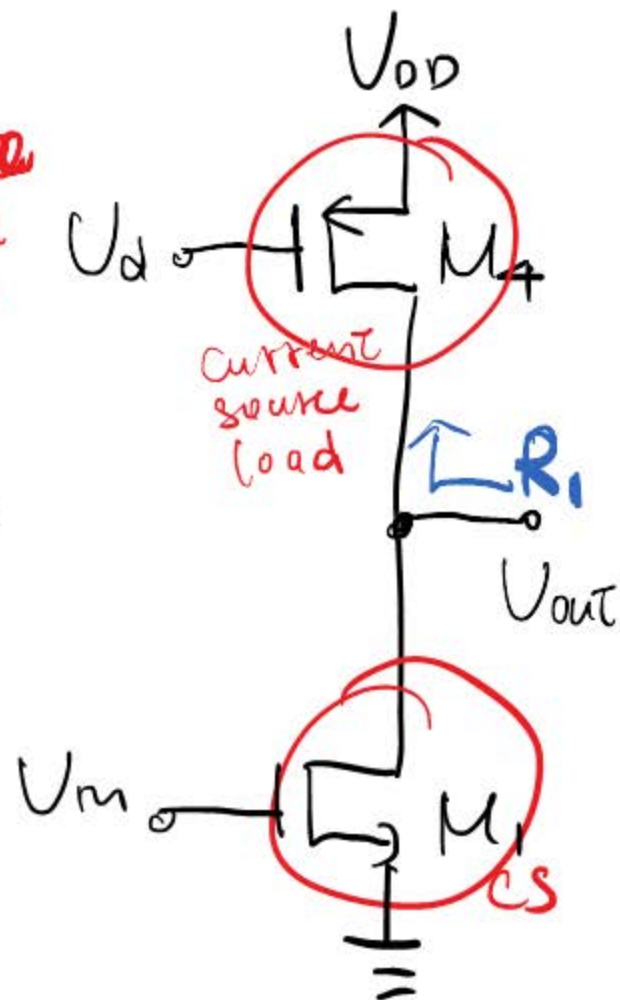

$$R_1 = r_{o4}$$

Comparison  
between  
CG + CS and CS  
with current  
source loads

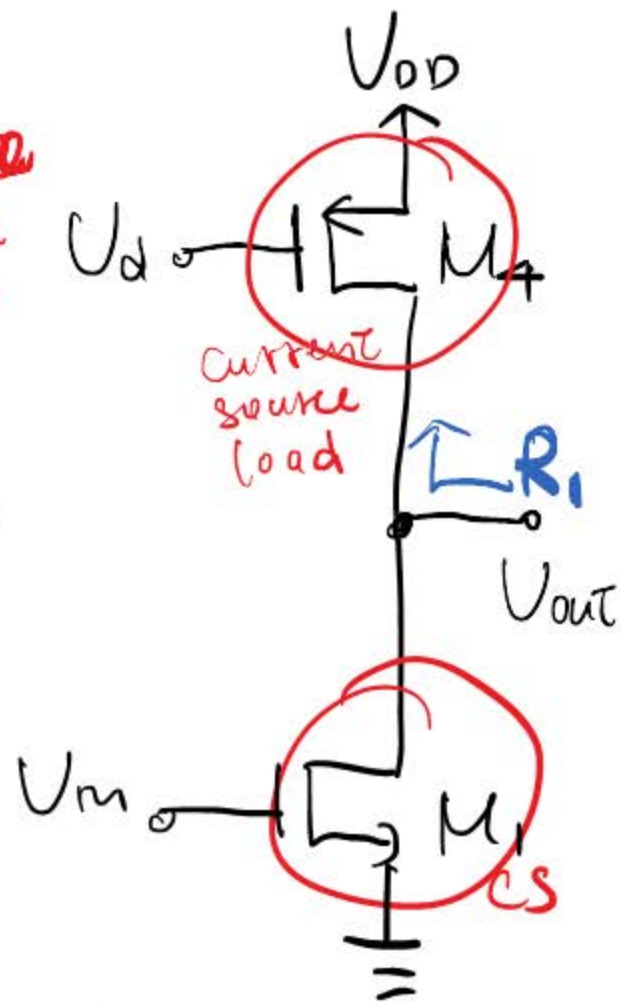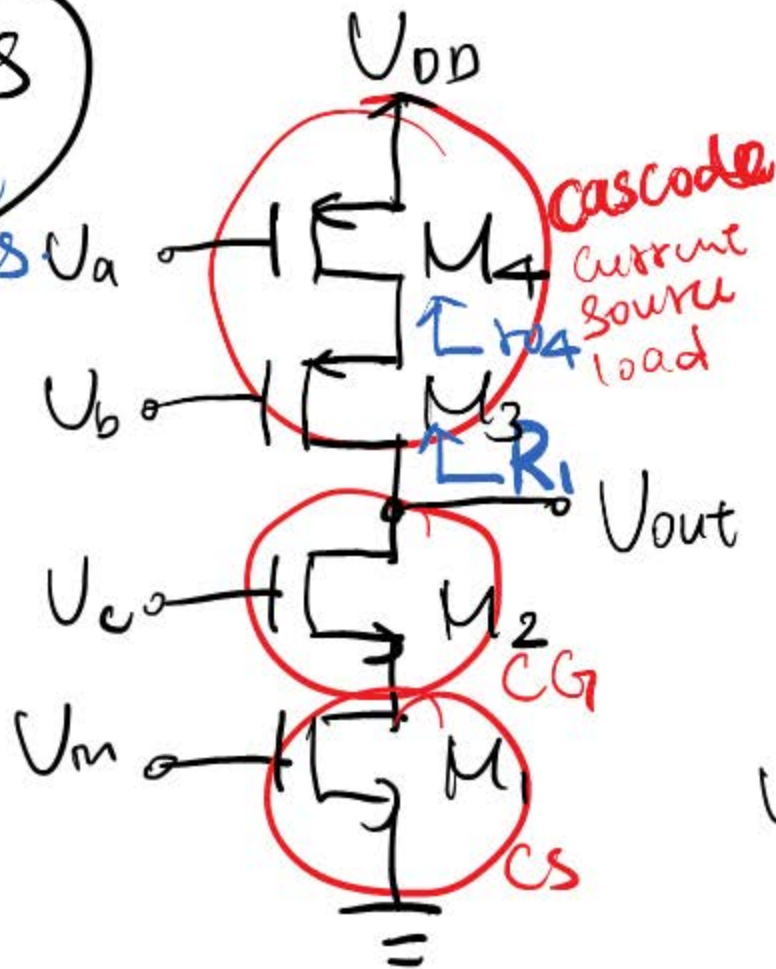
- \* Assume all  $m_{sat}$ .
- \* Assume  $\lambda \neq 0, r \neq 0$
- \*  $V_a, b, c, d$  are DC



$$G_m = -g_{m1}$$

$$R_{out} = r_{o1} \parallel r_{o4}$$

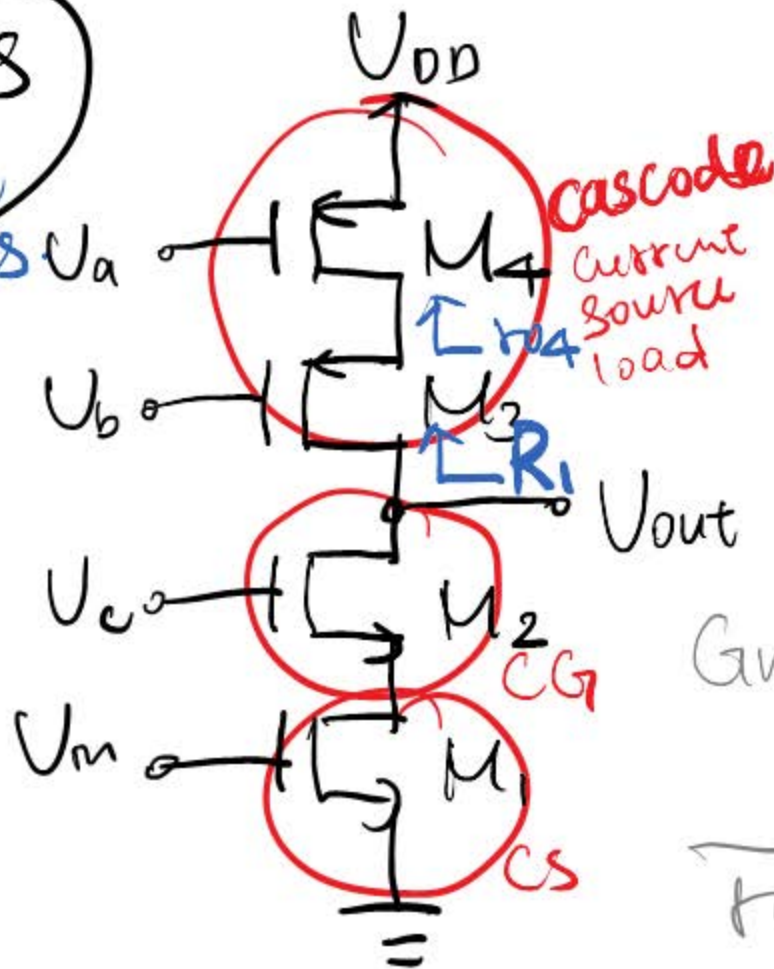Comparison  
between  
CG + CS and CS  
with current  
source loads



\* Assume all  
msat.

\* Assume  
 $\lambda \neq 0, r \neq 0$

\*  $V_a, b, c, d$  are DC

$$G_m = -g_{m1}$$


$$\frac{r_{o1}}{r_{o1} + (r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}})}$$

$$R_{out} = [r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3}r_{o4}] \parallel$$

$$[r_{o2} + r_{o1} + (g_{m2} + g_{mb2})r_{o2}r_{o1}]$$



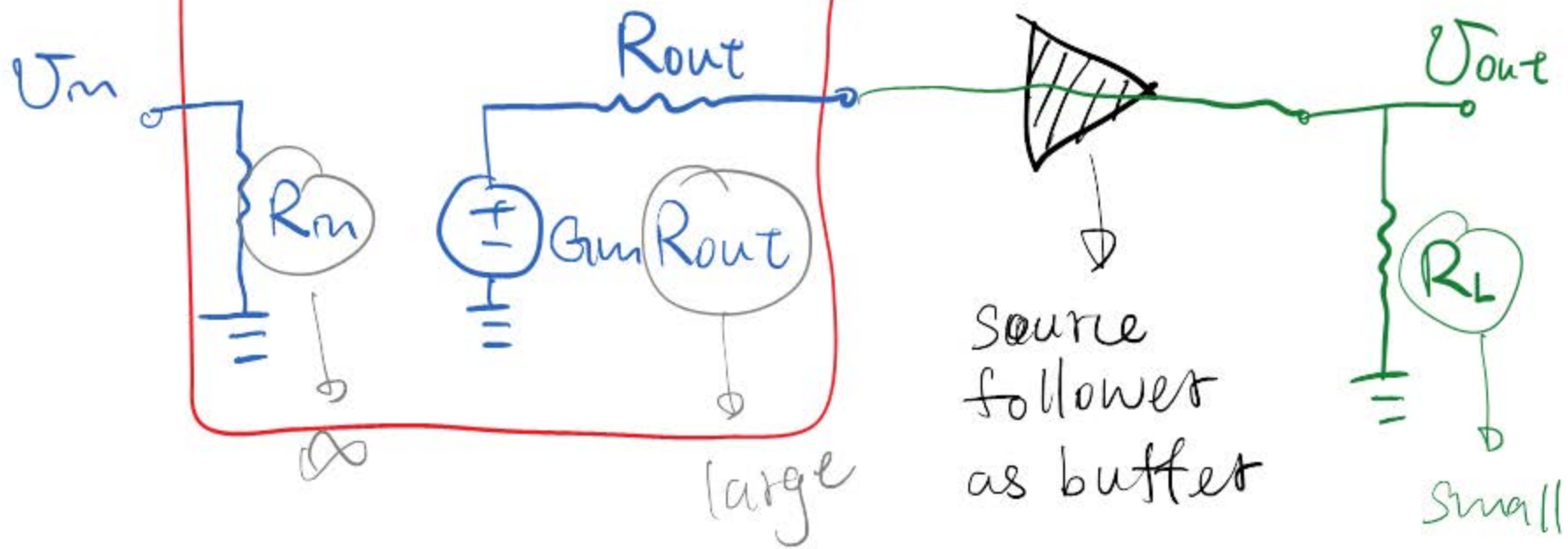Equivalent small signal  
circuit for cascode  
with cascode current source.



$$A_v = \frac{V_{out}}{V_m} = G_m R_{out} \frac{R_L}{R_{out} + R_L} \text{ (without buffer)}$$