
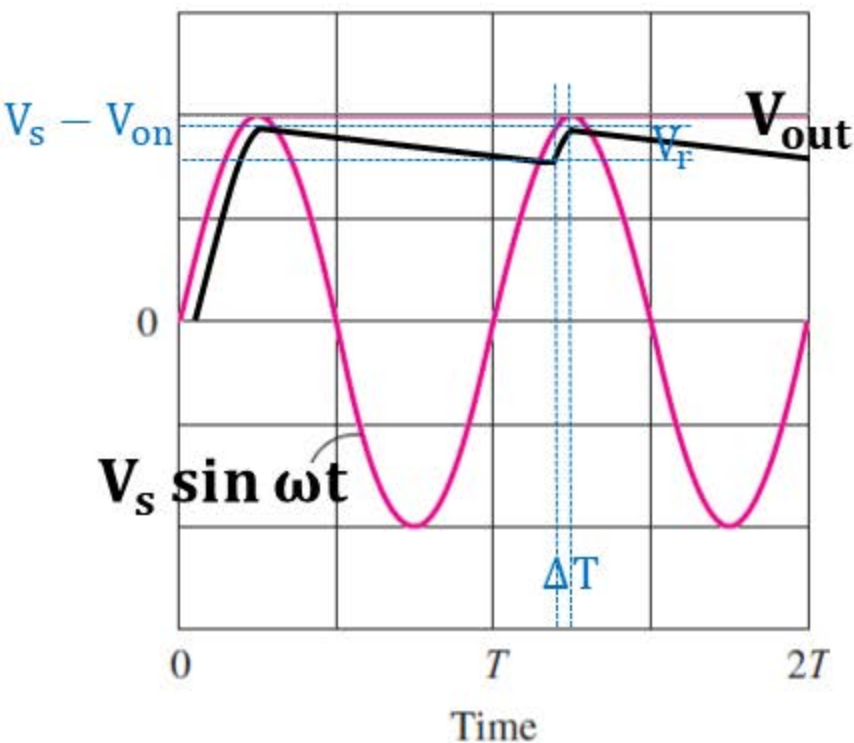


Half-Wave Rectifier with RC Load (I)

1

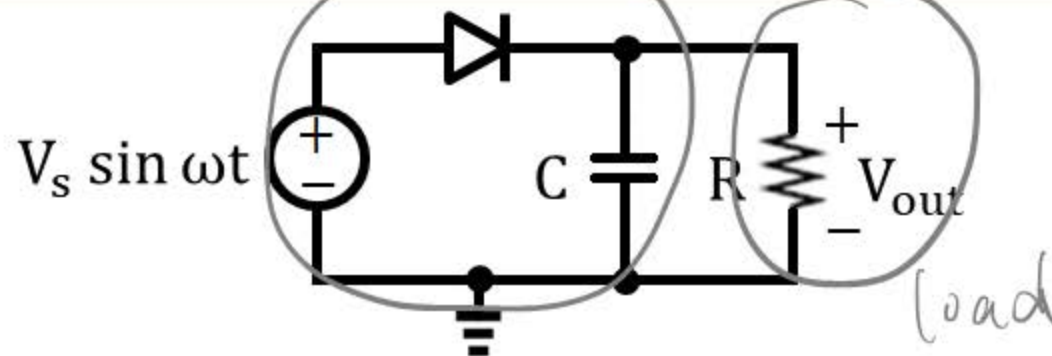

$$V_{dc} = V_s - V_{on}$$



$$I_{dc} = \frac{V_{dc}}{R}$$

ripple voltage

$$V_r = (V_s - V_{on}) \left(1 - e^{-\frac{T-\Delta T}{RC}} \right)$$

$$\cong (V_s - V_{on}) \left(\frac{T - \Delta T}{RC} \right) \text{ if } (T - \Delta T) \ll RC$$

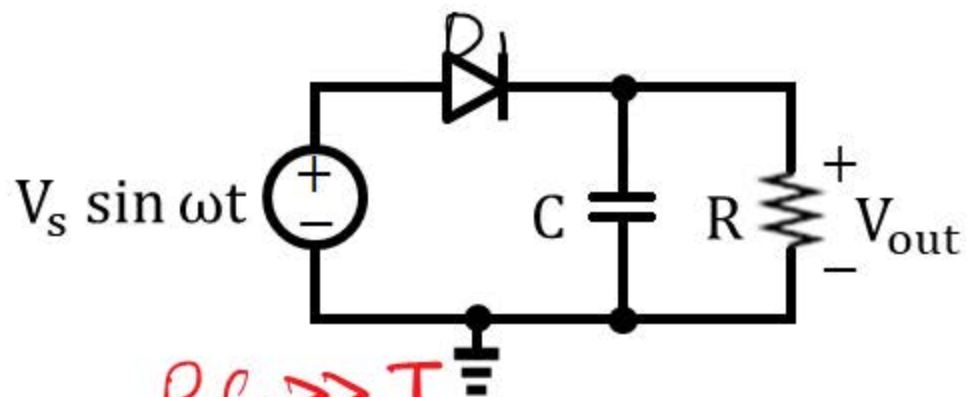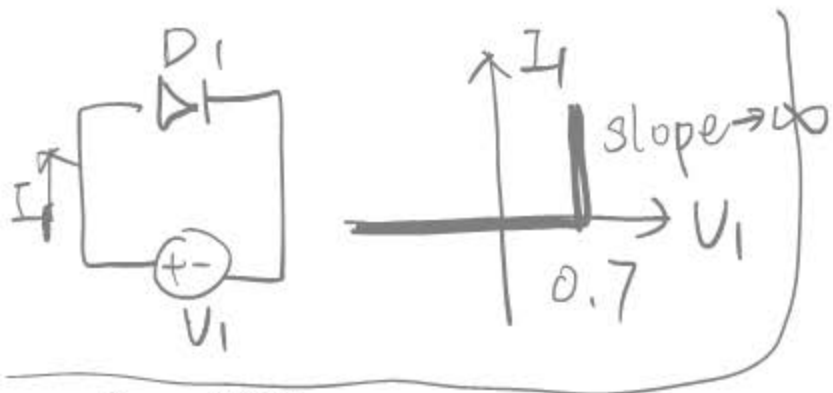
$$\cong (V_s - V_{on}) \left(\frac{T}{RC} \right) \text{ if } \Delta T \ll T$$



$$V_s = 10 \text{ V}$$


$$\omega = 2\pi f = 2\pi \frac{1}{0.01} = 200\pi \text{ (rad/sec)}$$

$$RC \gg T$$

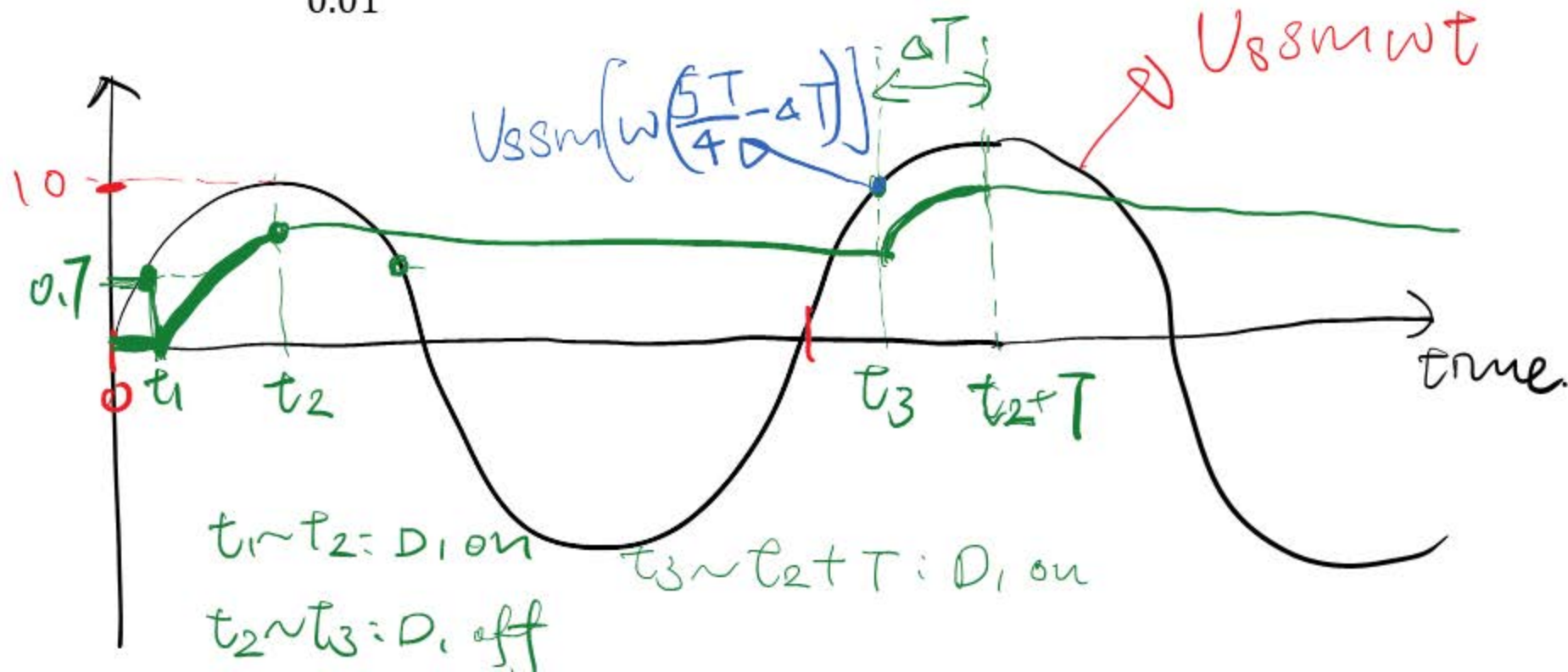


Half-Wave Rectifier with RC Load (II)

3

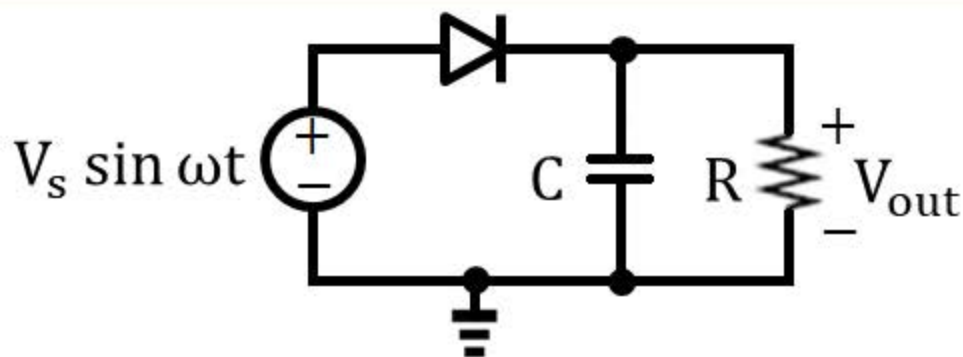

conduction angle and interval

$$\theta_c = \omega \Delta T$$

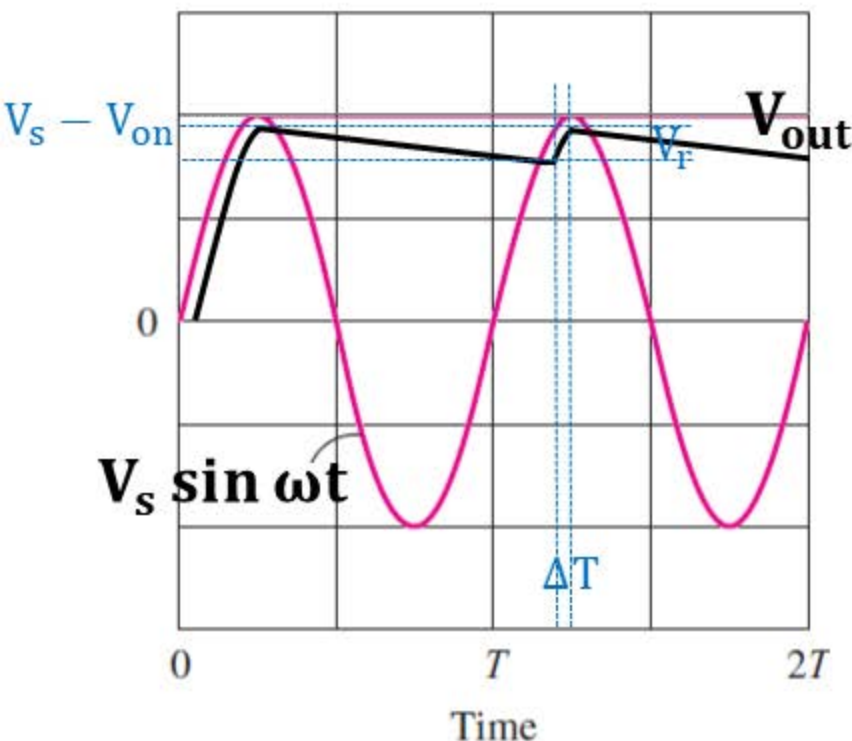

$$V_s \sin \left[\omega \left(\frac{5T}{4} - \Delta T \right) \right] - V_{on} = (V_s - V_{on}) - V_r$$

$$V_s \sin \left(\frac{5\pi}{2} - \theta_c \right) - V_{on} = (V_s - V_{on}) - V_r$$



$$V_s \cos \theta_c = V_s - V_r$$

$$\cos \theta_c = \frac{V_s - V_r}{V_s} \cong 1 - \frac{\theta_c^2}{2} \quad \text{if } \theta_c \text{ very small}$$

$$\theta_c = \sqrt{\frac{2V_r}{V_s}}$$

$$\Delta T = \frac{\theta_c}{\omega} = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_s}}$$

Half-Wave Rectifier with RC Load (III)

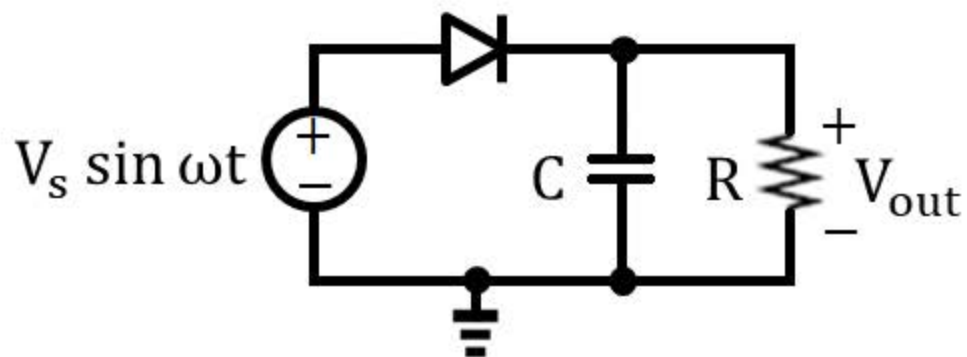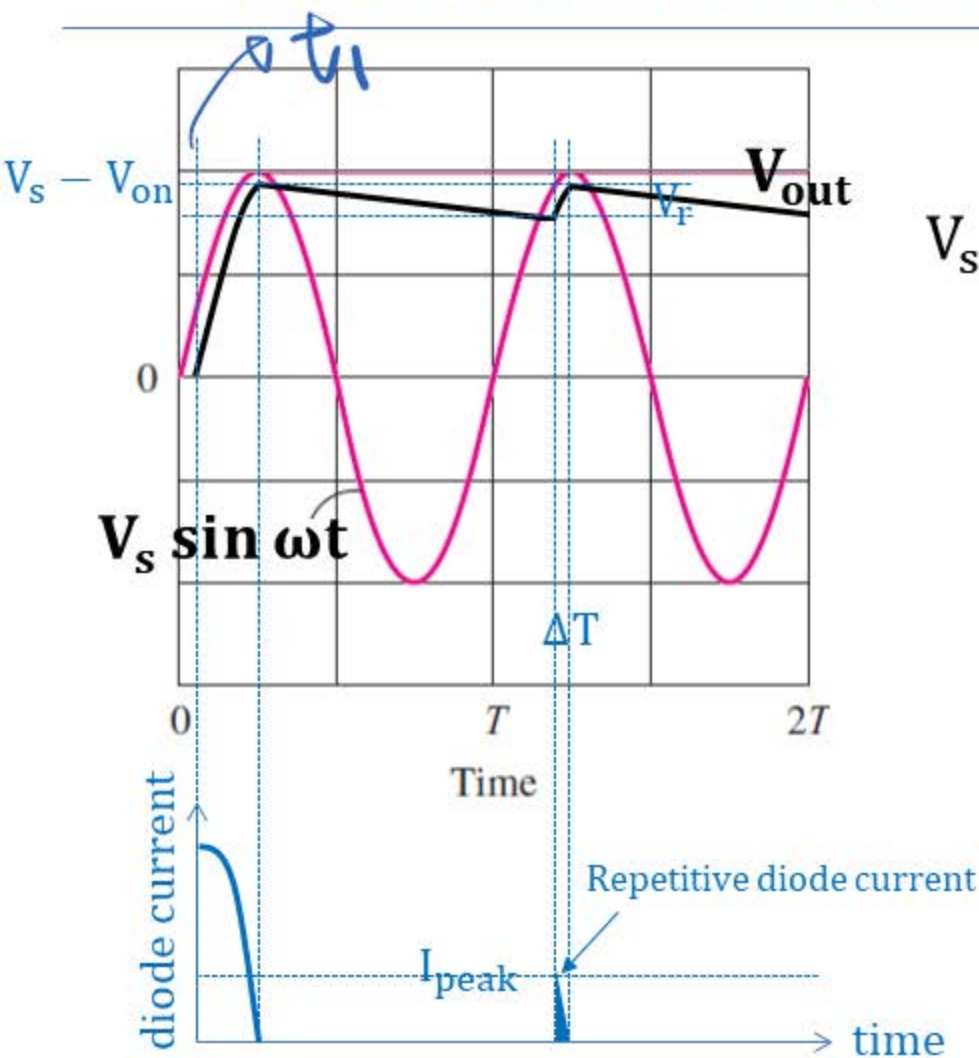

The charge filled on C during ΔT is discharged during $T - \Delta T$.

$$Q \cong \frac{I_{peak} \Delta T}{2} = I_{dc} (T - \Delta T) \cong I_{dc} T$$

$$I_{peak} = \frac{2I_{dc} T}{\Delta T}$$

$$I_{surge} = C \frac{d(V_s \sin \omega t - V_{on})}{dt} = \omega C V_s \cos \omega t \text{ if } t = 0$$



During charging period (ΔT), almost all diode current goes to C .

$$\left| \frac{1}{SC} \right| = \frac{1}{2\pi \frac{1}{T} C} = \frac{T}{2\pi C} \ll R \text{ if } RC \gg T$$



$$\dot{\varphi}_1 = C_1 \frac{d u_1}{d t}$$

Half-Wave Rectifier with RC Load (IV)

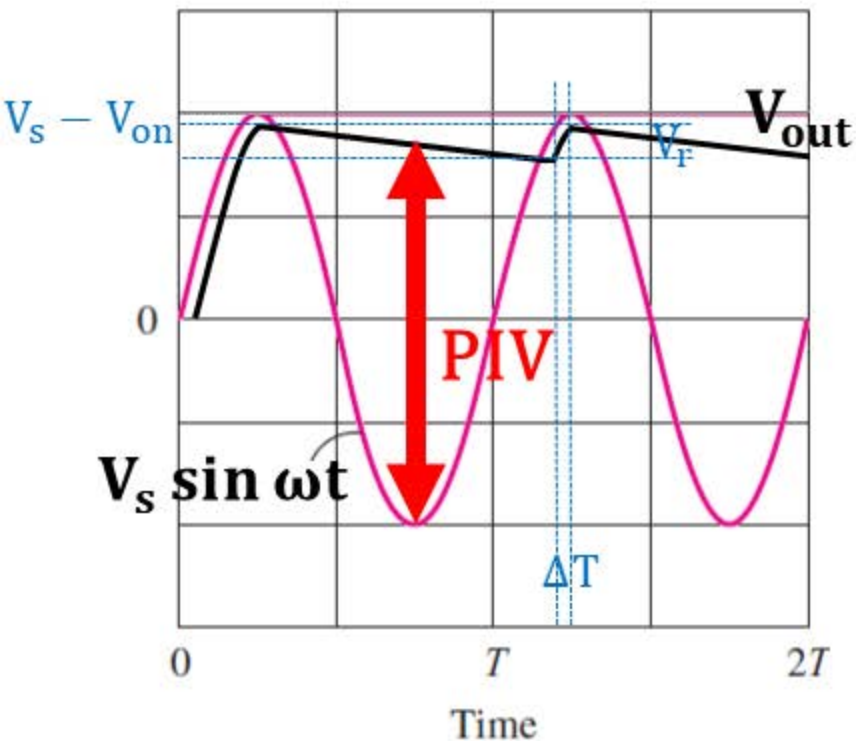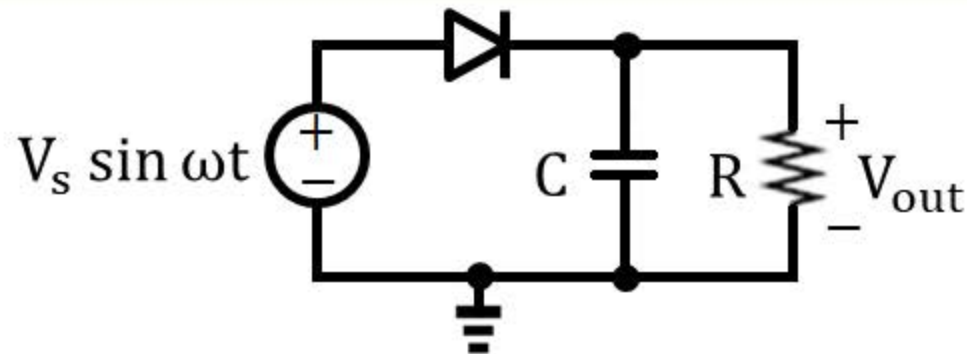

Peak-inverse-voltage (PIV) $\cong 2V_s - V_{on}$

If too large, the diode breaks down.

Example

Find the value of the dc output voltage, dc output current, ripple voltage, conduction interval, conduction angle and diode peak current for a half-wave rectifier driven from a transformer having a secondary voltage of $12.6 \text{ V}_{\text{rms}}$ (60 Hz) with $R = 15 \Omega$ and $C = 25,000 \mu\text{F}$. Assume $V_{\text{on}} = 1 \text{ V}$.

$$V_{\text{dc}} = 12.6\sqrt{2} - 1 = 16.8 \text{ (V)}$$

$$I_{\text{dc}} = \frac{16.8}{15} = 1.12 \text{ (A)}$$

$$V_r \cong V_{\text{dc}} \frac{T}{RC} = 16.8 \frac{1}{15 \times 25000 \times 10^{-6} \times 60} = 0.747 \text{ (V)}$$



$$\theta_c \cong \sqrt{\frac{2V_r}{V_s}} = \sqrt{\frac{2 \times 0.747}{12.6 \times \sqrt{2}}} = 0.29 \text{ (rad) or } 16.6^\circ$$

$$\Delta T \cong \frac{\theta_c}{\omega} = \frac{0.29}{2\pi \times 60} = 7.69 \times 10^{-4} \text{ (sec)}$$

$$I_{\text{peak}} = \frac{2 \times 1.12 \times \frac{1}{60}}{7.69 \times 10^{-4}} = 48.6 \text{ (A)}$$

- Make sure all assumptions are valid. \rightarrow Make sure $RC \gg T$
- Since R is small (15Ω), C needs to be large ($25,000 \mu\text{F}$) to maintain a low V_r .
- The diode must be able to handle these repetitively high peak currents.

Full-Wave Bridge Rectifier (I)

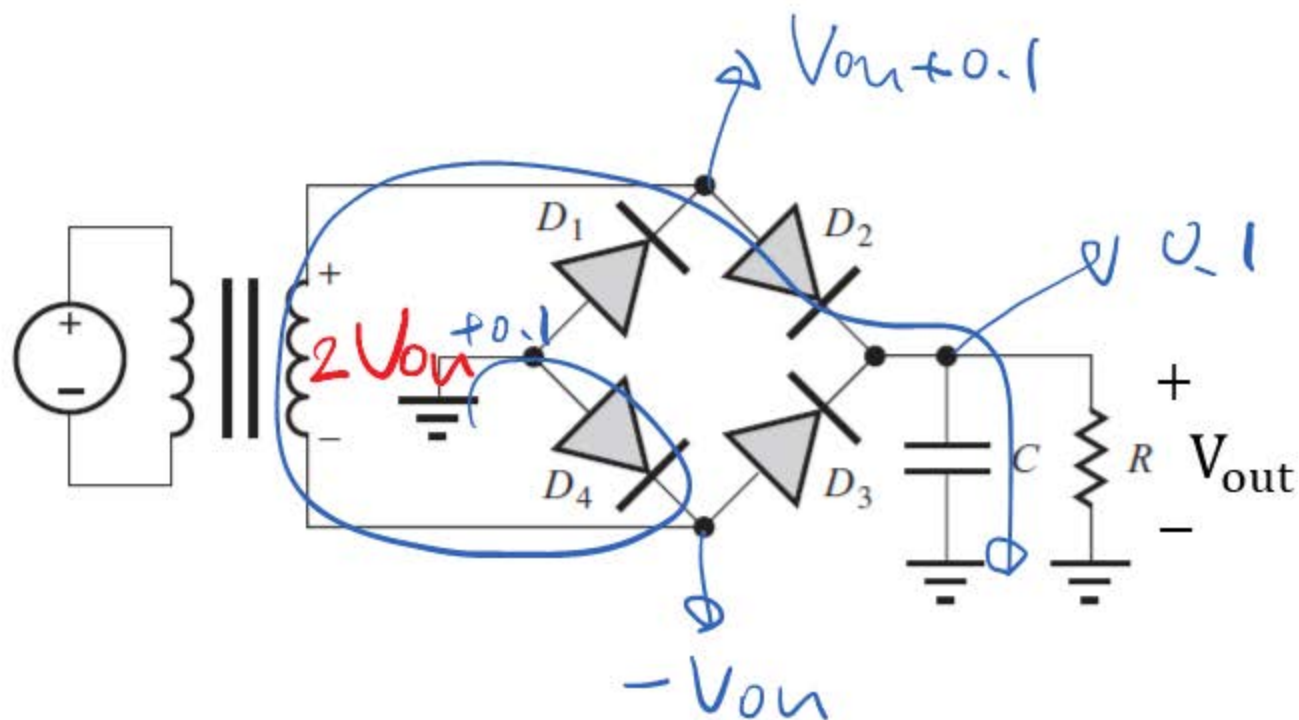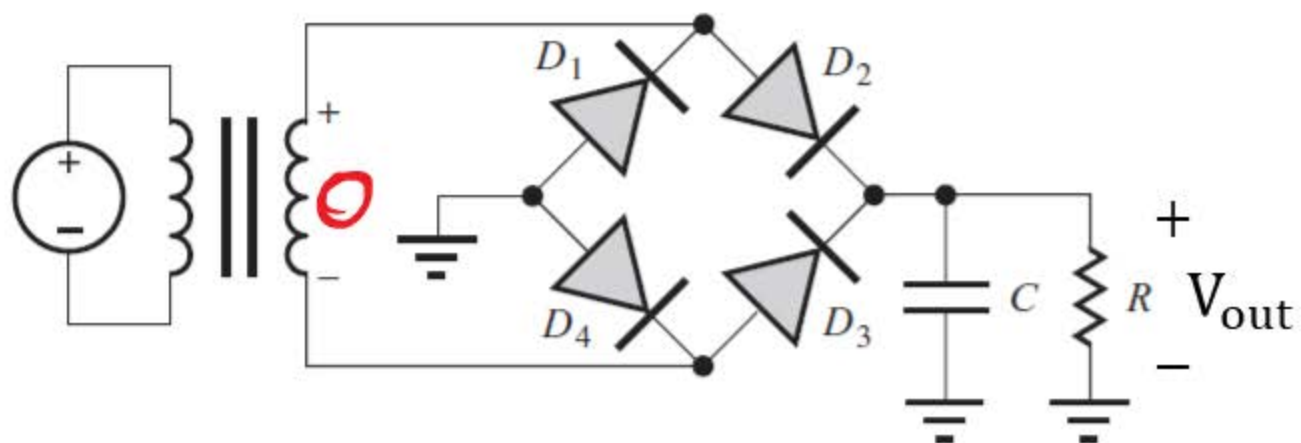

Full-Wave Bridge Rectifier (I)

