
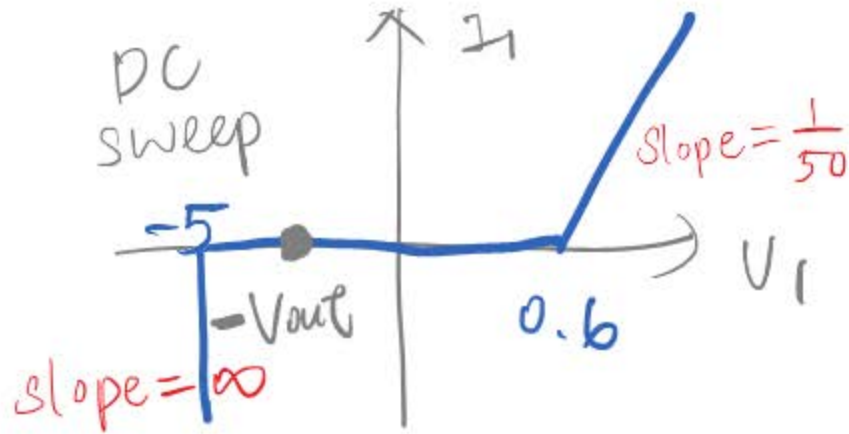



$$V_{out} = 5V$$

$$\frac{20-5}{5k} - I_L = I_8$$


$$\frac{5}{5k} = I_L$$

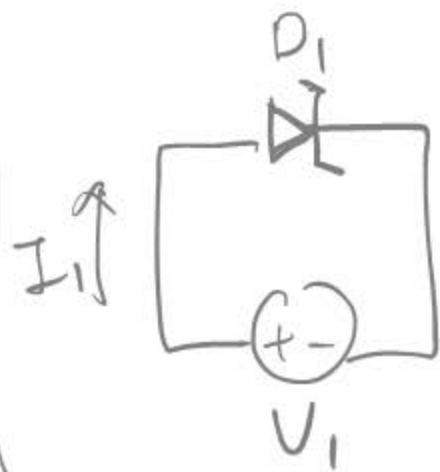

$$R = 5 \text{ k}\Omega$$

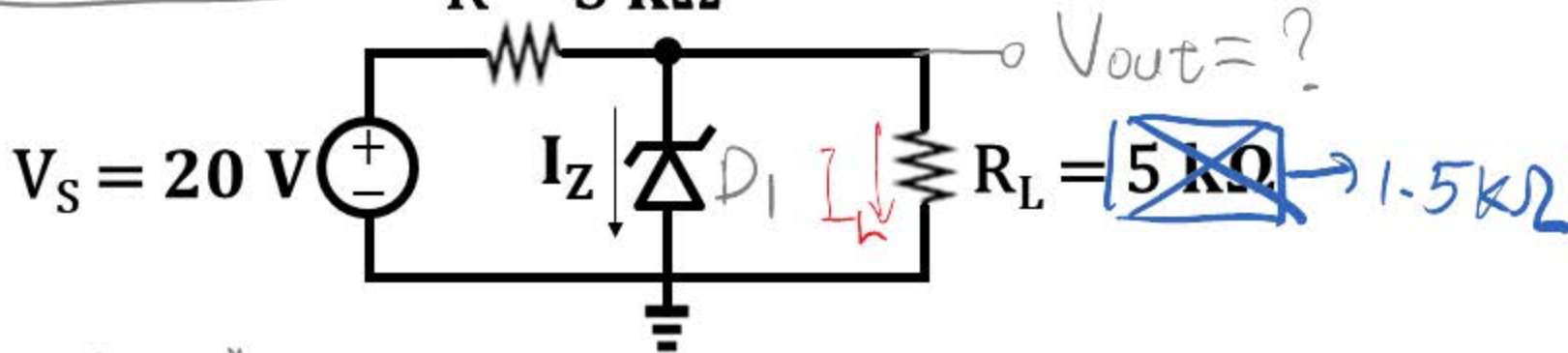



Assumption NOT valid

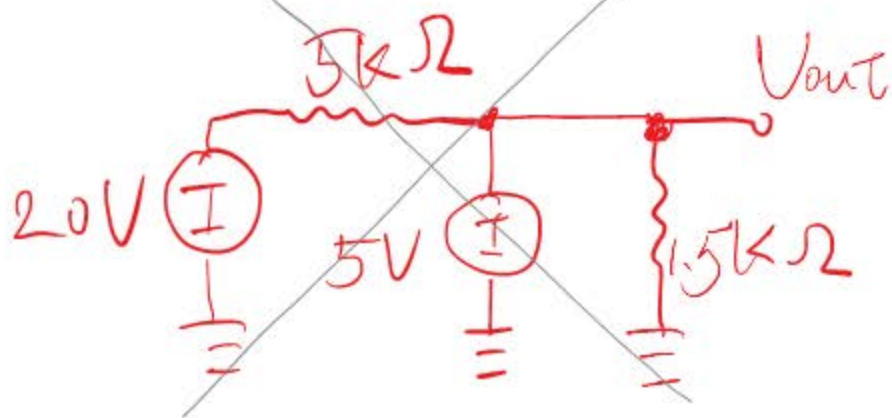



$$20 \cdot \frac{1.5 \text{ k}}{1.5 \text{ k} + 5 \text{ k}} = V_{out}$$

check:
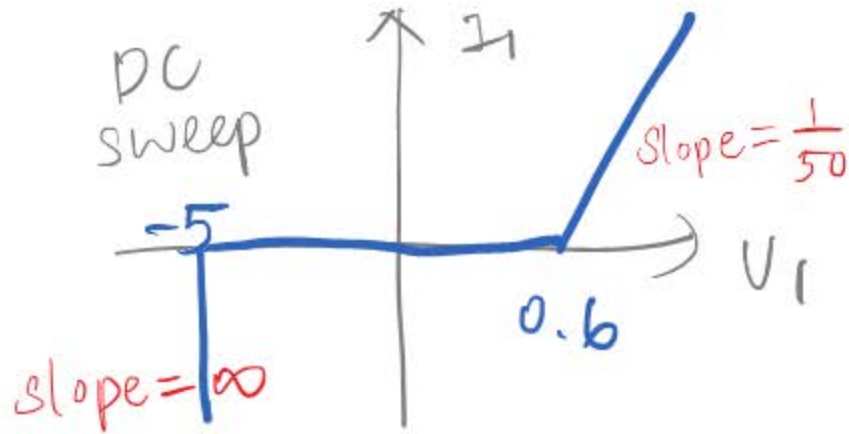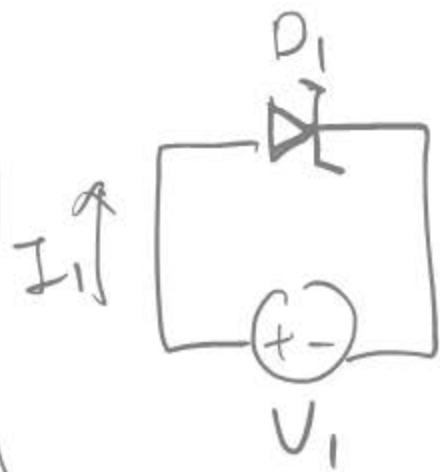
$$\frac{5}{1.5 \text{ k}} = I_L > \frac{20 - 5}{5 \text{ k}}$$




$R = 5 \text{ k}\Omega$

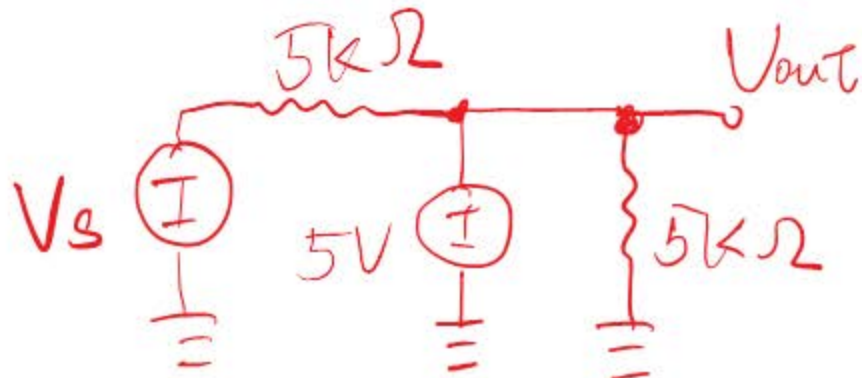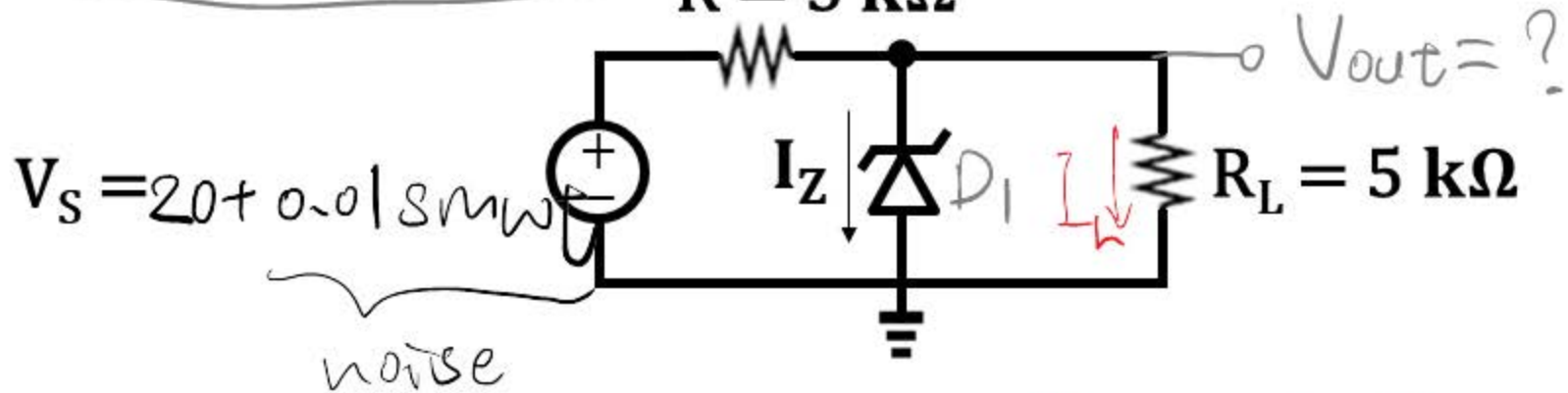



$$V_{out} = 5 \text{ V}$$

$$\frac{V_s - 5}{5 \text{ k}} - I_L = I_8$$

$$\frac{5}{5 \text{ k}} = I_L$$



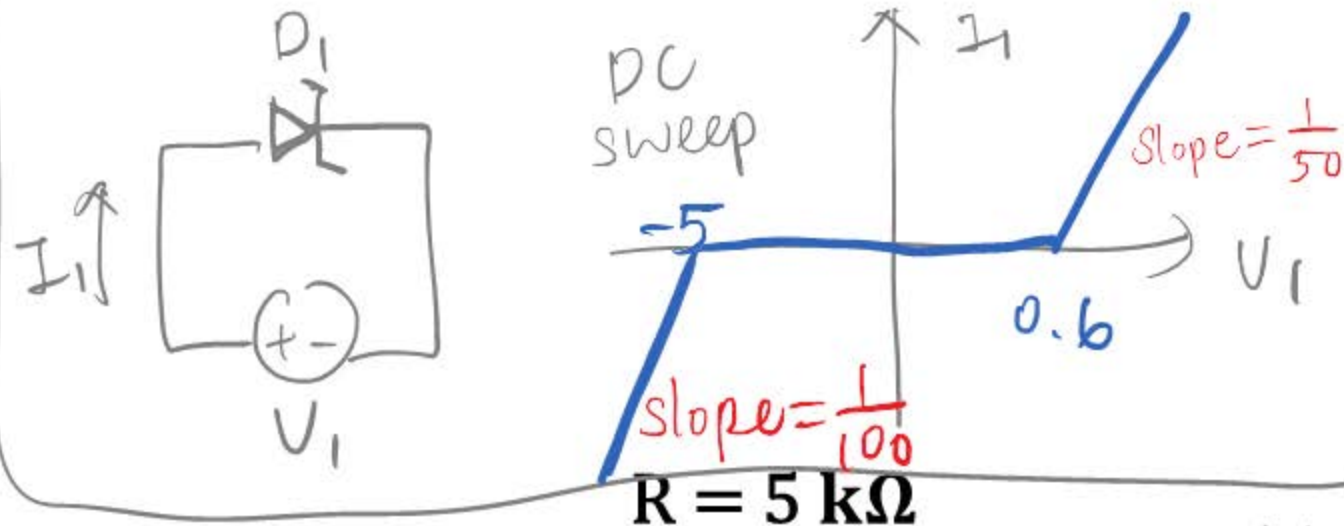


$$R = 5 \text{ k}\Omega$$

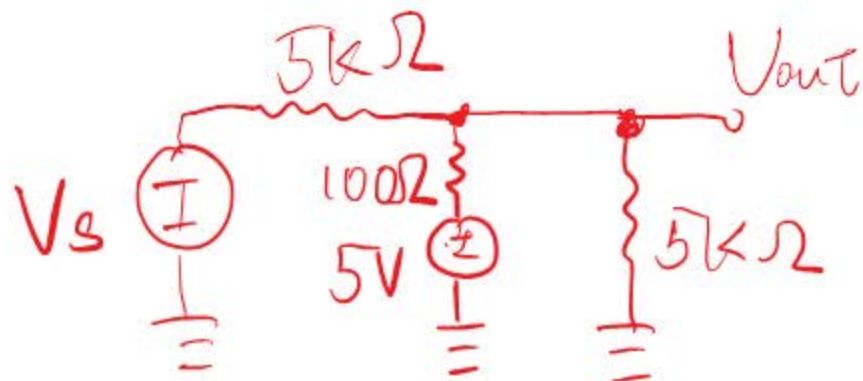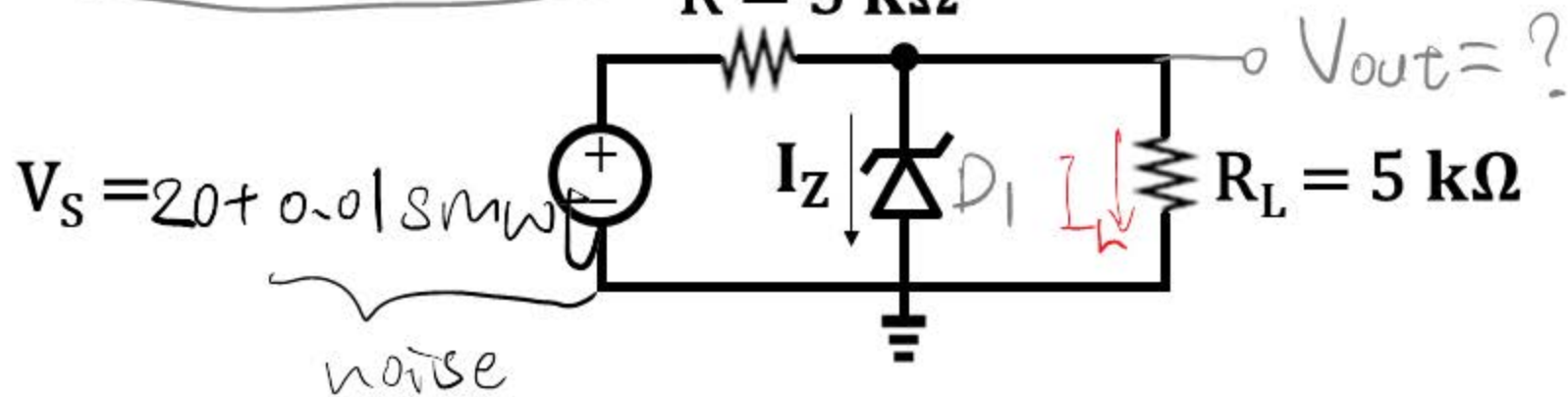


$$\frac{V_s - V_{out}}{5 \text{ k}} = \frac{V_{out}}{5 \text{ k}} + \frac{V_{out} - 5}{100}$$
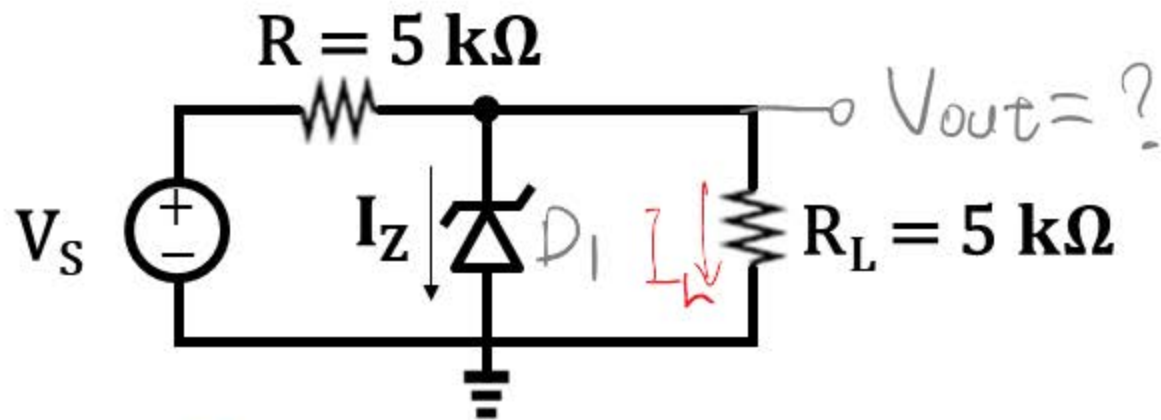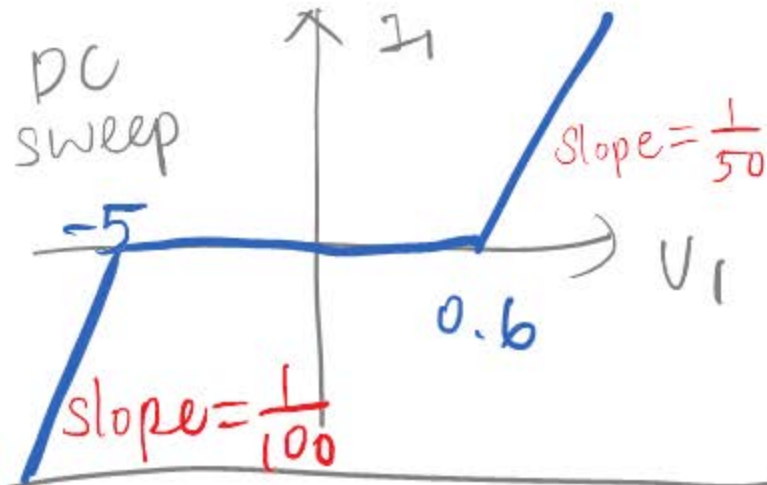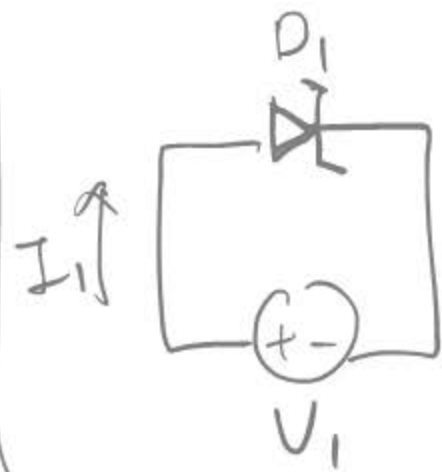
$$V_{out} = \boxed{\text{DC}} + \boxed{\text{AC}}$$




- * We want R_Z to be as small as possible.
- * If R too large, not enough supply current.
- If R too small, not enough voltage regulation.

Line Regulation and Load Regulation

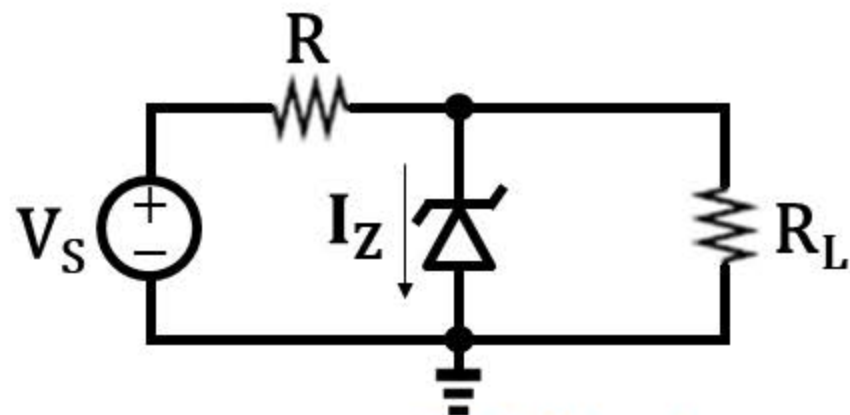

If $I_Z > 0$

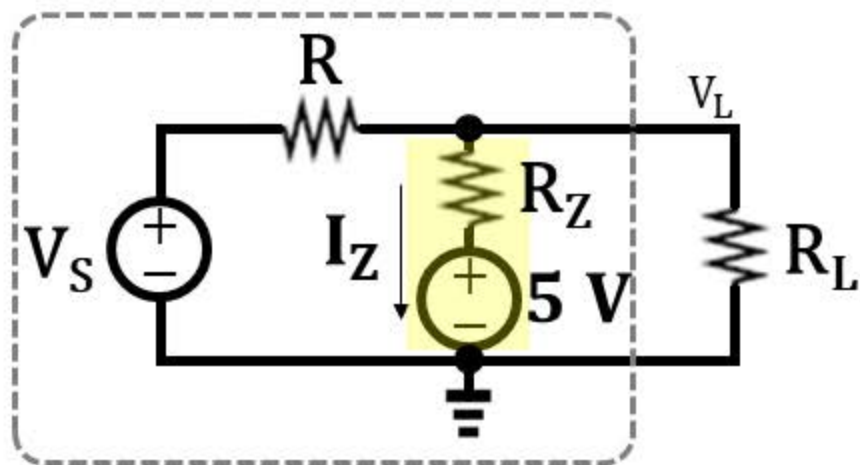

Voltage Regulator

- **Line Regulation:** how sensitive the output voltage (V_L) is to input voltage (V_S) changes, when $R_L = \infty$.


$$\text{Line Regulation} = \frac{dV_L}{dV_S} = \frac{R_Z}{R + R_Z}$$

The smaller, the better


- **Load Regulation:** output impedance of the voltage regulator.

$$\text{Load Regulation} = \frac{dV_L}{dI_L} = R \parallel R_Z$$

The smaller, the better.

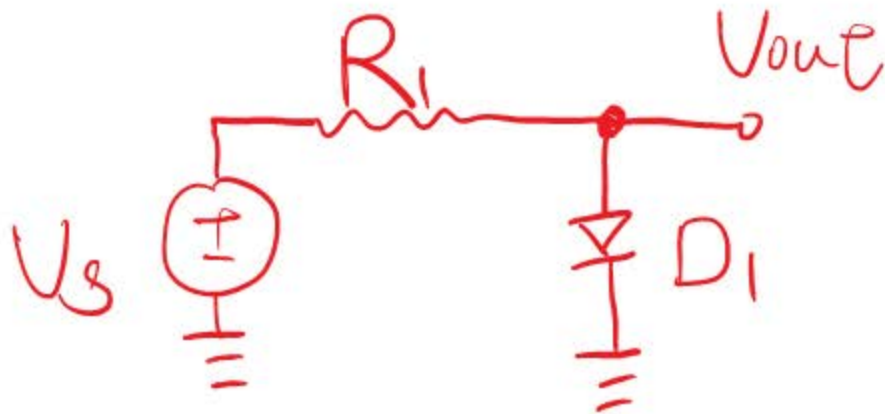

Regulator.

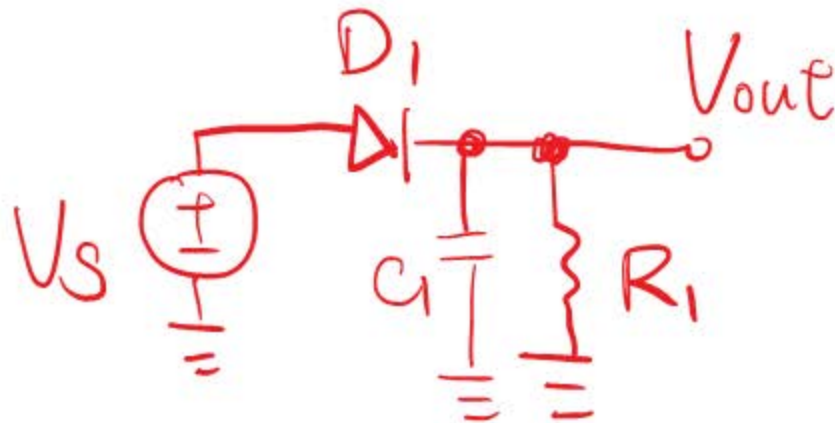


Rectifier.
(AC \rightarrow DC)

220 V
60 Hz

5 V DC




Half-Wave Rectifier with Resistive Load

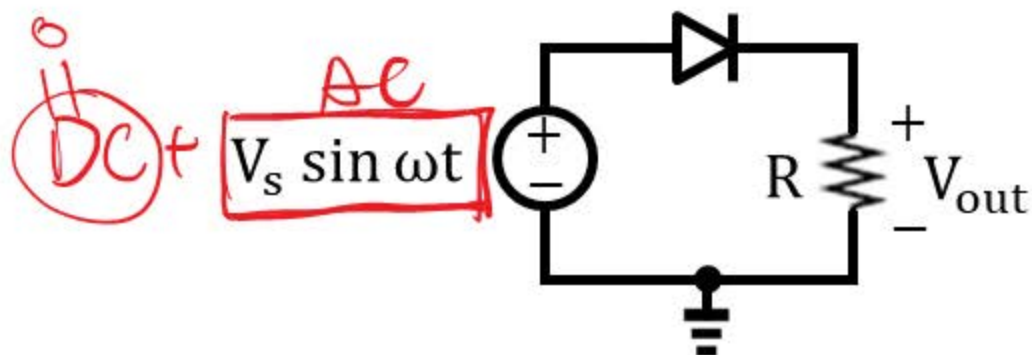



$$V_s = 10 \text{ V}$$

$$\omega = 2\pi f = 2\pi \frac{1}{0.01} = 200\pi \text{ (rad/sec)}$$

V_{out} is not DC.

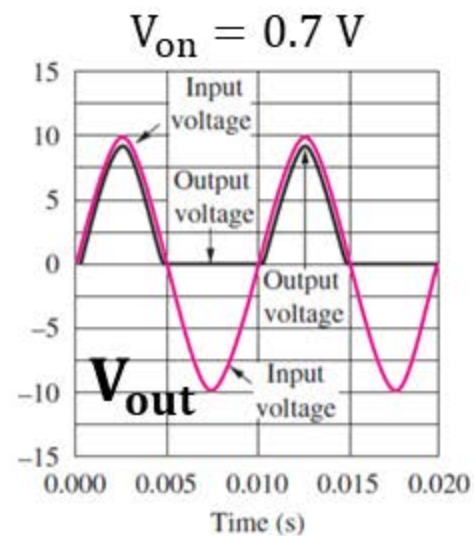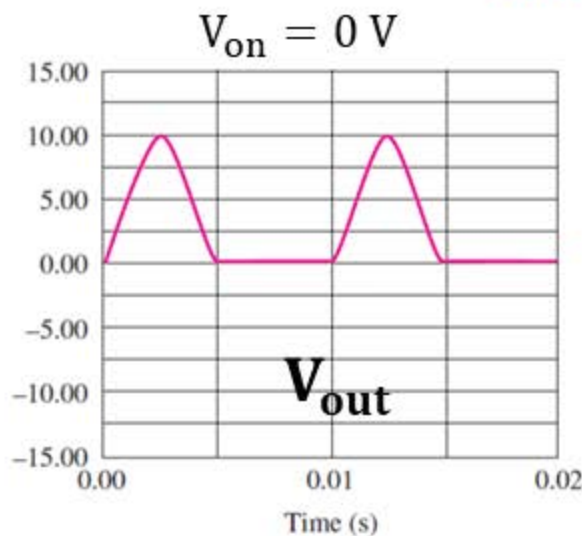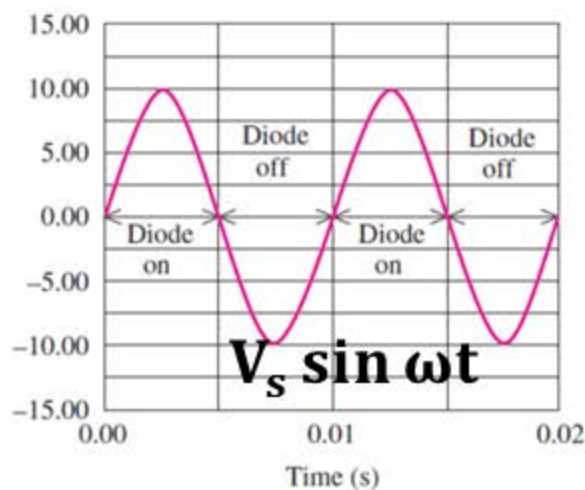


Half-Wave Rectifier with Resistive Load

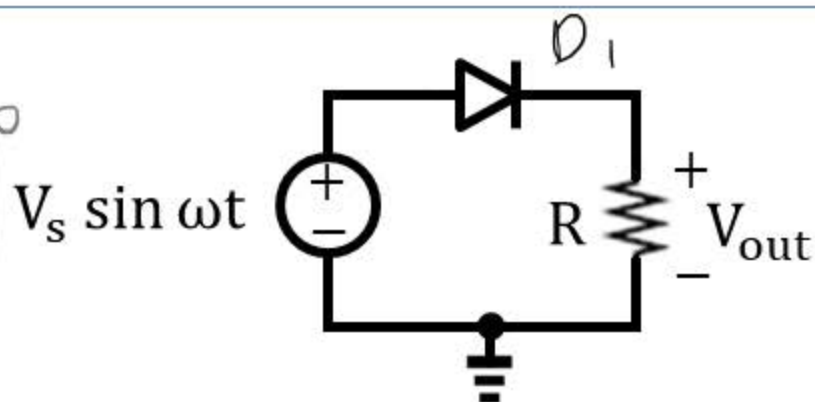
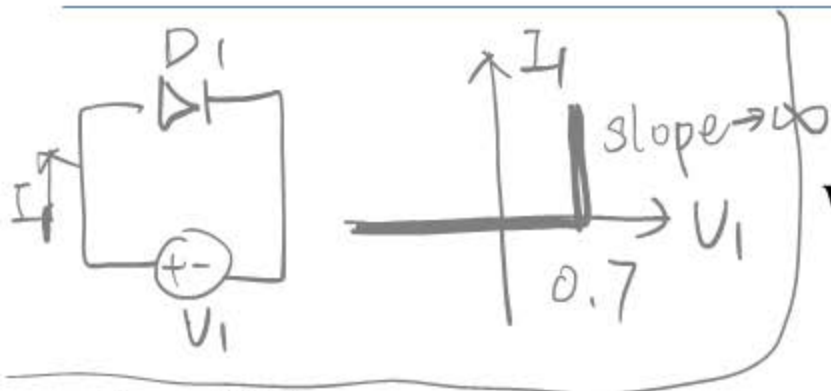


$$V_s = 10 \text{ V}$$
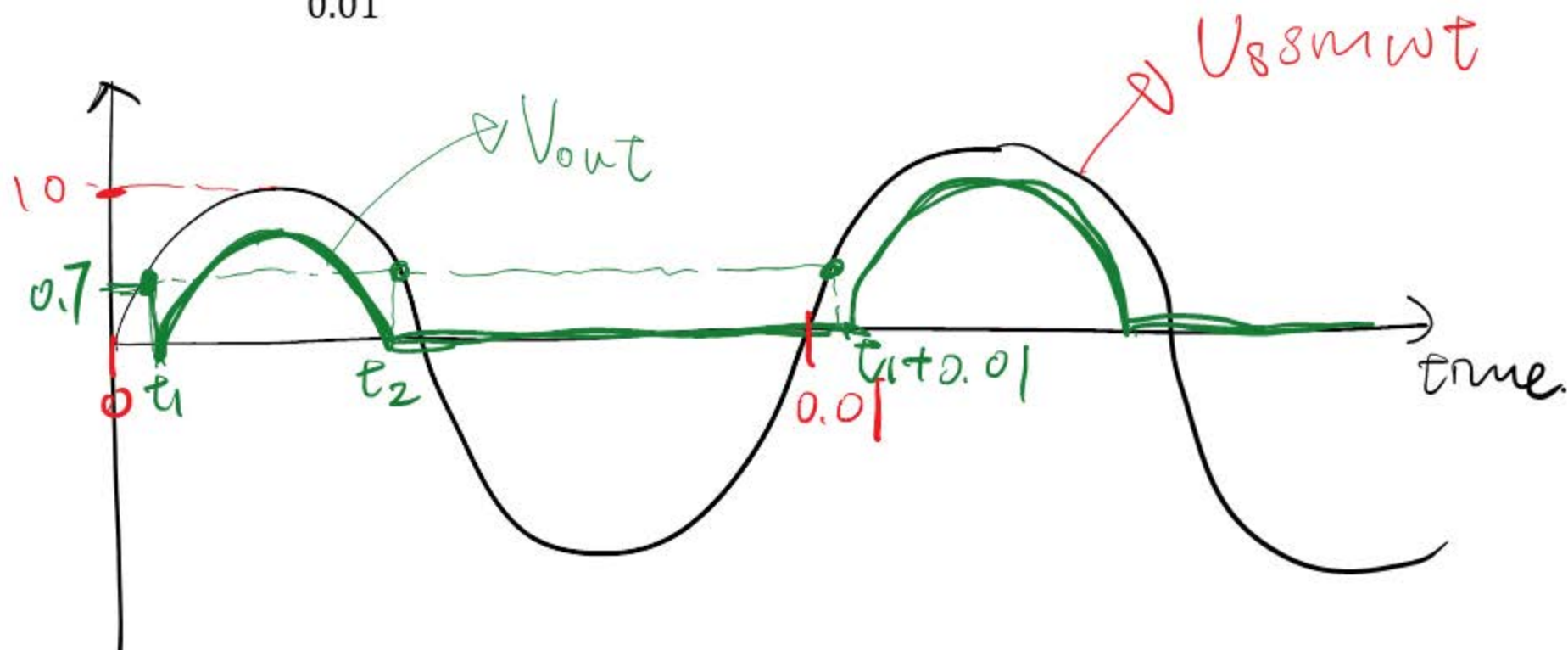
$$\omega = 2\pi f = 2\pi \frac{1}{0.01} = 200\pi \text{ (rad/sec)}$$





Half-Wave Rectifier with Resistive Load

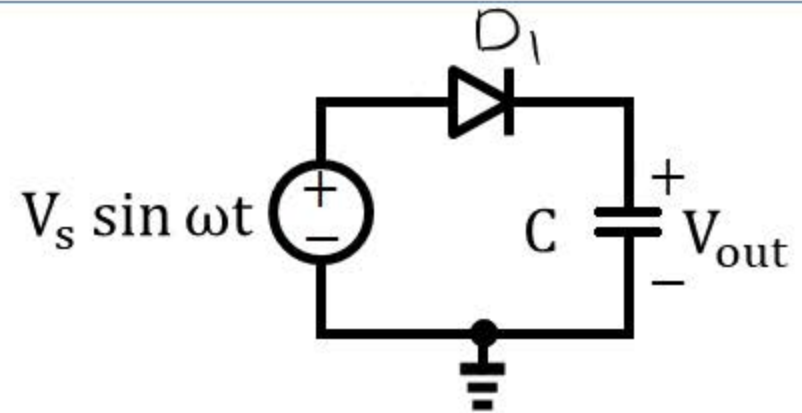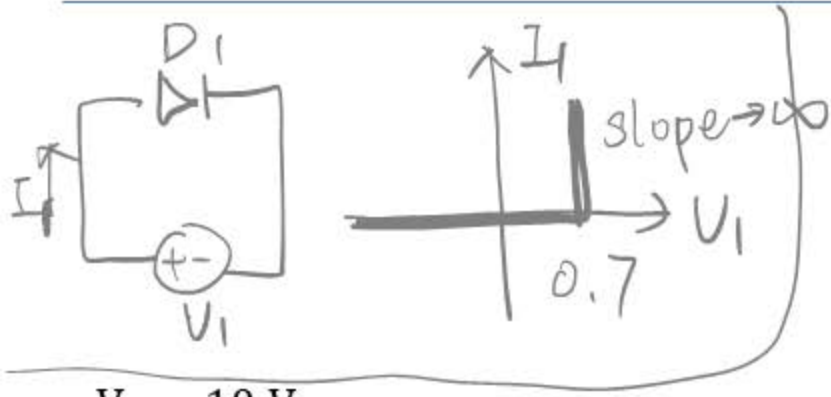


$$V_s = 10 \text{ V}$$
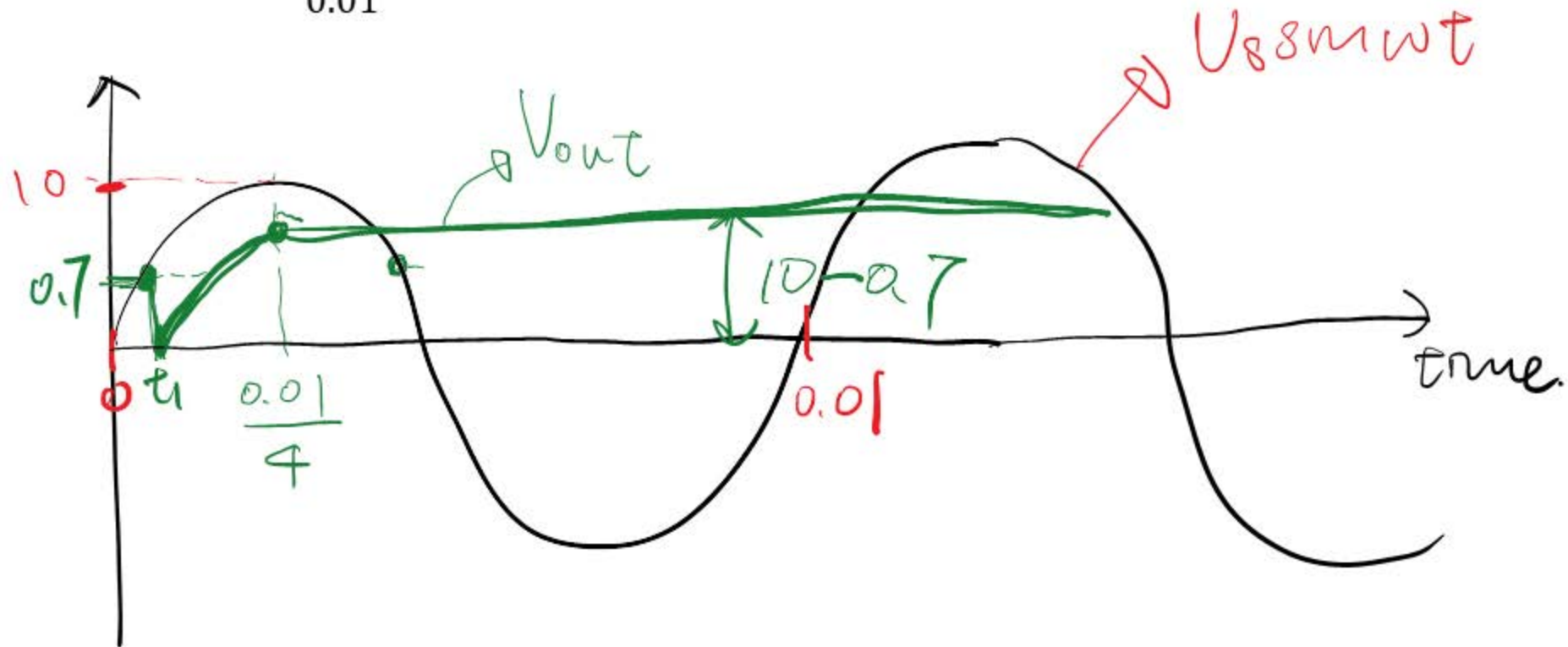
$$\omega = 2\pi f = 2\pi \frac{1}{0.01} = 200\pi \text{ (rad/sec)}$$





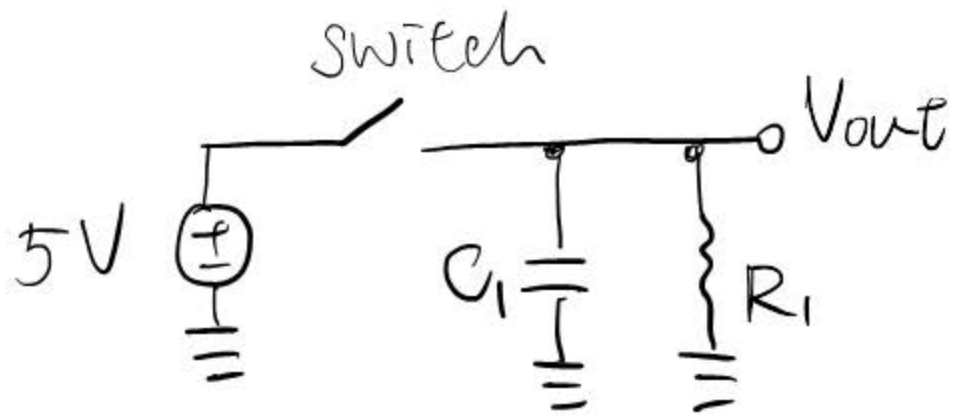

The switch is closed until t_1 .

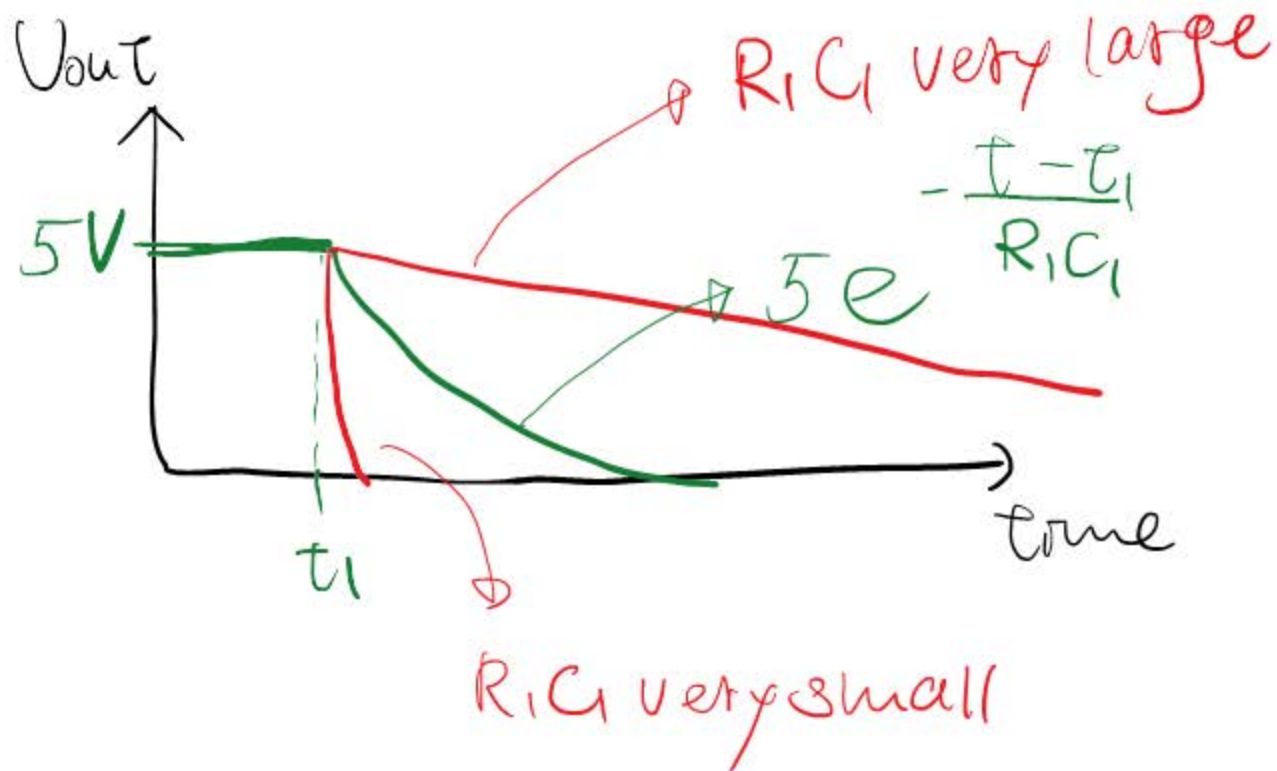

Half-Wave Rectifier with Resistive Load

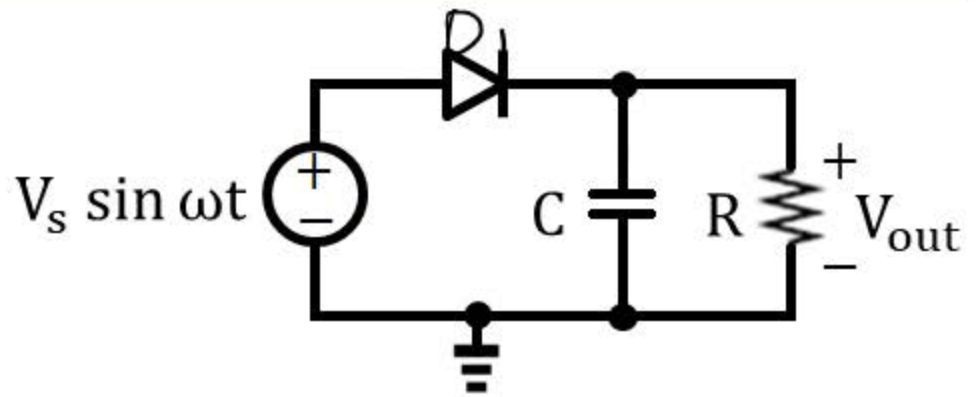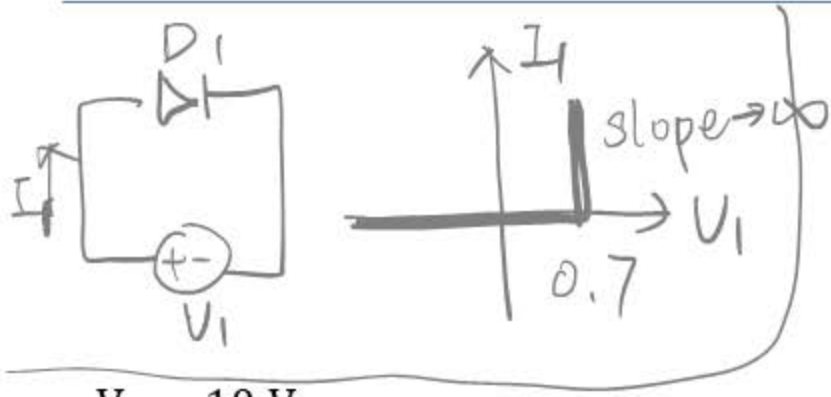

$$V_s = 10 \text{ V}$$

$$\omega = 2\pi f = 2\pi \frac{1}{0.01} = 200\pi \text{ (rad/sec)}$$

