
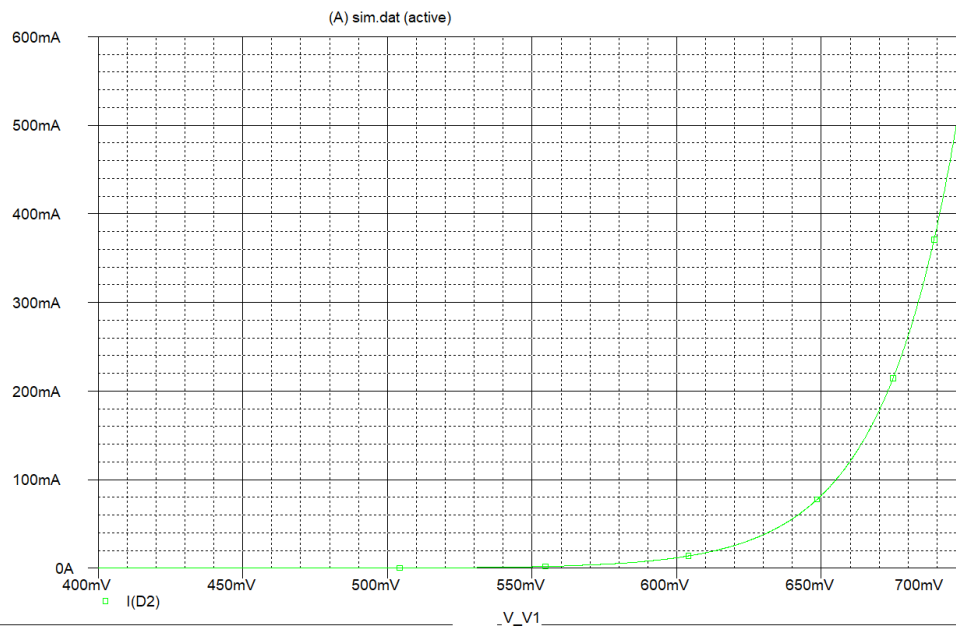


(a).

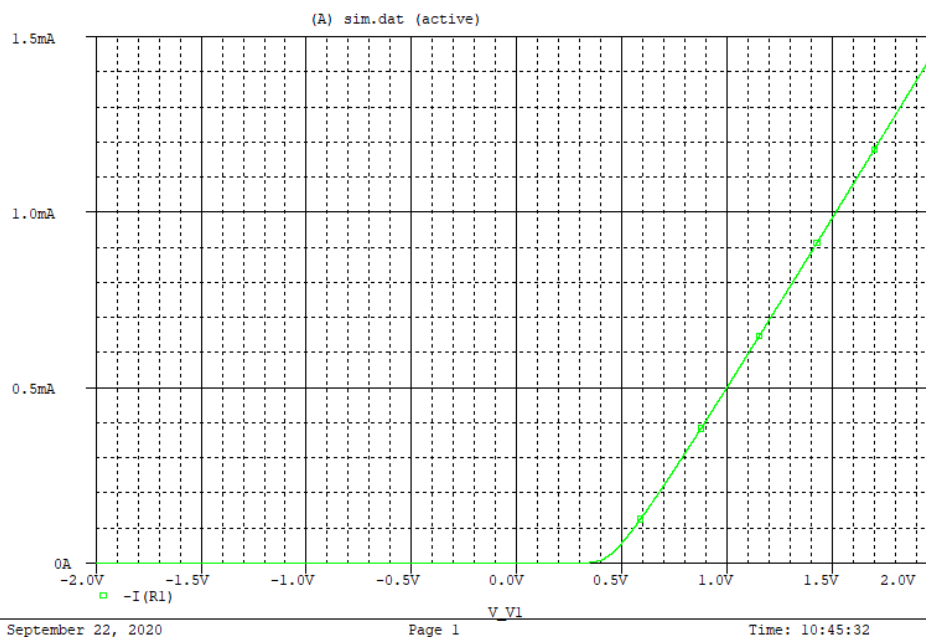


From the plot, we can get that  $V_{on} = 0.53V$

(b).



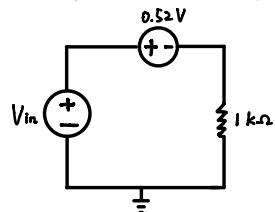We can consider the circuit as follows when the diode is turned on.




$$V_D = V_{on} = 0.53V$$

$$I_D = \frac{V_{in} - V_D}{R} = \frac{V_{in} - 0.53}{1000} = \frac{1}{1000} V_{in} - 5.3 \times 10^{-4} \quad (A)$$


Therefore, it is linear increase.

(c).

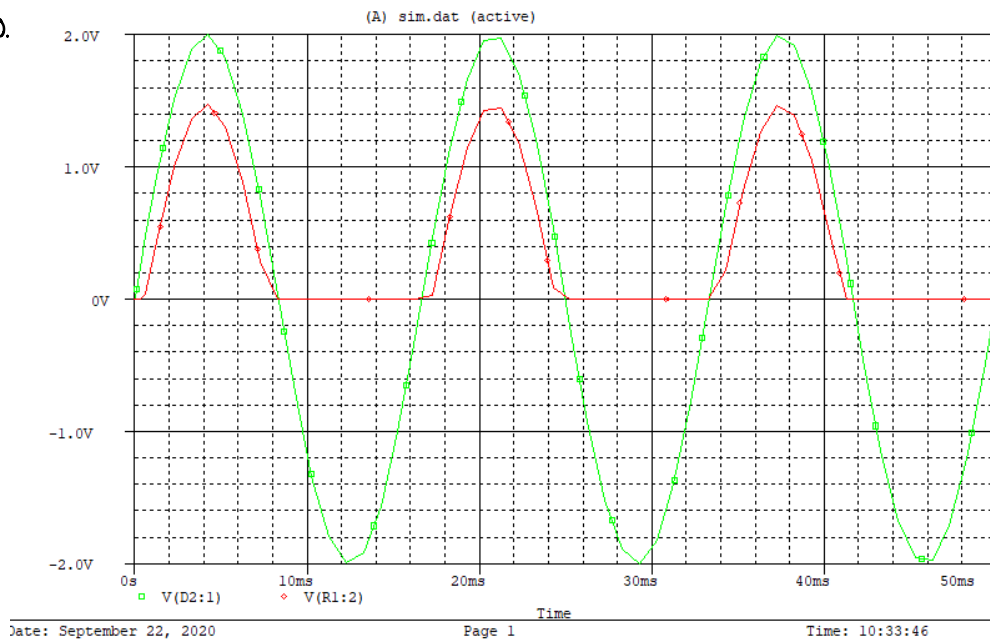

When  $V_{in} < V_{on}$ , there is almost no current flowing through the circuit, then we can regard  $V_{out} = 0$ .  
 When  $V_{in} > V_{on}$ , the voltage on the diode is  $V_{on}$ , then we can know that  $V_{out} = V_{in} - V_{on}$

(d).

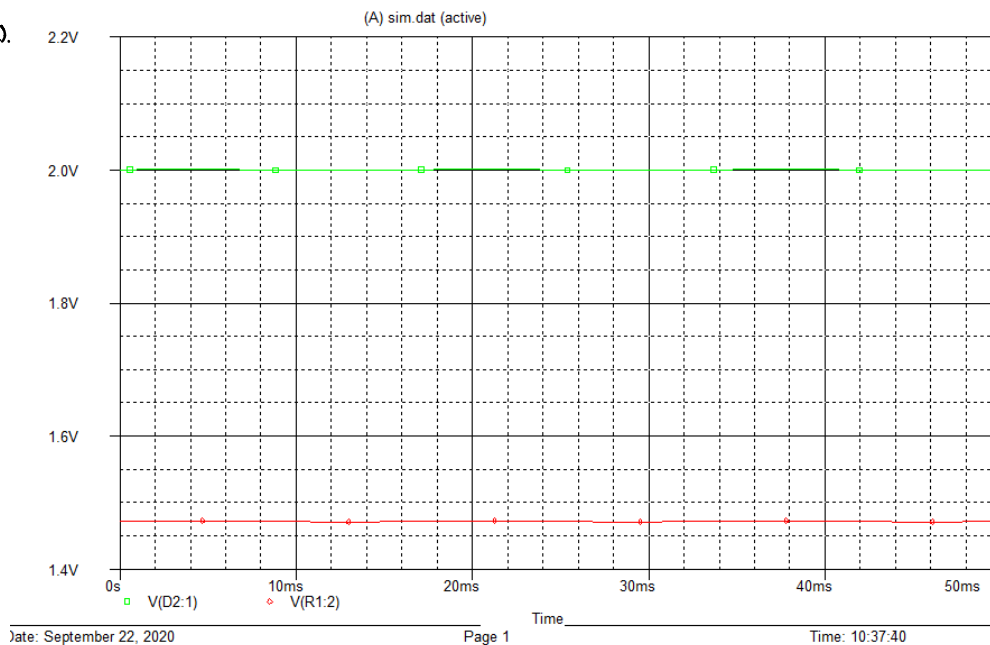

In this case  $V_{in}$  is always larger than  $V_{on}$ , then we have  $V_{out} = V_{in} - V_d = V_{in} - V_{on} = 1.47 + 0.001 \sin(120\pi t)$  (V).  
 Since  $0.001 \ll 2$  and  $0.001 \ll 1.47$ , both  $V_{in}$  and  $V_{out}$  looks like a straight line.