

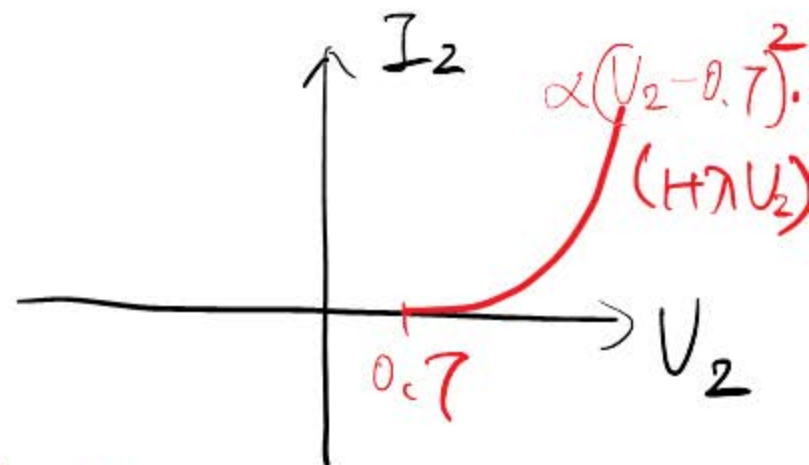
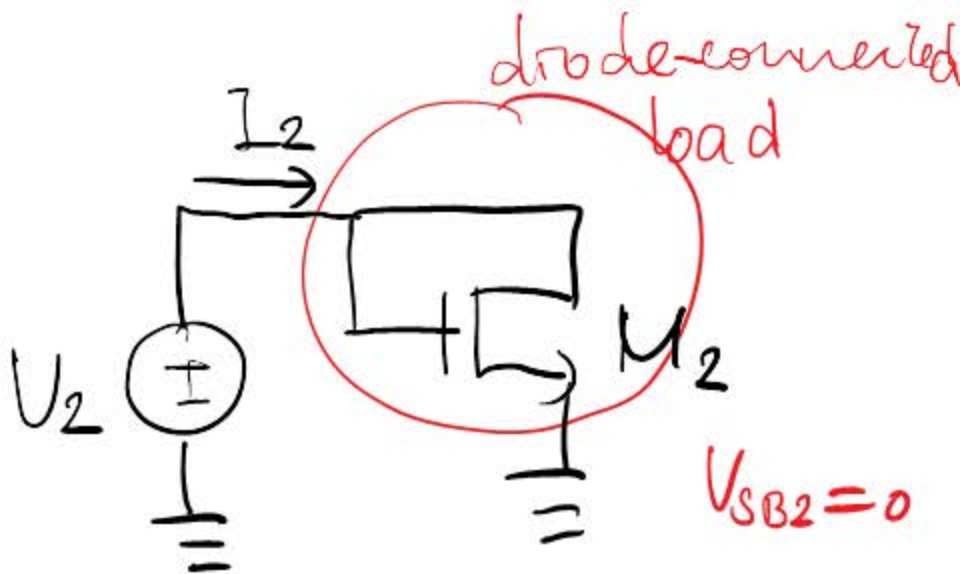
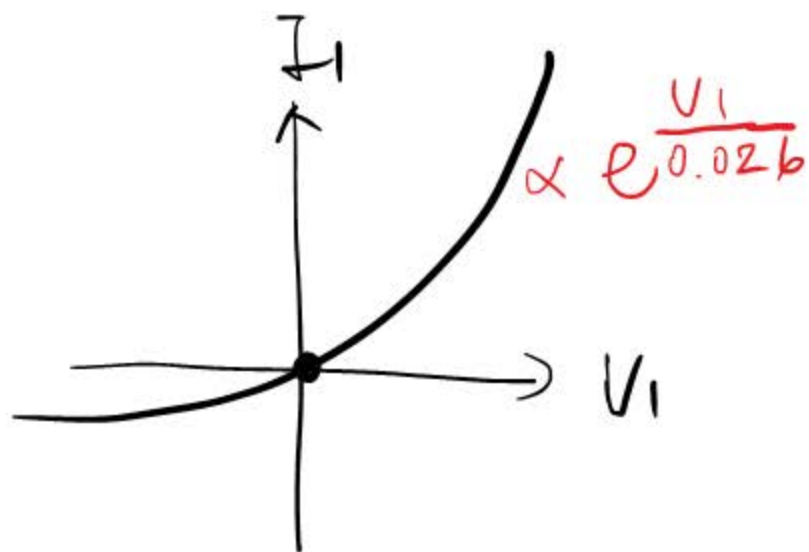


Common-Source with Diode-Connected Load

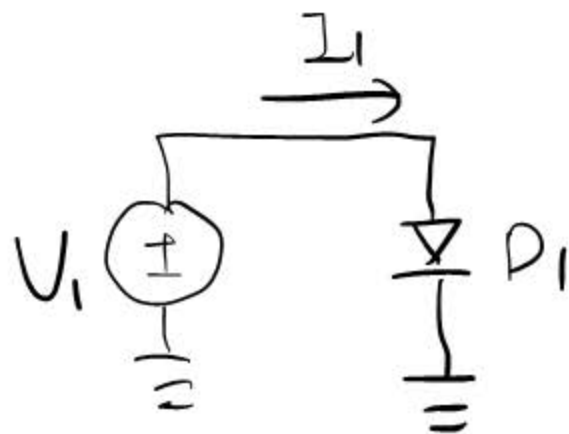


M_2 always in sat.
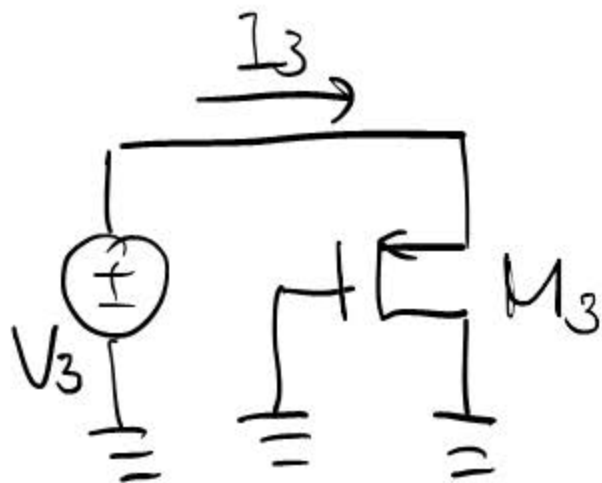
$$I_2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_2 - 0.7)^2 (1 + \lambda V_2)$$




M_3 always in Sat.

$$V_{BS3} = V_{DD} - V_3 > 0, |V_{TH3}| > 0.8$$

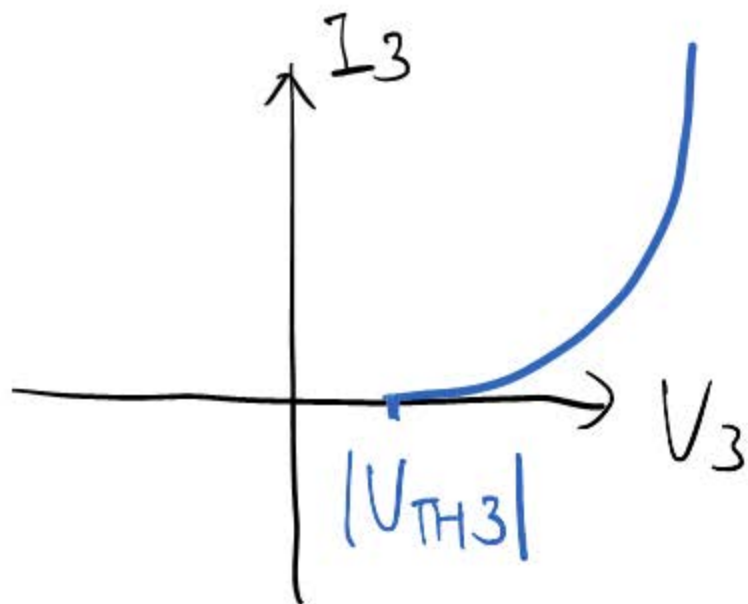

$$I_3 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right)_3 \cdot$$

$$(V_3 - |V_{TH3}|)^2 (1 + \lambda V_3)$$

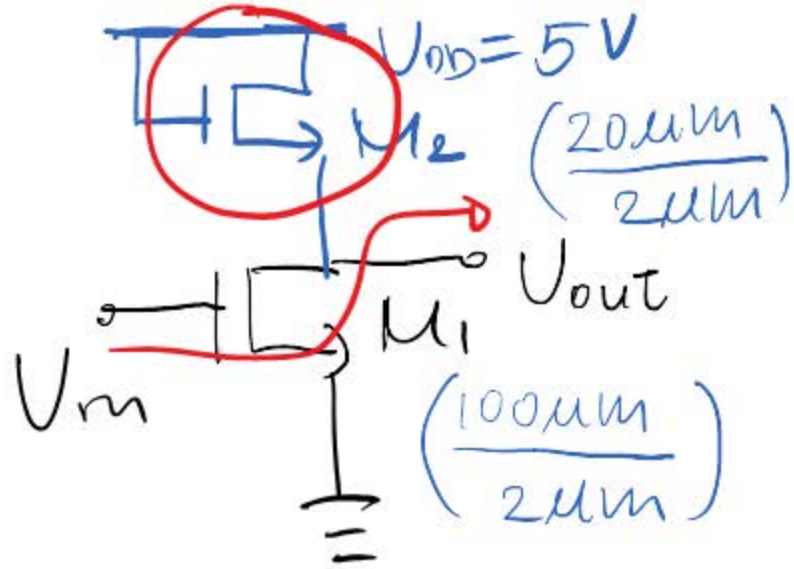

1° Find out $V_{out} = ?$
 Then we make sure
 M_1 and M_2 in sat.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{100\mu\text{m}}{2\mu\text{m} - 2LD} \right) (0.8 - 0.7)^2 \cdot (1 + \lambda V_{out})$$

$$\lambda \neq 0, r \neq 0$$

$$V_m = 0.8 + 0.0018 \sin(2\pi 100t)$$

$$V_{out} = V_{outT} + V_{outc} = ?$$


$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{20\mu\text{m}}{2\mu\text{m} - 2LD} \right) \cdot$$

$$(5 - V_{out} - V_{th1})^2 \cdot$$


$$[1 + \lambda(5 - V_{out})]$$

$$V_{SB1} = 0 \Rightarrow V_{th1} = 0.7$$
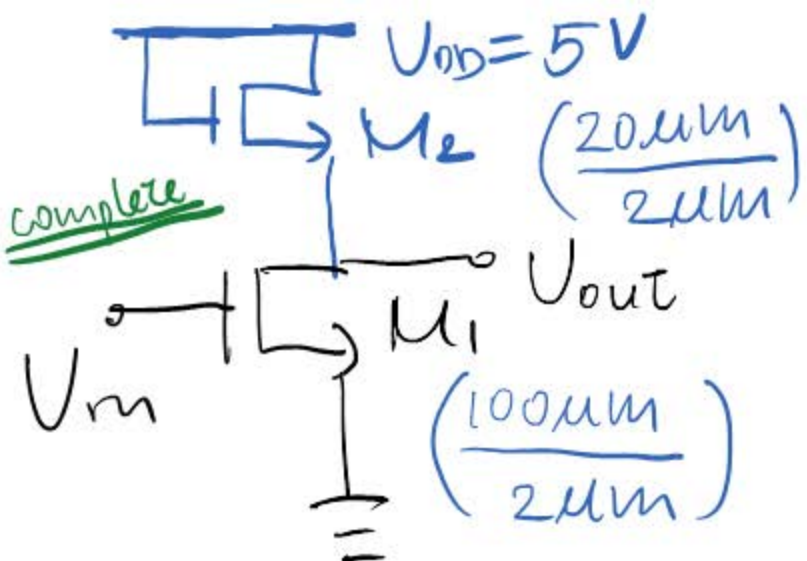
$$V_{SB2} = V_{out} \Rightarrow V_{th2} > 0.7$$






2° Find out $V_{out} = ?$

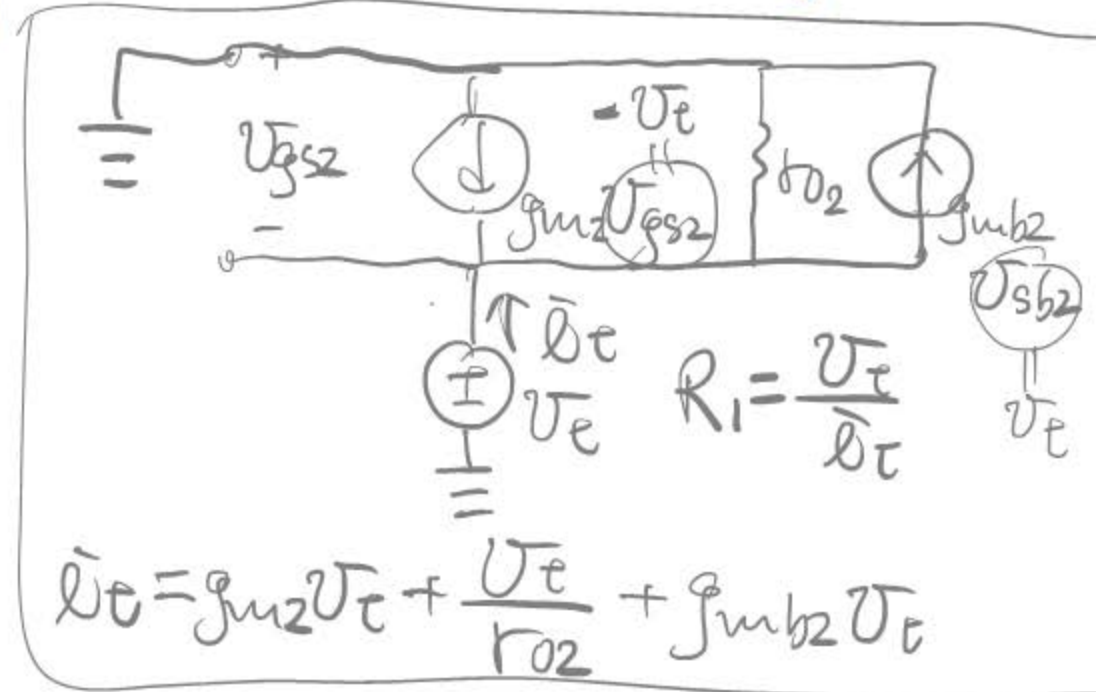

$$\tilde{V}_t = g_{m2} V_t + \frac{V_t}{r_{o2}} + g_{mb2} V_t$$

small-signal

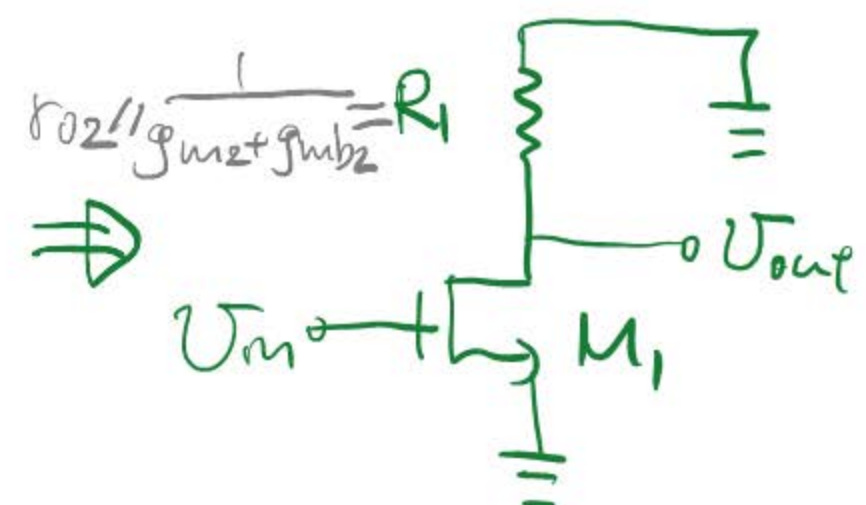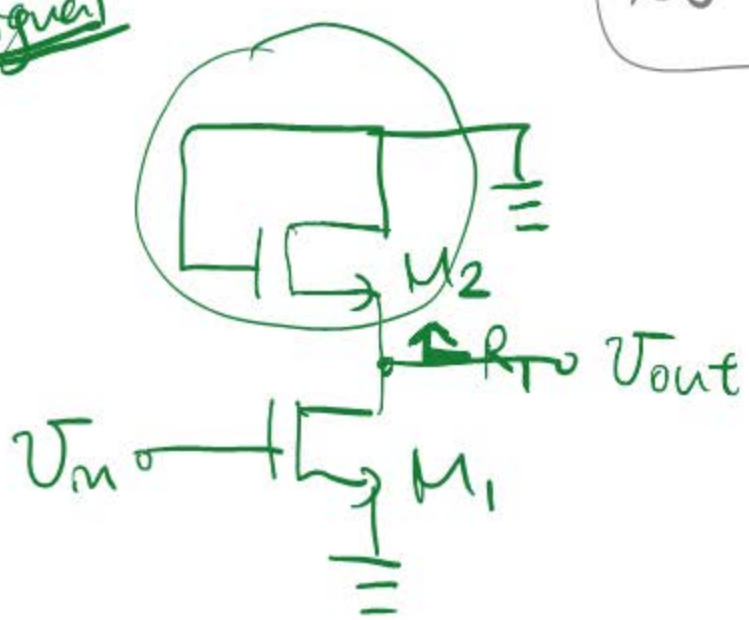

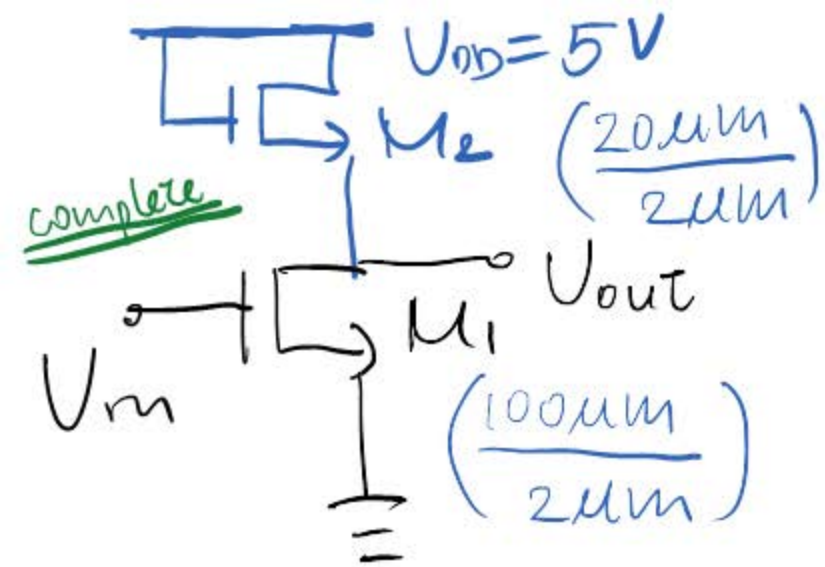



2 Find out $V_{out} = ?$


$$V_{out} = -g_{m1} V_{in} (r_{o1} \parallel R_1)$$

$$= -g_{m1} V_{in} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$$

$$\cong -g_{m1} V_{in} \frac{1}{g_{m2} + g_{mb2}} \cong -V_{in} \frac{g_{m1}}{g_{m2}}$$

small-signal

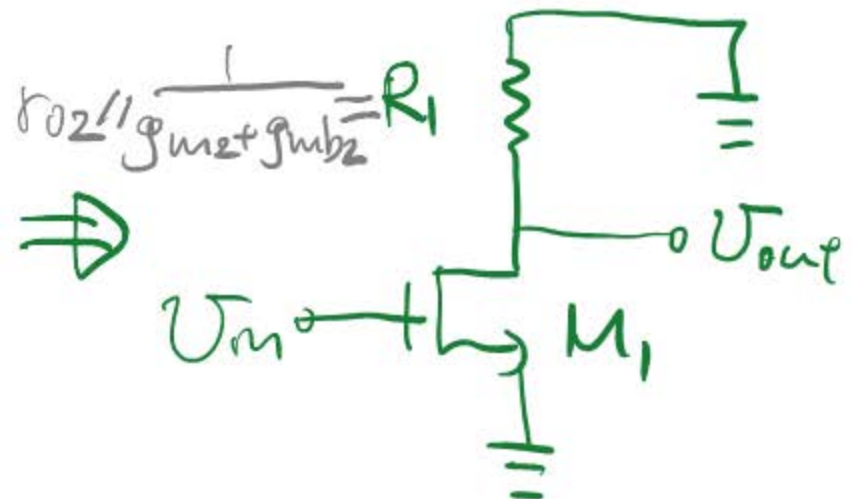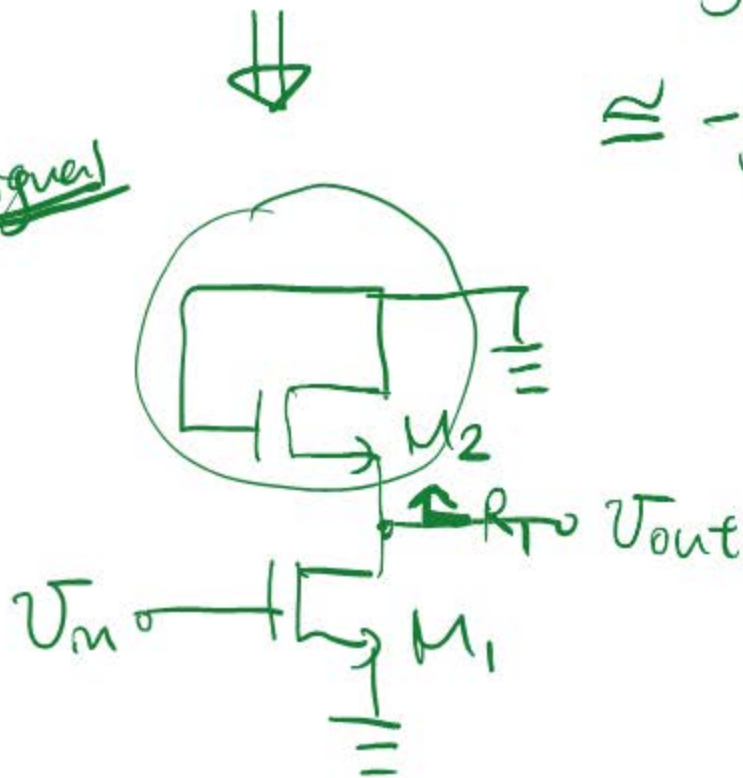

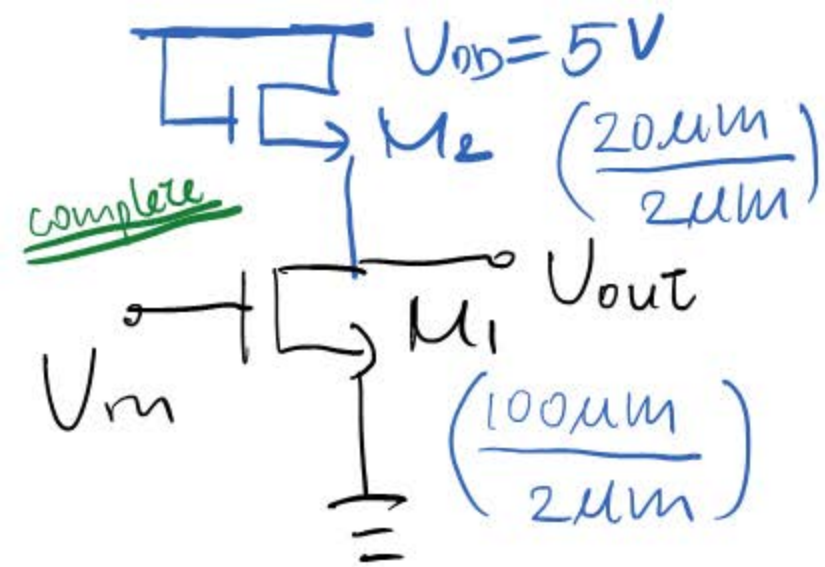


2 Find out $V_{out} = ?$

$$V_{out} = -g_{m1} V_{in} (r_{o1} \parallel R_1)$$

$$= -g_{m1} V_{in} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$$



small-signal

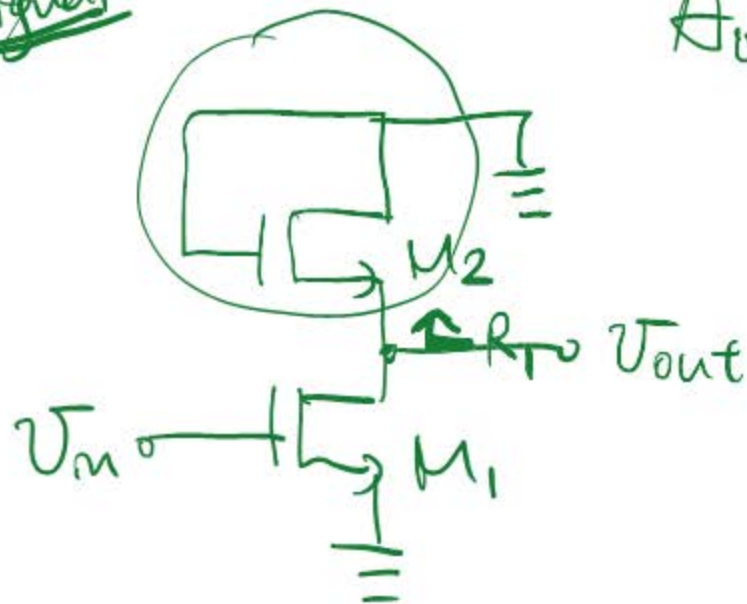


$$A_v = \frac{V_{out}}{V_{in}}$$

$$= -g_{m1} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$$

(if $\lambda = 0$, $r \neq 0$)

$$= -\frac{g_{m1}}{g_{m2} + g_{m2}\eta} = -\frac{g_{m1}}{g_{m2}(1+\eta)}$$

small-signal

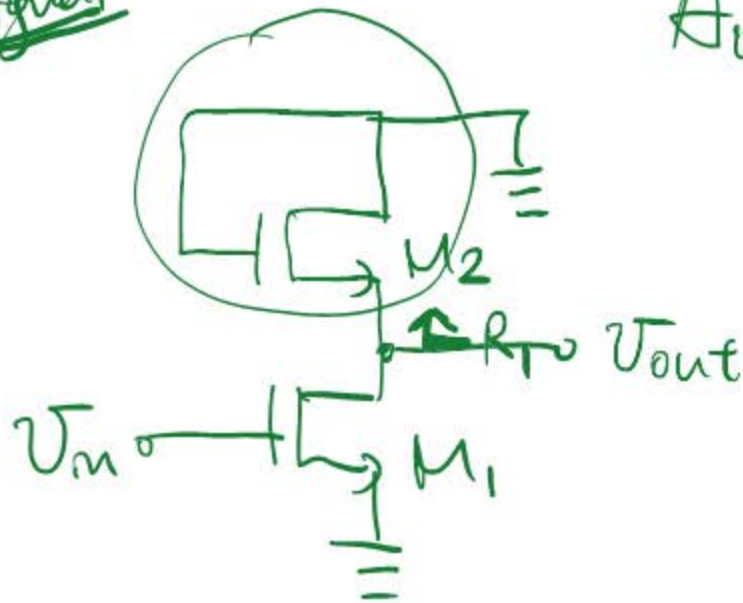

$$A_v = \frac{V_{out}}{V_{in}}$$

$$= g_{m1} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$$

(if $\lambda = 0$, $r \neq 0$)

$$= - \frac{g_{m1}}{g_{m2} + g_{m2}\eta} = - \frac{g_{m1}}{g_{m2}} \left(\frac{1}{1+\eta} \right)$$

$$= - \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L} \right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L} \right)_2 I_{D2}}} \left(\frac{1}{1+\eta} \right)$$


$$= - \sqrt{\frac{\left(\frac{W}{L} \right)_1}{\left(\frac{W}{L} \right)_2}} \left(\frac{1}{1+\eta} \right)$$

Common-Source with Diode-Connected Load

9

DC Analysis

$$\lambda = 0 \quad \gamma \neq 0$$

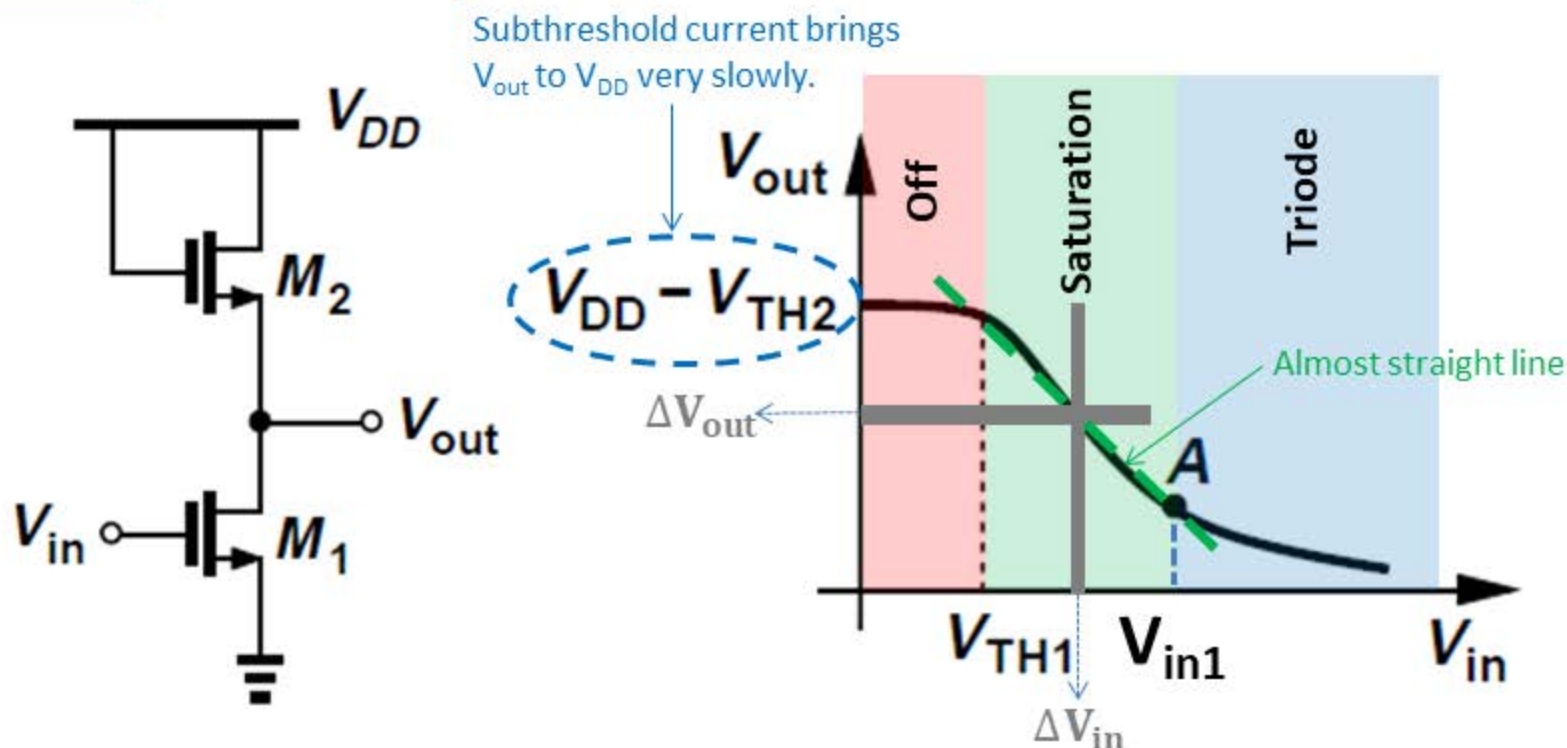

$$V_{out} = V_{in1} - V_{TH1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in1} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 [V_{DD} - (V_{in1} - V_{TH1}) - V_{TH2}]^2$$

- V_{gs} increases by $\Delta V_{in} \rightarrow I_d$ increases by $\Delta V_{in} \cdot g_m \rightarrow V_{out}$ decreases

Common-Source with Diode-Connected Load

10

DC Analysis

$$\lambda = 0 \quad \gamma \neq 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$ in Saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 [V_{DD} - V_{out} - V_{TH2}]^2$$

$$\sqrt{\left(\frac{W}{L} \right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L} \right)_2} (V_{DD} - V_{out} - V_{TH2})$$

$$\sqrt{\left(\frac{W}{L} \right)_1} = \sqrt{\left(\frac{W}{L} \right)_2} \left(-\frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH2}}{\partial V_{in}} \right)$$

$$V_{out} = V_{SD2}$$

$$\sqrt{\left(\frac{W}{L} \right)_1} = \sqrt{\left(\frac{W}{L} \right)_2} \left(-\frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH2}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}} \right)$$
$$= \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$


- η is a function of V_{SB} .
- A_v is almost linear for M_1 in saturation.

Common-Source with Diode-Connected Load


11

Small-signal
Analysis

$\lambda = 0 \quad \gamma \neq 0$

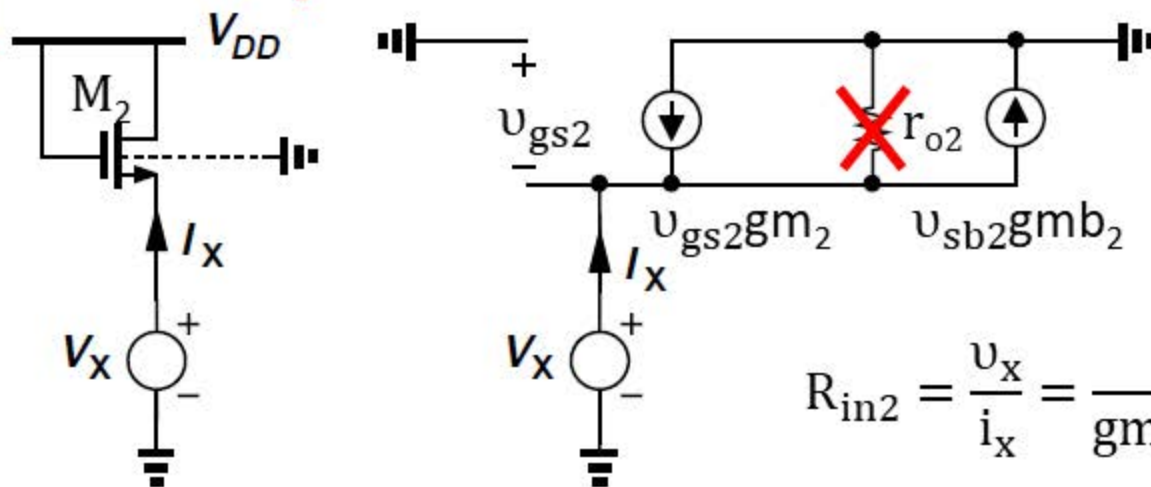
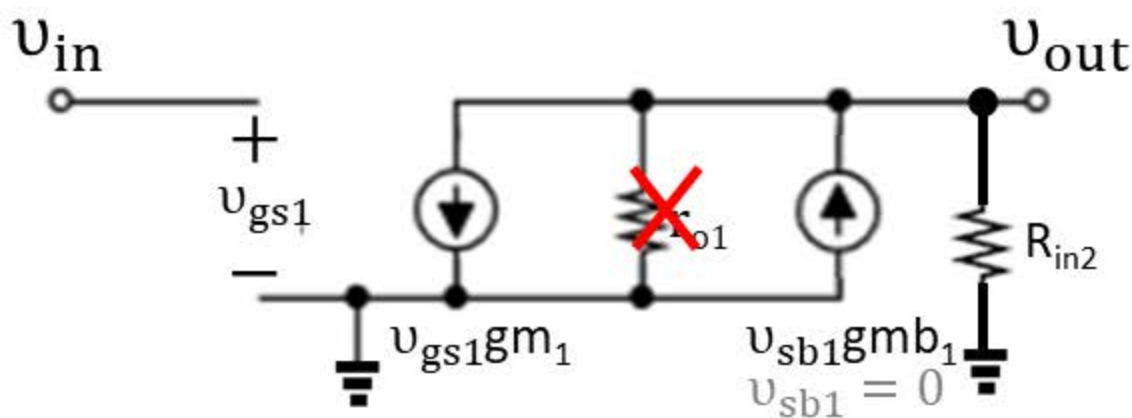
$$R_{in2} = \frac{v_x}{i_x} = \frac{1}{g_{m2} + g_{mb2}}$$



$$A_v = \frac{v_{out}}{v_{in}} = \frac{-g_{m1}}{g_{m2} + g_{mb2}}$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$



- Small-signal analysis leads to the same result as DC analysis.

Common-Source with Diode-Connected Load


12

Small-signal
Analysis

$\lambda \neq 0$ $\gamma \neq 0$

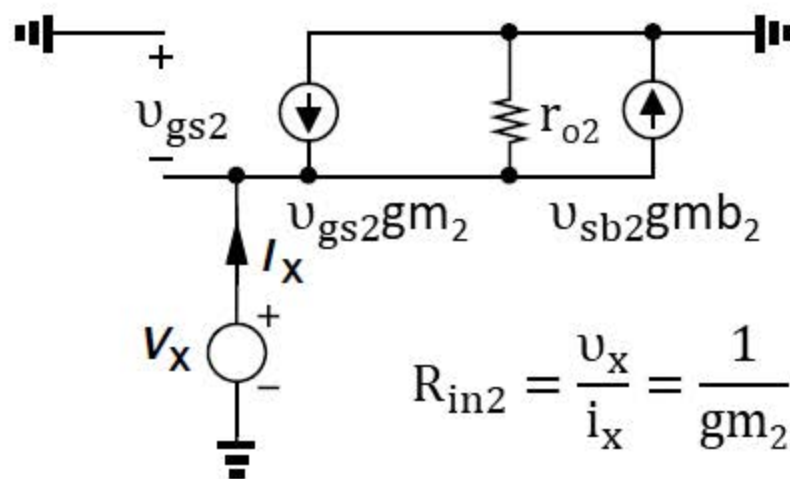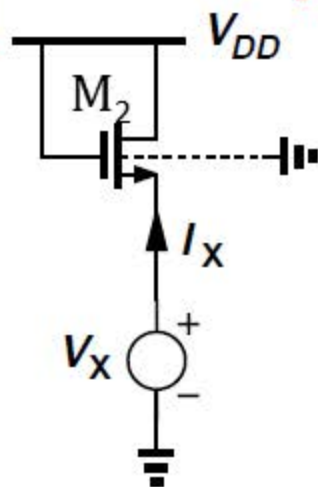
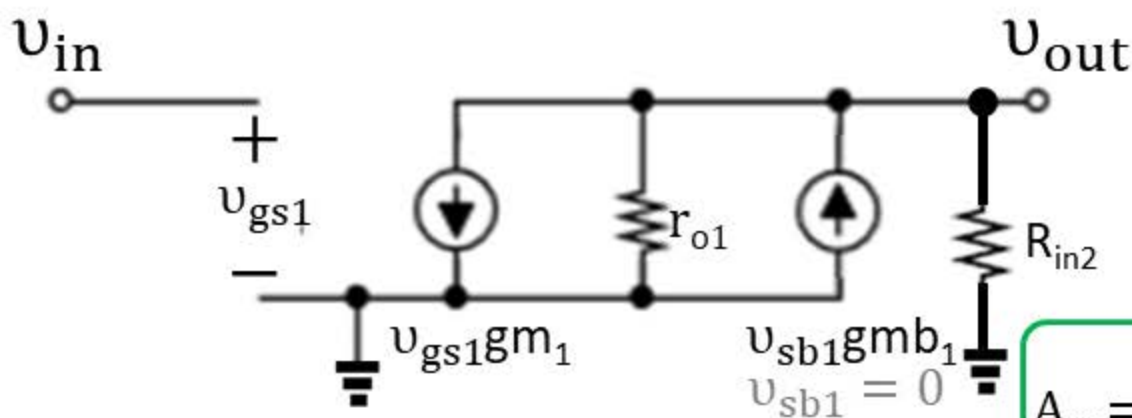
$$R_{in2} = \frac{v_x}{i_x} = \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2}$$



$$A_v = \frac{v_{out}}{v_{in}}$$

$$= -g_{m1} \left(\frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2} \parallel r_{o1} \right)$$


$r_o \gg 1/g_m$

Common-Source with Diode-Connected Load

13

Small-signal
Analysis


$\lambda \neq 0$ $\gamma \neq 0$

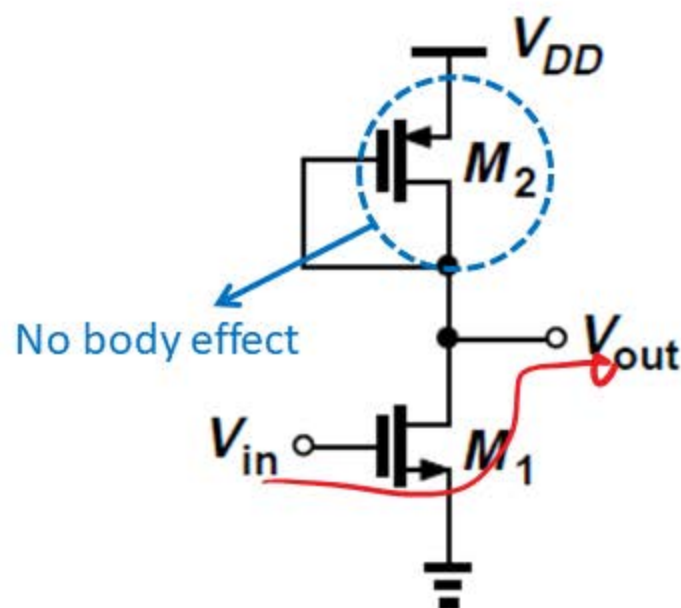


$$\begin{aligned}
 A_v &= \frac{v_{out}}{v_{in}} \\
 &= -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o1} \right) \quad r_o \gg 1/g_m \\
 &\approx -\frac{g_{m1}}{g_{m2}} = \frac{-\cancel{\sqrt{2\mu_n C_{ox}(W/L)_1 I_{D1}}}}{\cancel{\sqrt{2\mu_p C_{ox}(W/L)_2 I_{D2}}}} \\
 &= -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}} \\
 &= -\frac{V_{SG2} - V_{TH2}}{V_{GS1} - V_{TH1}} \quad \frac{2I_{D1}}{V_{GS1} - V_{TH1}} = \frac{2I_{D2}}{V_{SG2} - V_{TH2}}
 \end{aligned}$$

- For $A_v = 10$, $(W/L)_1 \gg (W/L)_2 \rightarrow$ **Disproportionally large transistor**
- For $A_v = 10$, $(V_{SG2} - V_{TH2}) = 10 \times (V_{GS1} - V_{TH1}) \rightarrow$ **Limited output swing**



complete

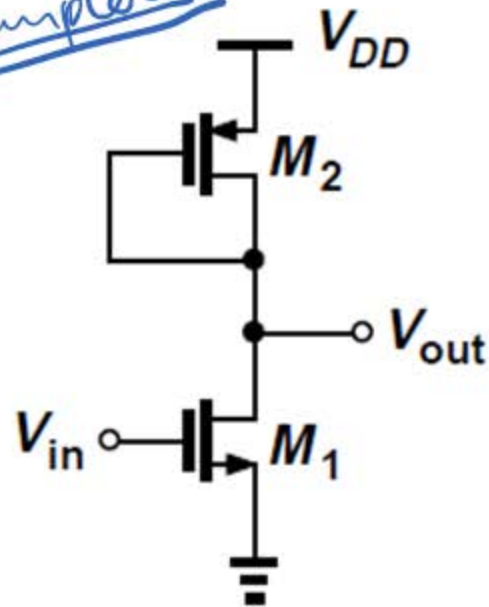

small-signal


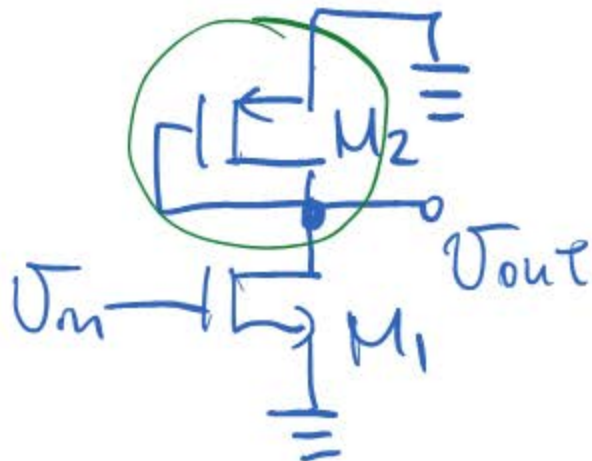


\Rightarrow

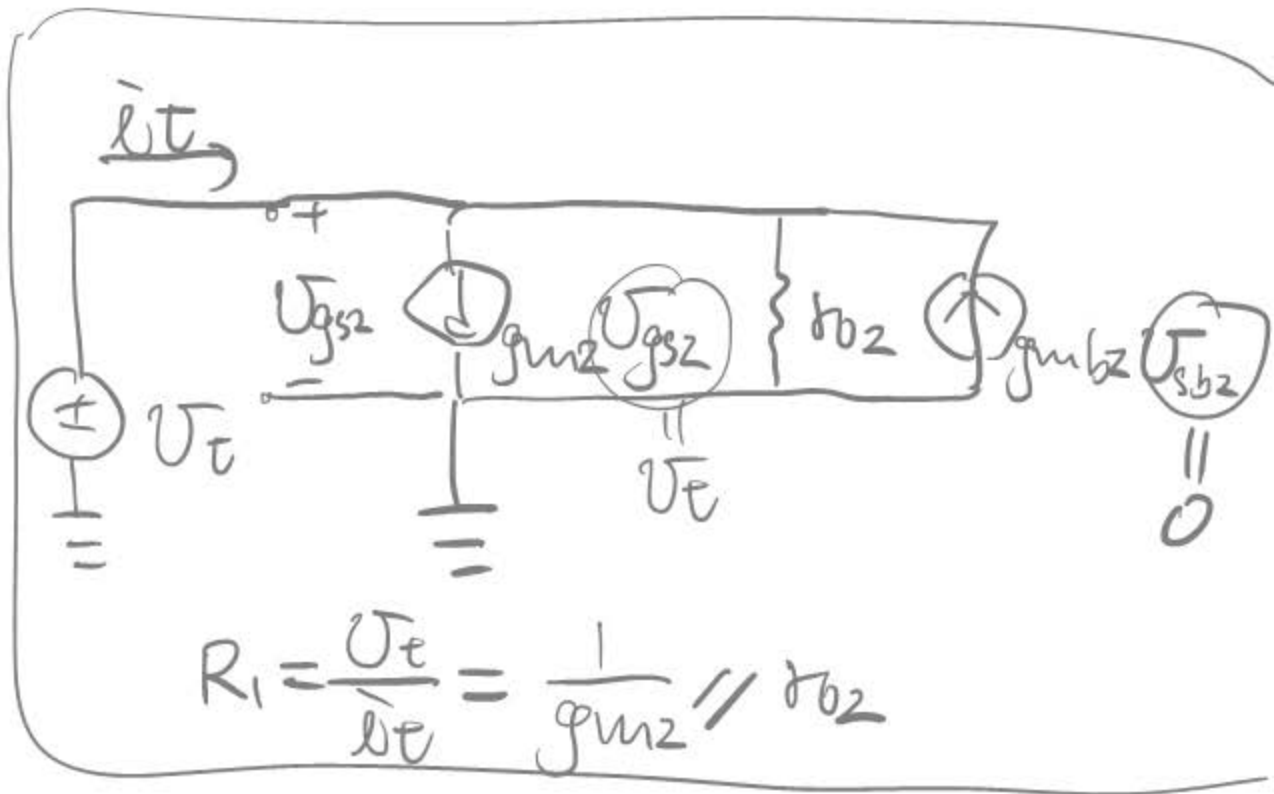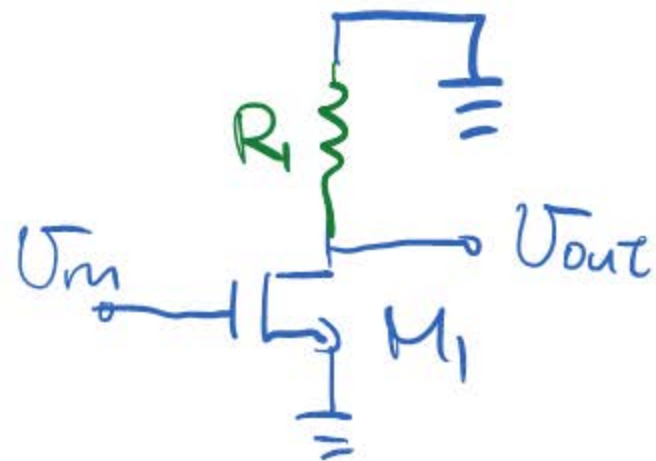

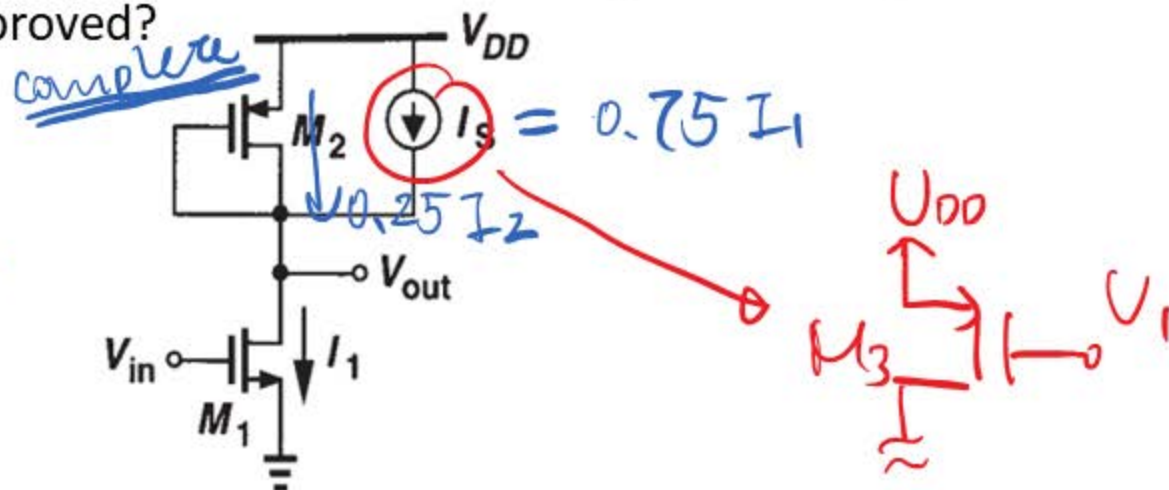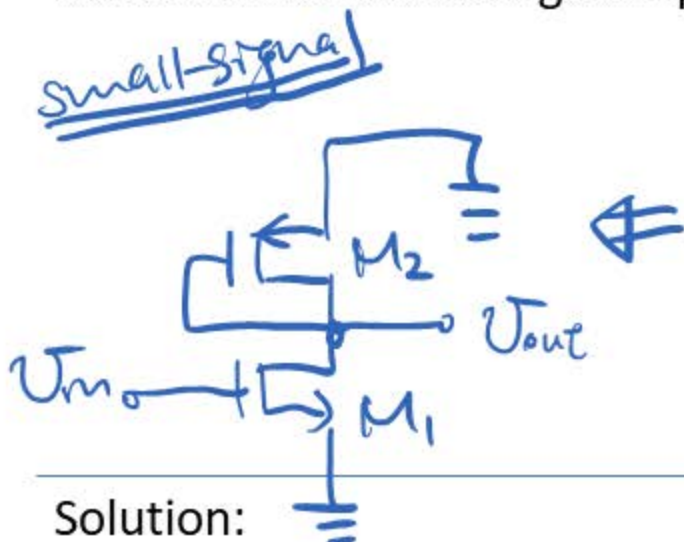Example


$\lambda = 0$
 $r \neq 0$
 M_1 in saturation and $I_S = 0.75 \times I_1$. How do the disadvantages of CS stage with diode-connected load get improved?



Solution:

- Small-signal Analysis ($\lambda = 0$):

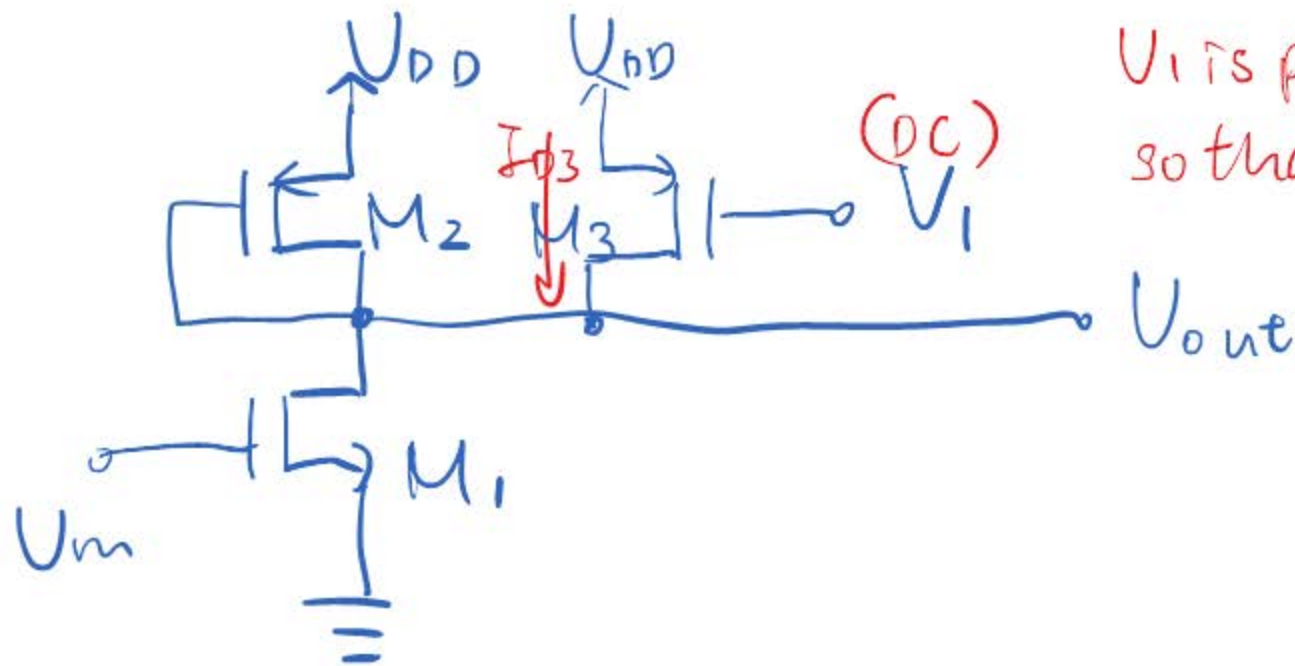
$$A_v = \frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2}} = -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} = -\frac{\sqrt{4\mu_n \left(\frac{W}{L}\right)_1}}{\sqrt{\mu_p \left(\frac{W}{L}\right)_2}} = -\frac{4(V_{SG2} - V_{TH2})}{(V_{GS1} - V_{TH1})}$$



$$I_{D3} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right)_3 (V_{DD} - V_1 - 0.8)^2 [1 + \lambda (V_{DD} - V_{OUT})]$$

↓ if $\lambda = 0$, $\lambda \neq 0$

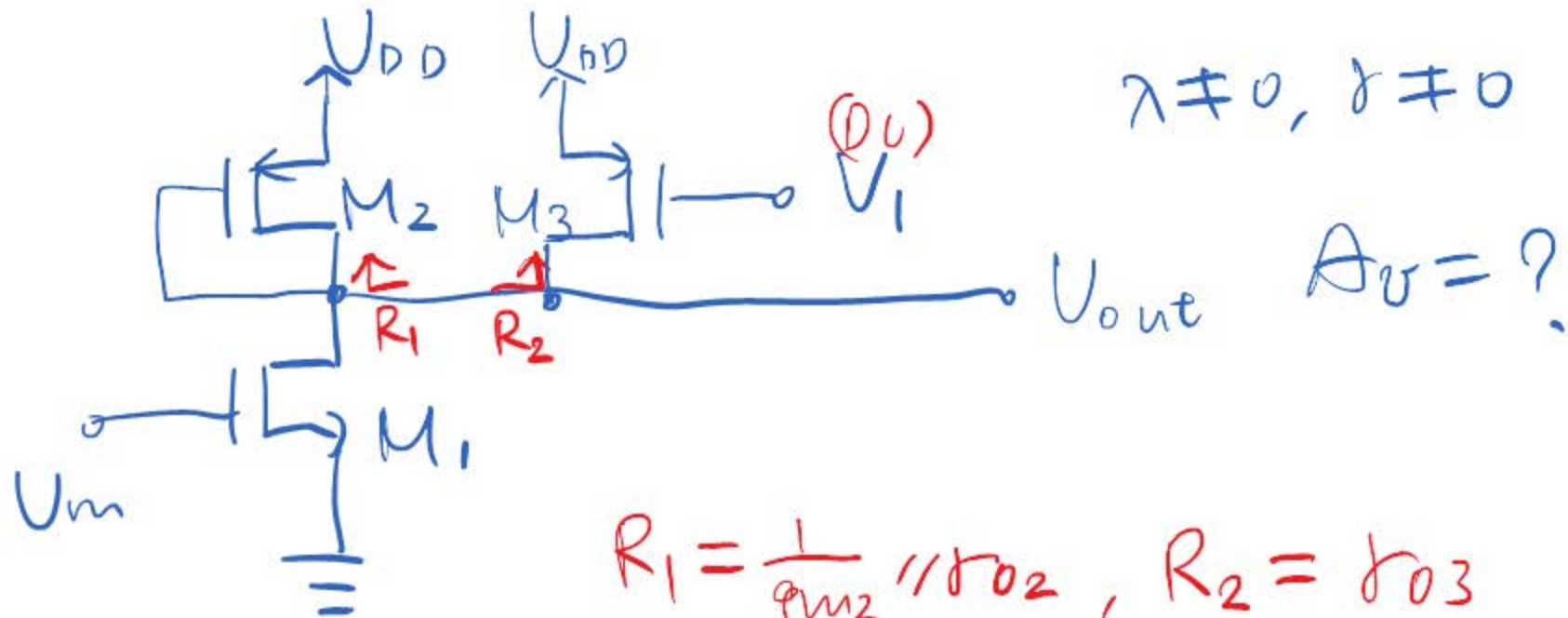
$$I_{D3} = \boxed{\text{constant}} (V_{DD} - 0.8 - V_1)^2 = \boxed{\text{constant}}$$



$$A_V = -g_{m1} (r_{o1} \parallel R_1 \parallel R_2)$$

$$= -g_{m1} \cdot$$
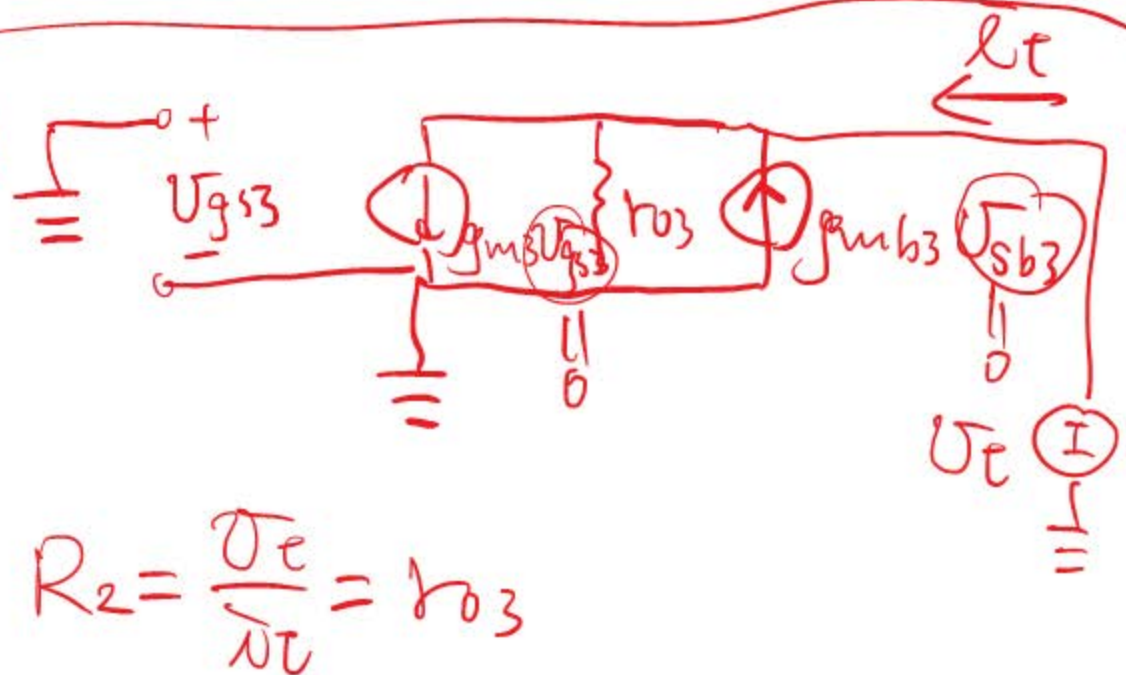
$$(r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o3})$$





Common-Source with Current-Source Load

Common-Source with Current-Source Load


Small-signal
Analysis

$\lambda \neq 0$ $\gamma \neq 0$

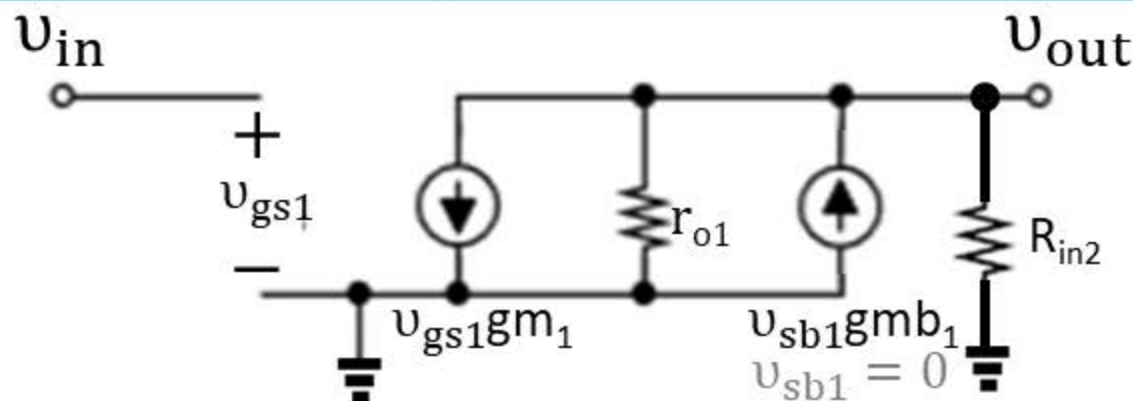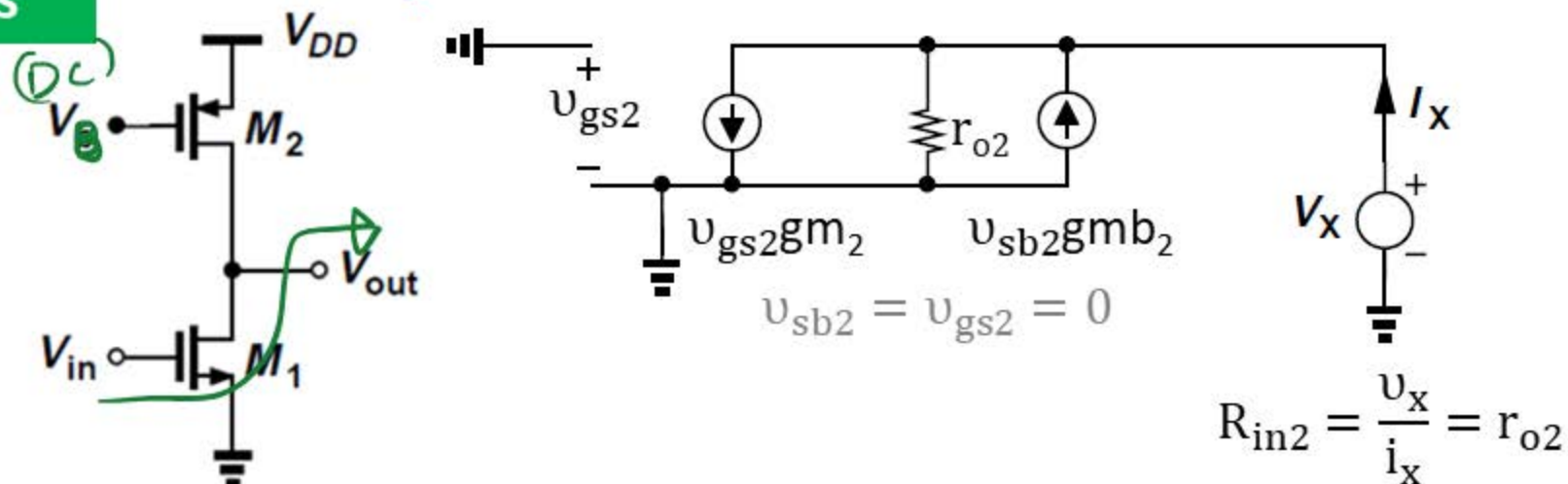


$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{o2} \parallel r_{o1})$$

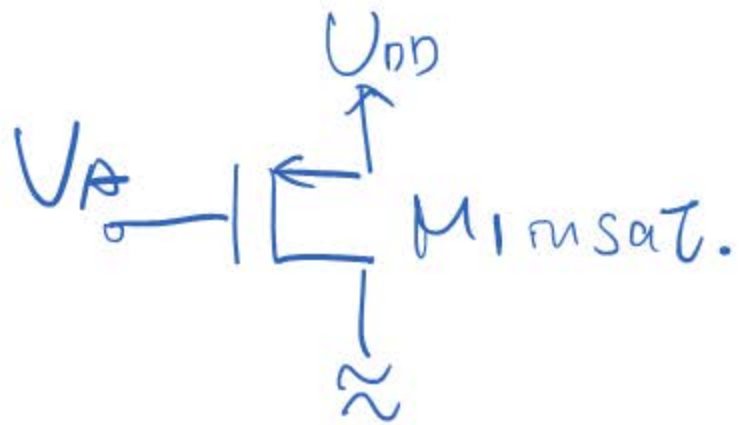- To achieve high A_v , the output swing is severely limited in the CS stages with resistive load and diode-connected load.
- Here $V_{out, max} = V_{DD} - (V_{SG2} - V_{TH2})$, which can be quite close to V_{DD} .



$\lambda = 0$

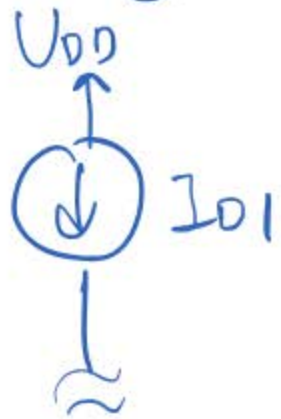

$\lambda \neq 0$

