
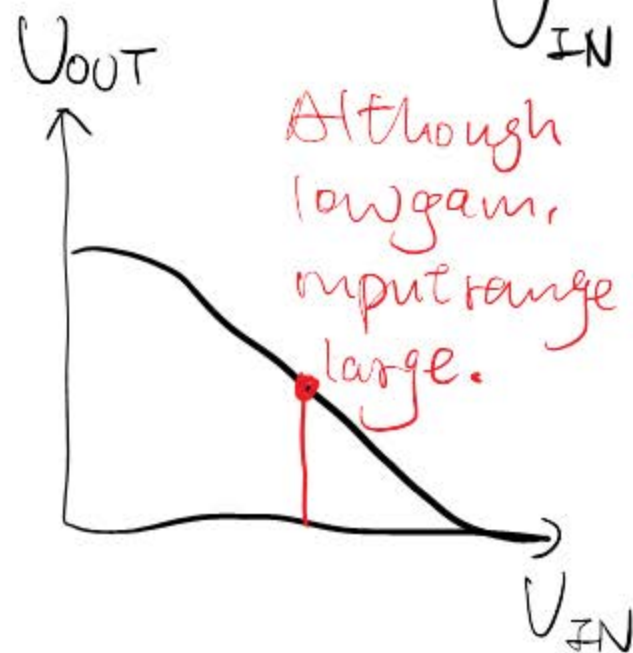


If R_c large

trade-off

If R_c small

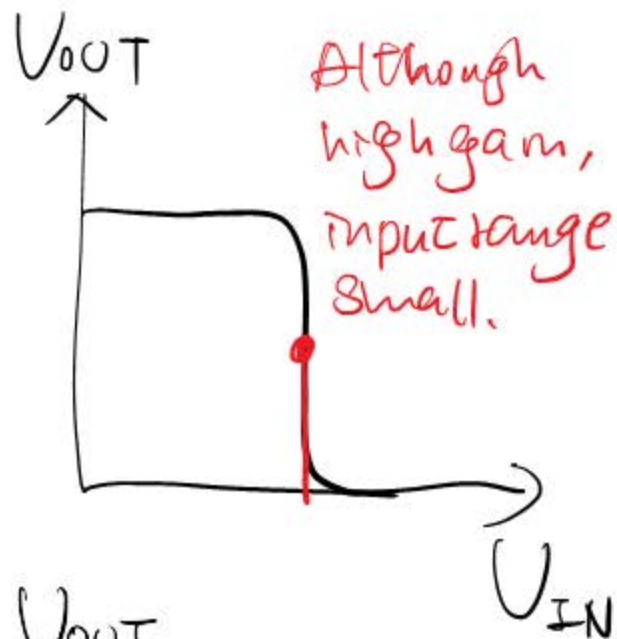





JOINT INSTITUTE

交大密西根学院


FET Single Stage Amplifier

Ve311 Electronic Circuits (Fall 2020)

Dr. Chang-Ching Tu

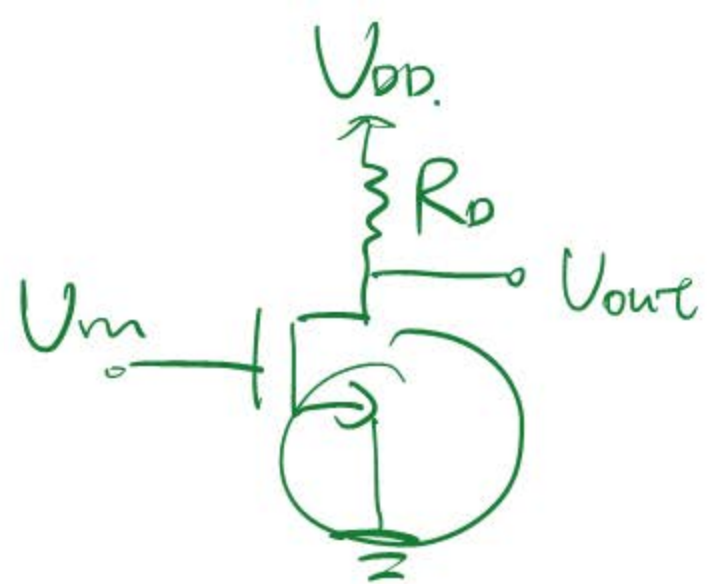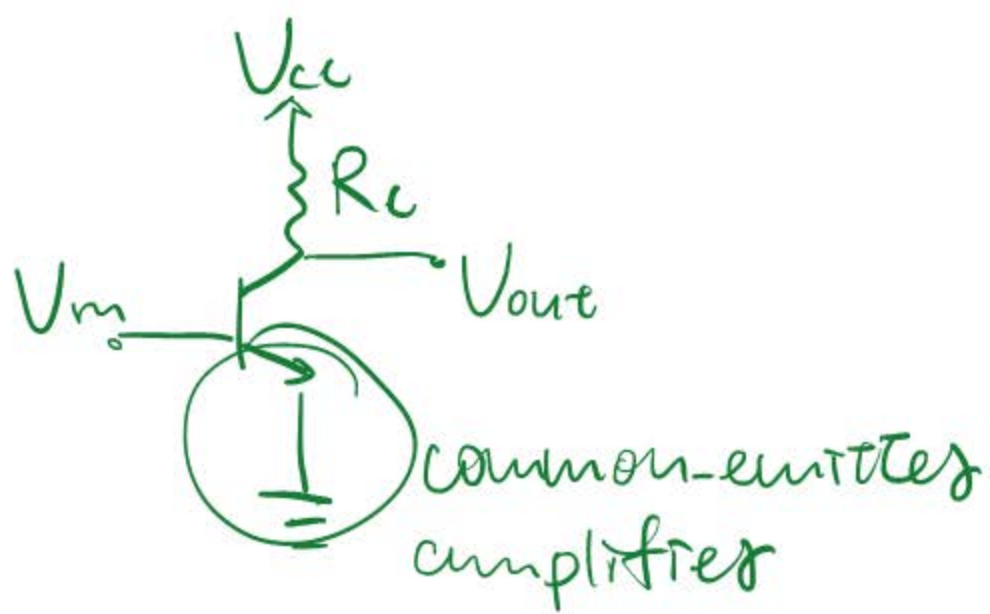

Common-Source with Resistive Load

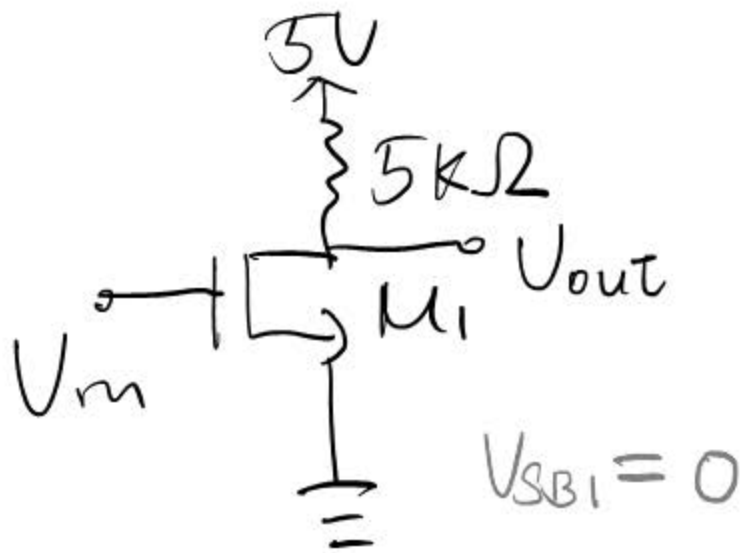

M_1 has size $\frac{10\mu m}{2\mu m} = \frac{W_{drawn}}{L_{drawn}}$

$\lambda \neq 0, r \neq 0$

$$V_m = 0.8 + 0.0018m(2\pi 100t)$$

$$V_{out} = V_{OUT} + V_{outc} = ?$$

1° Find out $V_{OUT} = ?$

then confirm whether


$$V_{DS} \geq V_{GS} - V_{TH}$$

$$V_{OUT} \geq \underbrace{V_{IN}}_{0.8} - \underbrace{V_{TH}}_{0.7} = 0.1$$

$$V_{OUT} = 5 - (5k) \cdot I_{D1}$$


$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{10\mu m}{2\mu m + 2L_D} \right)$$

$$(0.8 - 0.7)^2 (1 + \lambda V_{OUT})$$

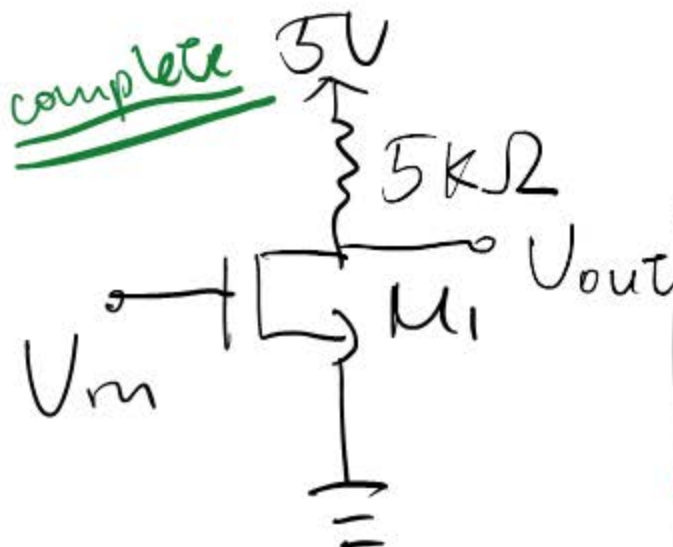

2° Find out $V_{out} = ?$


If using Pspice, do DC sweep.

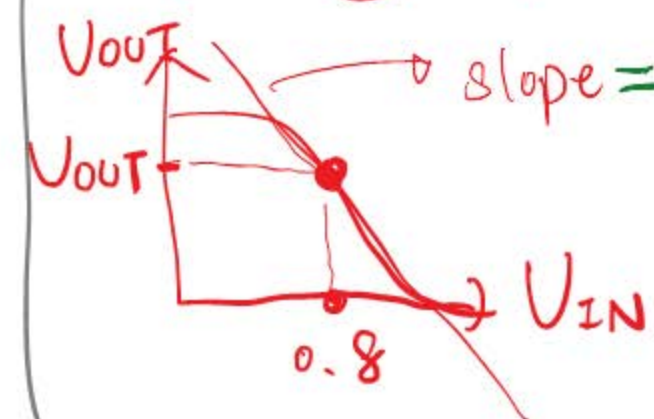


$$A_v = \left. \frac{dV_{out}}{dV_{in}} \right|_{@V_{in}=0.8}$$

$V_{out} = 0.001 A_v \sin(\omega t)$

Small-signal

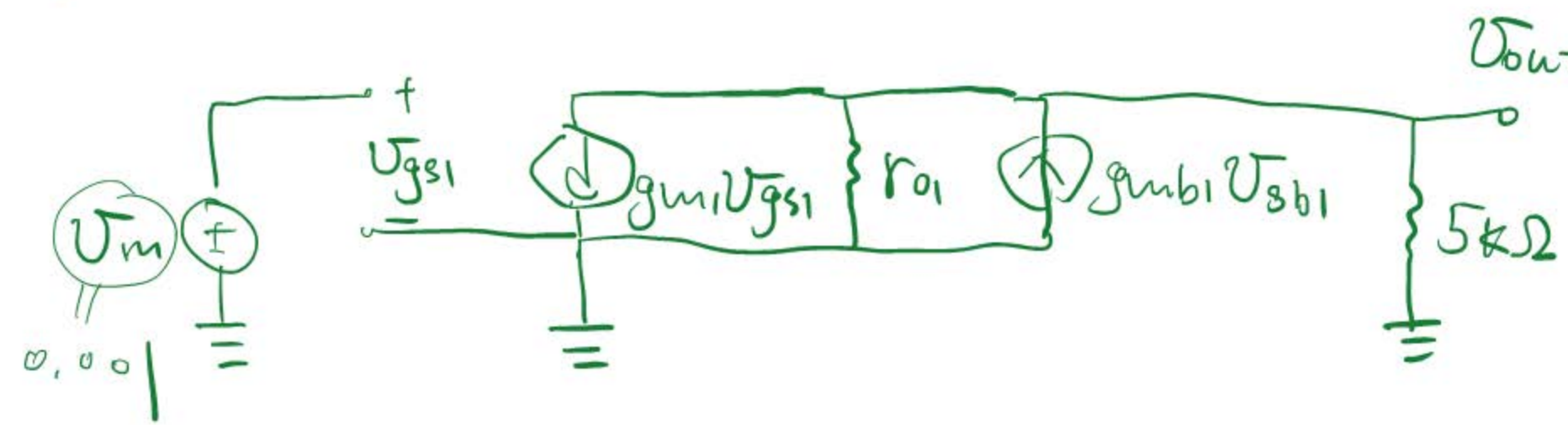

Small-signal

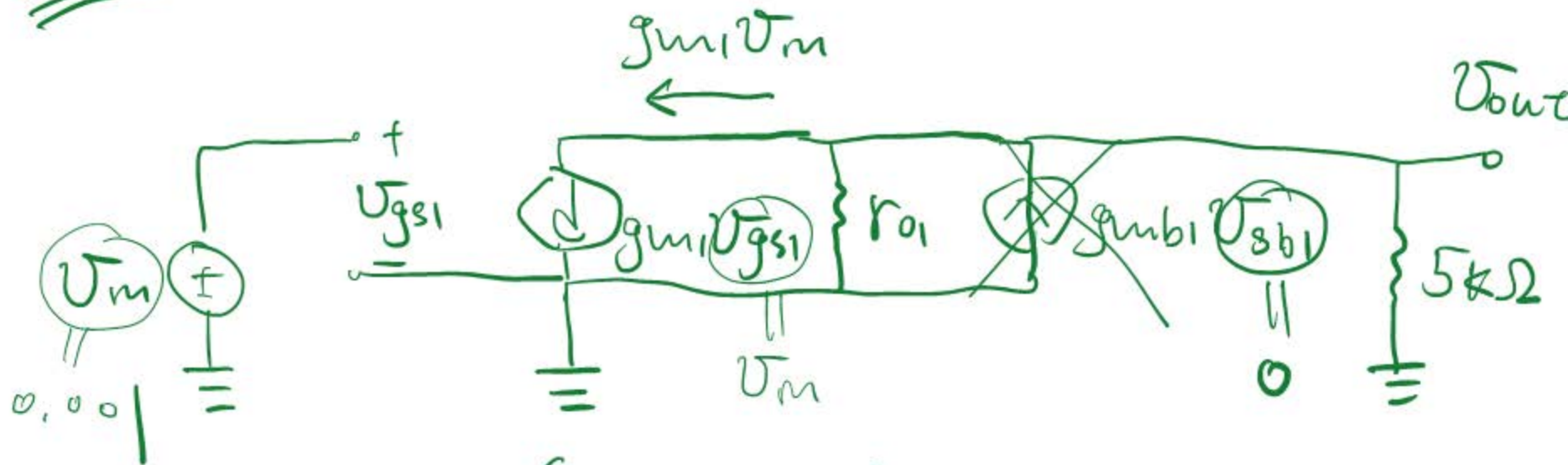

$$V_{out} = -(g_{m1}U_m)(r_{o1} \parallel 5k)$$

$$g_{m1} = \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (0.1)^2 (1 + \lambda V_{out})$$

$$r_{o1} \approx \frac{1}{I_{D1} \lambda}$$

$$A_v = \frac{V_{out}}{U_m} = -g_{m1}(r_{o1} \parallel 5k)$$



Common-Source with Resistive Load

7

DC Analysis

$$\lambda = 0$$

$$\gamma = 0$$

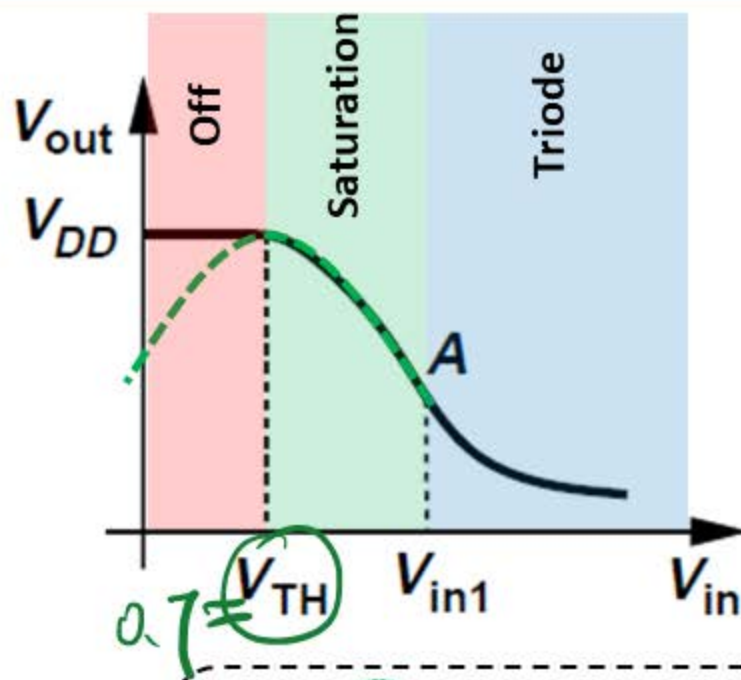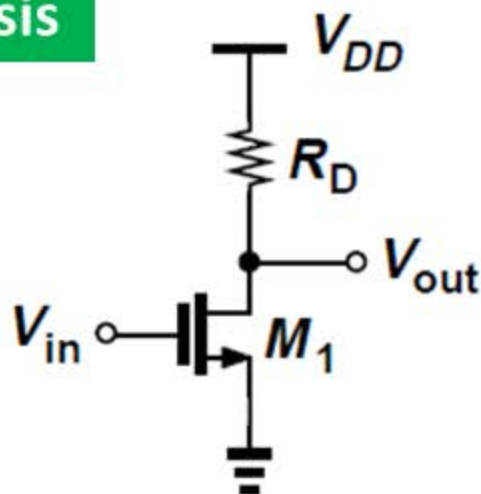

- $V_{in} < V_{TH} \rightarrow M_1$ Off

$$V_{out} = V_{DD}$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$ in Saturation

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 = I_{D1}$$

- $V_{in} > V_{in1} \rightarrow M_1$ in Triode

$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} [(V_{in} - V_{TH})V_{out} - \frac{1}{2} V_{out}^2] = I_{D1}$$

$$V_{out} = V_{in1} - V_{TH}$$


$$= V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$$

Common-Source with Resistive Load

DC Analysis

$$\lambda = 0$$

$$\gamma = 0$$

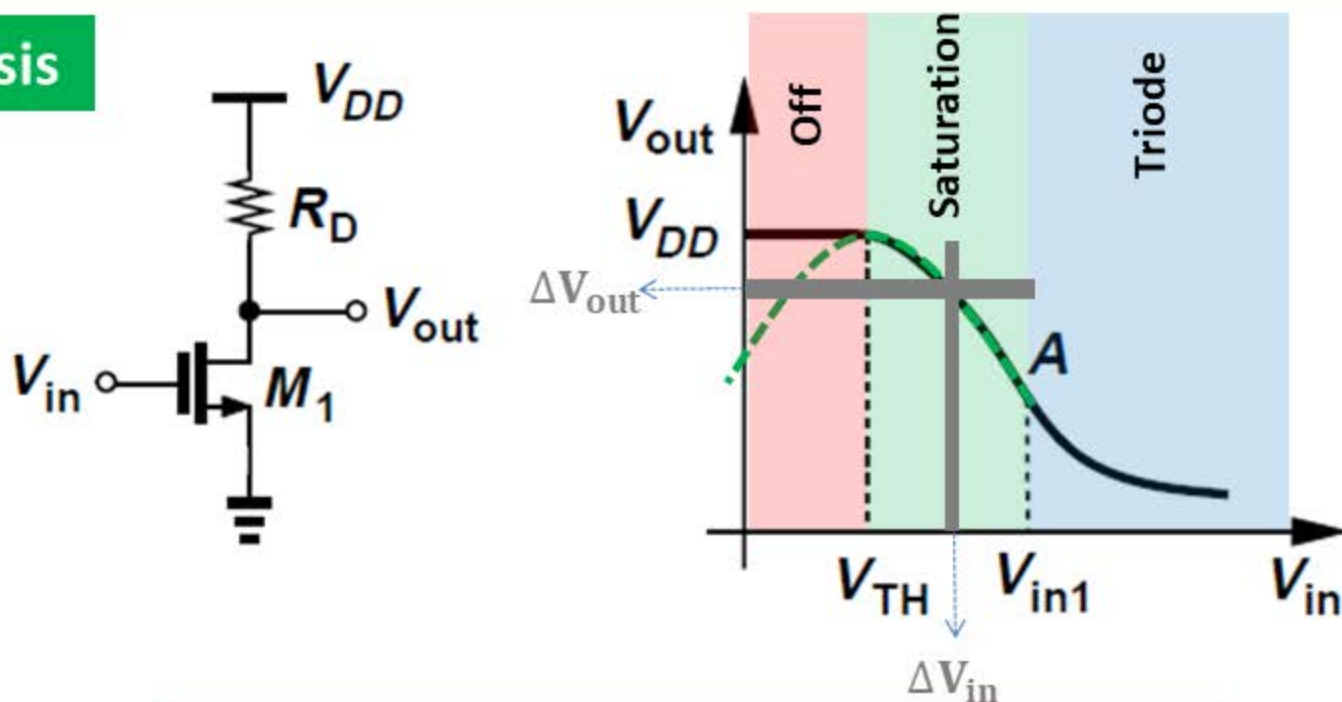

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$= -g_m \cdot R_D$$


- V_{gs} increases by $\Delta V_{in} \rightarrow I_d$ increases by $\Delta V_{in} \cdot g_m \rightarrow V_{out}$ decreases by $\Delta V_{in} \cdot (g_m \cdot R_D)$

Common-Source with Resistive Load

Small-signal
Analysis

$$\lambda = 0$$

$$\gamma = 0$$

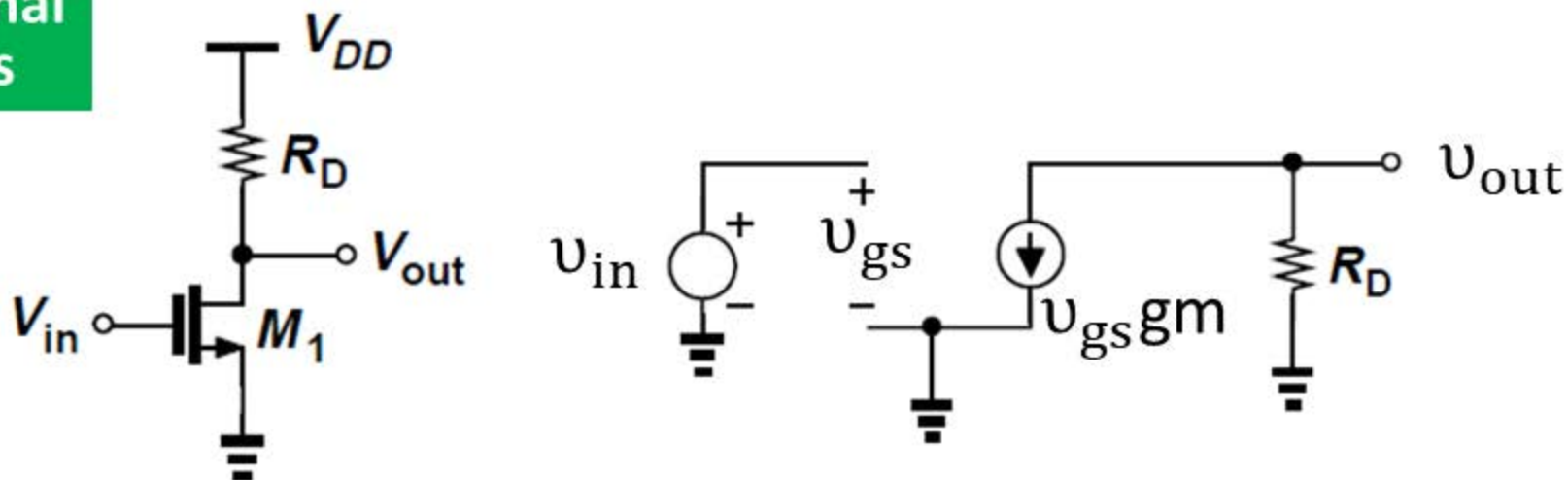

$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot R_D$$



- Small-signal analysis leads to the same result as DC analysis.

Common-Source with Resistive Load

DC Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

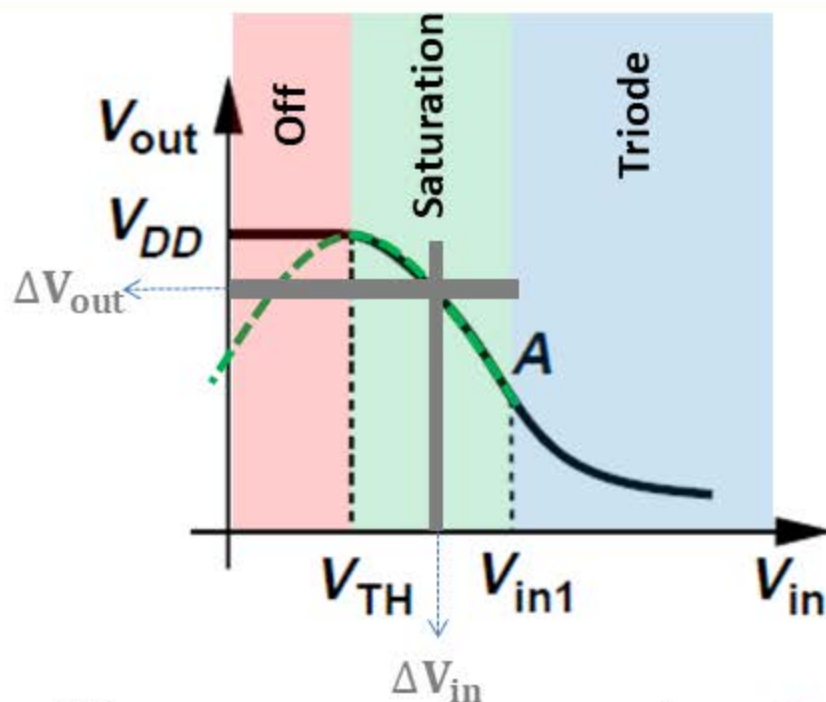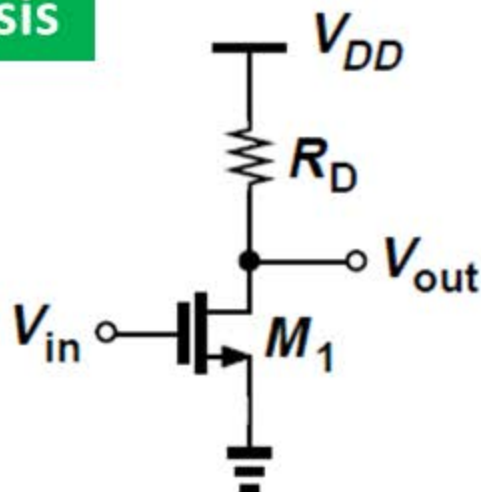

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = \frac{\partial \left[V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out}) \right]}{\partial V_{in}} \quad \text{or } I_{D1}$$

$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$

$\quad \quad \quad = g_m \quad \quad \quad \approx I_{D1} \quad \quad \quad = A_v$

$$A_v = \frac{-g_m R_D}{1 + R_D I_{D1} \lambda} = -g_m \frac{1}{\frac{1}{R_D} + \frac{1}{r_o}} = -g_m (R_D \parallel r_o)$$


$\quad \quad \quad = 1/r_o$

Common-Source with Resistive Load

Small-signal Analysis

$\lambda \neq 0$

$\gamma \neq 0$

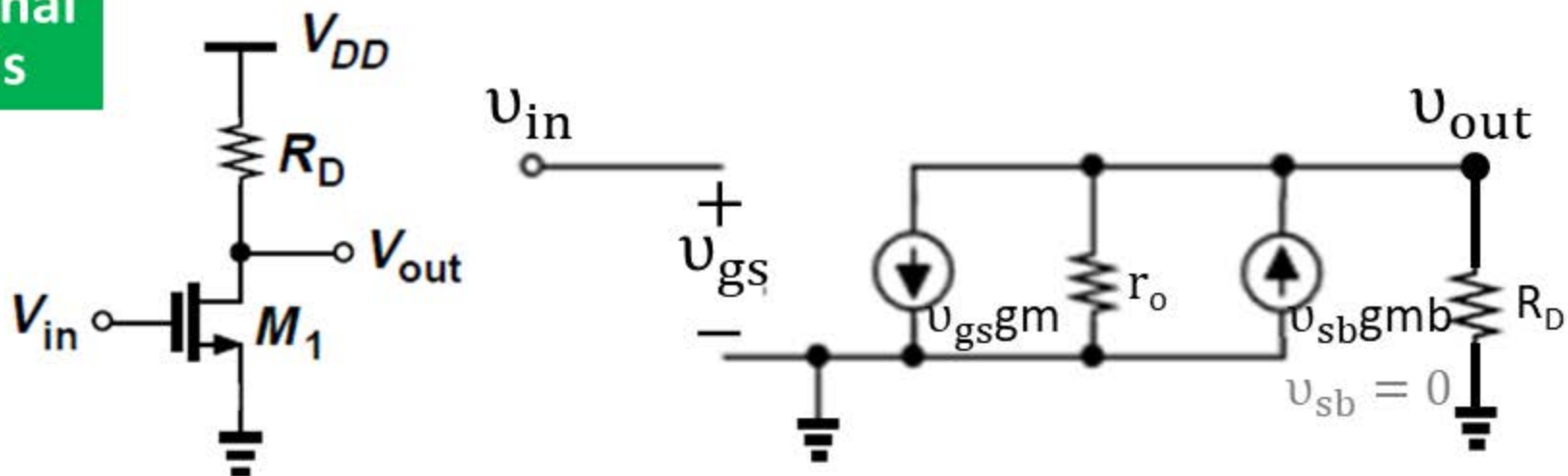


$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot (R_D \parallel r_o)$$

- Small-signal analysis leads to the same result as DC analysis.
- g_m is a function of V_{GS} and V_{DS} , while r_o is a function of I_D . → **Nonlinearity**

$$r \neq 0, \lambda \neq 0$$

(A)

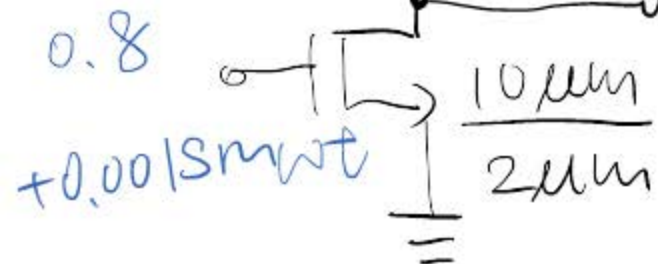


$$\boxed{V_{SB} = 0}$$

$$\boxed{V_{sb} = 0}$$

$$V_{TH} = V_{TH0} = 0.7$$


(B)


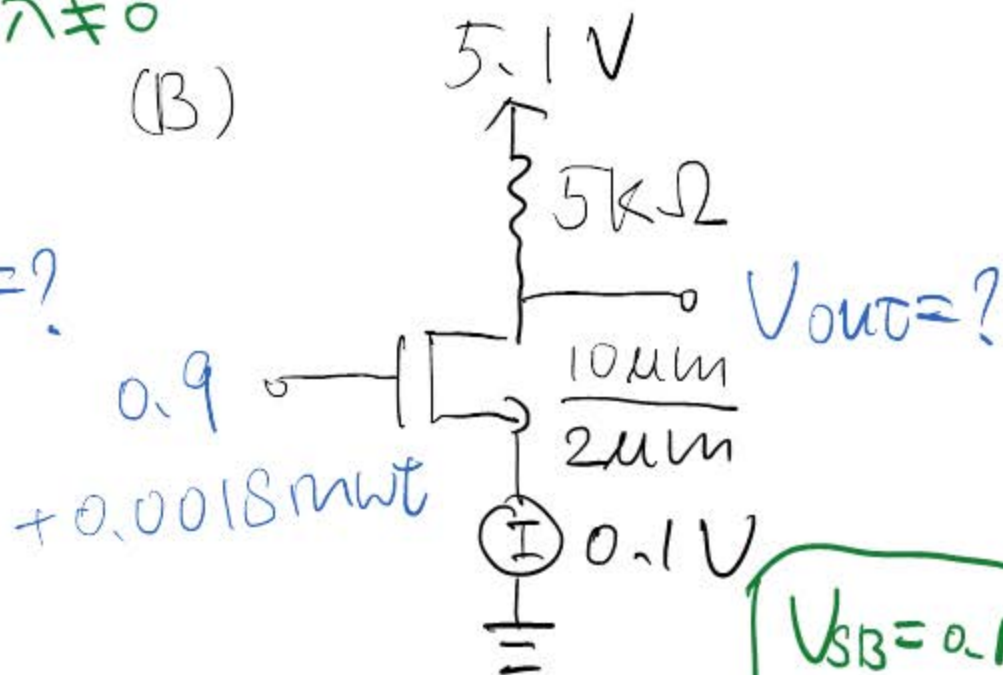


$$\boxed{V_{SB} = 0.1}$$

$$\boxed{V_{sb} = 0}$$


$$V_{TH} > V_{TH0} = 0.7$$

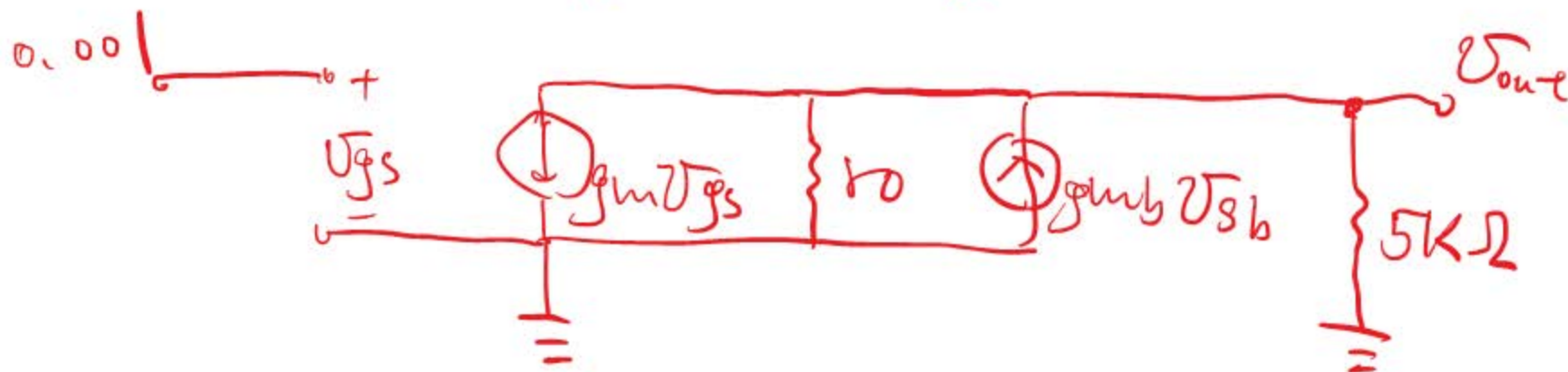

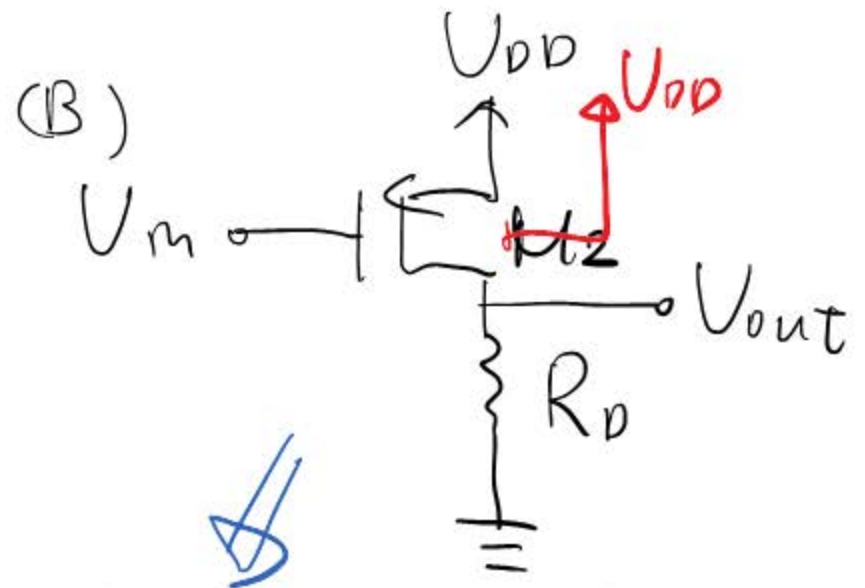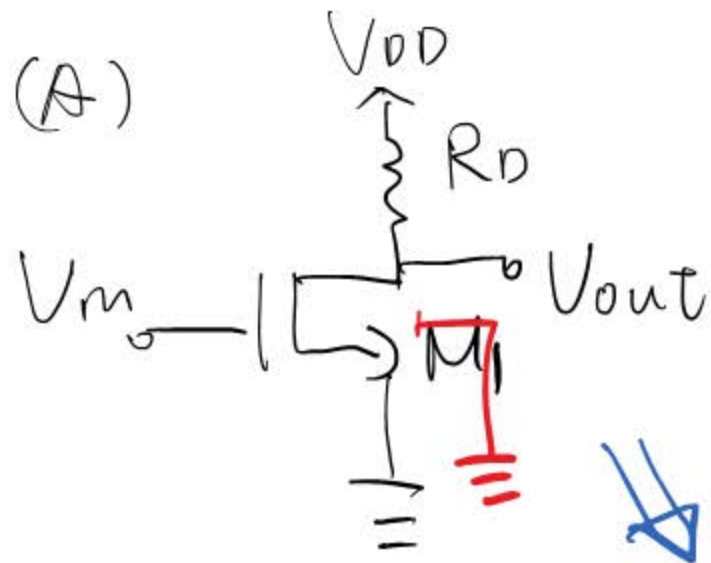


What are the analytical expressions for A_v ?

$$A_v = -g_{m1,2}(r_{o1,2} || R_{D1,2})$$


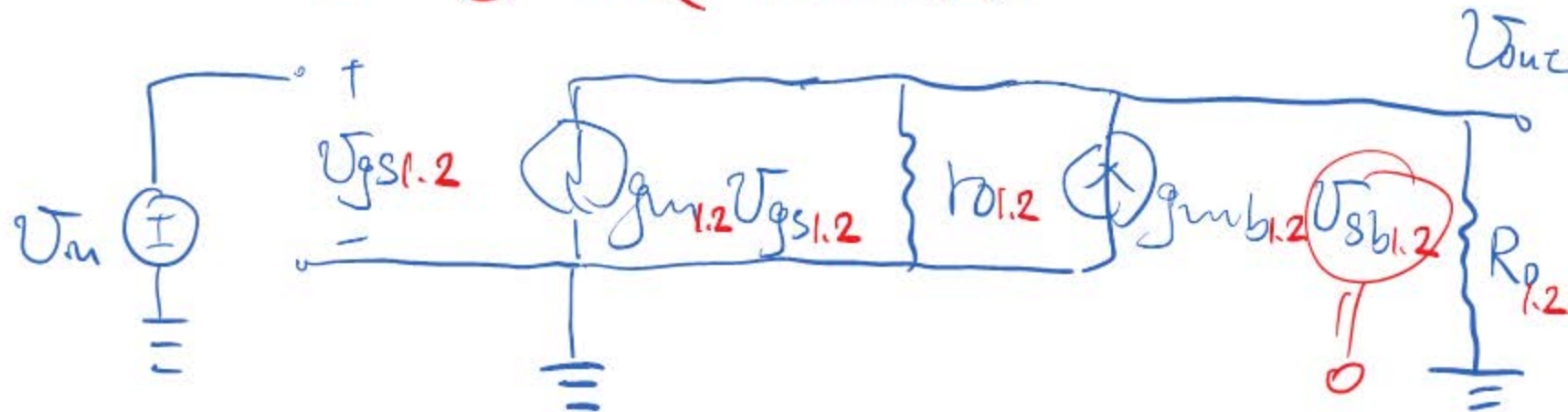


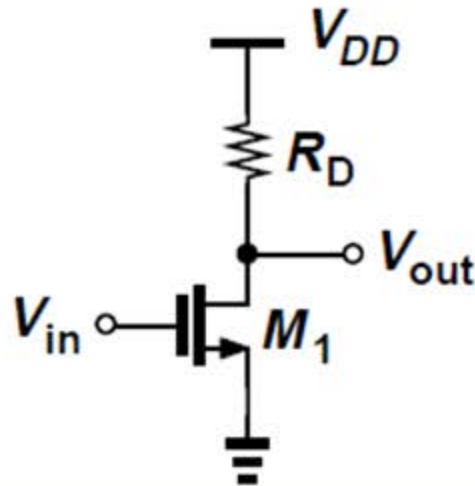Example

Sketch the drain current and transconductance of M_1 as a function of input voltage. Assume $\lambda = \gamma = 0$.





Solution:

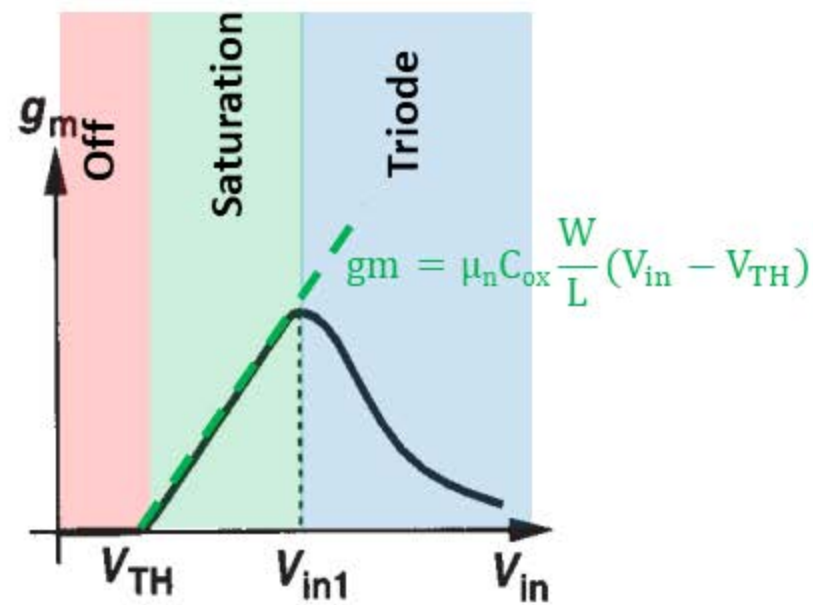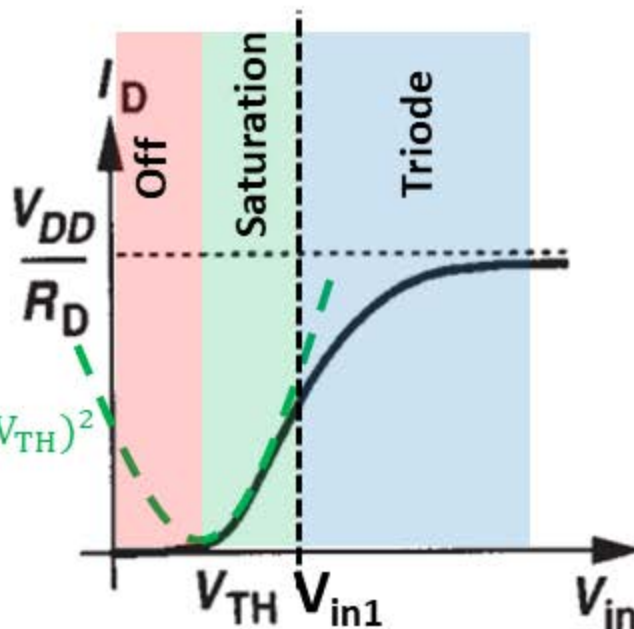

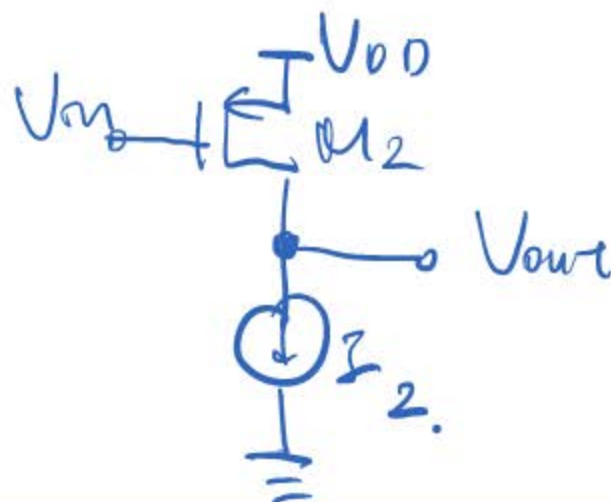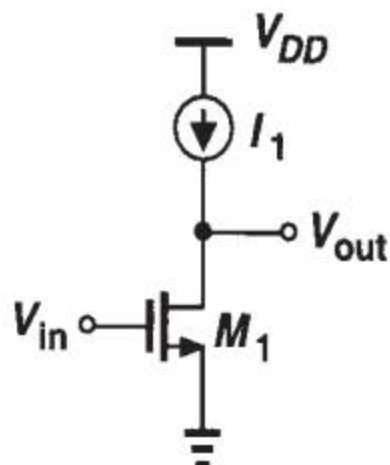Example

Assuming M_1 in saturation, calculate its small-signal gain.



Solution:

- Small-signal Analysis:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} r_{o1}$$



- DC Analysis:

$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{DS})$$


Example

Assuming M_1 in saturation, calculate its small-signal gain.

$\lambda \neq 0$
 $r \neq 0$

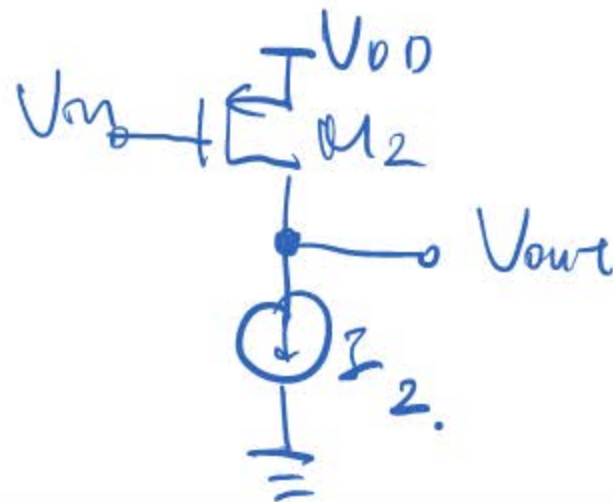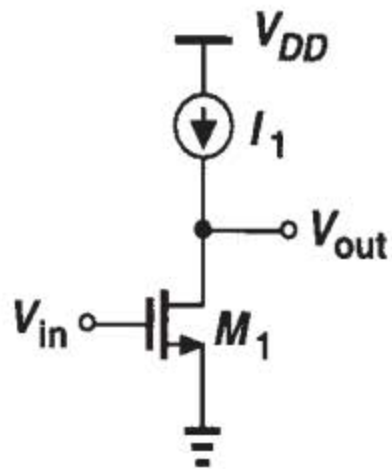

Solution:

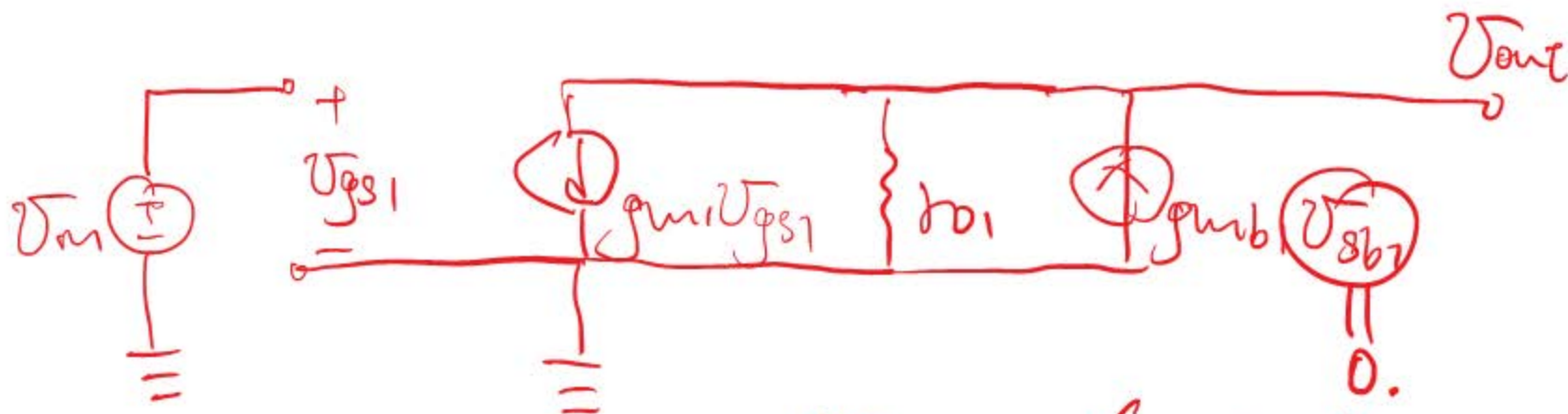

$$V_{out} = (g_{m1} V_{in}) r_{o1}$$